

Department of Computer Science and Engineering (CSE) BRAC University

Summer 2022

CSE250 – Circuits and Electronics

Practice Problems


(Nodal analysis, Mesh analysis, Source transformation)



Purbayan Das, C. Lecturer
Department of Computer Science and Engineering (CSE)
BRAC University

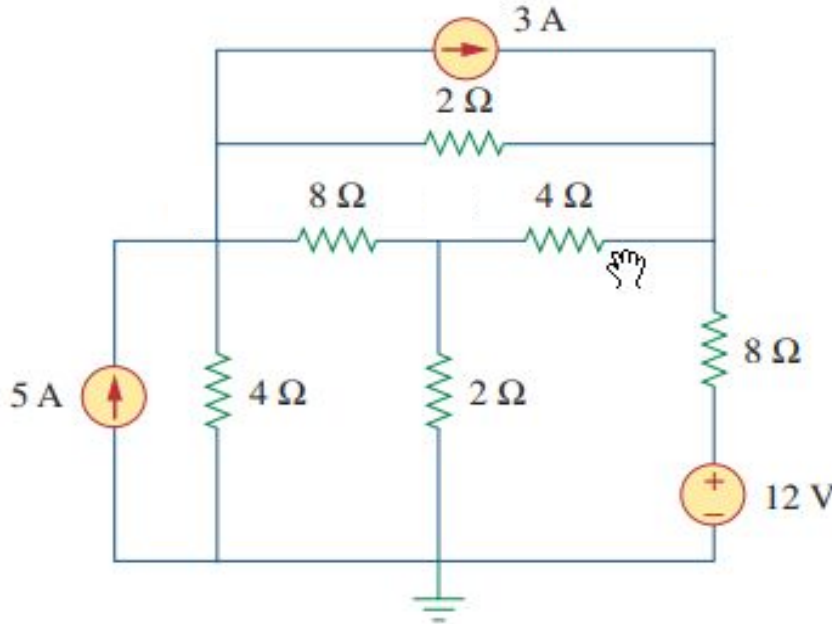Problem 1


Use nodal analysis to determine the voltage across the **3A** current source. What is the power of the it? Is it absorbing or supplying?



Ans: Node voltages = 0 V; 10 V; 4.933 V; 12.267 V;
Voltage across the 3A source = ± 2.267 V

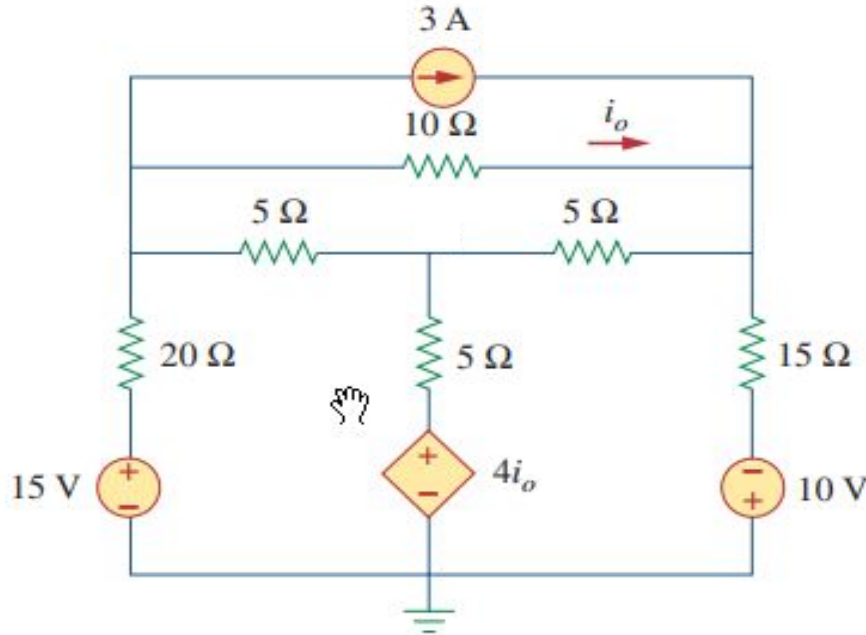Problem 2


Use nodal analysis to determine the voltage across the **3A** current source. What is the power of the it? Is it absorbing or supplying?



Ans: Node voltages = 0 V; -7.19 V; -2.78 V; 2.89 V;
Voltage across the 3A source = -10.08 V

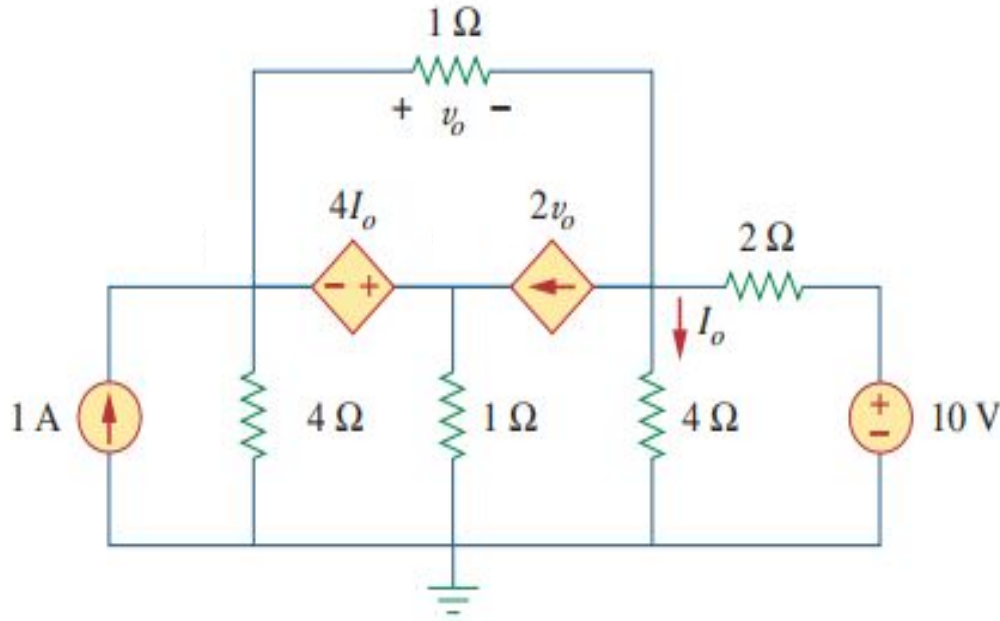Problem 3


Use nodal analysis to determine the current through the $4I_o$ source.



Ans: Node voltages = 0 V; 4.97 V; 4.85 V; -0.12 V;
Current through the $4I_o$ source = ± 5.33 A

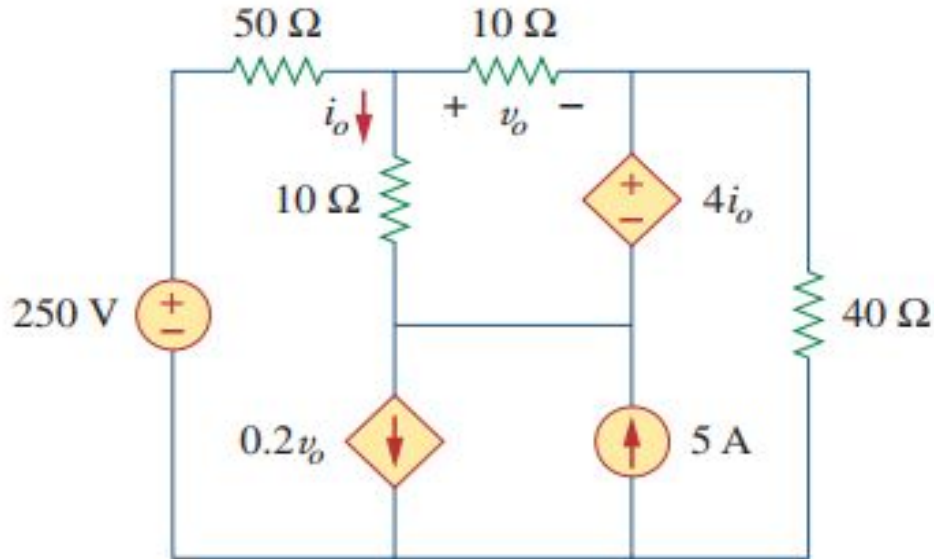Problem 4


Use mesh analysis to determine v_o and i_o . What is the voltage across the 5A source?



Ans: $v_o = 2.941 \text{ V}$; $i_o = 0.49 \text{ A}$

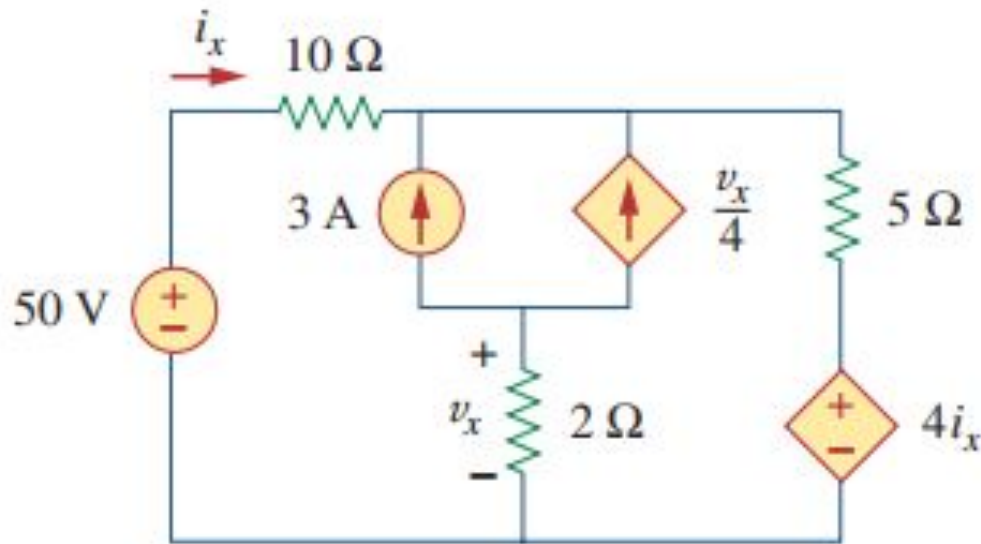Problem 5


Use mesh analysis to determine $\mathbf{v_x}$ and $\mathbf{i_x}$. What is the voltage across the 3A source?



Ans: $\mathbf{v_x} = -4\text{ V}$; $\mathbf{i_x} = 2.105\text{ A}$

Problem 6

Use source transformation to find v_o

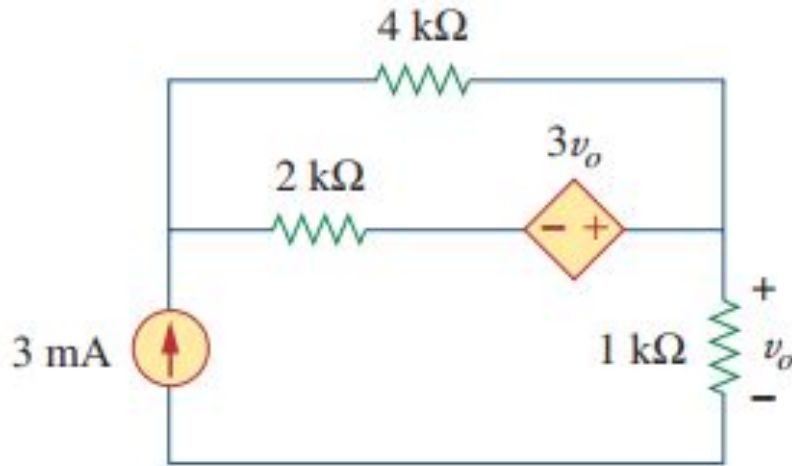

$$\text{Ans: } v_o = 3 \text{ V}$$

Thank you for your attention