



CSE251

Electronic Devices and Circuits

Exp -01: Study of Diode Characteristics

Submitted By

Name: Shihab Muhtasim

ID: 21301610

Group: 05

Semester: Fall 22

Cooperated by

ID: 21301611

ID: 20101443

ID: 20201066

Date of performance: 03/10/22

Date of Submission: 09/10/22

2. Circuit Diagram:

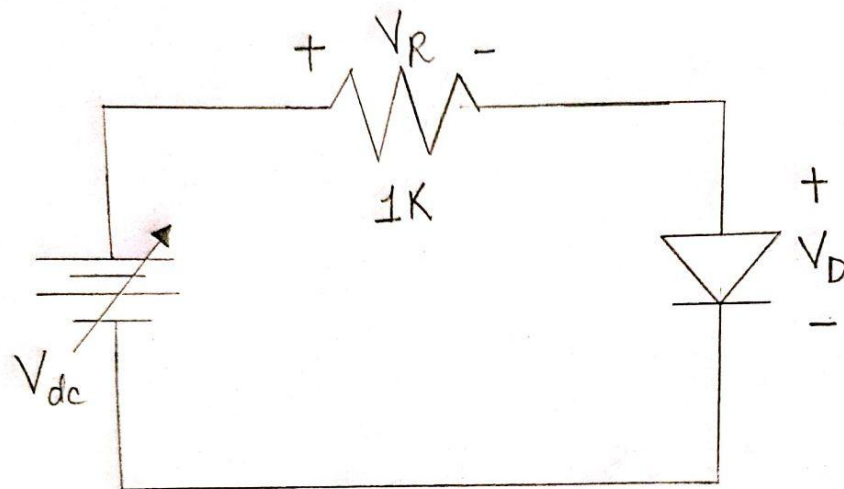


Figure: Circuit diagram for finding out the diode IV characteristics

3. Signed Data Sheet:

Group 5 : ① 21301611, ② 21301610
③ 20101443 ④ 20201066

- For each value of V_{dc} , also calculate the diode current using $I_R = V_R$.
- Plot diode IV characteristics of the diode for different readings obtained.
- Calculate the diode ideality factor n and the reverse saturation current I_S , using the diode equation assuming $V_D \gg V_T$.
- Calculate the static and dynamic resistances for $I_D = 4, 8$ and 12 mA.

Data Table

$R = 1k\Omega$ (measure the accurate resistance using the digital multi-meter)

$f = 0.080 K.2$

Supply Voltage, V_{DC} (v)	Diode Voltage, V_D (v)	Voltage across the Resistor, V_R (v)	Diode Current, $I_D = I_R = V_R/R$ (mA)
0	0	0	0
0.1	31.6×10^{-3}	0	0
0.2	126.4×10^{-3}	0.0736	0.7441
0.3	243.5×10^{-3}	0.0565	0.0565
0.4	341.7×10^{-3}	6.8×10^{-3}	6.8156×10^{-3}
0.5	0.406	44.2×10^{-3}	0.04469
0.6	0.441	119.7×10^{-3}	0.12103
0.7	0.458	182.8×10^{-3}	0.18483
0.8	0.473	263.3×10^{-3}	0.2662
0.9	0.486	374.6×10^{-3}	0.3787
1	0.495	0.453	0.458
2	0.550	1.406	1.421
4	0.602	3.404	3.441
6	0.630	5.35	5.409
8	0.656	7.34	7.421
10	0.670	9.27	9.373
12	0.684	11.30	11.425 $\rightarrow I_{D1}$
13	0.690	12.28	12.416
14	0.696	13.24	13.387 $\rightarrow I_{D2}$

Calculation

Determining Ideality Factor, n

Let, $\alpha = \frac{1}{nV_T}$

Take any two data from the table: $I_{D1} = I_S \exp(\alpha V_{D1})$ and $I_{D2} = I_S \exp(\alpha V_{D2})$

Taking ratio of I_{D1} and I_{D2} ,

$$\Rightarrow \frac{I_{D1}}{I_{D2}} = \exp(\alpha(V_{D1} - V_{D2}))$$

$$\Rightarrow \alpha = \frac{\ln\left(\frac{I_{D1}}{I_{D2}}\right)}{V_{D1} - V_{D2}} = \frac{1}{nV_T} \Rightarrow n = \frac{1}{\alpha V_T}$$

Determining Static (R_D) and Dynamic (r_D) Resistance

$$R_D = V_D / I_D$$

$$r_D \approx \frac{nV_T}{I_D}$$

$$V_T = 0.025 V$$

$$a = 13.206$$

$$n = 3.028$$

$$I_S = 1.364 \times 10^{-3}$$

Calculations:

By letting, $ID1 = 11.425$, $ID2 = 13.387$

We get, $VD1 = 0.684$, $VD2 = 0.696$

Value of α :

$$\begin{aligned}\alpha &= \ln(ID1/ID2)/(VD1-VD2) \\ &= \ln(11.425/13.387)/(0.684-0.696) \\ &= 13.206\end{aligned}$$


Value of n :

$$\begin{aligned}n &= 1/\alpha \cdot VT \\ &= 1/(13.206 \cdot 0.025) \\ &= 3.028\end{aligned}$$

Value of I_s :

$$\begin{aligned}I_s &= ID1/\exp(\alpha \cdot VD1) \\ &= 11.425/\exp(13.206 \cdot 0.684) \\ &= 1.364 \cdot 10^{-3} \text{ mA}\end{aligned}$$

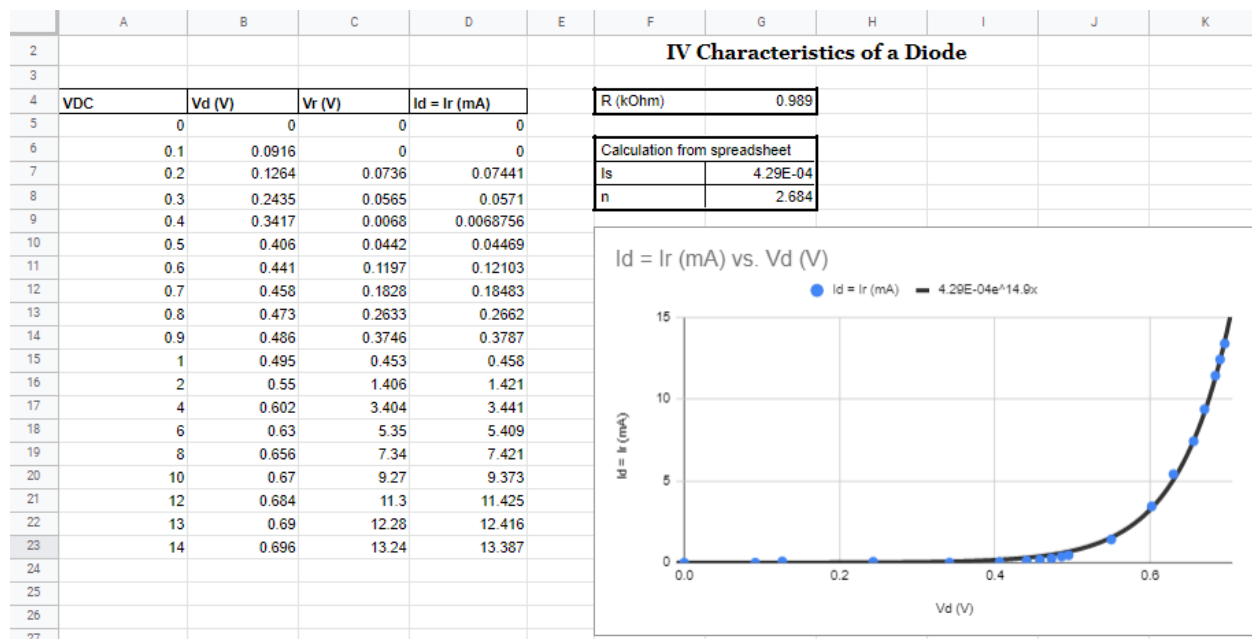
4. Graph From Task 2 and Calculated Parameters from graph:



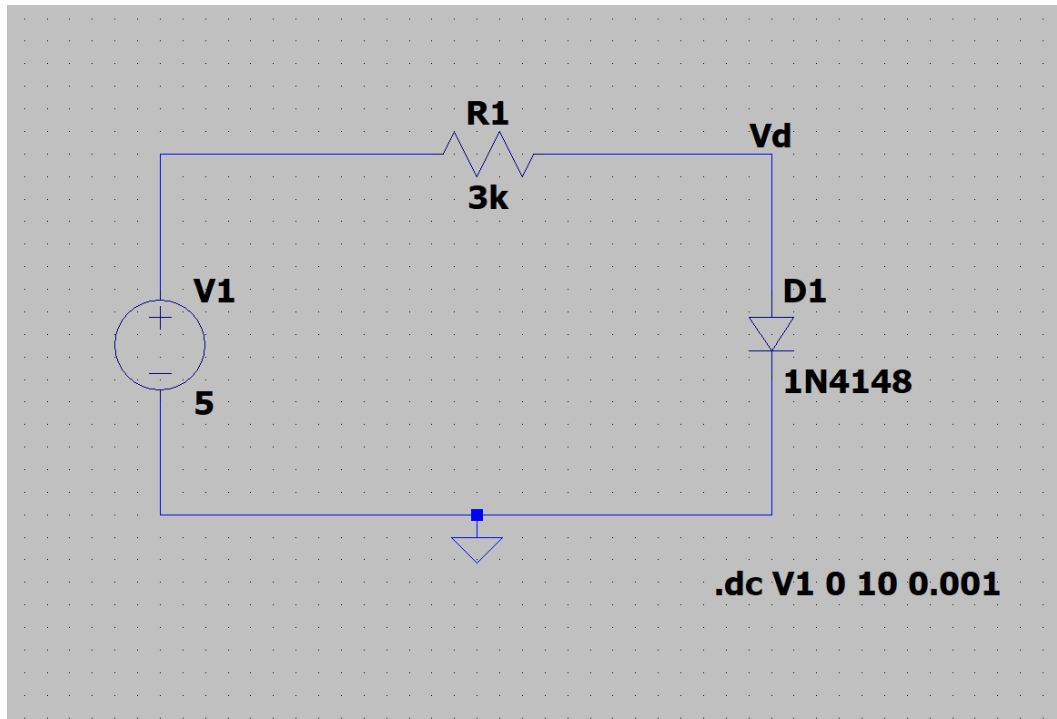5. Simulated Circuit in Lt spice:


Here, The last two digits of my student id are 1 and 0

Hence, $R = [2 + (10/10)] = 3k \text{ ohm}$



IV Graph from the circuit:

(I_D Vs V_D)

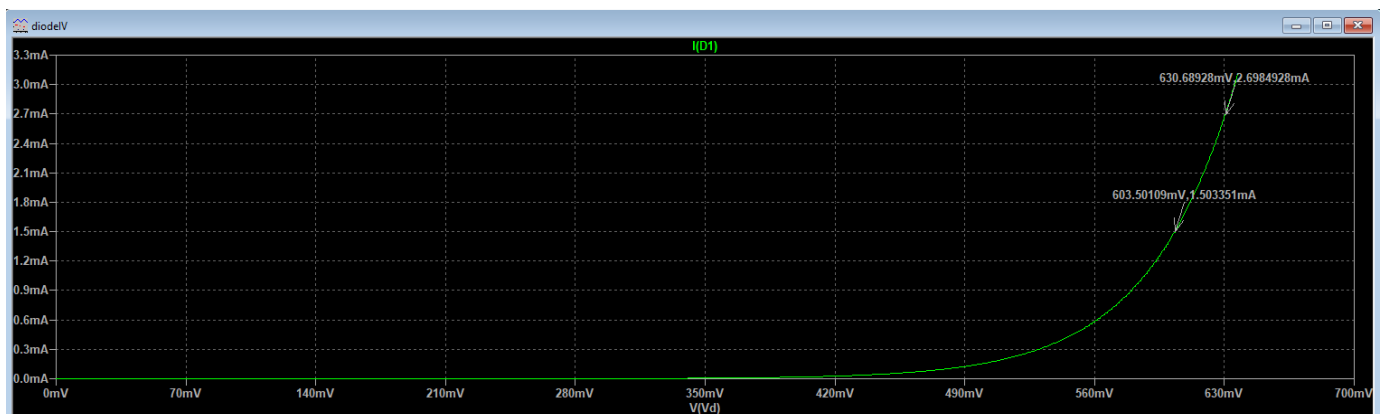

Differences in Graphs of Task 2 and Task 3:

By comparing the graphs we can see that this graph and the one generated in task 2 are similar and have the same shape even though they have different resistance which leads us to conclude that, the diode's nature doesn't depend on the resistance connected to it.

However, if we try to analyze closely we can see that the plot in LT spice shows different values of current I_D for horizontally active voltage V_D than the graph in task 2. For instance, in the hardware lab, we obtained $I_D = 5.409 \text{ mA}$ for $V_D = 630 \text{ mV}$ whereas in LT spice we get $I_D = 2.67 \text{ mA}$ current for $V_D = 630.30 \text{ mV}$ which is a different value than the hardware lab's value. If we analyze the data sets for all other voltages we will face differences in values for all of those. Two reasons can be inferred for this to happen.

Firstly, because the current I_D of the circuit depends on the resistance and we have used a different resistance in LT spice which occurs in different datasets.

Secondly, hardware lab datasets don't give accurate results as there are usually small errors from the hardware, and also these are manmade operations that altogether don't give the perfect results.

Nevertheless, the datasets for both graphs being different they both provide similar exponential graph curves which proves that the diode follows its nature in both cases.

5. DISCUSSION

1. We could understand all the tasks of this experiment and get the expected results from our hardware along with software operations. We could measure V_D and V_R using a voltmeter. Then we were able to find the current through diode I_D by dividing the voltages across resistors for each dataset by the resistance value of our circuit. Furthermore, we calculated the values for I_s , n , and α for these datasets manually using the equations.
2. We were able to draw an I_D vs V_D graph for the hardware datasets in a spreadsheet and generated an equation that gave us more accurate results for I_s and n than our manual calculations.
3. We know that the value of the diode ideality factor (n) is between 1 and 2. However, in the hardware lab, with manual calculations in task 1, we obtained $n = 3.028$ for our circuit which is outside its general parameters. Nevertheless, when

we used the same values in a spreadsheet while doing task 2 to generate a graph, we obtained a more efficient value for n from the equation auto-generated by the graph. There we could see that the value of n was 2.684 which is much closer to the given parameters. The extra 0.684 can be considered as an error from our hardware operations since all the datasets were manmade manual calculations which usually don't provide theoretical perfect results. Hence, we can conclude that when we were calculating the values for I_s and n manually, we had to use two equations and we could only work with two different datasets (eg. I_{d1} , V_{d1} , and I_{d2} , V_{d2}) for which we received less accurate values for I_s and n . However, the spreadsheet automatically generated one equation comparing all of our data sets from the graph which gave us more accurate results of I_s and n .

4. We successfully implemented the circuit in LT spice and generated an I_d vs V_d graph from that circuit. However, we used a different resistance value in that circuit yet the graph generated was the same as the one generated from the spreadsheet. This leads us to prove that, the nature of the diode doesn't depend on the resistor connected to it. No matter what the value of the resistor is, the diode will act according to its nature which is, in this case, to behave as a short circuit after a minimal amount of voltage has been applied where the voltage becomes 0.