

1.



CSE251

Electronic Devices and Circuits

Exp-06: Study of Operational Amplifier(op-Amp)

Submitted By:

Name: FAHAD MOHAMMAD REJWANUL ISLAM

ID: 20101443

Group: 05

Semester: Fall 22

Cooperated by:

ID: 21301610


ID: 21301611

ID: 20201066


Date of Performance: 14/11/22

Date of Submission: 21/11/22


2. Circuit Diagrams:

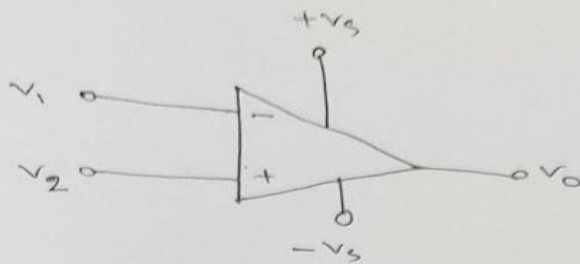


circuit 1 : OP-Amp comparator

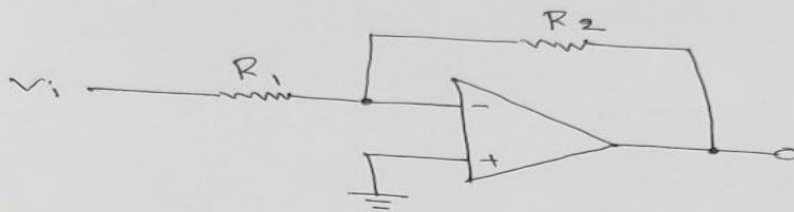

circuit 2 : inverting Amplifier

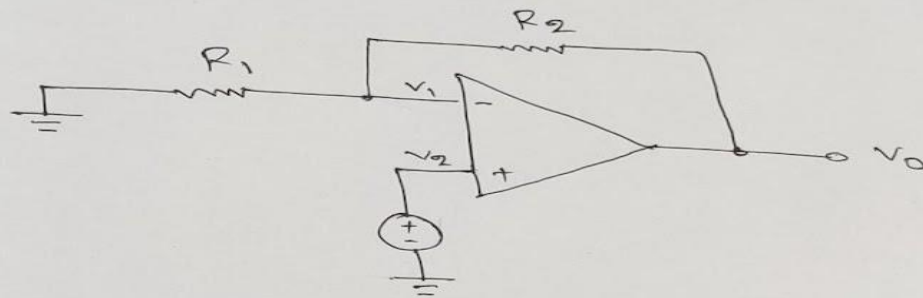


circuit 3 : Non-Inverting Amplifier

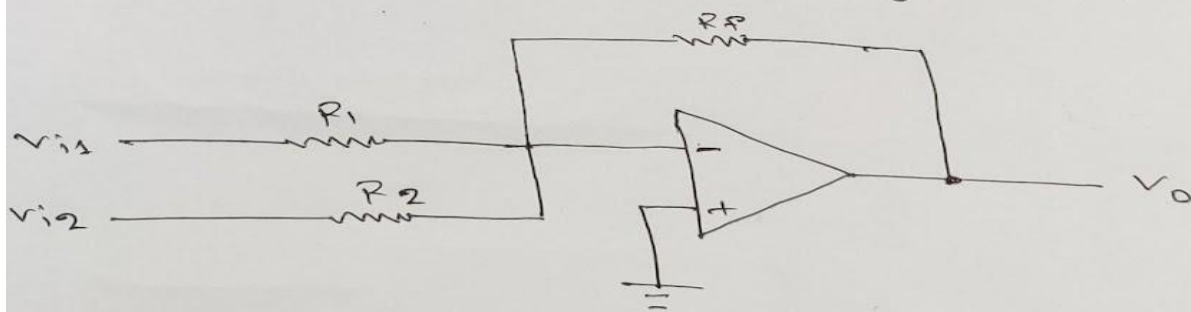

circuit 4 : Inverting Summing Amplifier.

3. Signed data sheet:




Op-Amp Integrator

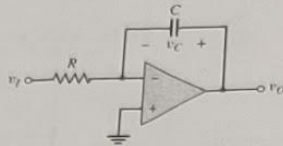

The figure above shows an Op-Amp circuit that can do integration operation on the given input voltage. The figure above shows an Op-Amp circuit that can do integration operation on the given input voltage. The following equation shows the relationship between the input and the output.

$$v_O(t) = -\frac{1}{CR} \int_0^t v_I(t) dt - v_C$$


Task-01: Op-Amp Comparator

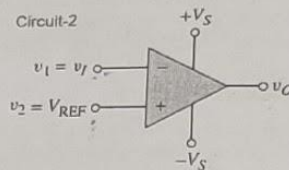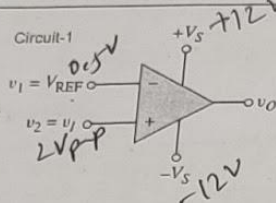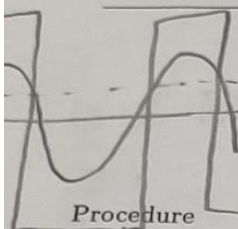

Procedure

1. Construct Circuit-1 with $v_I = 2$ V (p-p), 1 kHz sine wave and $V_{REF} = 0.5$ V. The supply voltage $+V_S$ and $-V_S$ should be $+15$ V and -15 V respectively which can be taken from the trainer board. Use this supply voltage throughout the experiment. The input voltage v_I can be taken from the oscilloscope.
2. Connect the Ch1 and Ch2 of the oscilloscope to v_I and v_O respectively. Observe the input and output waveform and capture them using a camera.
3. Now, construct Circuit-2 and repeat the experiment with same values given above. Observe the input and output waveform and capture them using a camera.

Task-02: Inverting Amplifier

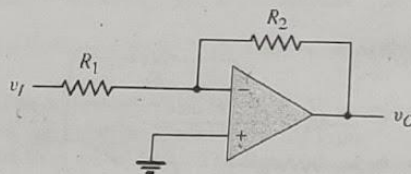

$$-\frac{2.2}{1} \times 2.2 = -2.22$$

Procedure

1. Construct the circuit with $v_I = 2$ V (p-p), 1 kHz sine wave. Use $R_1 = 1$ k Ω , $R_2 = 2.2$ k Ω .
2. Connect the Ch1 and Ch2 of the oscilloscope to v_I and v_O respectively. Observe the input and output waveform and capture them using a camera.

Observation and Calculation


output waveform should be amplified and inverted compared to the input waveform.

Amplitude from oscilloscope, $v_I = 1$ V

Amplitude from equation, $v_O = -\left(\frac{R_2}{R_1}\right) \times v_I =$

Amplitude from oscilloscope, $v_O = 2.08$

Task-03: Inverting Summing Amplifier

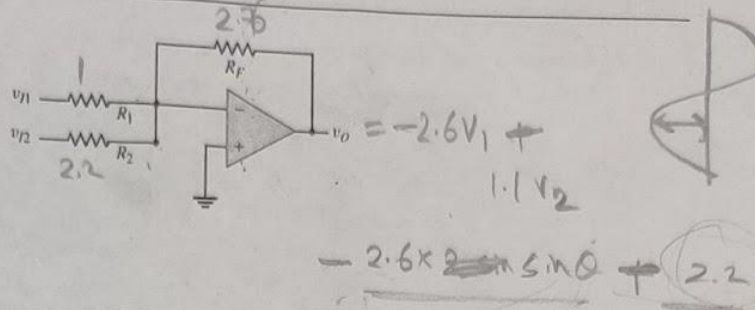

Procedure

Part-01

1. Construct the circuit with $v_{I1} = v_{I2} = 2$ V. Use $R_1 = 1$ k Ω , $R_2 = 2.2$ k Ω , $R_F = 2.7$ k Ω .
2. Use the digital multimeter to measure the output voltage.

Part-02

1. Construct the circuit with $v_{I1} = 2$ V (p-p), 1 kHz sine wave and $v_{I2} = 2$ V (from the DC Supply). Use $R_1 = 1$ k Ω , $R_2 = 1$ k Ω , $R_F = 1$ k Ω .
2. Connect the Ch1 and Ch2 of the oscilloscope to v_I and v_O respectively.

Observation and Calculation

For Part-01,

from multimeter, $v_{I1} = 2.005$

from multimeter, $v_{I2} = 2.005$

Output Amplitude from equation, $v_O = -\left(\frac{R_F}{R_1} \times v_{I1} + \frac{R_F}{R_2} \times v_{I2}\right) = -\left(\frac{2.6}{0.98} \times 2.005 + \frac{2.6}{2.18} \times 2.005\right)$

Output Amplitude from multimeter, $v_O = -7.777$

$$= -\left(\frac{2.6}{0.98} \times 2.005 + \frac{2.6}{2.18} \times 2.005\right) = -7.71067$$

For Part-02,


The output waveform should be amplified and inverted compared to the input waveform. Observe the input and output waveform and capture them using a camera.

Task-04: Simulation (Home Task)


In this part, we will simulate a Non-inverting Amplifier and a 3 input Inverting Summing Amplifier in LTspice.

Non-inverting Amplifier

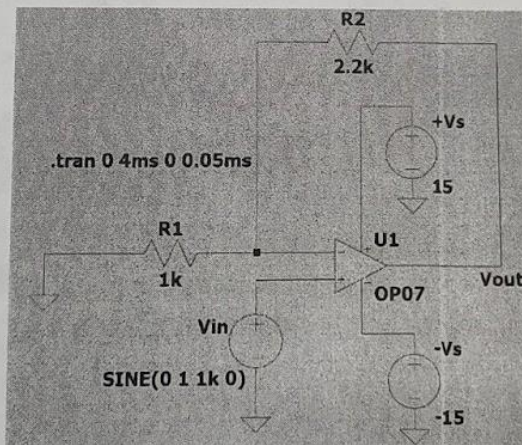
1. Open a new schematic and build the following circuit. To insert an Op-Amp in LTspice, type 'op07' in the Select Component Symbol window and select the Op-Amp from there.




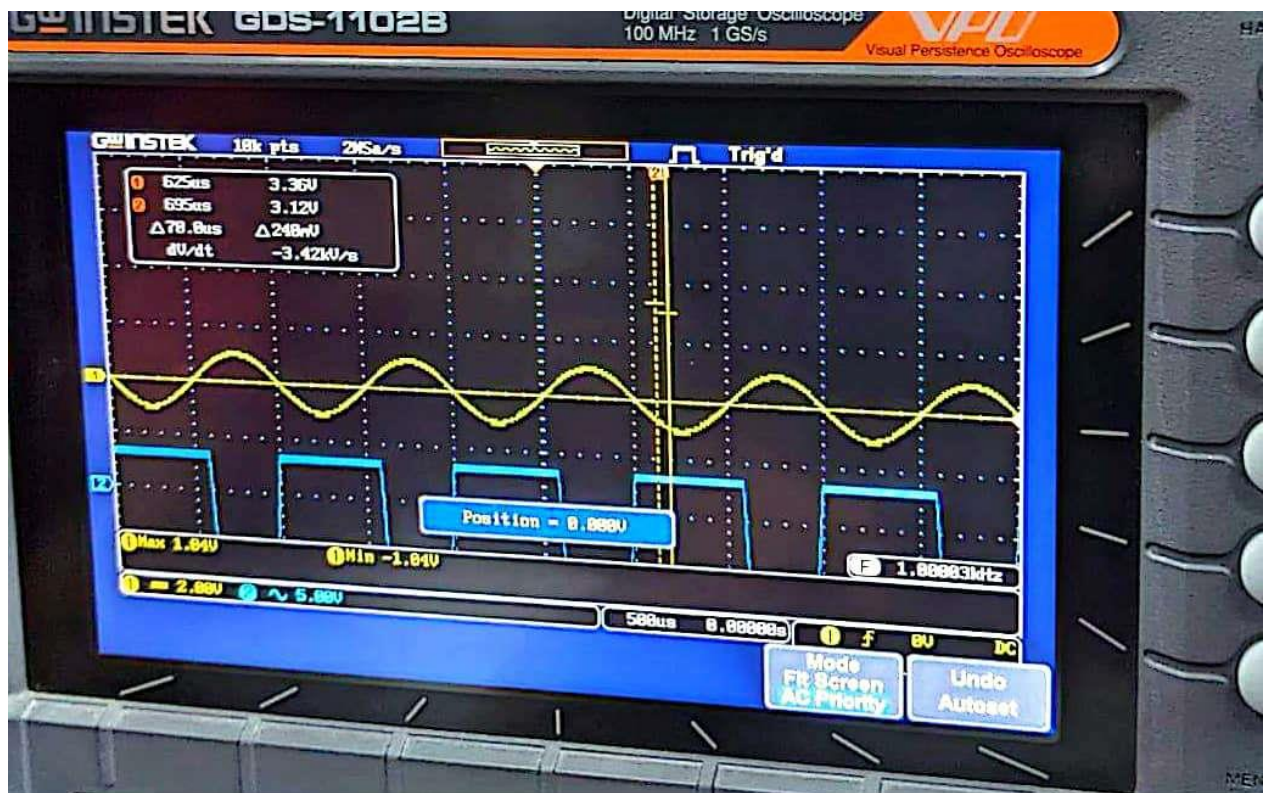4. captured photos of all the waveforms from the oscilloscope:




Scanned with CamScanner

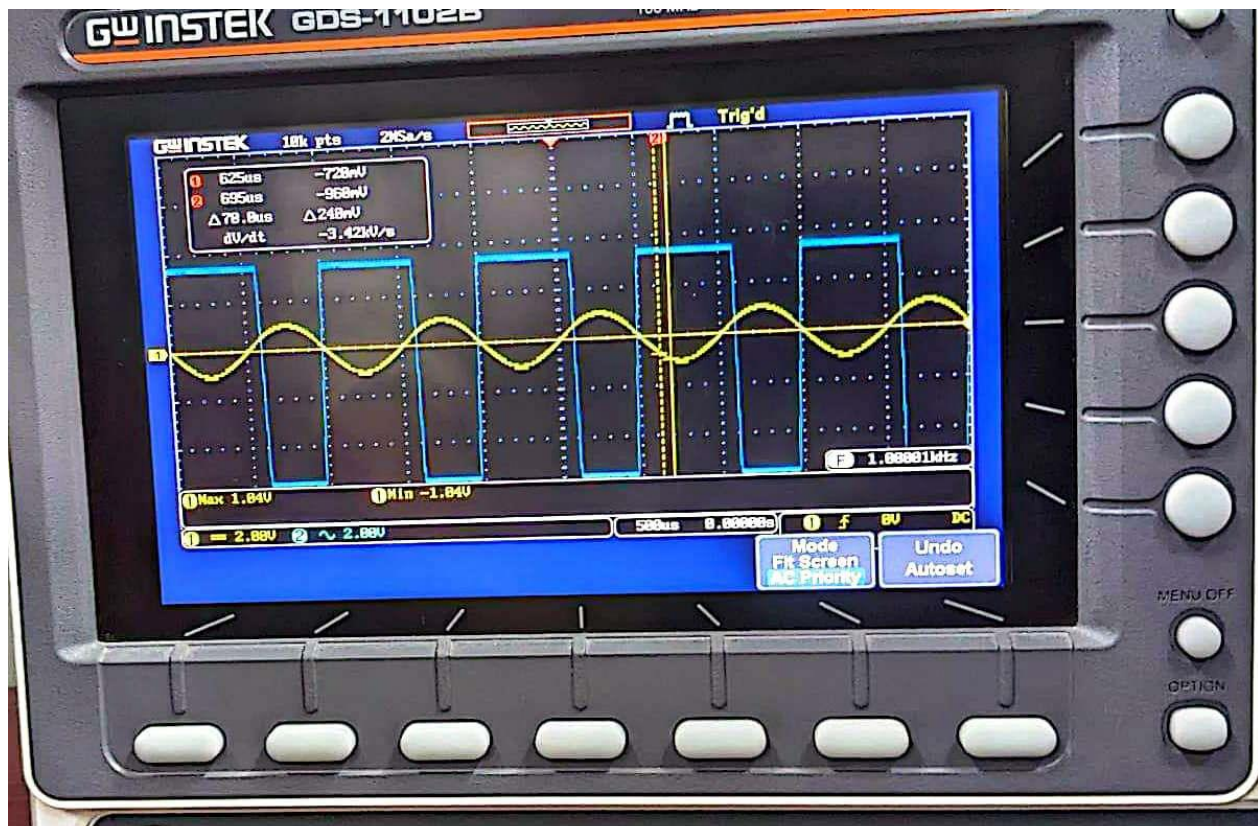


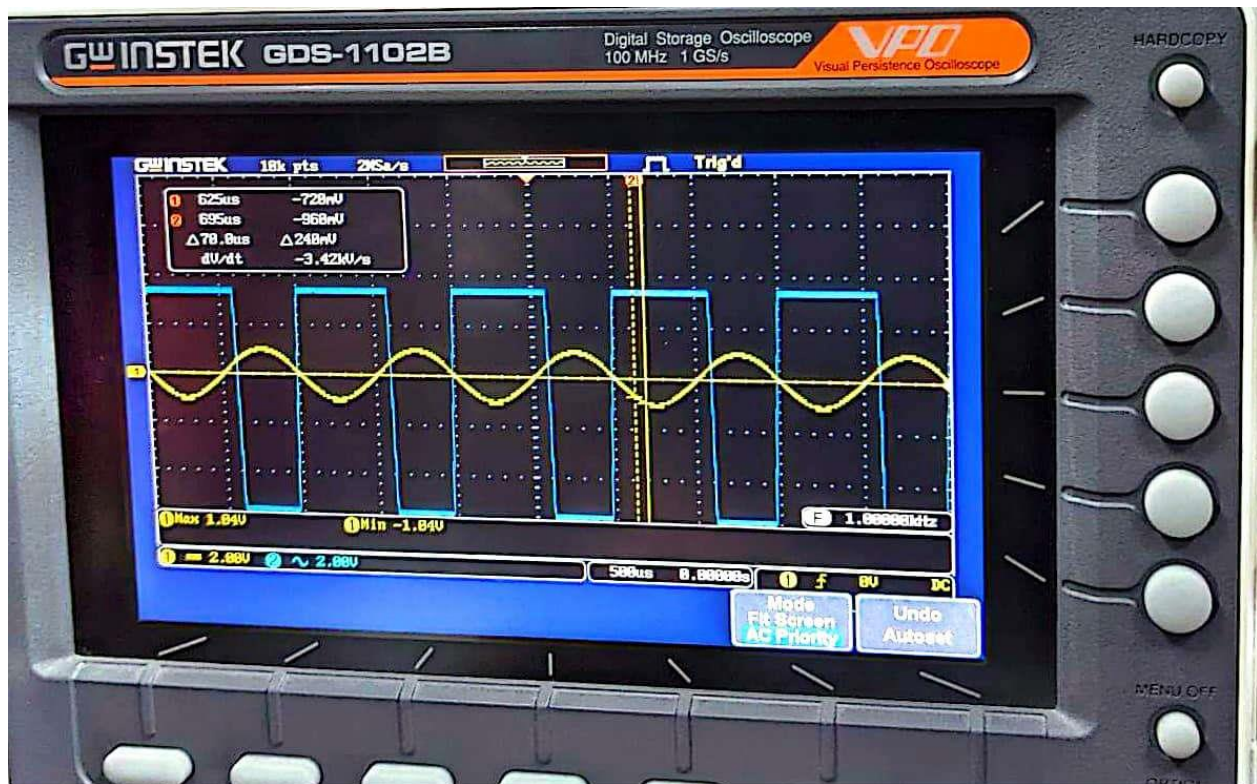

Scanned with CamScanner

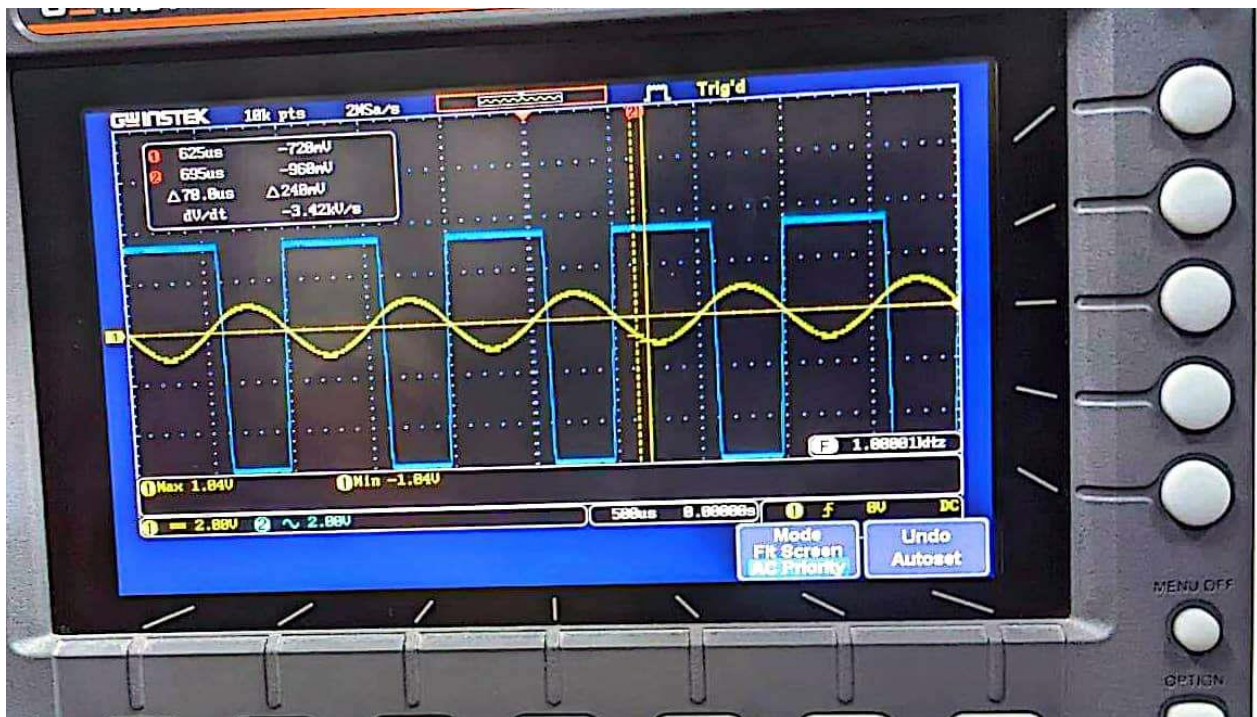


Scanned with CamScanner

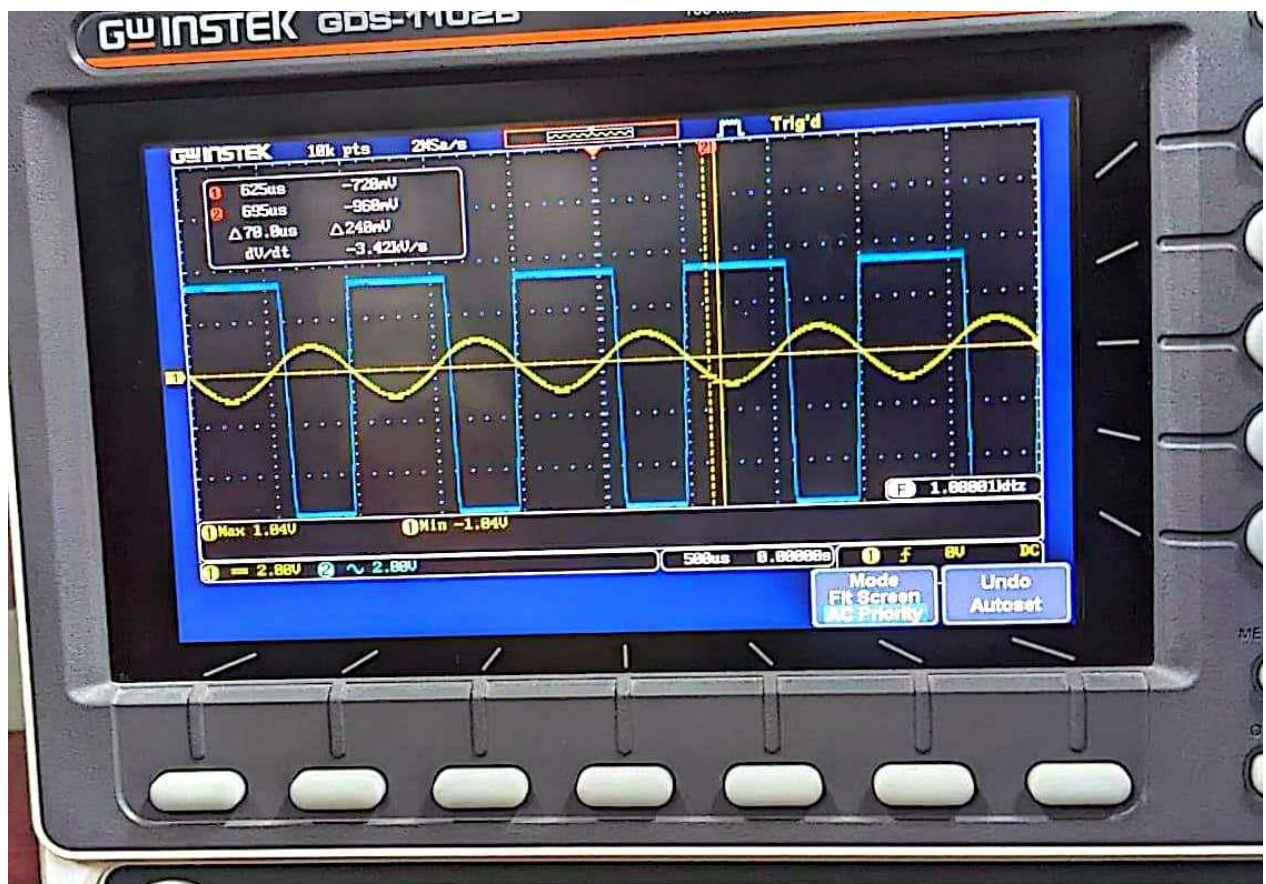





Scanned with Can

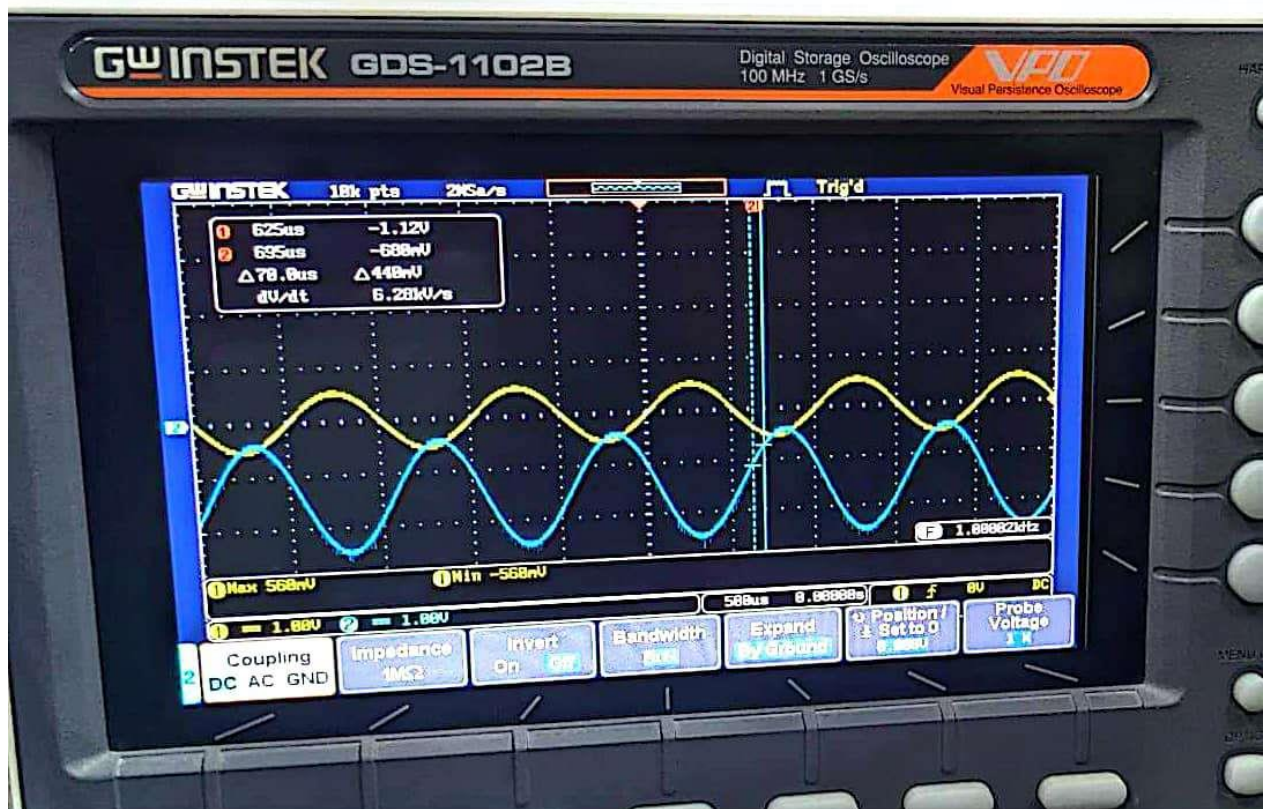


Scanned with CamScanner

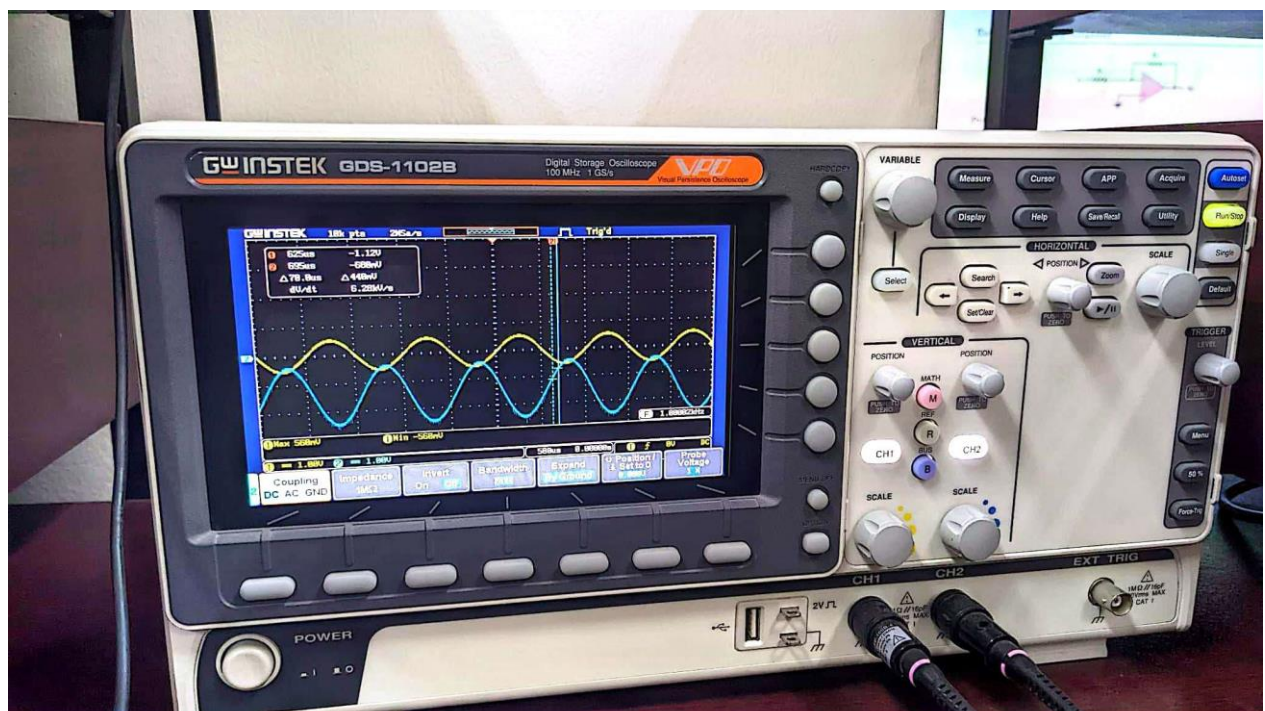

Scanned with CamScanner

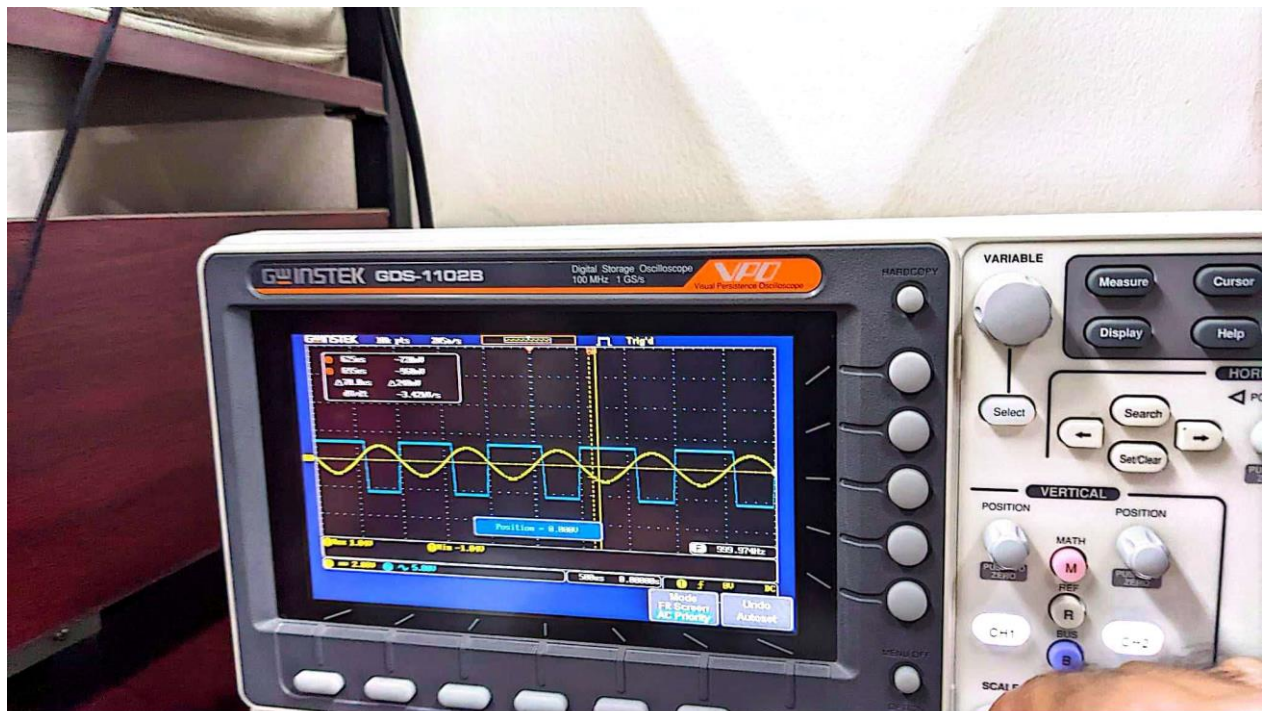


CS Scanned with CamScanner

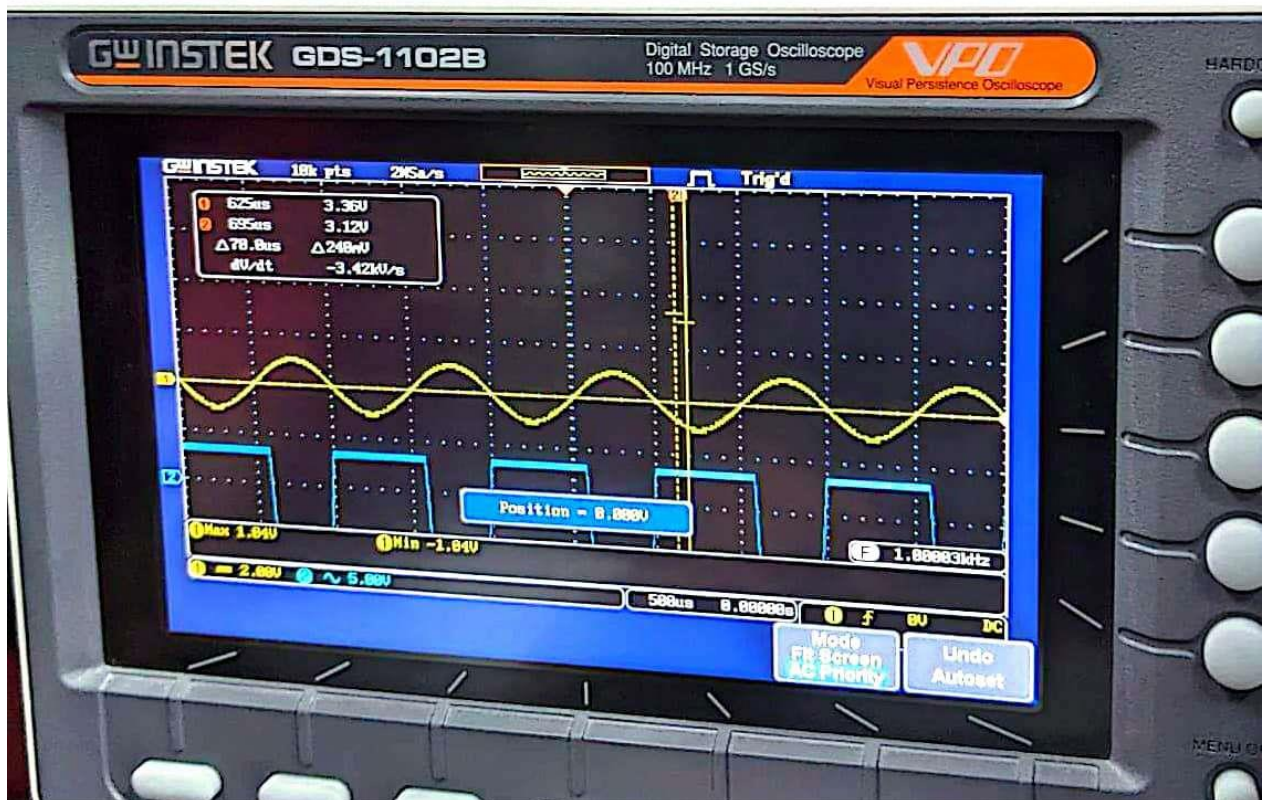


CS Scanned with CamScanner

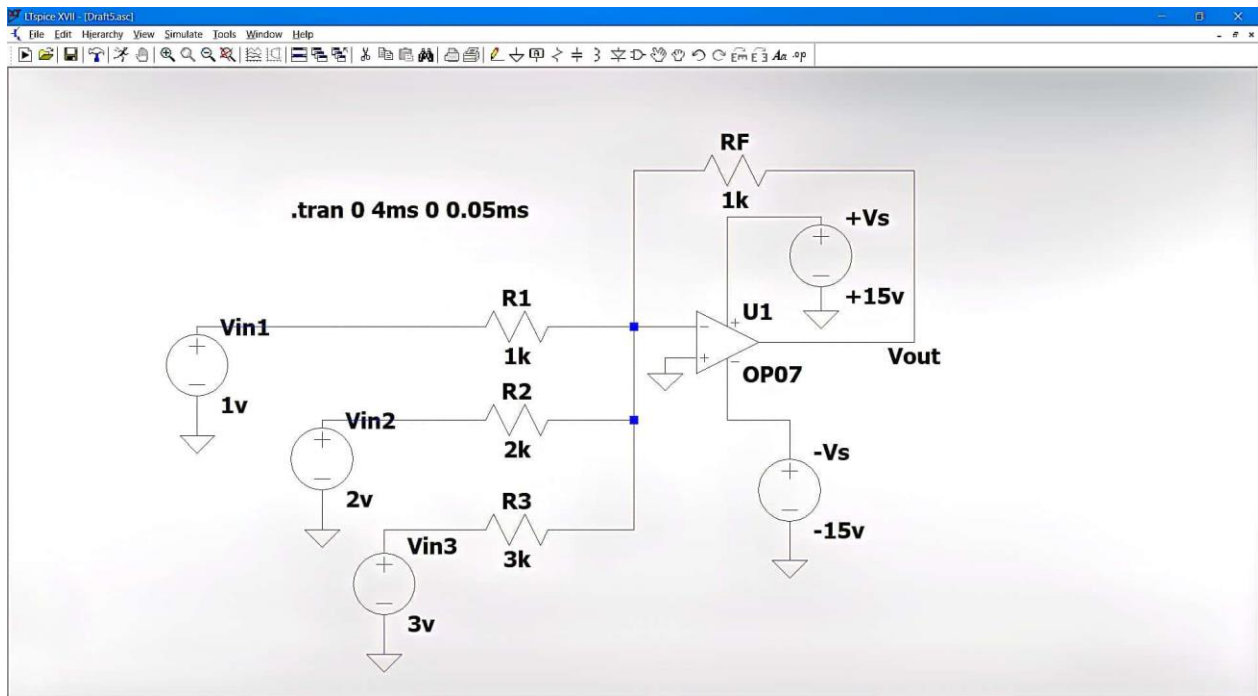
5. screenshots of circuits from simulation part:



CS Scanned with CamScanner

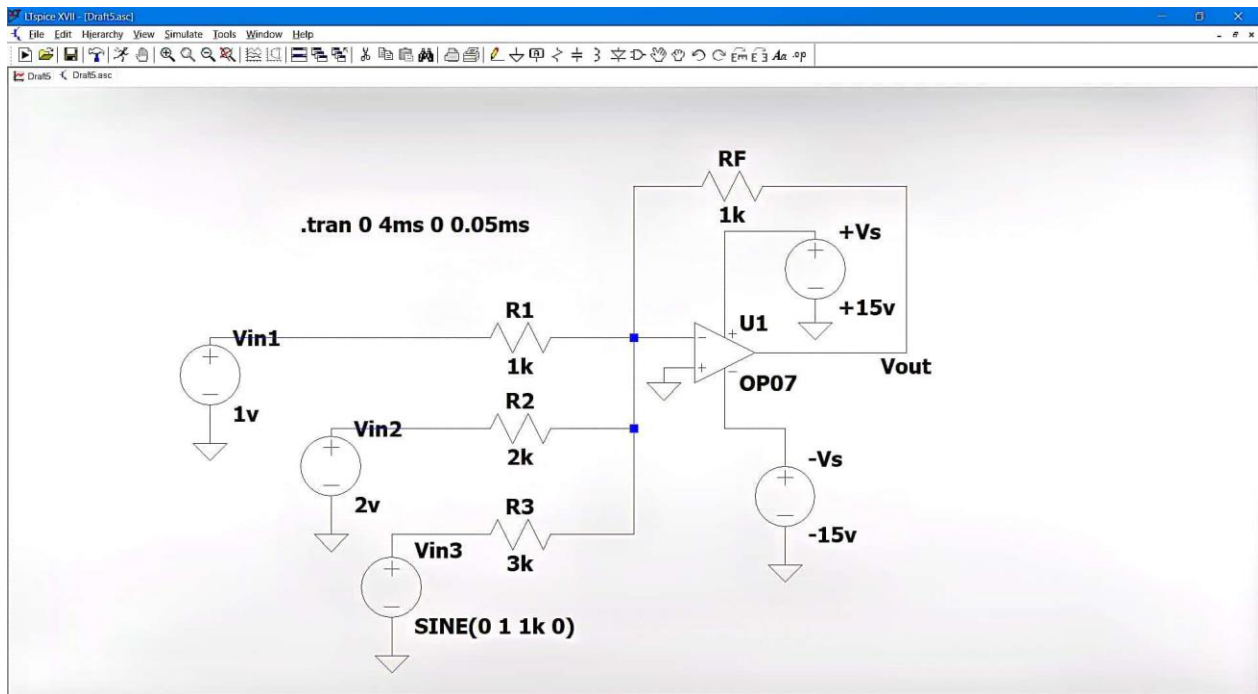


CS Scanned with CamScanner

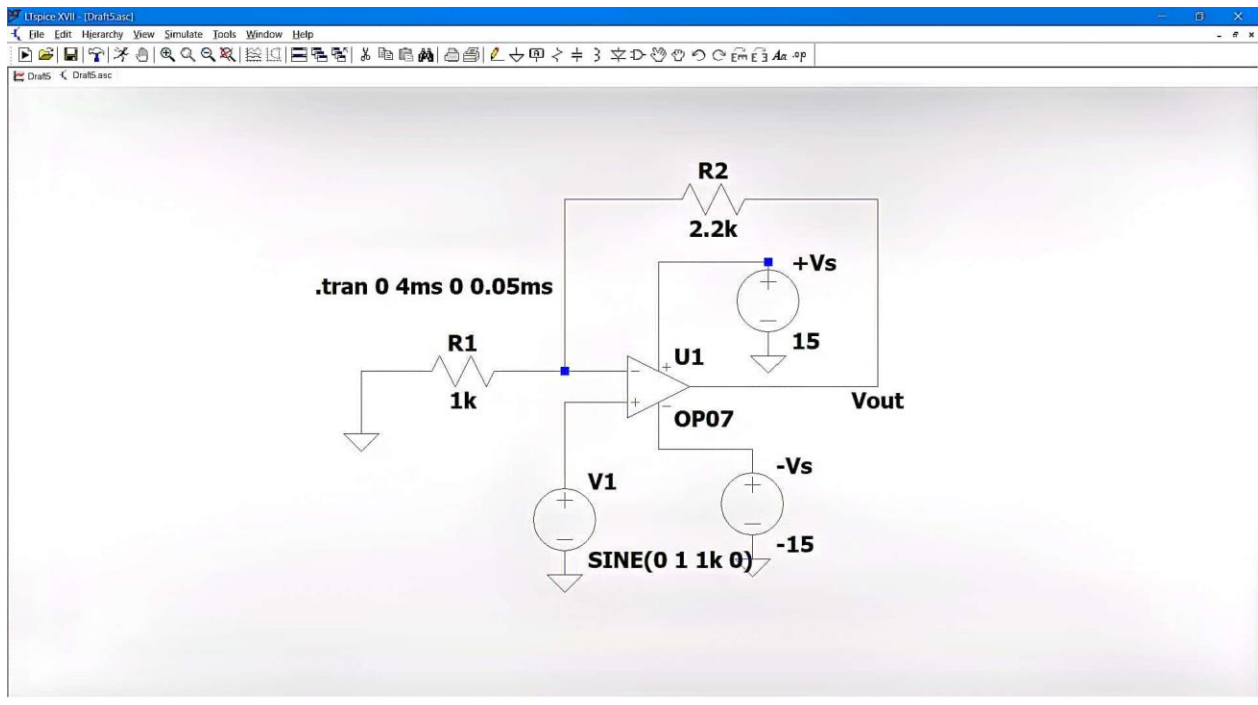


CS Scanned with CamScanner


6. generated graph from simulation part:

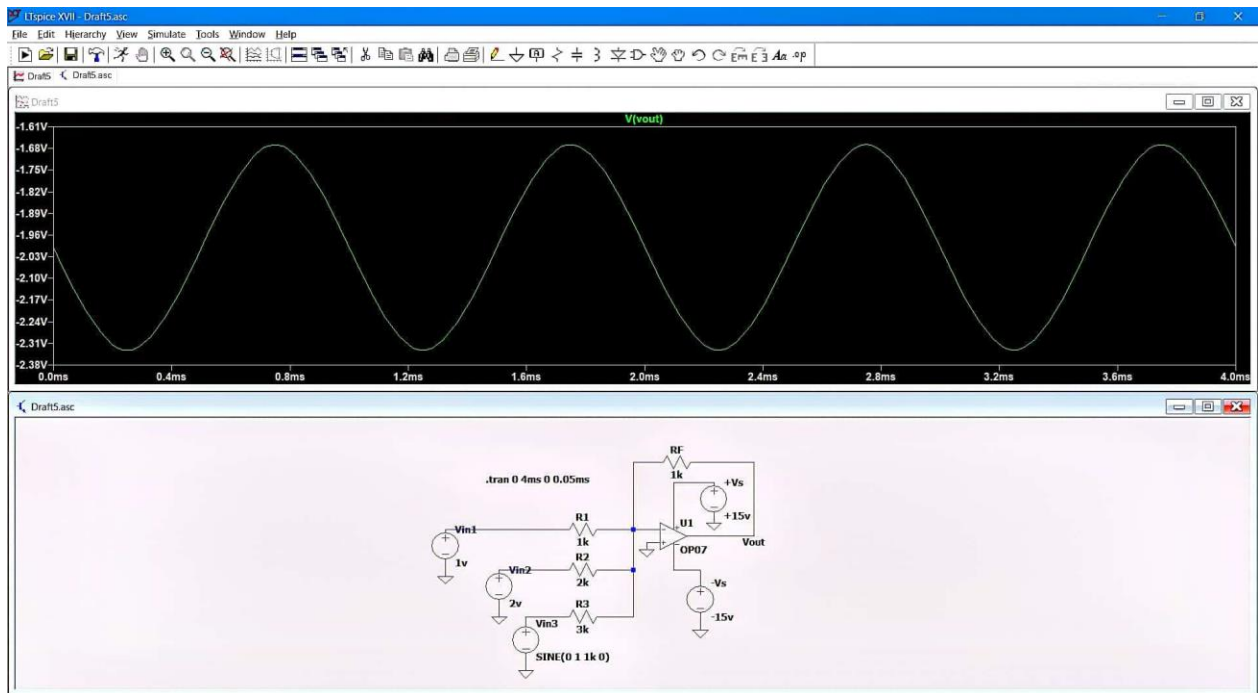

CS Scanned with CamScanner

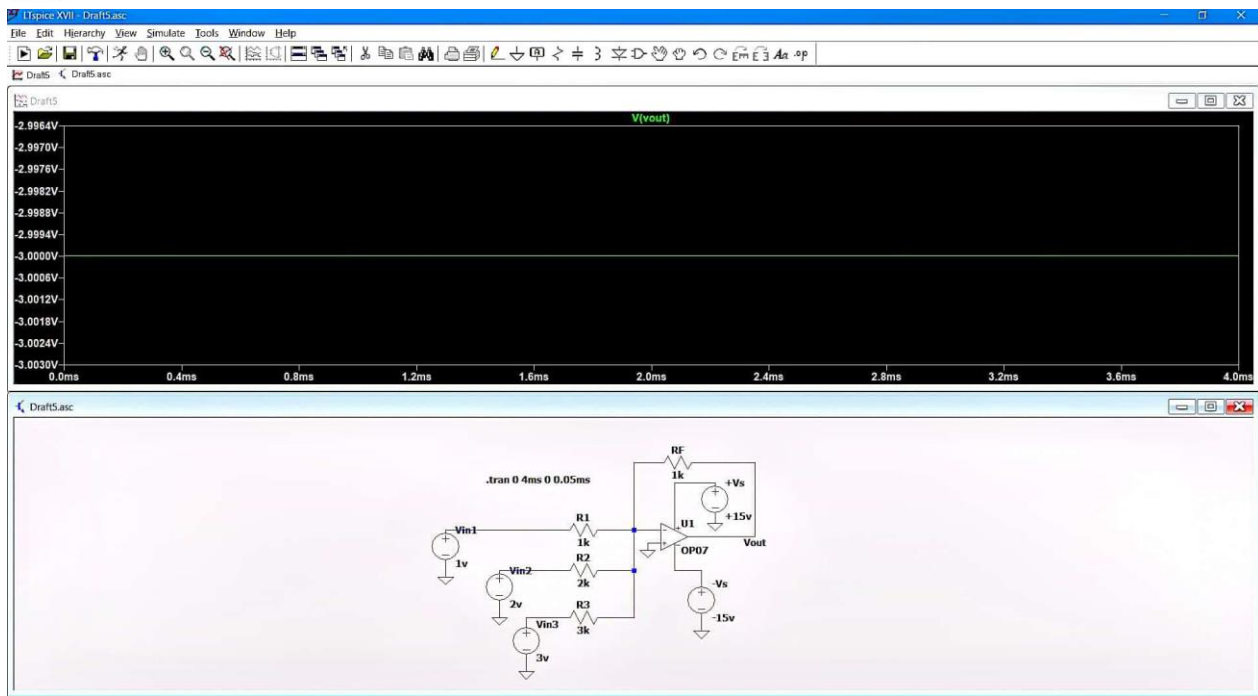

CS Scanned with CamScanner

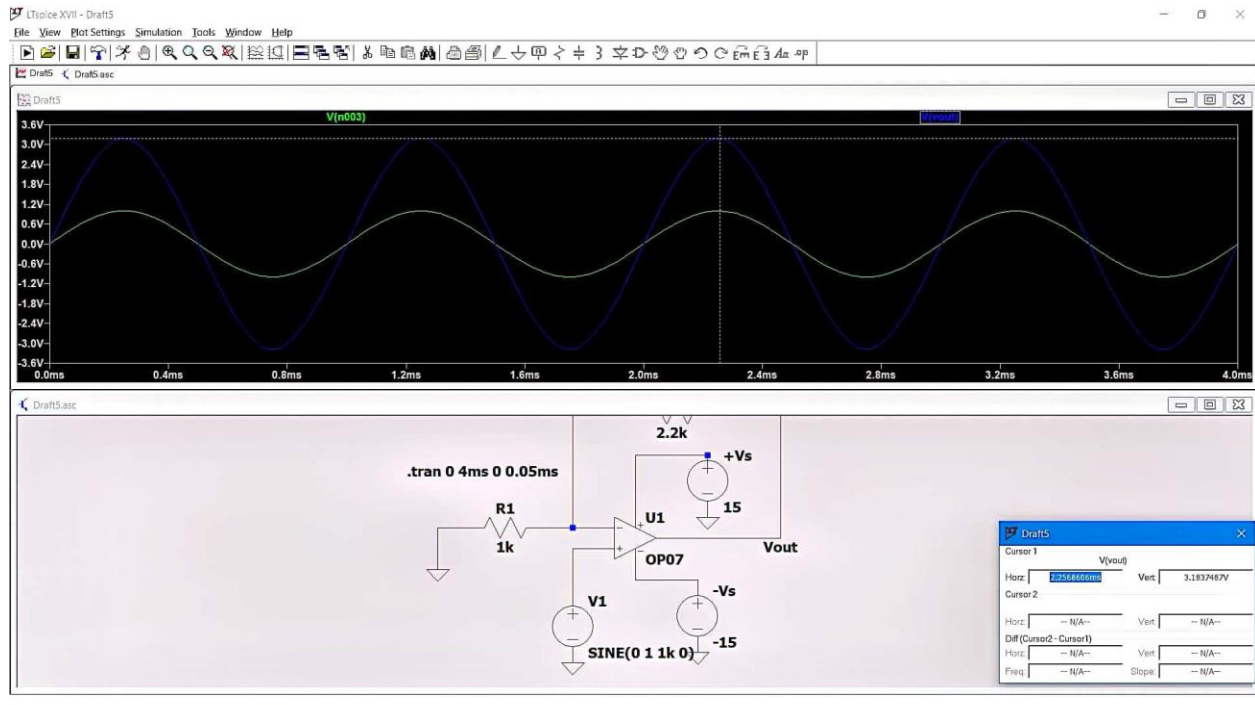

7. calculations:

For non inverting amplifier:

$$V_{out} = (1 + R_2/R_1) * V_i; \text{ where gain} = (1 + R_2/R_1)$$

And from the simulation the peak output voltage,

$V_{output_peak} = 3.18375$ volt which is almost close to gain, $(1 + 2.2/1 = 3.2)$ volt.

8. Discussions:

For inverting amplifier, we can say that it is clear that a feedback signal is provided in the operational amplifier so that the circuit can perform the closed loop operation. It may also be noted that the feedback provided is the negative one, which increases the accuracy of operation of the circuit. Inverting amplifiers are used in a number of applications like phase shifter, integration, signal balancing, mixer circuits, etc.

And for non-inverting amplifier, we can say that the input signal is applied at the non-inverting terminal, while the feedback is provided at the inverting terminal. Thus, the non-inverting amplifier has a negative feedback. Non-inverting amplifiers are used in circuits where high input impedance is required. They are used as a voltage follower,

isolation of cascaded circuits, to perform mathematical simulations, etc. Moreover, the most significant difference is that an inverting amplifier introduces a phase shift of 180° between the input and output signals, whereas a non-inverting amplifier has 0° phase shift (nophase shift) between input and output signals. Both inverting and non-inverting amplifiers use negative feedback which increases the controllability of the gain of the amplifier.