

CSE 260 Lab Report

Experiment Name : Familiarization of
Fundamental Logic Gates.

Submitted by :

Name : Shihab Muhtasim

ID : 21301610

Section : 01

Date : 30/11/2021

Experiment Name : Familiarization of fundamental logic Gates.


Objective :

1. To get familiarized with fundamental logic gates and demonstrate the input - output relationship of 2-input AND (IC-7408), OR (IC-7432) and NOT (IC-7404) gates by constructing their truth tables.
2. To get familiarized with other logic gates like NAND (IC-7400), NOR (IC-7402), XOR (IC-7486) and XNOR (IC-74266).


Required Components :

- | | |
|------------------------|-------------|
| 1. Logicprobe (output) | 5. Not gate |
| 2. Logicstate (input) | 6. NOR gate |
| 3. And gate | 7. XOR gate |
| 4. OR gate | |


Experimental setup:

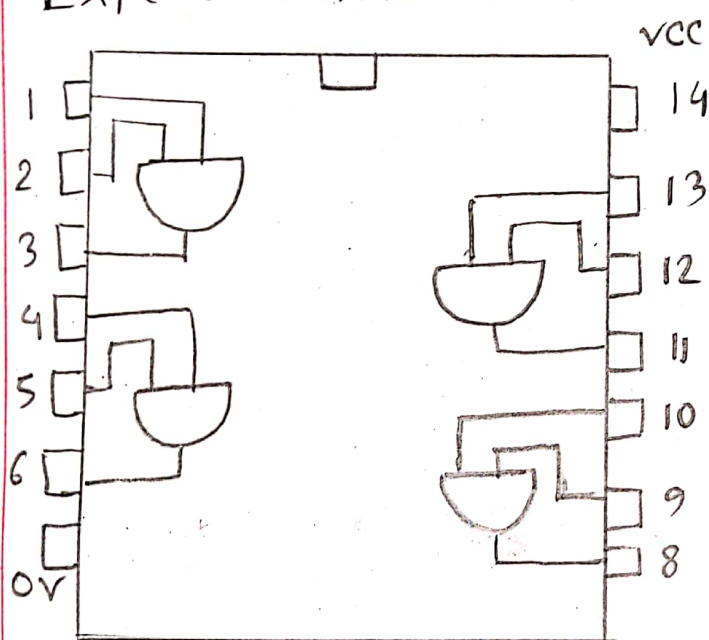


Pin- 7408 (AND gate)

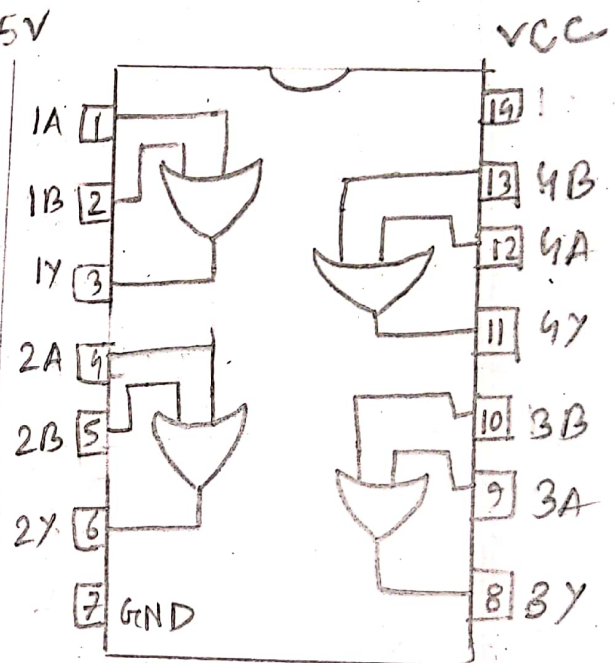


Pin 7432 (OR gate)

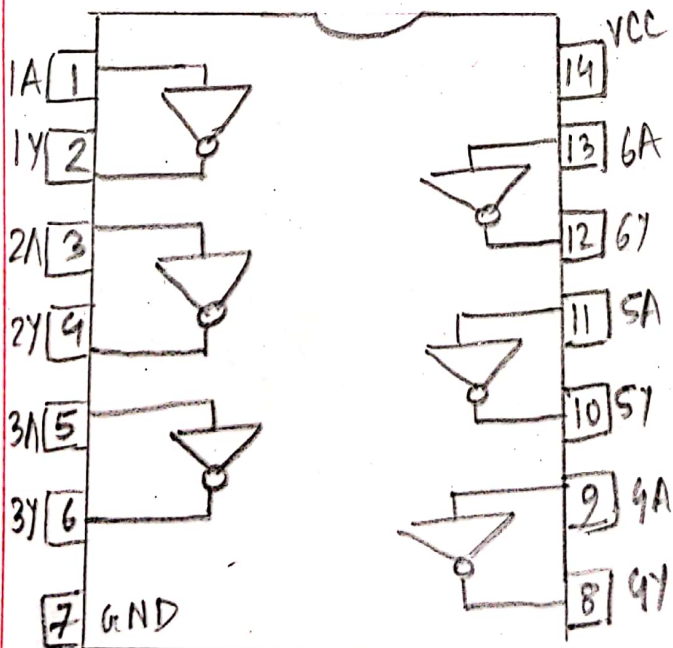


Pin 7404 (NOT gate)

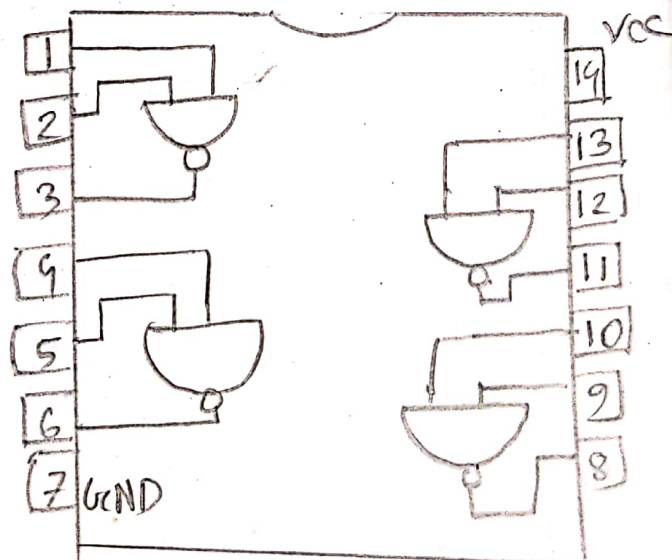


Pin 7400 (NAND gate)

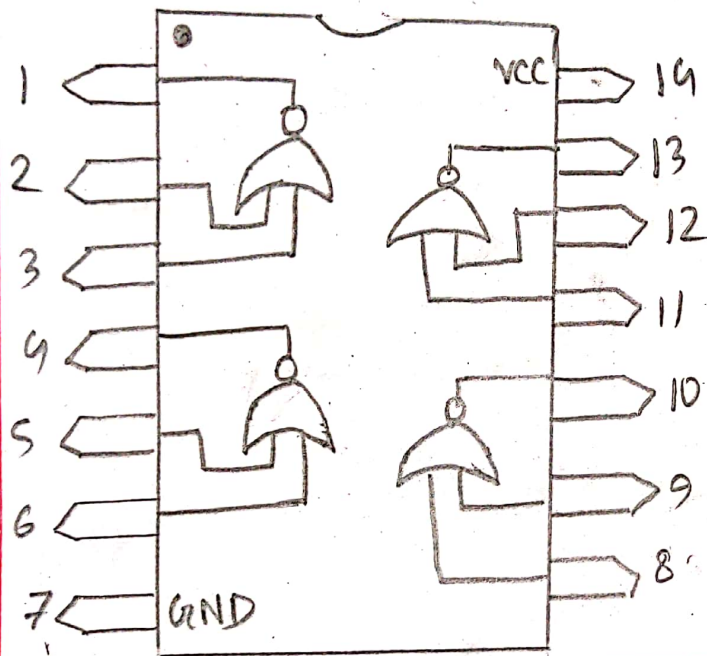

Pin layout of 7402 (NOR gate)

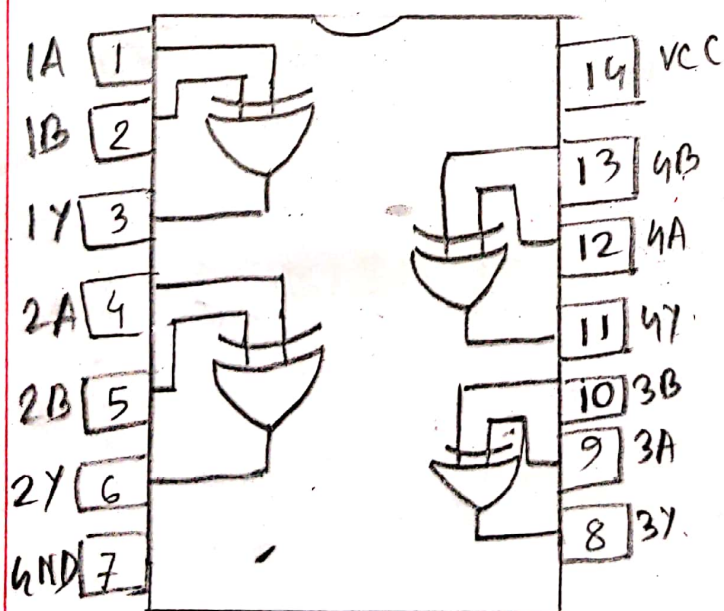

Pin layout of 7486
XOR gate

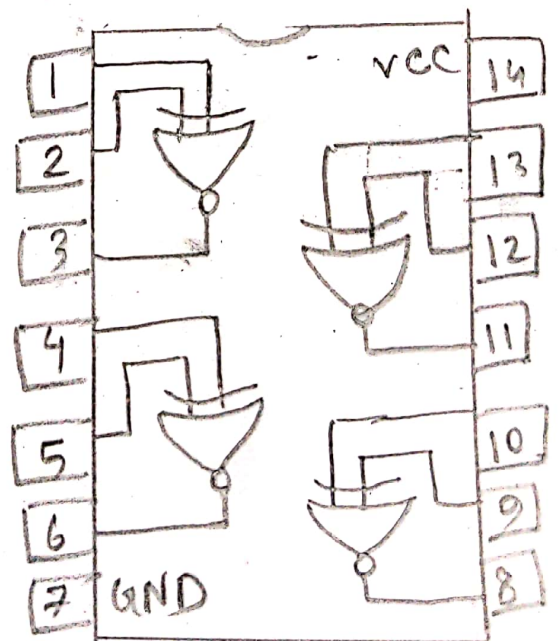

Pin layout of
74266 (X-NOR gate)

Results (Truth Table) :

1. AND Gate (IC-7408) :

A	B	output
0	0	0
0	1	0
1	0	0
1	1	1

2. OR Gate (IC-7432) :

A	B	output
0	0	0
0	1	1
1	0	1
1	1	1

3. Not Gate (IC-7404) :

Input	Output
0	1
1	0

4. NAND Gate (IC-7400) :

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

5. NOR Gate (IC-7402) :

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

6. XOR Gate (IC-7486) :

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

7. XNOR Gate (IC-74266) :

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

Discussions : In our CSE 260 lab report 1, we have learnt the basic use of the software protius. In this process of getting familiarized with fundamental logic gates I was able to see proof of the truth tables of logic gates that we have learnt before. I was able to see results of different combinations in different logic gates. In addition, I did not face any problems in this project. Protius seemed a very fascinating software to me.