



CSE251

Electronic Devices and Circuits

Semester: Fall 22

**Exp -05: Study of I-V Characteristics of BJT and
Implementation of CE Amplifier Using BJT**

Submitted By

Name: Shihab Muhtasim

ID: 21301610

&

Tasnia Jannat Ayesha

ID: 21301611

Group: 05

Cooperated by

ID: 20101443, 20201066

Date of performance: 31/10/22

Date of Submission: 21/11/22

2. Circuit Diagrams:

Diagram 1:

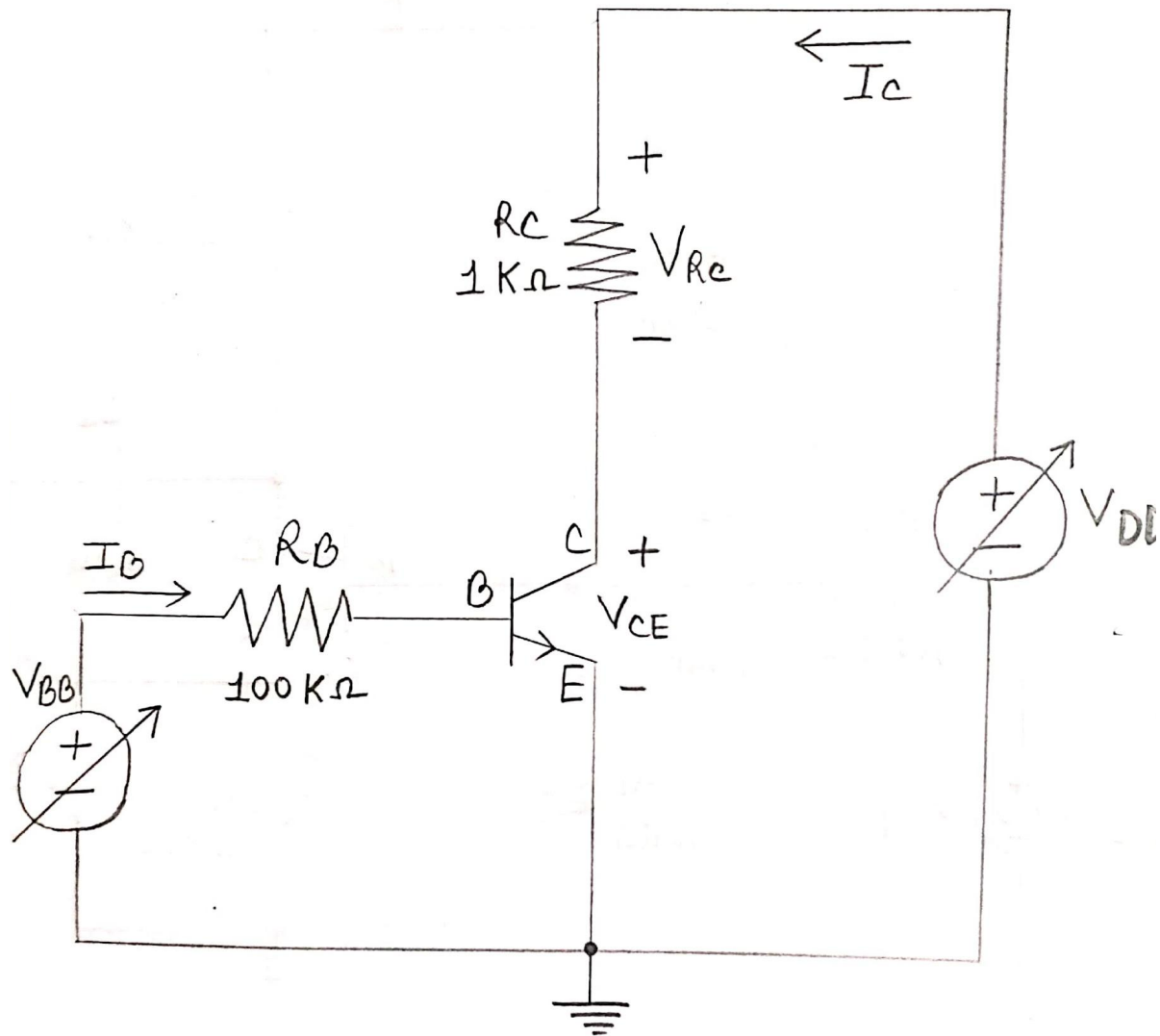


Figure: Circuit for determining the IV characteristic (I_C vs. V_{CE}) of BJT

Diagram 2:

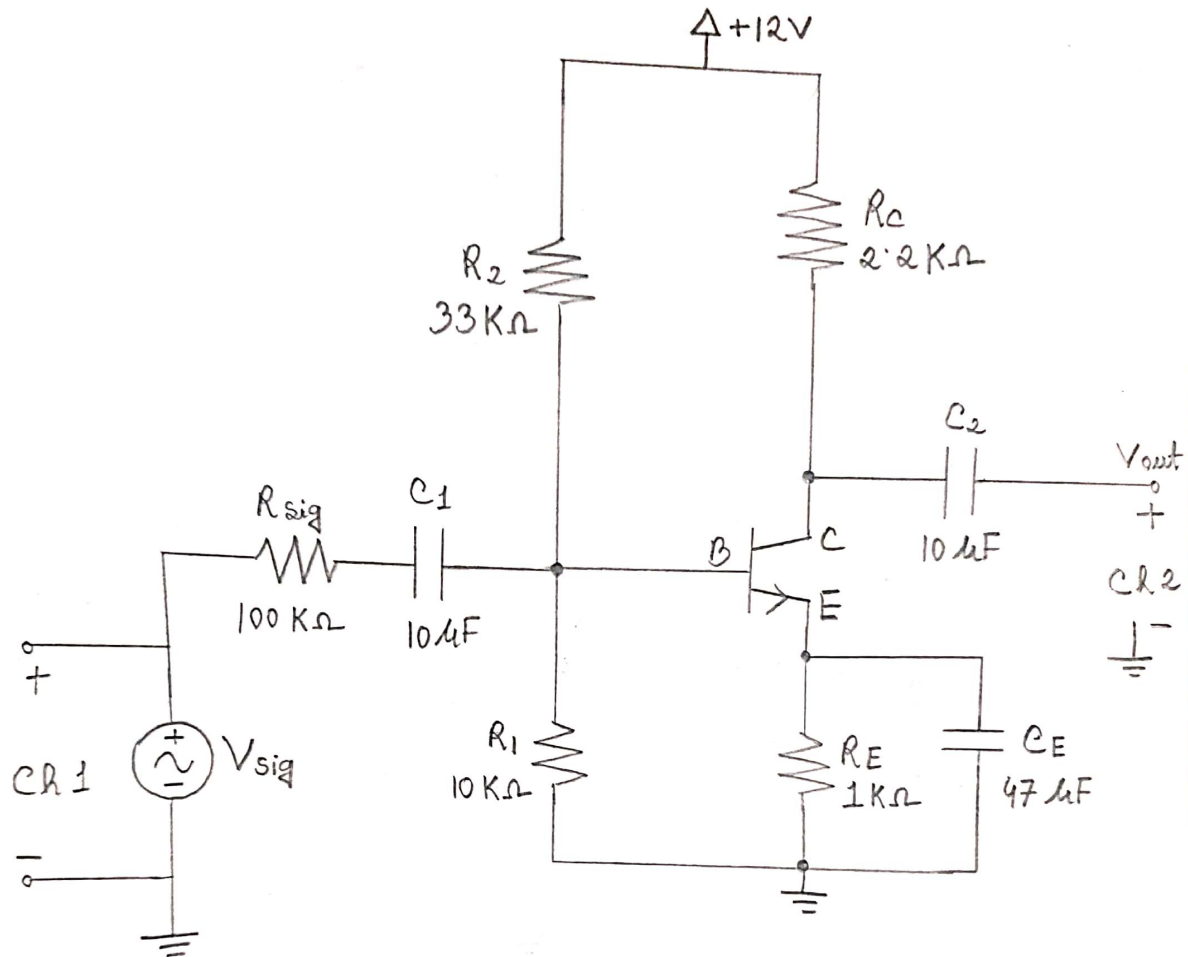


Figure : BJT CE Amplifier Circuit

3. Signed Data Sheets and Calculations:

DATA TABLE 1: OUTPUT I-V CHARACTERISTICS

Actual value of $R_B = 97.5 \text{ k}\Omega$ and $R_C = 0.983 \text{ k}\Omega$ (using multimeter)

1. $V_{BB} = 2 \text{ V}$

V_{DD} (V)	$I_B = \frac{V_{BB} - 0.7}{R_B \text{ (k}\Omega\text{)}} \times 10^3$ (μA)	V_{CE} (V)	V_{RC} (V)	$I_C = \frac{V_{RC}}{R_C \text{ (k}\Omega\text{)}}$ (mA)	$\beta = \frac{I_C}{I_B}$
0.0	$13.33 \text{ } \mu\text{A}$ $= 13.33 \times 10^{-3} \text{ mA}$ $= 0.0133 \text{ mA}$	0.0148	0.0053	0.005392	0.4054
0.1		0.0226	0.0297	0.0302	2.2707
0.2		0.0467	0.1126	0.1146	8.6165
0.3		0.051	0.1792	0.1823	13.7067
0.4		0.0596	0.2555	0.2599	19.5413
0.5		0.0658	0.359	0.3652	27.4586
0.6		0.0746	0.440	0.4476	33.6541
0.7		0.0787	0.565	0.5748	43.2181
0.8		0.0835	0.664	0.6755	50.7895
0.9		0.0869	0.754	0.7670	57.6692
1.0		0.0902	0.857	0.8718	65.5489
2.0		0.1204	1.835	1.8667	140.3534
3.0		0.146	2.783	2.8311	212.8647
4.0		0.181	3.75	3.8149	286.8346
5.0		0.497	4.55	4.6287	348.0225
6.0		1.412	4.60	4.6800	351.8797
7.0		2.298	4.68	4.7609	357.9624
8.0		3.264	4.73	4.8118	361.7895
9.0		4.29	4.78V	4.8627	365.6165
10.0		5.14	4.80V	4.8830	367.1428

2.556V

2. $V_{BB} = 2.5 \text{ V}$

V_{DD} (V)	$I_B = \frac{V_{BB} - 0.7}{R_B [k\Omega]} \times 10^3$ (μA)	V_{CE} (V)	V_{RC} (V)	$I_C = \frac{V_{RC}}{R_C [k\Omega]}$ (mA)	$\beta = \frac{I_C}{I_B}$
0.2	$= 19.0359 \mu\text{A}$ $= 19.0359 \times 10^{-3}$ mA	0.0288	0.0858	0.0873	4.586
0.5		0.0543	0.3169	0.3224	16.9364
1.0		0.0822	0.885	0.9003	47.2948
2.0		0.1086	1.842	1.8739	98.4403
3.0		0.13	2.819	2.8678	150.652
4.0		0.1523	3.81	3.8759	203.61
5.0		0.1821	4.81	4.8932	257.051
6.0		0.265	5.71	5.8087	305.144
7.0		0.976	5.98	6.0834	319.5751
8.0		1.865	6.04	6.1444	322.7796
9.0		2.812	6.13	6.2360	327.5915
10.0		3.698	6.26	6.3683	334.5416
11.0		4.730	6.30	6.4089	336.6744
12.0		5.650	6.36	6.4699	339.8788
13.0		6.640	6.41	6.5208	342.5527
14.0		7.560	6.47	6.5819	345.7625

~~Am~~
31.10.22

DATA TABLE 2: COMMON EMITTER AMPLIFIER


Measured values of resistances (Using multimeter)				
R_{sig} (k Ω)	R_1 (k Ω)	R_2 (k Ω)	R_C (k Ω)	R_E (k Ω)
97.5	9.98	32.77	2.178	0.989

Amplitude of the input signal, v_{sig} (from signal generator) (mV)	Amplitude of the output signal, v_{out} (from oscilloscope) (V)	Gain = $\frac{ v_{out} }{ v_{sig} }$
244.0 mV 96.8	460 mV	4.83

~~Handwritten signature~~
1.10.22


4. Graphs of I_C vs V_{ce} :

For $V_{bb} = 2V$:

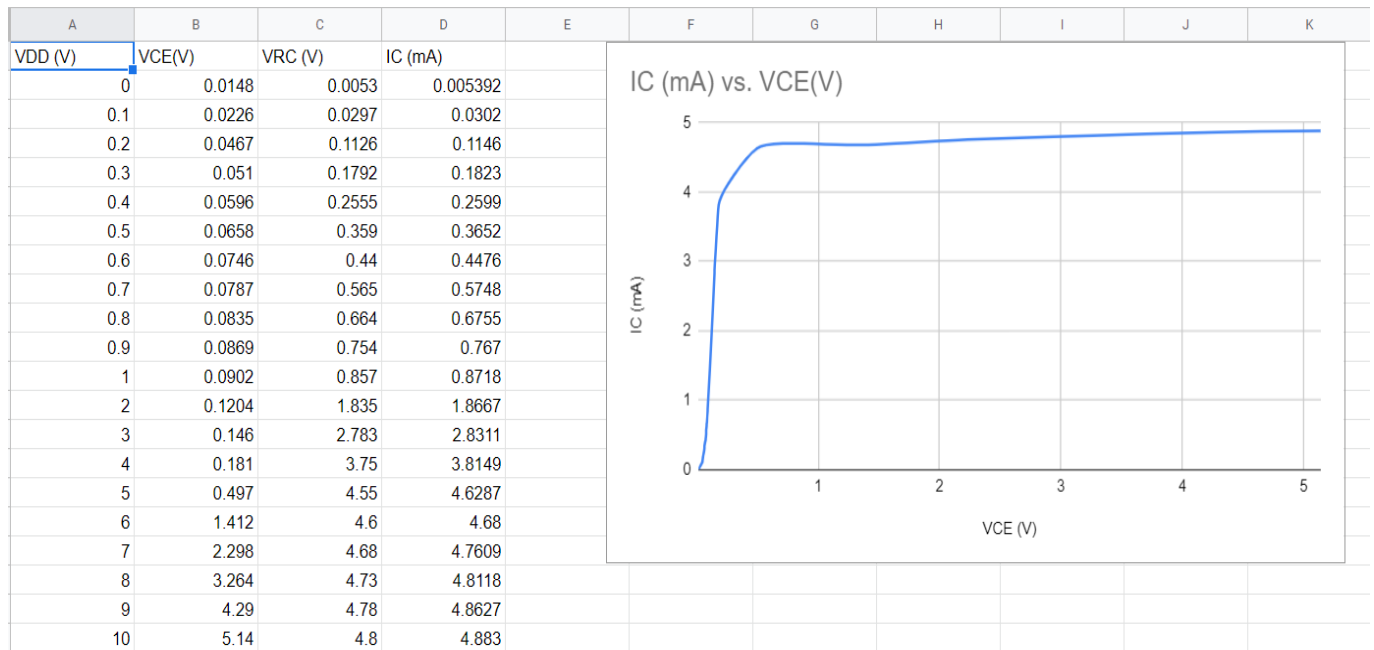

For $V_{bb} = 2.5\text{V}$:

VDD (V)	VCE (V)	VRC(V)	IC (mA)
0.1	0.0288	0.0858	0.0873
0.5	0.0543	0.3169	0.3224
1	0.0822	0.885	0.9003
2	0.1086	1.842	1.8739
3	0.13	2.819	2.8678
4	0.1523	3.81	3.8759
5	0.1821	4.81	4.8932
6	0.265	5.71	5.8087
7	0.976	5.98	6.0834
8	1.865	6.04	6.1444
9	2.812	6.13	6.236
10	3.698	6.26	6.3683
11	4.73	6.3	6.4089
12	5.65	6.36	6.4699
13	6.64	6.41	6.5208
14	7.56	6.47	6.5819

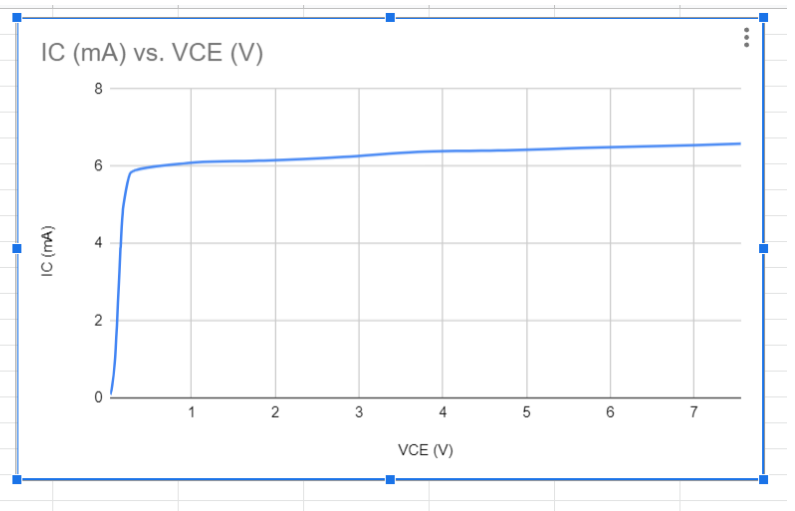

5. LT spice Circuit Diagrams:

Diagram 1:



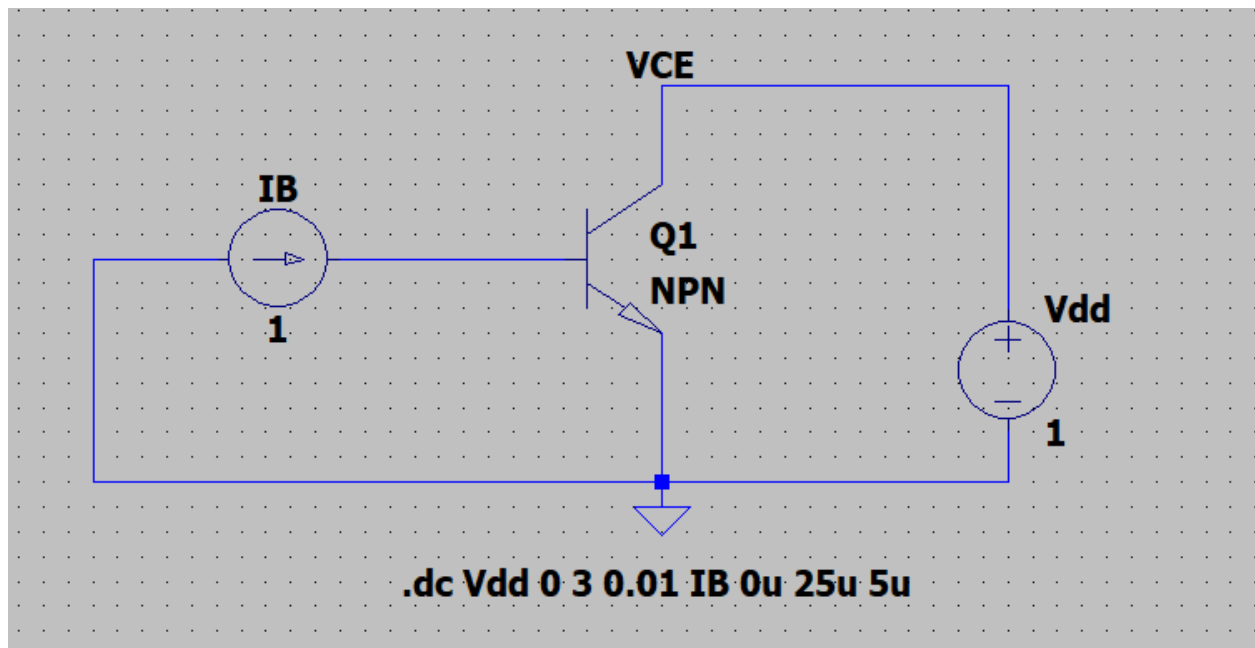


Diagram 2:

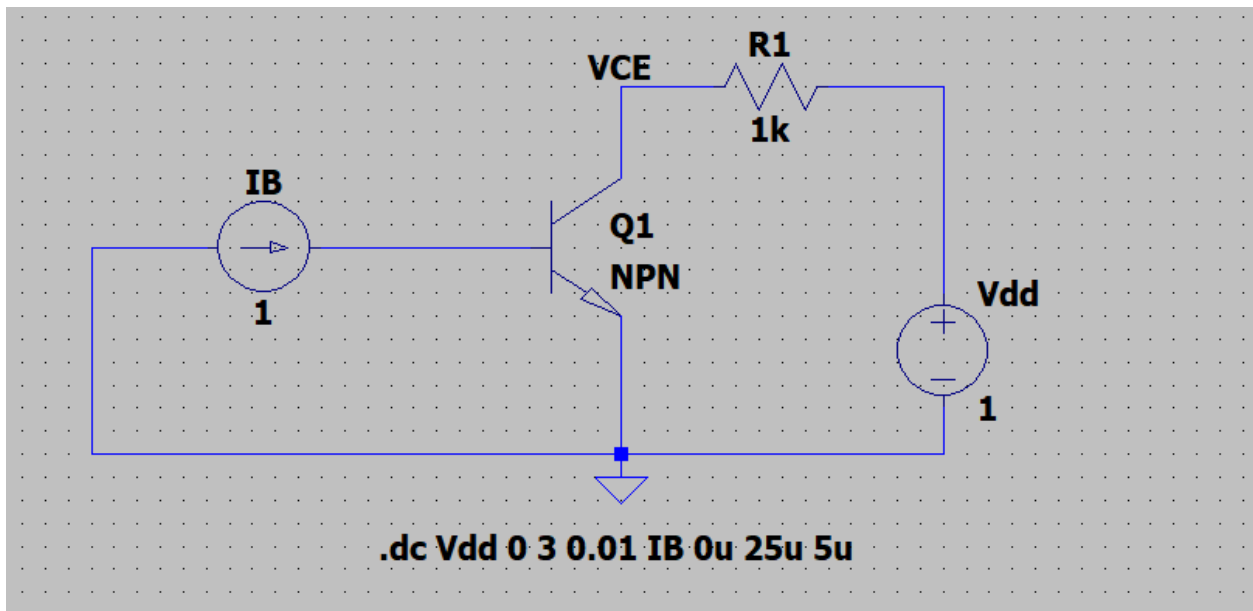


6. Plots Generated in LT spice simulation:

Plot 01:

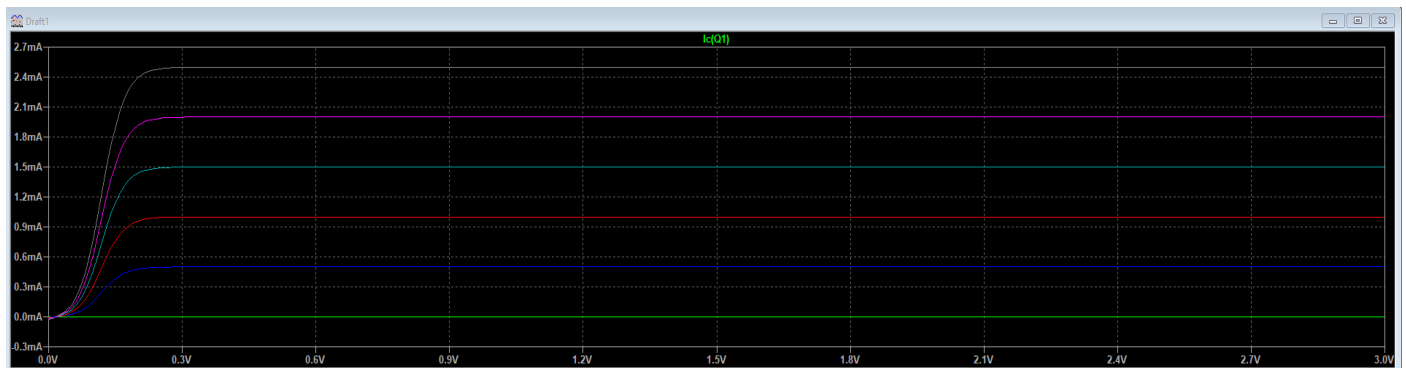

Plot 2:

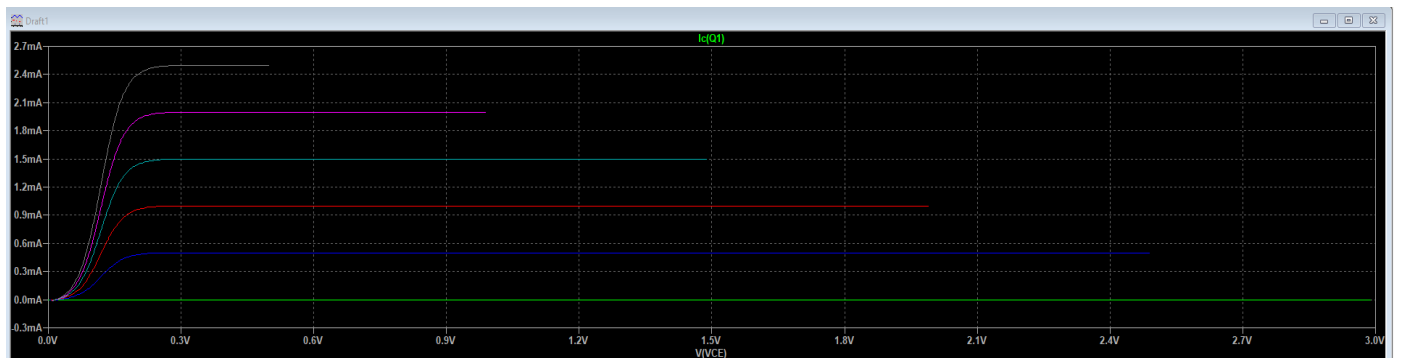

7. Discussion:

I_C varies with changes in V_{ce} while I_B is held constant, as seen by the I-V characteristics produced from the datasets of the hardware experiment of circuit 1. We can observe from the graph that it was created that the collector current starts off rapidly increasing until becoming almost constant. Three regions can be identified on this graph: When V_{ce} is increased by a specific amount and the output current stays the same, this region is known as the active region. Second, the saturation region, where I_C rapidly increases from 0 to the active region. Third is the Cut-off Region, where there is almost no current. The output I-V characteristics show that, in the active region, I_C increases with an increase in I_B if V_{CE} is maintained constant. In fact, the relationship between I_C and I_B in active mode is linear, and the following equation can be used to illustrate it: $I_C = \beta I_B$.

In the second plot of the Lt spice diagrams, we could notice that the I_c (collector current) was not reaching the end of V_{ce} in the plot. We know that, $V_{ce} = V_{dd} - I_c \cdot R_c$. Hence, when I_b is increased I_c also increases as I_b initially passes through the BJT to provide collector current. Hence, V_{ce} decreases due to more I_c . In the same way, when I_b is decreased, I_c is also decreased. Hence, in that case, V_{ce} is increased. However, after a time we cannot reach our collector current for a higher V_{ce} as it keeps decreasing.

We noticed some of the discrepancies in the hardware experiment such as some values we measured were not theoretically accurate. For some of the inputs, we measured V_{ce} and V_{rc} which were not theoretically accurate. Although our final graph generated after smoothing out looked correct yet some of the data were faulty due to the human and hardware errors we usually see in hardware experiments. As per precautions, we were careful about how much voltage we were giving as input so that no device gets harmed in the process.