

## Brac University

Semester: Summer 2022

Course No: CSE251

Course Title: Electronic Devices and Circuits

Section: 2 to 14

Midterm

Full Marks: 40



Time: 2 hours

Date: July 27, 2022

Answer **any 4** questions. All the questions carry equal marks.

## Question 1 [CO1]


10

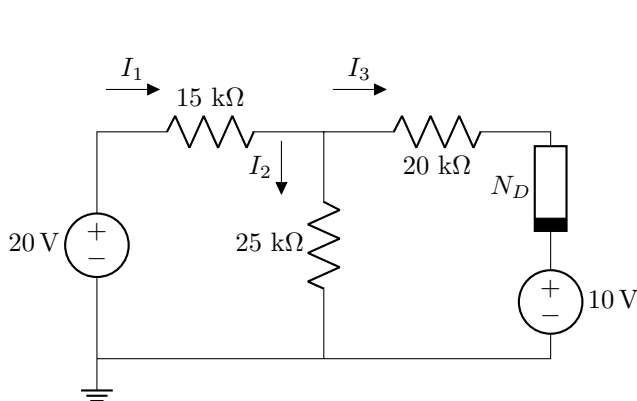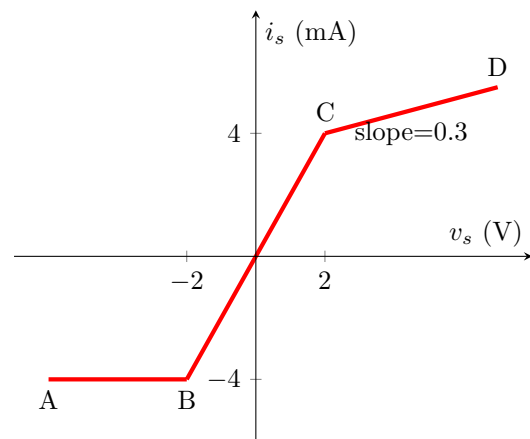(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear regions (AB, BC, CD) shown in the IV characteristics of the non-linear device  $N_D$  (Figure (b)) and **calculate** the model parameters. [3]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage (hint: use Figure (b) and answers from previous part). [1+1]
- Show** the alternative representation of the circuit in Figure (a). [1.5]
- Assume that the non-linear device  $N_D$  has been replaced with its equivalent linear device of segment BC. **Draw** the alternative representation of the circuit again by replacing  $N_D$ . [0.5]
- Apply** KVL and KCL on the circuit of part (d) to calculate the values of  $I_1$ ,  $I_2$ , and  $I_3$ . [3]

## Question 2 [CO2]

10

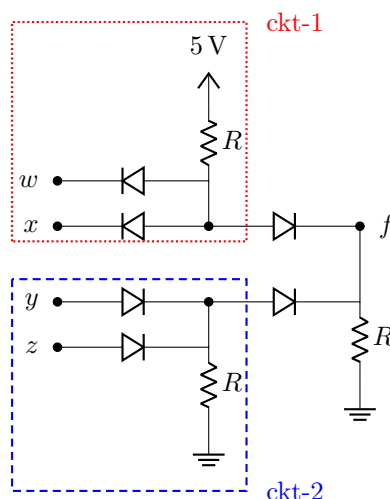

**Part a:** Analyze of the circuit on the left. Assume all the diodes are ideal diodes.

- Assuming  $w$ ,  $x$ ,  $y$ ,  $z$  are boolean variables, **analyze** the circuit to find an expression of ckt-1 (the dotted ... rectangle) in terms of  $w$  and  $x$ , and an expression of ckt-2 (the dashed - - rectangle) in terms of  $y$  and  $z$ . [2+2]
- Analyze** the circuit again to find an expression of  $f$  in terms of  $w$ ,  $x$ ,  $y$ ,  $z$ . Use results from (a). [2]

**Part b:** Jawad has created a new ride sharing app - *Juber*. When you request a Juber ride, Juber's algorithm generates 4 signals to determine whether it will be forwarded to a rider. (1) Signal F determines if the rider is free. (2) Signal R determines if the rider is within close proximity. (3) Signal G determines if

## Set: 01

the rider has good rating. (4) Signal N determines if the rider is new. If both conditions 1 and 2 are satisfied, **and** either condition 3 or condition 4 are satisfied, the request will be connected


(c) **Deduce** the logic function using boolean signals F, R, G and N to implement Juber's algorithm. [2]

(d) **Design** a circuit using ideal diode logic gates to implement this function. [2]
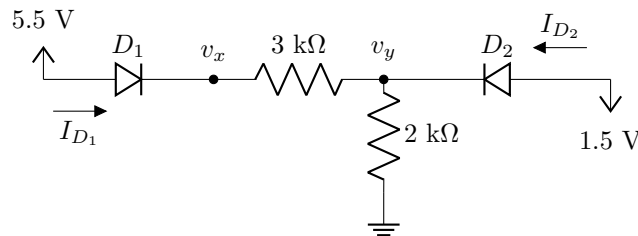
### Question 3 [CO1]

7+3

**Analyze** the circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$  [ $V_{D0} = 0.5$  V]. You must **validate** your assumptions.



### Question 4 [CO2]

10

The input of a half-wave rectifier is a sinusoidal voltage with peak  $V_M = 10$  V and frequency 60 Hz, and output load resistance is  $R = 2$  kΩ. Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7$  V.

(a) Briefly **explain** the purpose of a rectifier and **describe** its operation. [2]

(b) **Show** the input and output waveforms. [2]

(c) **Calculate** the DC value of the output voltage. [1]


Now after connecting a capacitor in parallel with the load, the output becomes a ripple voltage  $V_{out} = V_{DC} \pm 0.2$  V.

(d) **Calculate** the peak-to-peak ripple voltage, and from that, the value of the capacitor. [1+2]

(e) **Calculate** the average of the output voltage  $V_{DC}$  after connecting the capacitor. [2]

### Question 5 [CO1, CO2]

10

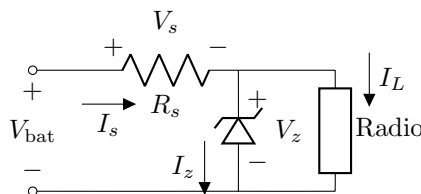

The circuit above is a voltage regulator used to power a car radio (which requires  $\approx 9$  V) from the car battery,  $V_{bat}$  whose voltage may vary between 11 and 13.6 V. The current in the radio,  $I_L$ , will vary between 0 (off) to 9 mA (full volume). The Zener diode in the circuit is specified with parameter  $V_{z0} = 9$  V,  $r_z = 0.05$  kΩ, and  $I_{zk} = 1$  mA.

(a) **Identify** the worst-case conditions and **calculate** the Zener current ( $I_z$ ), Zener voltage ( $V_z$ ), the input voltage ( $V_{bat}$ ), and the load current ( $I_L$ ) in this worst-case scenario. [1+1+1+1+1]

(b) **Calculate** the current ( $I_s$ ) and the voltage ( $V_s$ ) the input resistor  $R_s$  in the worst-case scenario. [2]

(c) **Design** the circuit, i.e., find the value of  $R_s$ , such that even in the worst-case scenario voltage regulation is maintained. Calculate the line regulation for this circuit. [2+1]