

Assignment 3

CSE251

Fall 22


Name : Shihab Muhtasim

sec : 13

ID : 21301610

Ans to q no 1

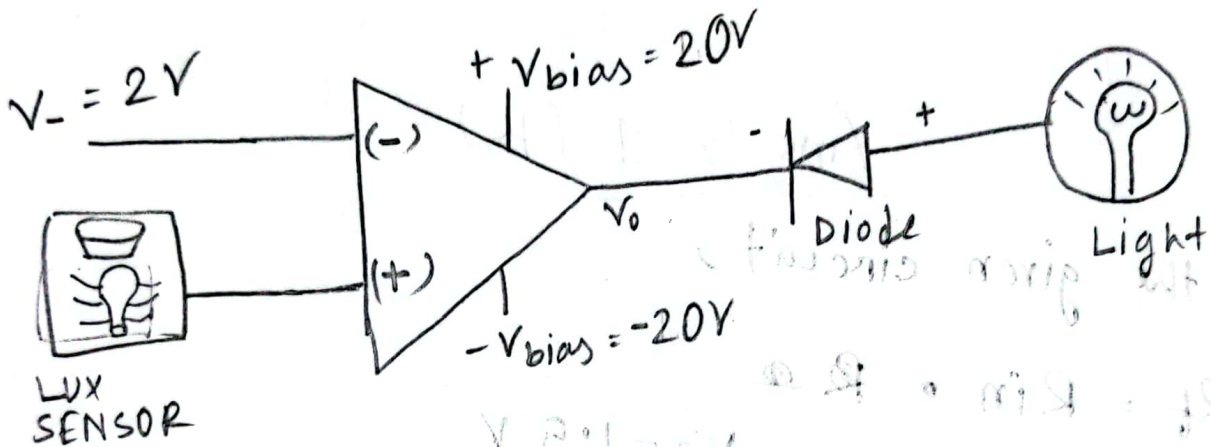Given, $V_{\text{night}}, 0 \text{ lux} = 1 \text{ V}$
 $V_{\text{dusk}}, 20 \text{ lux} = 2 \text{ V}$
 $V_{\text{dawn}}, 80 \text{ lux} = 3 \text{ V}$



At night, $V_+ = 1 \text{ V}$

$$\therefore V_o = A(V_+ - V_-) = A(1 - 2) = -A$$

$\therefore V_o = -20 \text{ V}$; light required to be ON

At dusk, $V_+ = 2$,

here, $V_+ < V_-$ as in dusk, V_+ keeps decreasing from 2 V .

$\therefore V_o = -20 \text{ V}$; light required to be ON.

At dawn, $V_+ = 3 \text{ V}$

$$A(V_+ - V_-) = A(3 - 2) = A$$

$V_o = +20 \text{ V}$; light required to be OFF.

Since the diode is set in reverse bias, current will pass through when V_0 is negative, making the cathode terminal voltage less than the anode and light will turn ON.

Ans to 1 (b)

In the given circuit,

$$R_f = R_{in} \cdot R$$

$$V_1 = 1V, V_2 = 2V, V_3 = 1.5V$$

$$V_{out} = - \left(\frac{R_f}{R_{in}} V_1 + \frac{R_f}{R_{in}} V_2 + \frac{R_f}{R_{in}} V_3 \right)$$


$$= - (V_1 + V_2 + V_3) = - (1 + 2 + 1.5)$$

$$= -4.5 \checkmark$$

$$\therefore V_{out} = -4.5V$$

Ans to or 1 (c) | i)

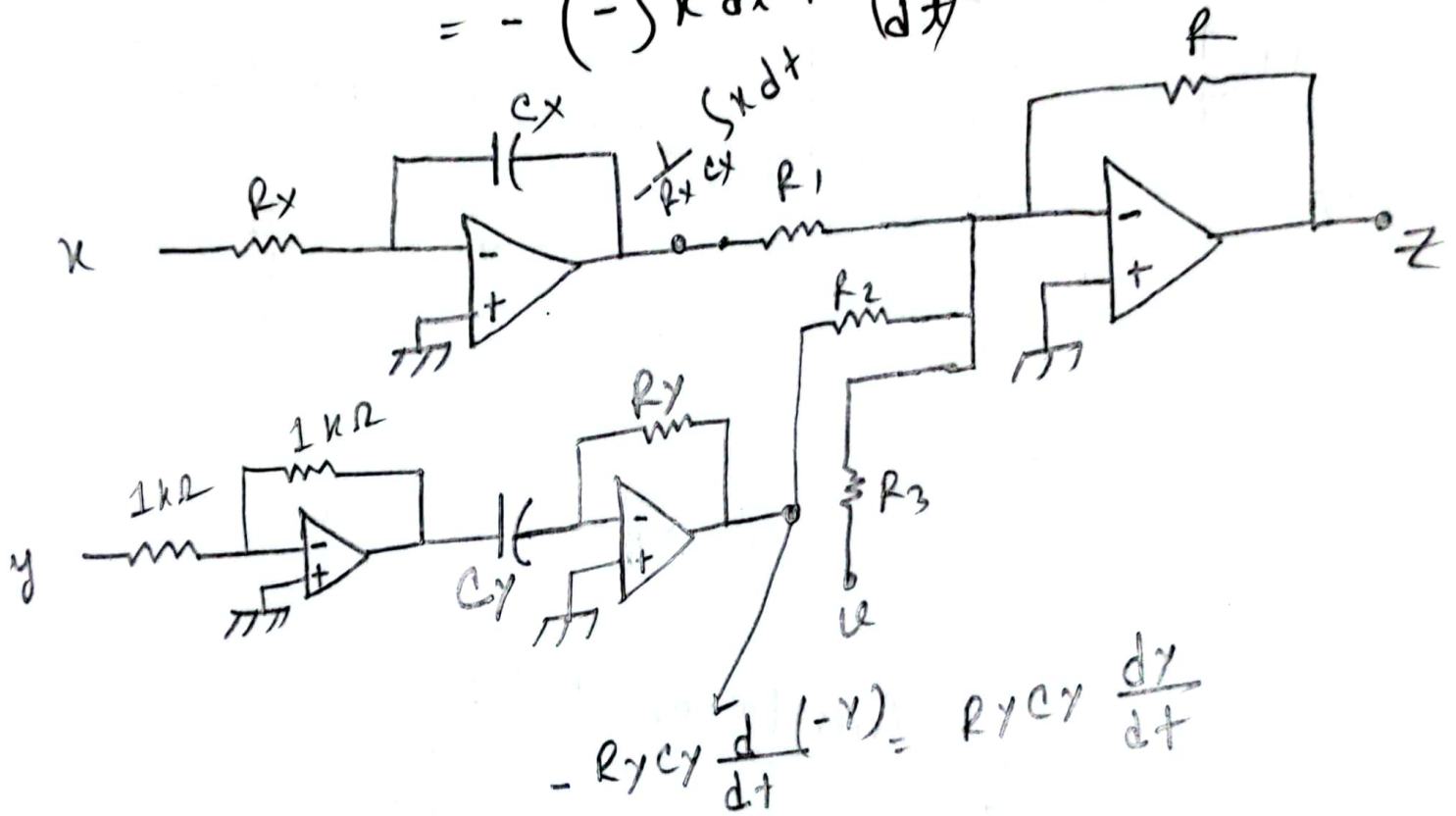Expression, $z = \int x dt - 2 \frac{dy}{dt} - u$
 $= - \left(- \int x dt + \frac{2 \frac{dy}{dt} - 1}{1} u \right)$



Here, $\frac{-1}{R_x C_x} = -1$

Let, $C_x = 47 \mu F$

$R_x = 21.2766 k\Omega$

Again, $-R_y C_y = -1$

Let, $C_y = 47 \mu F$

$R_y = 21.2766 k\Omega$

Again,

$\frac{R}{R_1} = 1, \frac{R}{R_2} = 2, \frac{R}{R_3} = 1$

Let, $R = 10 k\Omega$


$R_1 = 10 k\Omega$

$R_2 = 5 k\Omega$

$R_3 = 10 k\Omega$

Ans to or 1 (c) (ii)


Expression, $y = 12 \text{ mV}$

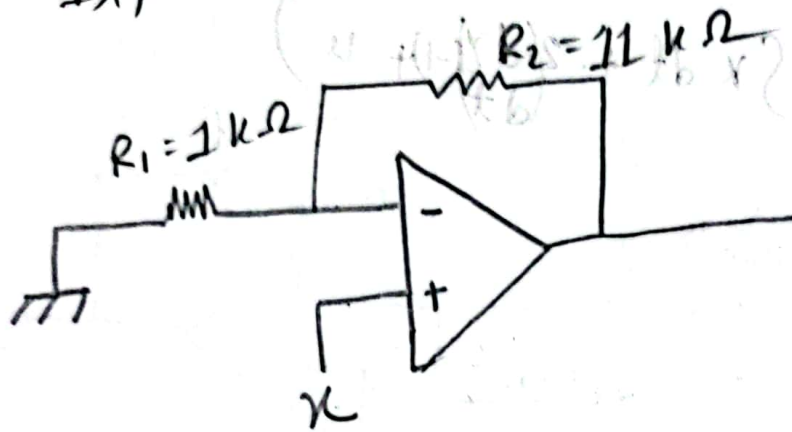

$$\begin{aligned} V_o &= V_i \left(1 + \frac{R_2}{R_1} \right) \\ &= x \left(1 + \frac{11}{1} \right) \\ &= x (1 + 11) \\ &= x (12) \\ &= 12 \text{ mV} \end{aligned}$$

$\therefore y = 12 \text{ mV}$

Ans to or 1 (d)

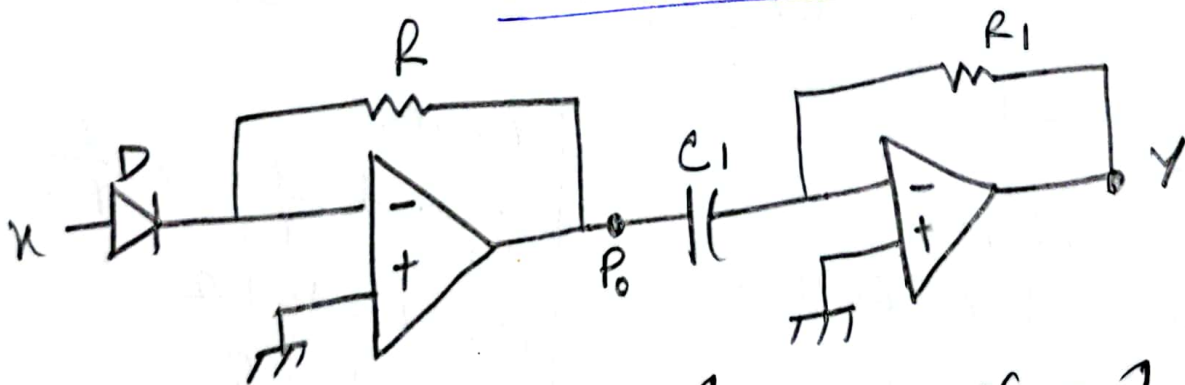

Here, $I_S R = 1 \Rightarrow R = \frac{1}{I_S} ; V_T = 1$


$$\begin{aligned}
 P_0 &= -R I_s \exp\left(\frac{x}{\eta \cdot V_T}\right) \\
 &= -\frac{1}{I_s} \times I_s \times \exp\left(\frac{x}{\eta \cdot 1}\right) (8+1) = 1 \\
 &= -\exp\left(\frac{x}{\eta}\right)
 \end{aligned}$$

Again,

$$\begin{aligned}
 y &= -R_1 \cdot C_1 \cdot \frac{dP_0}{dt} \\
 &= -R_1 \cdot C_1 \cdot \frac{d\left(-\exp\left(\frac{x}{\eta}\right)\right)}{dt} \\
 &= R_1 C_1 \frac{d}{dt} \exp\left(\frac{x}{\eta}\right)
 \end{aligned}$$


Ans to q 2 (a)

$$f = (A + B) \cdot C$$

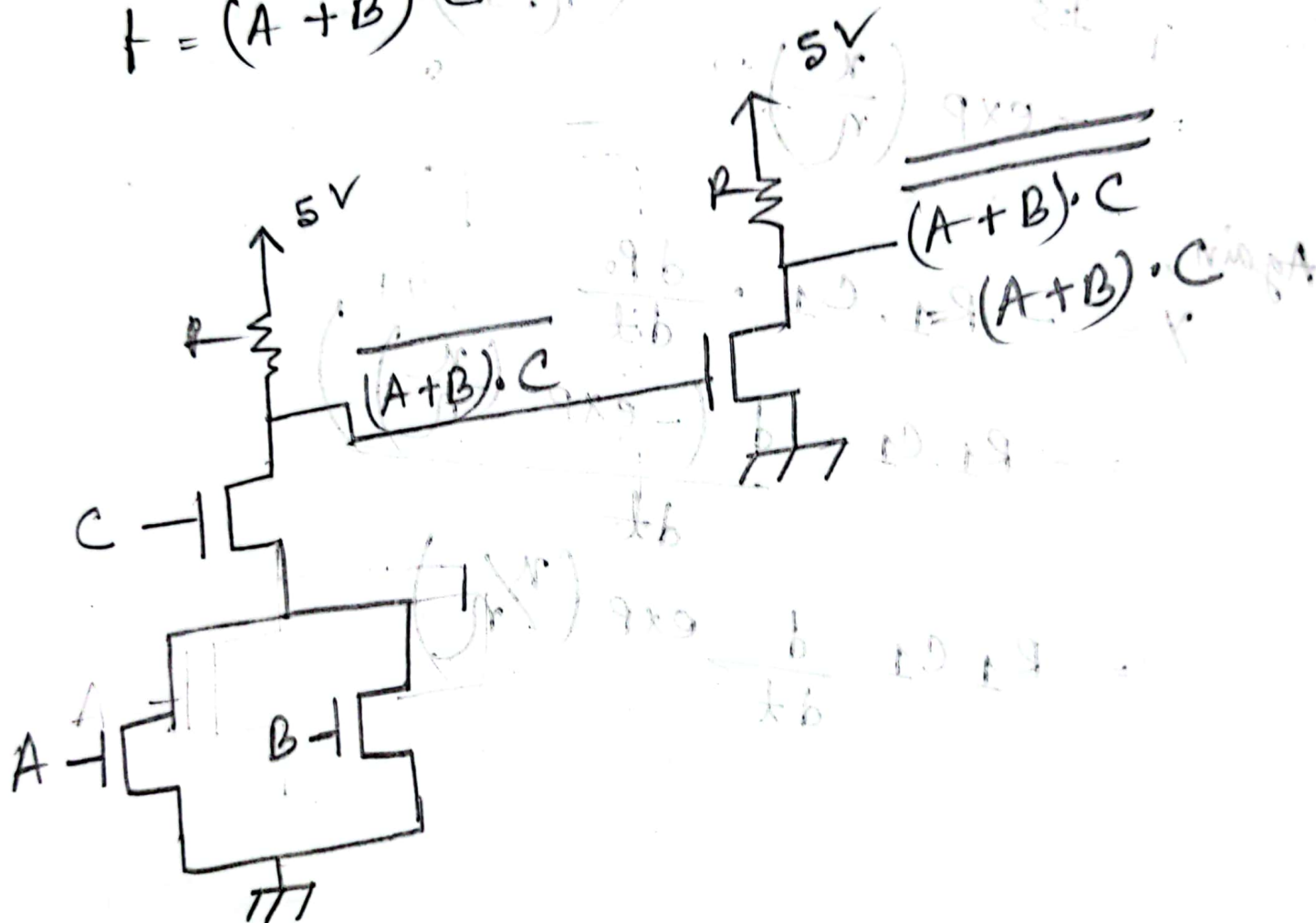

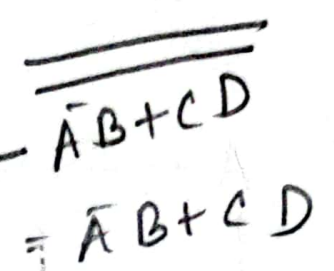(b) $\frac{1}{2} \times 10 = 5$ units

$$\frac{d}{dt} \left(\frac{1}{2} m v^2 \right) = \frac{d}{dt} \left(\frac{1}{2} m \dot{x}^2 \right)$$




Ans to 2

Absorption law: $\therefore AB + A = A$


\uparrow SV $\quad \quad \quad \underline{\underline{A + 1B = A}}$

$$\underline{\underline{A+CD}} = A+CD$$

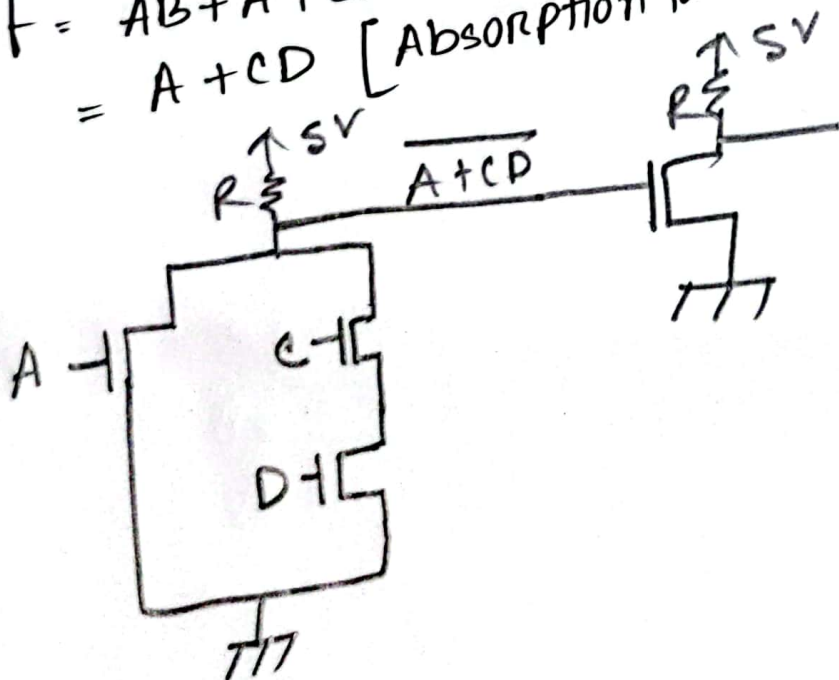

Without simplifying:

$$f = AB + A + CD$$

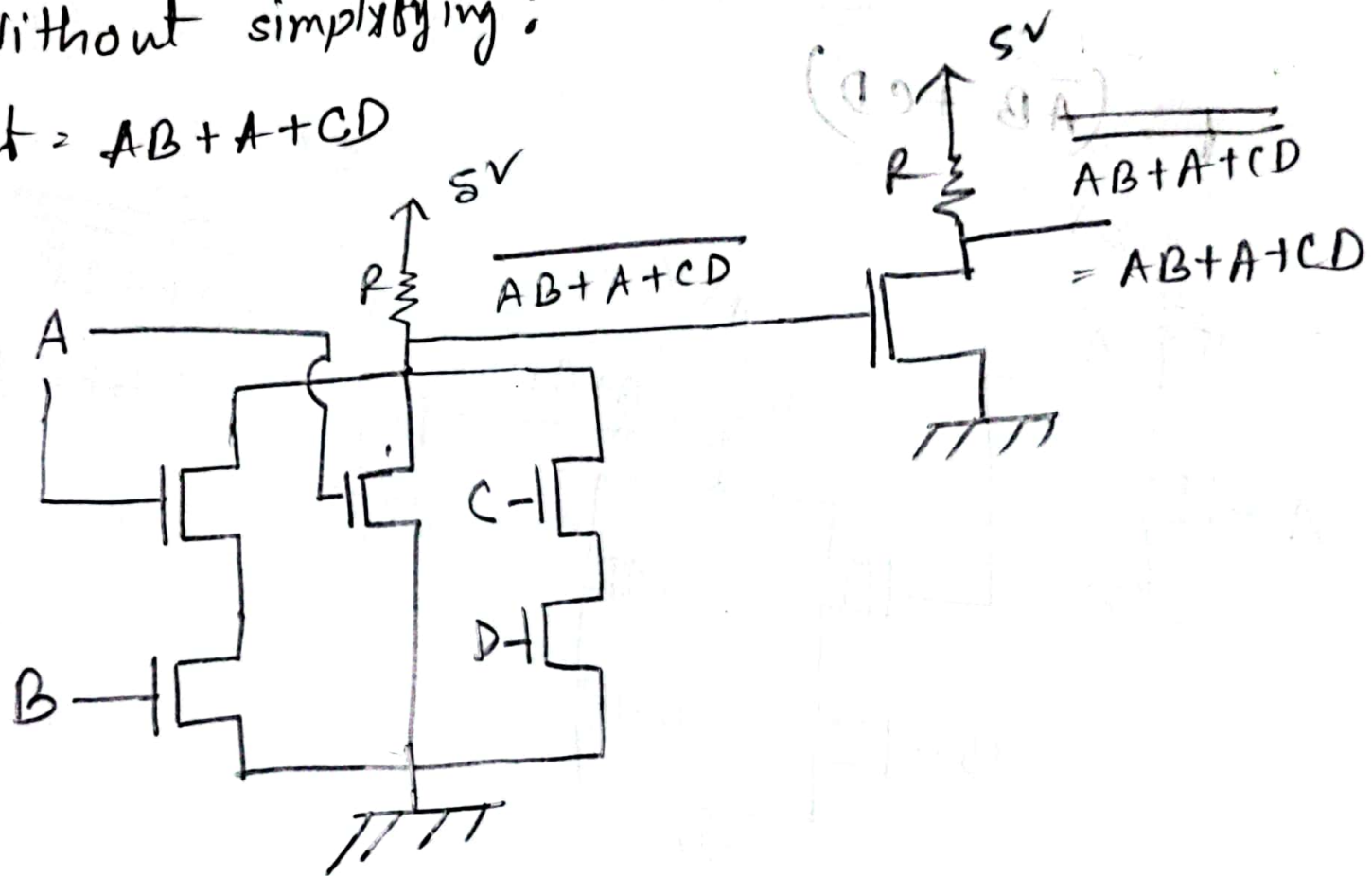

$$[A = A + BA \therefore \text{Absorption law}] \quad AB + A + CD = A + CD [A + B] = A + CD$$