


TOPIC NAME: Emitter Coupled Logic family

DAY: _____


TIME: _____

DATE: / /

basic differential amp

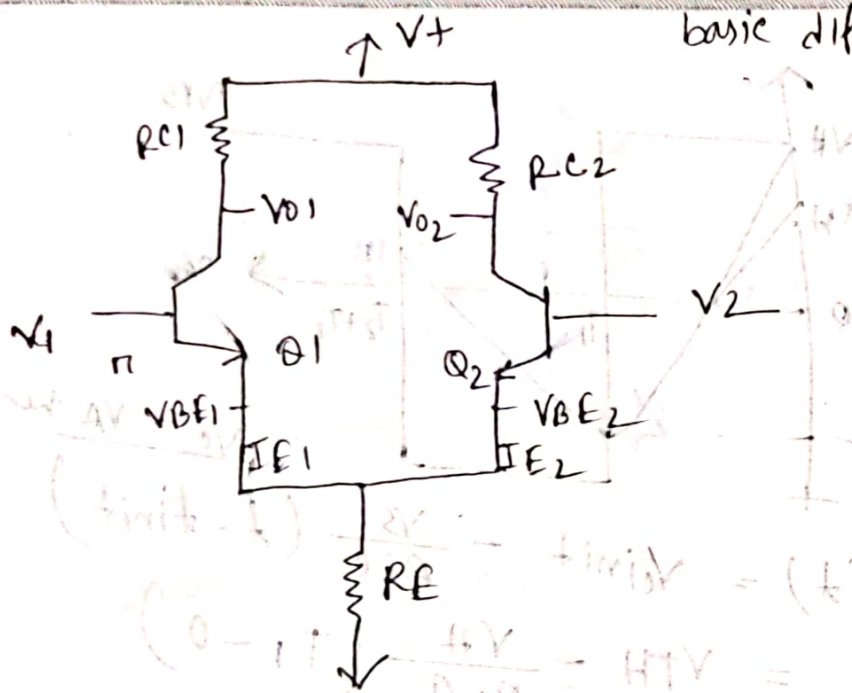

$$V_I = V_1 - V_2$$

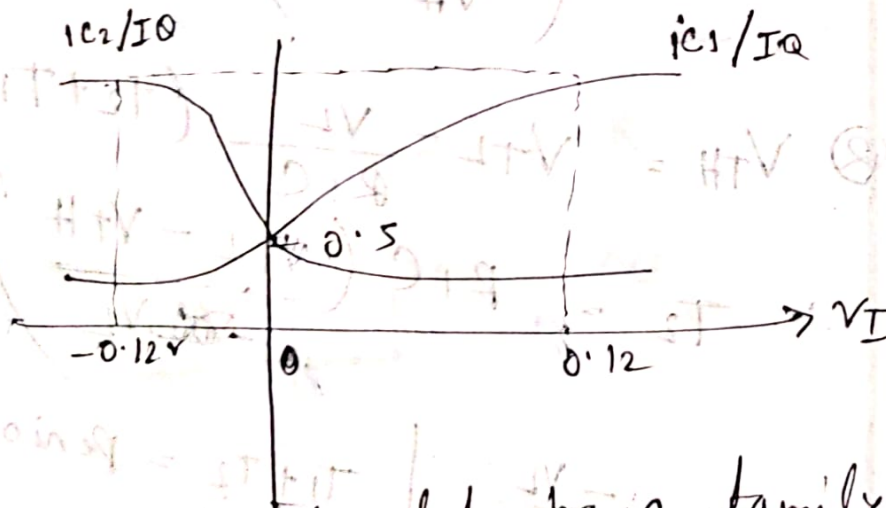

- No saturation / unsaturated logic family
- only f.A and cutoff

TOPIC NAME : _____


DAY : _____

TIME : _____ DATE : / /

forward (active :)

$$\textcircled{1} V_{BE} = 0.7 \text{ V}$$

frw biased pn junction

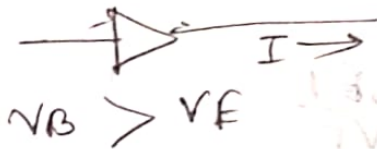

$$\textcircled{2} I = I_S \exp \left(\frac{n V_{BE}}{V_T} \right), \quad n = 1$$

$$V_T = 25.9 \text{ mV @ } 300 \text{ K}$$

$$I_B \approx 0 \text{ as } i_c, i_E \gg$$

$$i_E = i_c + i_B \rightarrow 0$$

$$\textcircled{3} \underline{i_E = i_c}$$

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

$$I_{E1} = I_S \exp\left(\frac{V_{BE1}}{V_T}\right)$$

$$I_{E2} = I_S \exp\left(\frac{V_{BE2}}{V_T}\right)$$

$$\frac{I_{E1}}{I_{E2}} = \frac{I_S e^{\frac{V_{BE1}}{V_T}}}{I_S e^{\frac{V_{BE2}}{V_T}}}$$

$$= e^{\frac{V_{BE1} - V_{BE2}}{V_T}}$$

if $I_{E1} = 100 I_{E2}$

$$\frac{100 I_{E2}}{I_{E2}} = e^{\frac{V_{BE1} - V_{BE2}}{V_T}}$$

$$V_T \ln(100) = \frac{V_{BE1} - V_{BE2}}{V_T}$$




$$\rightarrow V_{BE1} - V_{BE2} = 0.12 V_T$$

TOPIC NAME: Logic family

DAY: _____

TIME: _____

DATE: 19 / 8 / 23

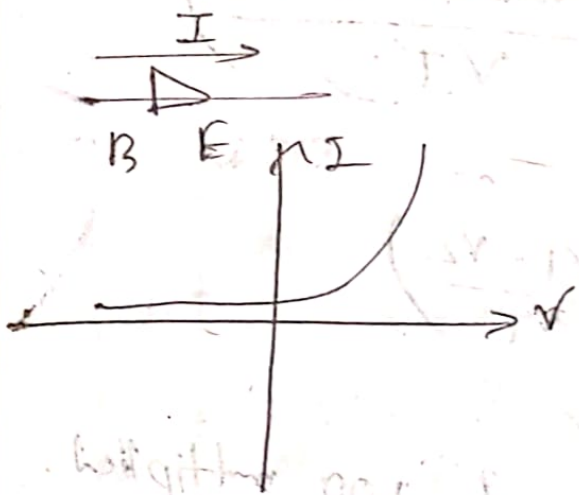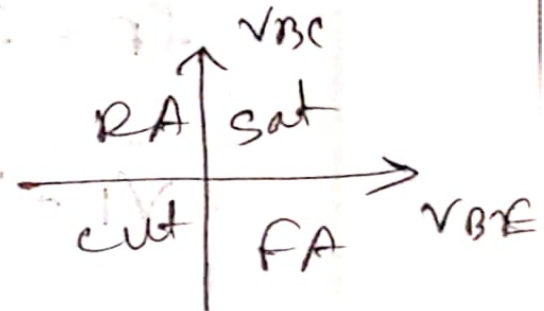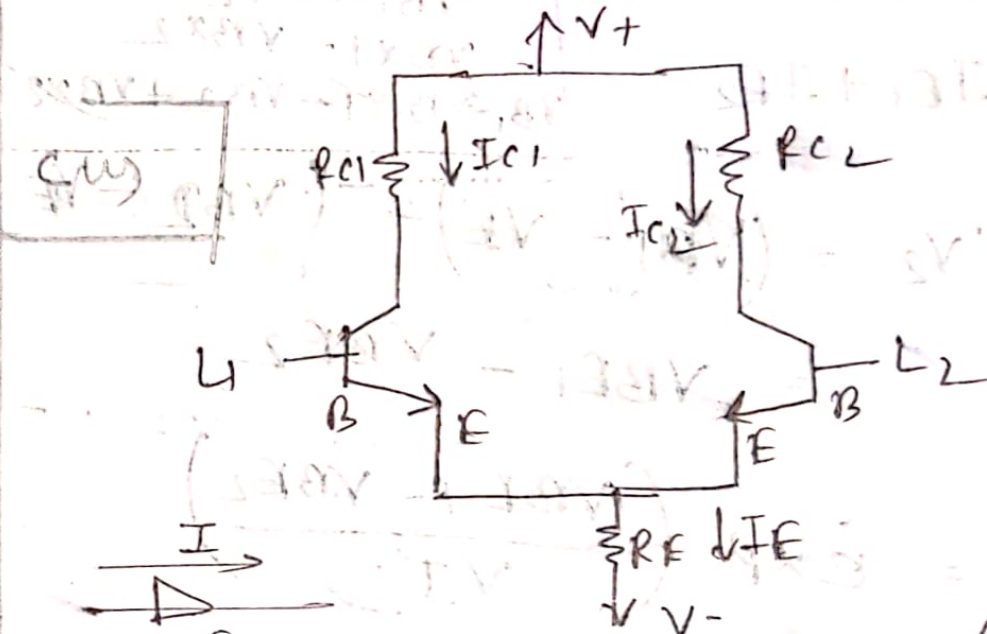

$$I = I_s e^{\left(\frac{n V_{BE}}{V_T} \right)}$$

$$V_T = 0.0259 \text{ V}$$

Any PN junction

if $V_1 > V_2$:

$$n = 1$$

$$\textcircled{1} I_{E1} = I_s \exp \left(\frac{V_{BE1}}{V_T} \right) \approx I_{C1}$$

$$\textcircled{2} I_{E2} = I_s \exp \left(\frac{V_{BE2}}{V_T} \right) \approx I_{C2}$$

In FA: $I_C, I_E > 0$

$I_C, I_E \gg I_B \rightarrow \text{negligible}$

$$I_E = I_C + I_B \rightarrow 0$$

TOPIC NAME: _____

DAY: _____

TIME: _____

DATE: / /

$$I_E = I_{E1} + I_{E2}$$

$$\begin{aligned} & V_{B1} - V_{B2} \\ & V_{B1} - V_{B2} \\ & V_{B1} - V_{B2} - V_{B2} + V_{B2} \end{aligned}$$

$$V_1 - V_2 = (V_{B1} - V_E) - (V_{B2} - V_E)$$

$$= V_{BE1} - V_{BE2}$$

$$\frac{I_{E1}}{I_{E2}} = \exp\left(\frac{V_{BE1} - V_{BE2}}{V_T}\right)$$

$$\text{Wt, } I_{E1} = 100 I_{E2}$$

$$\Rightarrow 100 = \exp\left(\frac{V_1 - V_2}{V_T}\right)$$

$$\Rightarrow V_1 - V_2 = 0.12 \text{ V}$$

for 0.12 V diff current 100 multiplied.


In this case:

$$I_E \approx I_{E1}$$


if $V_1 > V_2$: V_1 FA $\times 2 I = 14 I$ ①

$$V_1 = V_2 = 5: \text{FA } V_1 - V_2 = 0$$

cutoff both

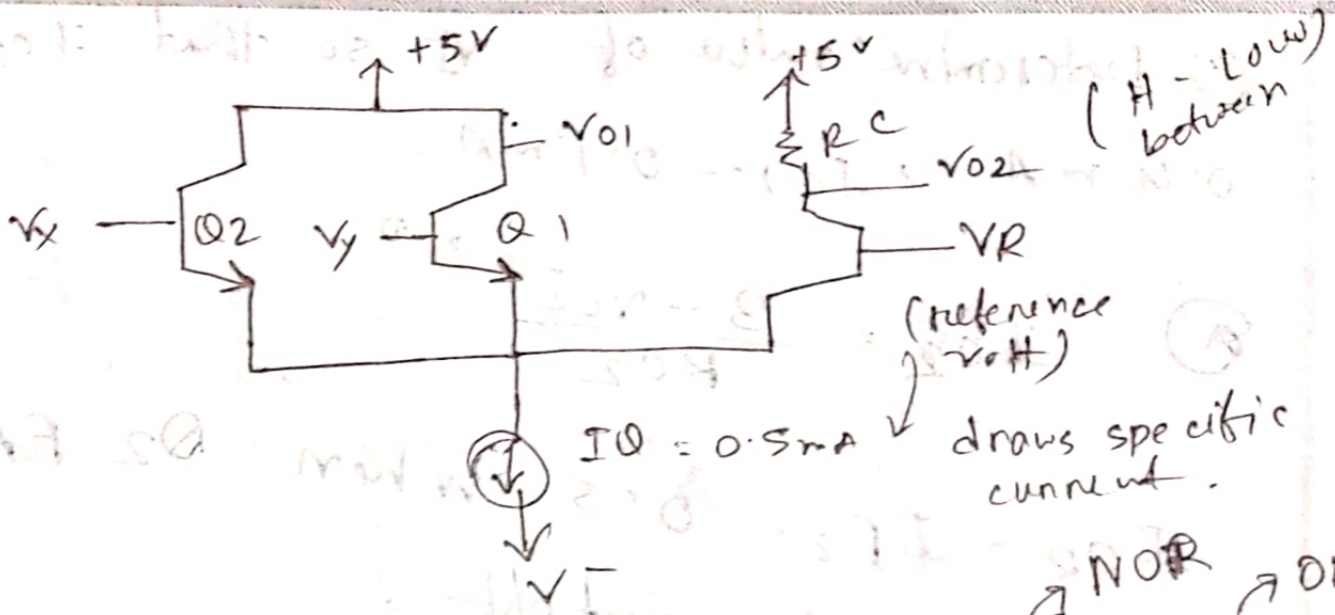

V_x	V_y	Q_1	Q_2	Q_R	V_{01}	V_{02}
L	L	C/O	C/O	FA	H	L
L	H	FA	C/O	C/O	L	L
H	L	C/O	FA	C/O	L	H
H	H	FA	FA	C/O	L	H

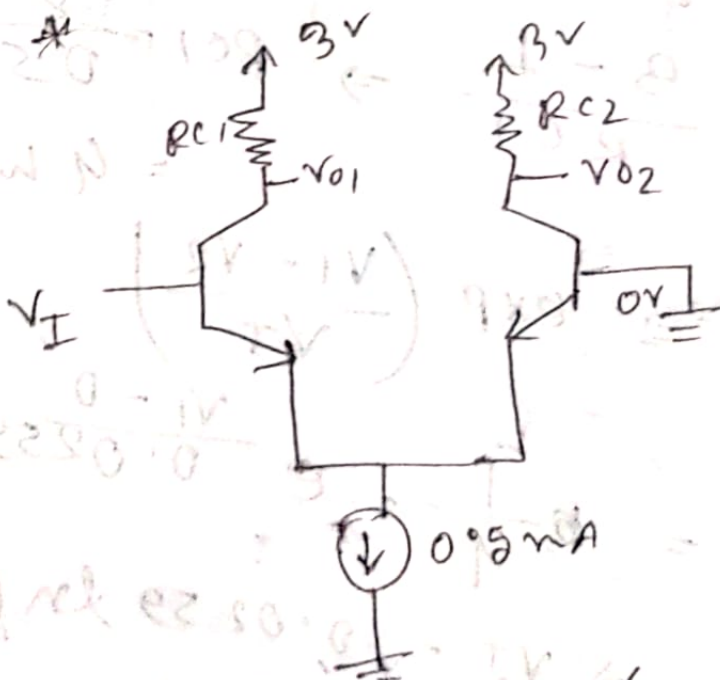

Neglect base current

- (a) Determine value of R_{C2} such that the min value of $V_{O2} = 0V$.
- (b) value of R_{C1} such that $V_{O1} = 1V$ when $V_I = 1V$.

TOPIC NAME: _____

DAY: _____

TIME: _____

DATE: / /

③ Determine value of V_I so that $I_{C2} = 0.4 \text{ mA}$, $I_{C1} = 0.1 \text{ mA}$.

① $I_{C2} = \frac{3 - V_{O2}}{R_{C2}}$

$I_{C2} = I_{E2} = 0.5$ when Q_2 FA and Q_1 in cutoff.

Max drop when $I_{C2} = \text{all current}$

② $0.5 = \frac{3}{R_{C2}} \Rightarrow R_{C2} = \frac{3}{0.5} = 6 \text{ k}\Omega$

③ $Q_1 \rightarrow \text{FA}, Q_2 \rightarrow \text{C/O}$

$I_{C1} = 0.5 = \frac{3 - V_{O1}}{R_{C1}} \Rightarrow R_{C1} = \frac{2}{0.5} = 4 \text{ k}\Omega$

④ $\frac{I_{E1} = I_{C1}}{I_{E2} = I_{C2}} = \exp\left(\frac{V_{I1} - V_{I2}}{V_T}\right)$

$\Rightarrow \frac{0.1}{0.4} = \frac{1}{4} = e^{\frac{V_I - 0}{0.0259}}$


$\Rightarrow V_I = 0.0259 \ln(1/4)$

TOPIC NAME : _____

DAY : _____

TIME : _____

DATE : / /

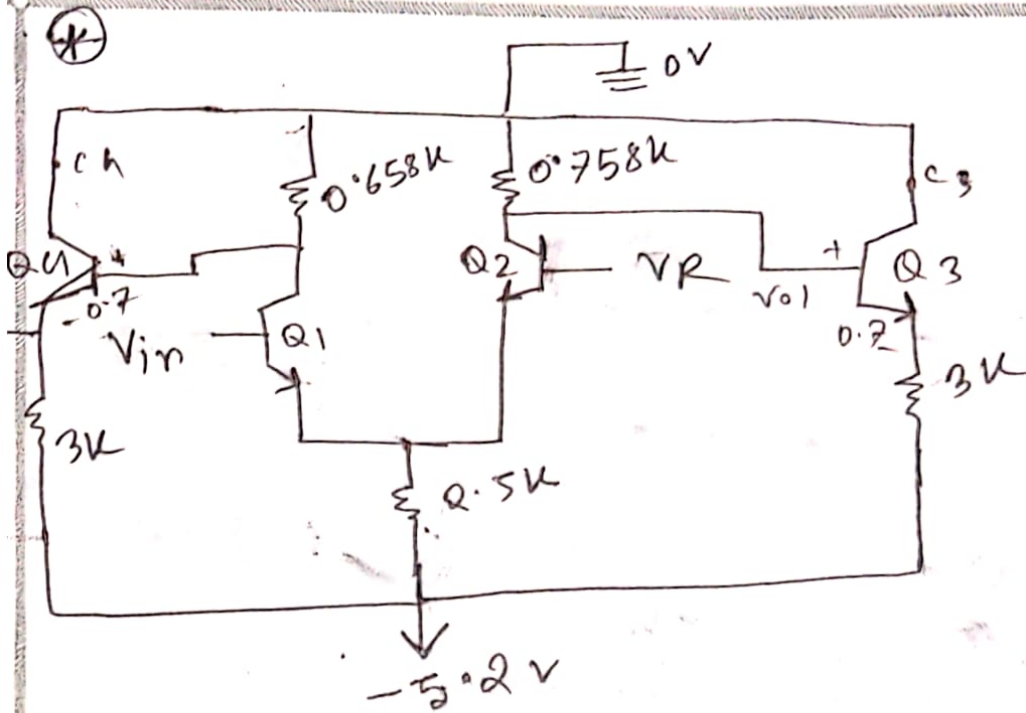

$V_{BC} < 0$
 $V_{BE} = +POS$

(a) V_{in} logic low [much smaller voltage V_R]

V_{in}	V_R	Q1	Q2	V_{o1}	V_{o2}
L					