

BRAC University**Set: 01**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA



Midterm

Full Marks: 40



Time: 2 hours

Date: March 10, 2022

Answer all 4 questions. All the questions carry equal marks.

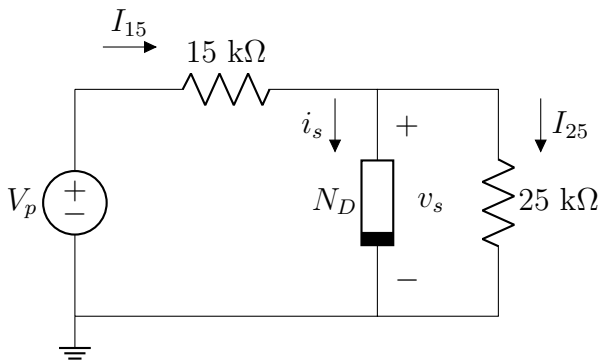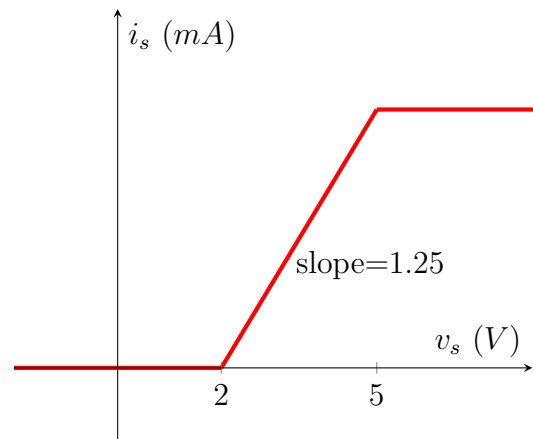Question 1 [CO1]**10**(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- (a) **Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- (b) **Show** the alternative representation of the circuit in Figure (a). [2]
- (c) **Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- (d) **Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

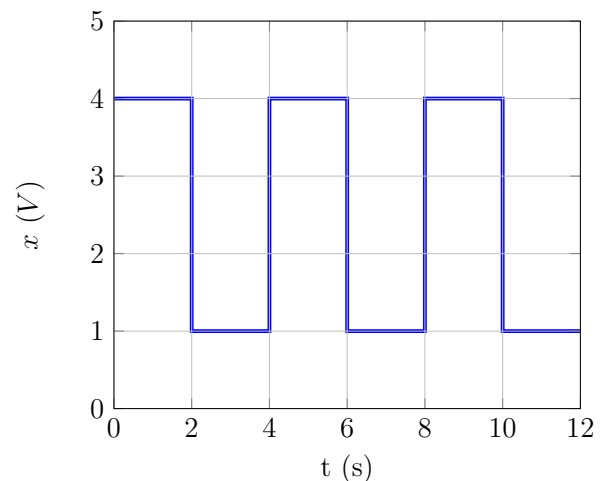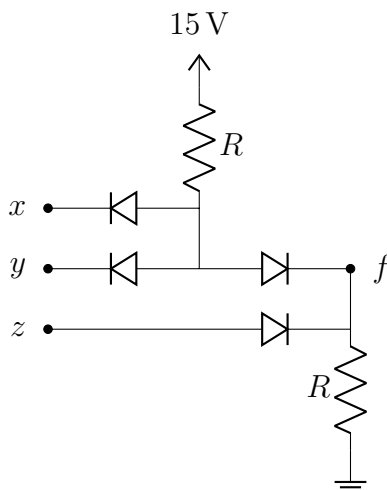Question 2 [CO2]**10**

Set: 01

For this question, all of the diodes are ideal.


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x.y.z$. Here “.” denotes logical AND. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

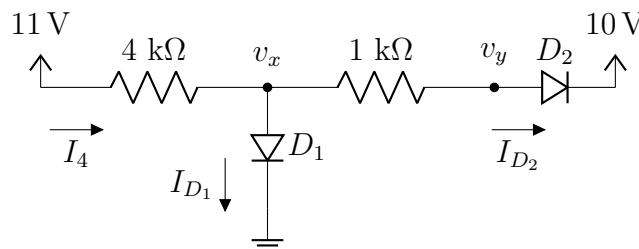- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a **full-wave rectifier** with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the **DC value** of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 02

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

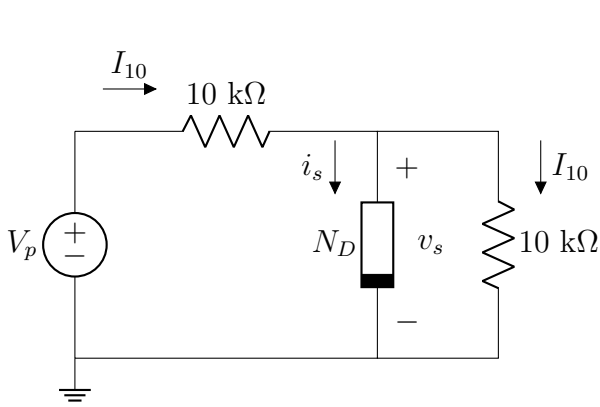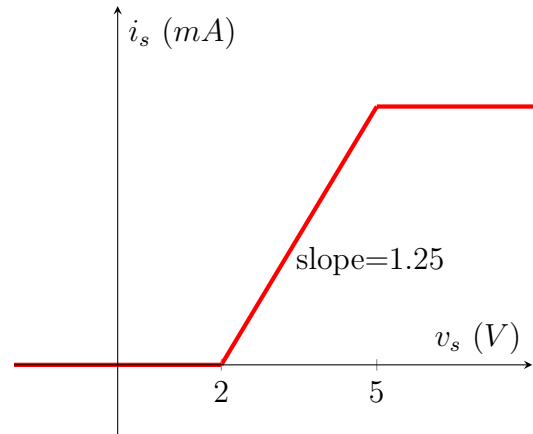(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

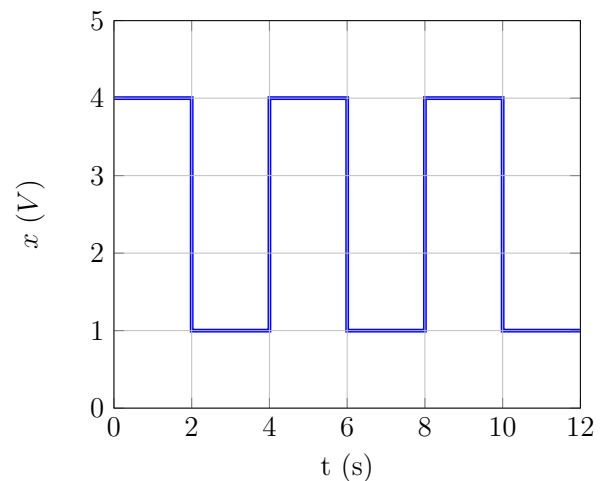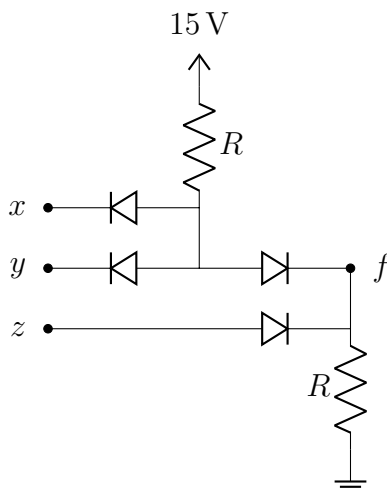

For this question, all of the diodes are ideal.

Set: 02


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x.y.z$. Here “.” denotes logical AND. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

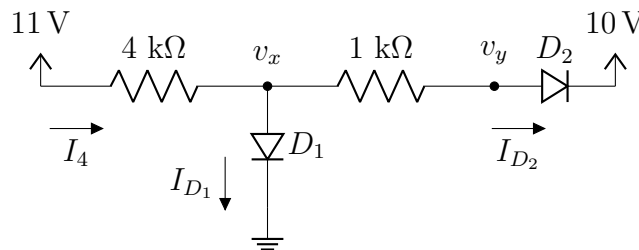- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 03

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

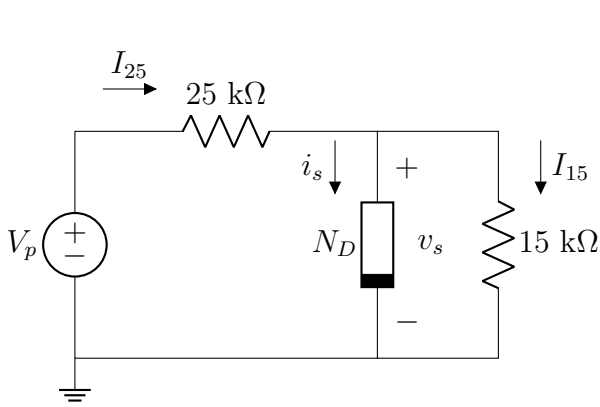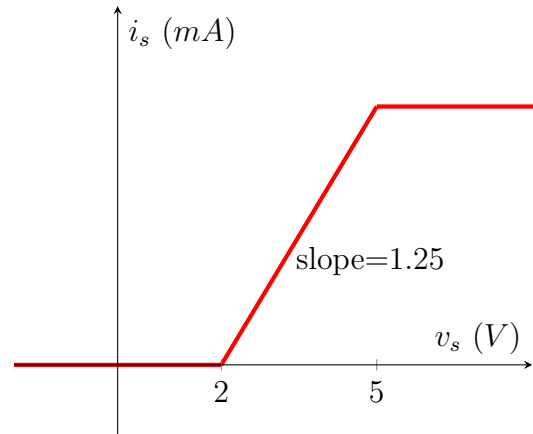(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

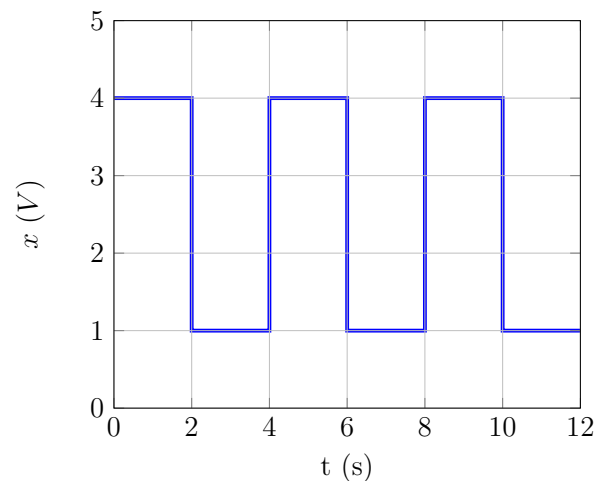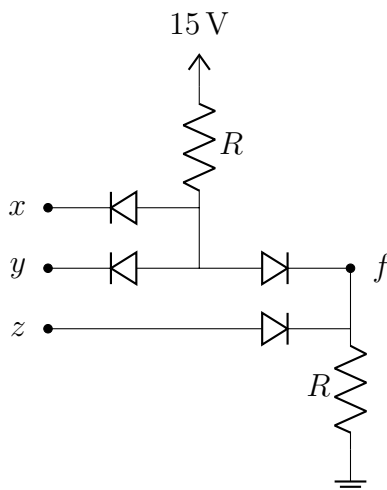

For this question, all of the diodes are ideal.

Set: 03


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

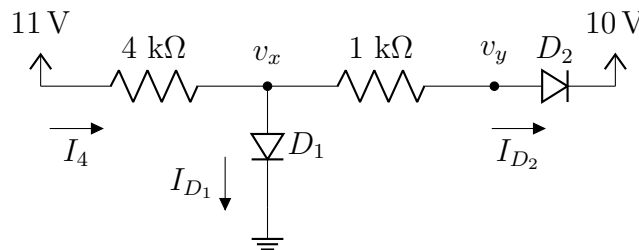- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 04

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

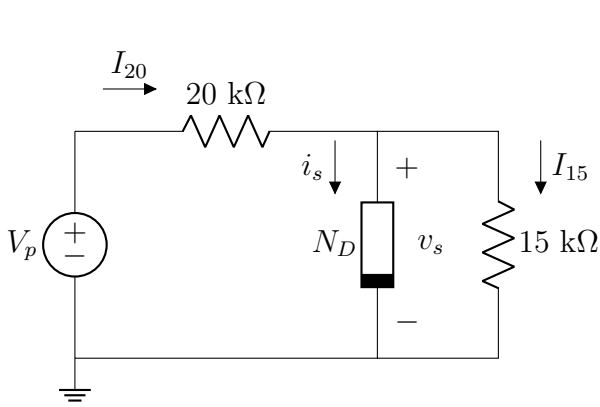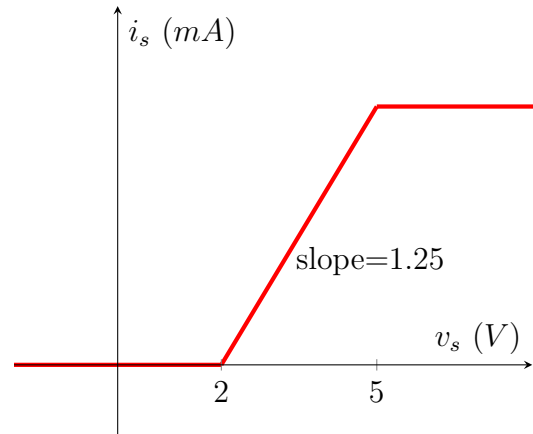(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

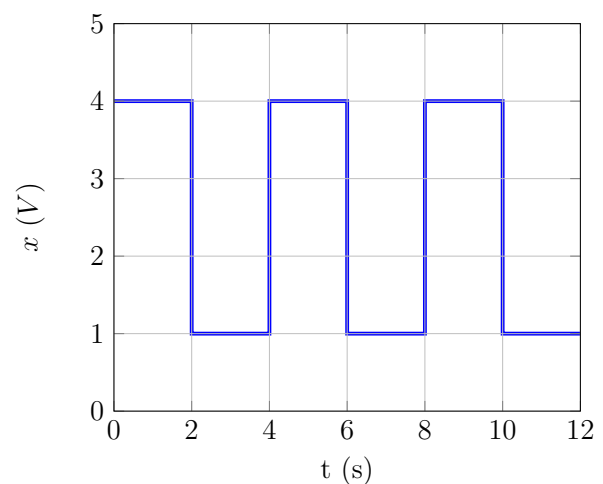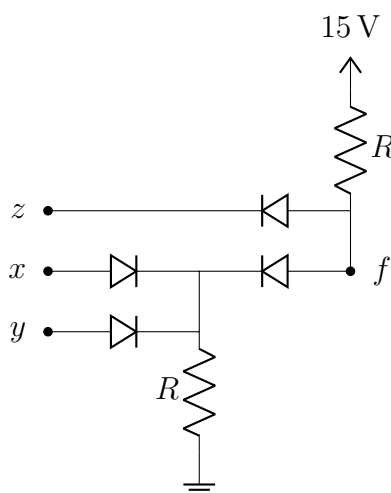

For this question, all of the diodes are ideal.

Set: 04


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

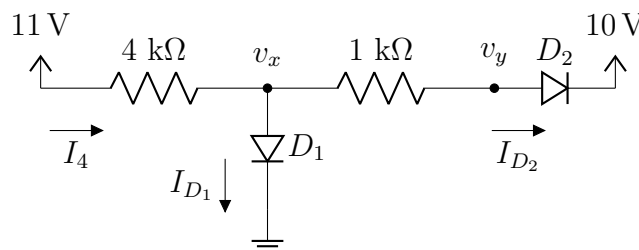- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 05

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

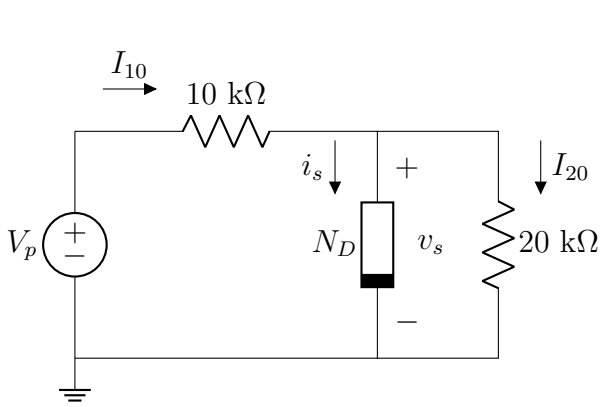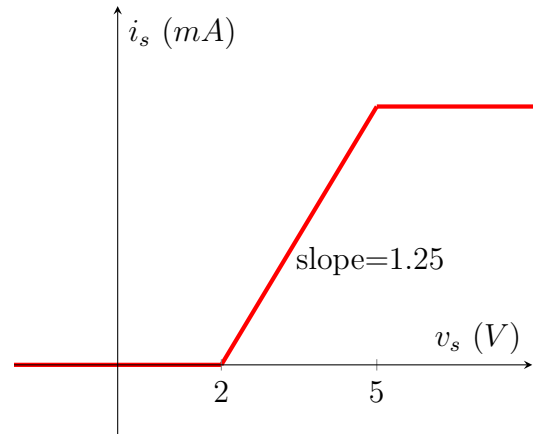(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

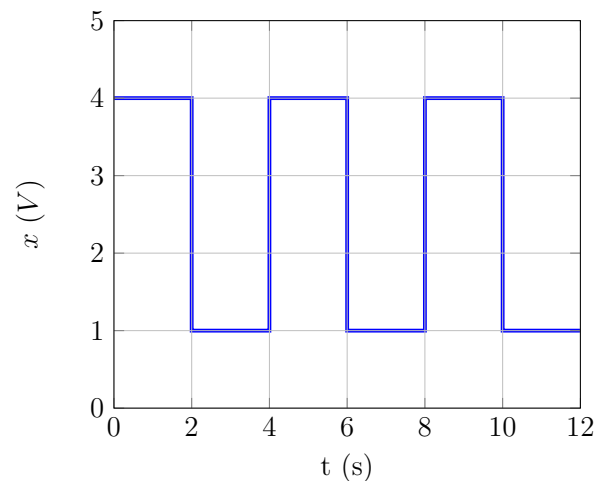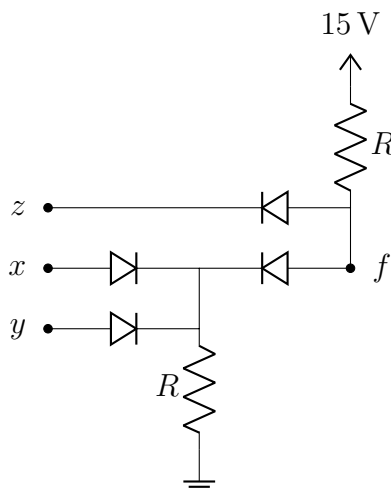

For this question, all of the diodes are ideal.

Set: 05


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

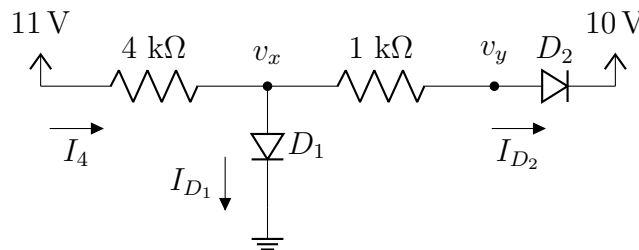- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 06

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

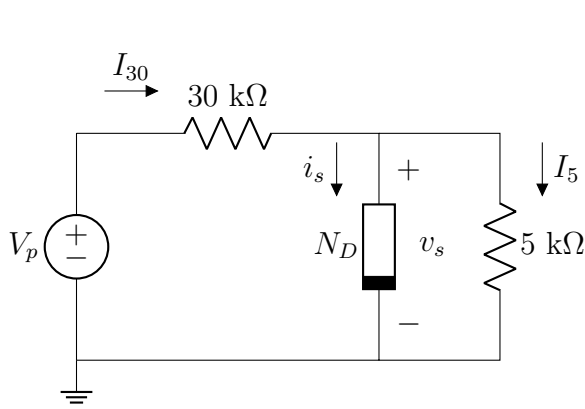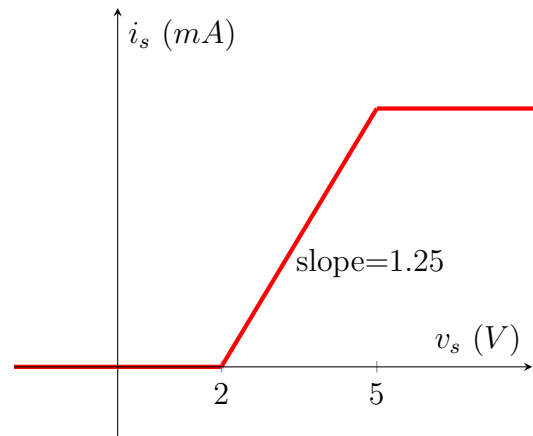(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

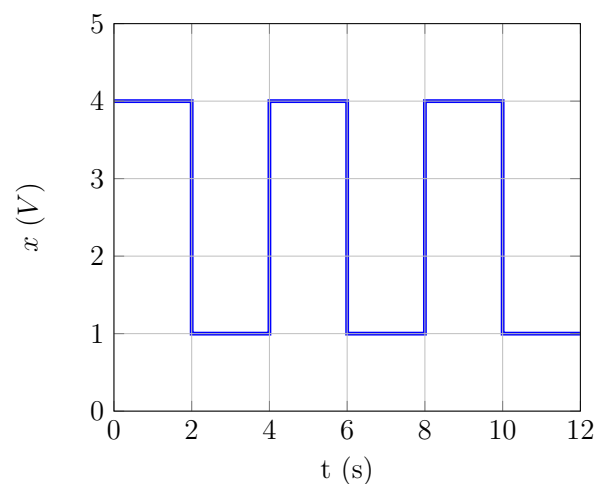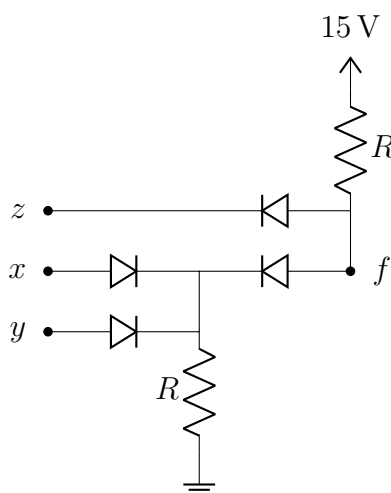

For this question, all of the diodes are ideal.

Set: 06


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

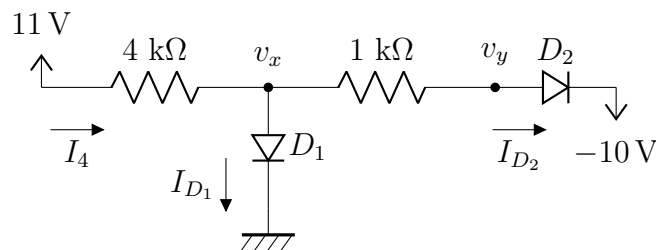- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 07

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

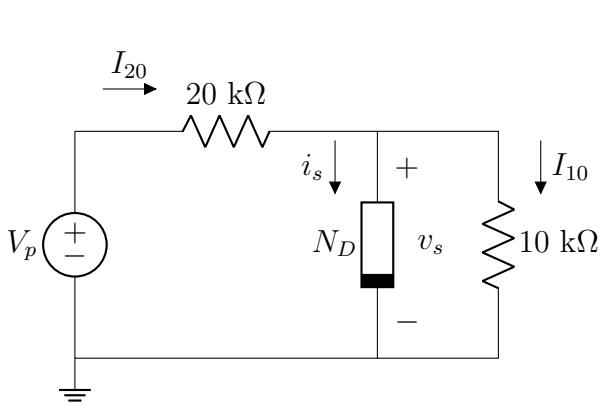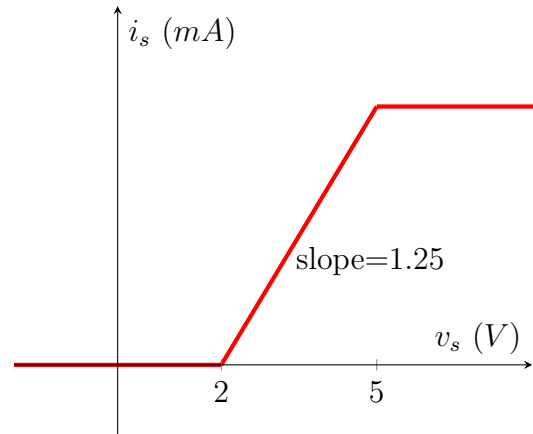(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

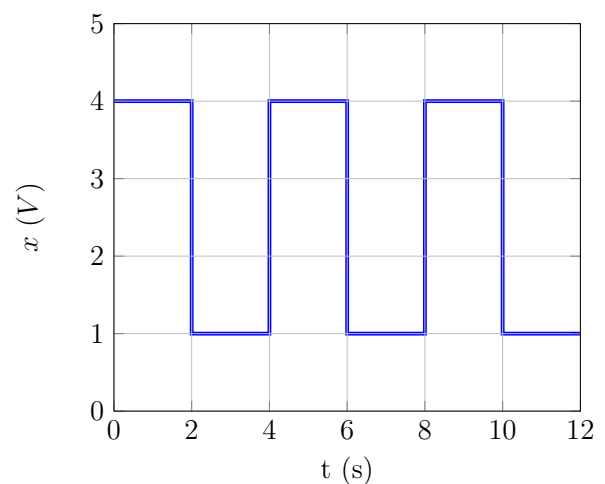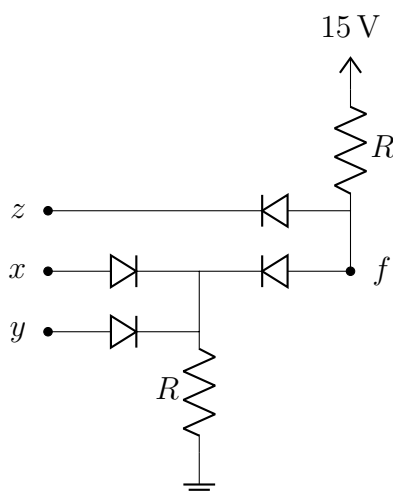

For this question, all of the diodes are ideal.

Set: 07


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

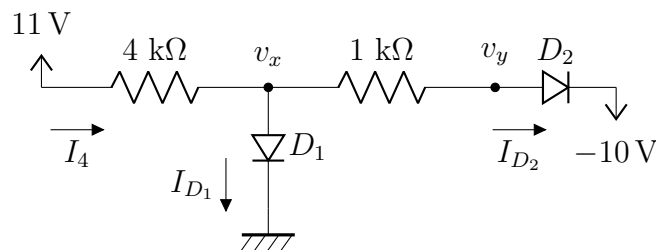- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 08

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

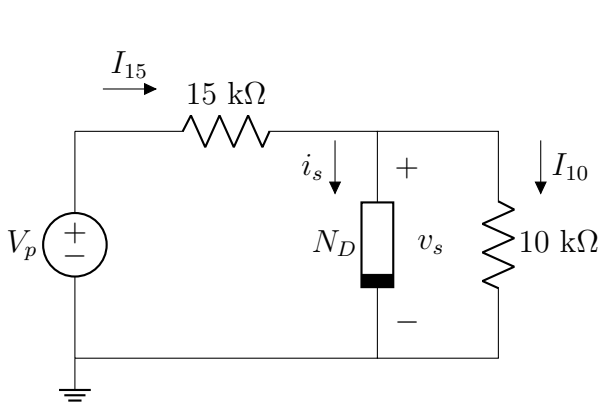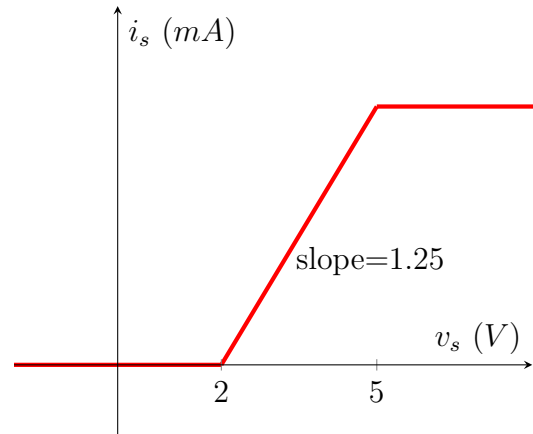(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

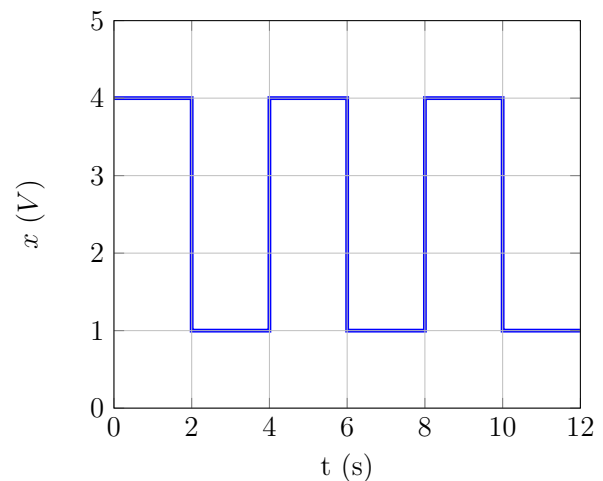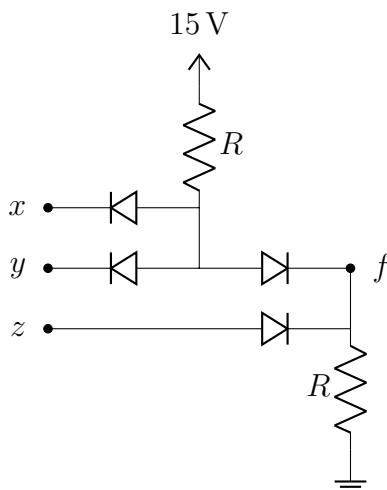

For this question, all of the diodes are ideal.

Set: 08


-
- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

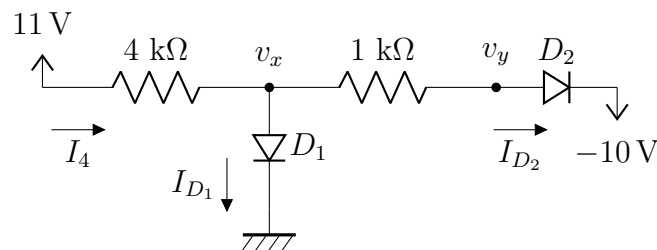- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University
Set: 09

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

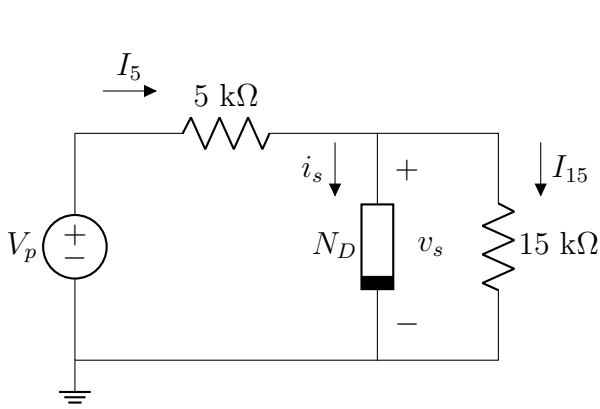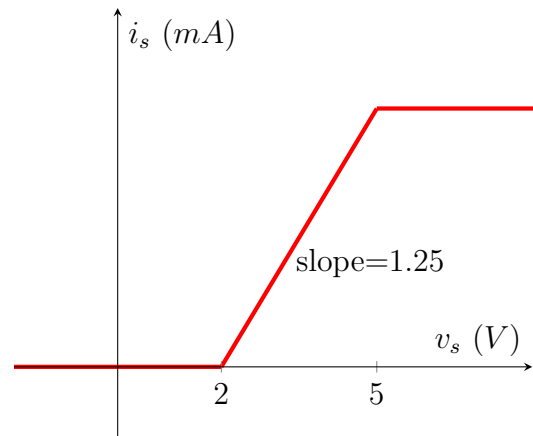(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

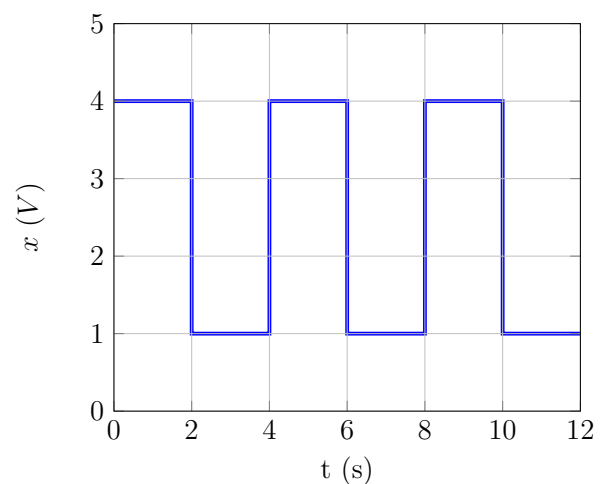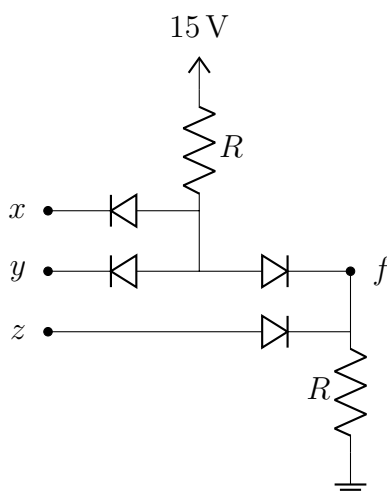

For this question, all of the diodes are ideal.

Set: 09


-
- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

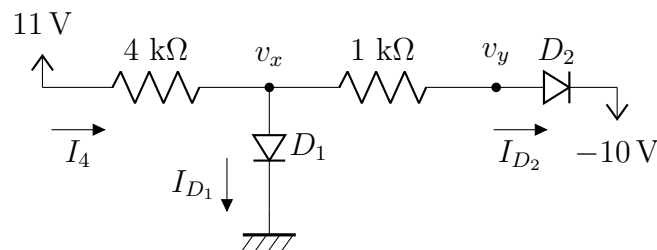- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

BRAC University

Set: 10

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

Question 1 [CO1]



10

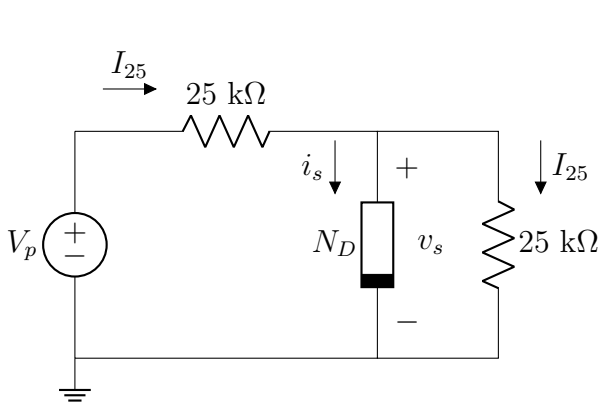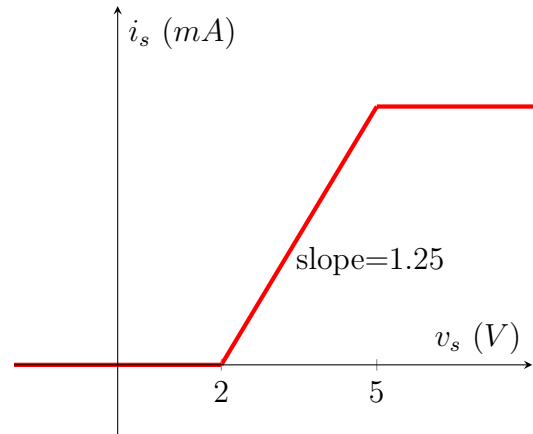(a) A circuit with a non-linear device N_D (b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3$ V and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3$ V. [3]

Question 2 [CO2]

10

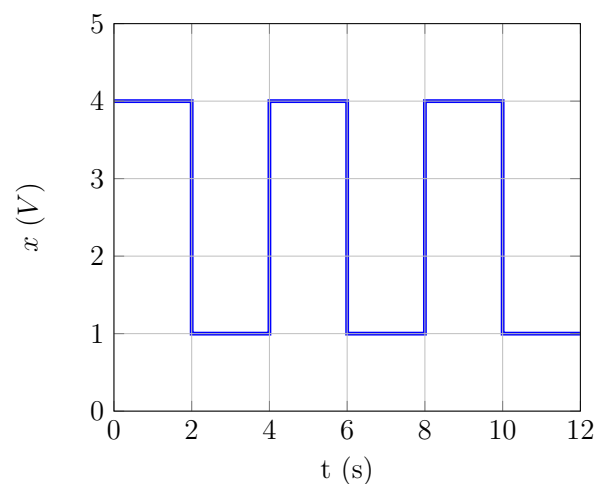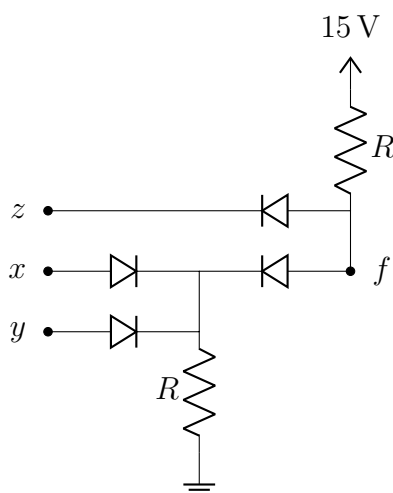

For this question, all of the diodes are ideal.

Set: 10


- (a) Assuming x, y, z are boolean variables, **analyze** the circuit on the left to find an expression of f in terms of x, y , and z . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of f assuming x, y, z are voltage signals, where $y = 2\text{ V}$, $z = 3\text{ V}$, and x has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function $f = x + y + z$. Here “+” denotes logical OR. [2]

Bonus: Design a circuit using ideal diodes to implement the XOR logic function between x and y , assuming you have access to x, \bar{x}, y , and \bar{y} . [3]

Question 3 [CO1]

10

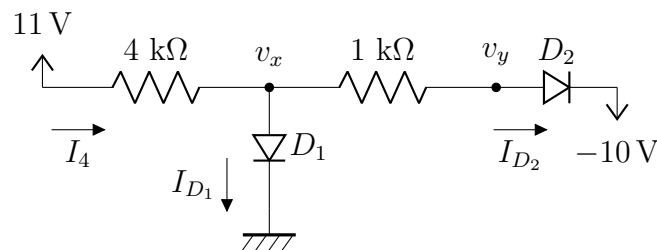- (a) **Analyze** the following circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y . Here, **use** the Method of Assumed State using the CVD model of diode with $V_{D0} = 0.5\text{ V}$. [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



Question 4 [CO2]

10

A voltage waveform $v_i = 10 \sin(100\pi t)\text{ V}$ is input to a full-wave rectifier with a load resistance of $R = 50\text{ k}\Omega$. Silicon diodes are used in this circuit for which the forward drop is $V_{D0} = 0.7\text{ V}$.

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a $5\text{ }\mu\text{F}$ capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [$V_{D0} = 0.2\text{ V}$].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]