

# Group Assessment

**BRAC University**

Semester: Fall 2022

Course No: CSE251




Course Title: Electronic Devices and Circuits

**Student IDs:**
 
## Set-1

(i)

In the circuit shown in Fig. the voltage at the emitter was measured and found to be  $-0.7\text{ V}$ .  
If  $\beta = 50$ , find  $I_E$ ,  $I_B$ ,  $I_C$ , and  $V_C$ .



**Solution:**

Let, the BJT is in **active** mode.

Given,  $V_E = -0.7V$

$$I_E = \frac{-0.7 - (-10)}{10} = 0.93 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta+1} I_E = \frac{50}{51} \times 0.93 = 0.92 \text{ mA}$$


$$\therefore I_B = I_E - I_C = 0.01 \text{ mA}$$

now,  $I_C = \frac{10 - V_C}{5} = 0.92$

$$\Rightarrow V_C = 10 - 5 \times 0.92 \approx 5.45 \text{ V}$$

Here,  $V_{CE} = V_C - V_E = 5.45 - (-0.7) > 0.2V$

 **(ii)** Consider the circuit shown below. Does it follow the Static Discipline? Calculate the noise margins  $NM_0$  and  $NM_1$ .



**Solution:** See the slides on MOSFET.

## Set-2

Consider an NMOS transistor fabricated with  $L = 0.18 \mu\text{m}$  and  $W = 2 \mu\text{m}$ . The process technology is specified to have  $k_n' = 387 \mu\text{A/V}^2$ , and  $V_T = 0.5 \text{ V}$ . Find  $V_{GS}$  and  $V_{DS}$  that result in the MOSFET operating at the edge of the saturation region with  $I_{DS} = 100 \mu\text{A}$ . If  $V_{GS}$  is kept constant, find  $V_{DS}$  that results in  $I_D = 50 \mu\text{A}$ .

For MOSFET

$$k = k'_n \frac{W}{L}$$

$$I_D = 0, \text{ if } V_{GS} < V_T$$

$$I_D = k \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right], \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} < (V_{GS} - V_T)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2, \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} \geq (V_{GS} - V_T)$$

**Solution:**

the transistor transconductance parameter  $k_n$ ,

$$\begin{aligned} k_n &= k'_n \left( \frac{W}{L} \right) \\ &= 387 \left( \frac{2}{0.18} \right) = 4.3 \text{ mA/V}^2 \end{aligned}$$

With the transistor operating in saturation,

$$I_D = \frac{1}{2} k_n V_{OV}^2$$

Thus,

$$100 = \frac{1}{2} \times 4.3 \times 10^3 \times V_{OV}^2$$

which results in

$$V_{OV} = 0.22 \text{ V}$$

Thus,

$$V_{GS} = V_{in} + V_{OV} = 0.5 + 0.22 = 0.72 \text{ V}$$

and since operation is at the edge of saturation,

$$V_{DS} = V_{OV} = 0.22 \text{ V}$$

With  $V_{GS}$  kept constant at 0.72 V and  $I_D$  reduced from the value obtained at the edge of saturation, the MOSFET will now be operating in the triode region, thus

$$\begin{aligned} I_D &= k_n \left[ V_{OV} V_{DS} - \frac{1}{2} V_{DS}^2 \right] \\ 50 &= 4.3 \times 10^3 \left[ 0.22 V_{DS} - \frac{1}{2} V_{DS}^2 \right] \end{aligned}$$

which can be rearranged to the form

$$V_{DS}^2 - 0.44 V_{DS} + 0.023 = 0$$

This quadratic equation has two solutions

$$V_{DS} = 0.06 \text{ V} \quad \text{and} \quad V_{DS} = 0.39 \text{ V}$$

The second answer is greater than  $V_{OV}$  and thus is physically meaningless, since we know that the transistor is operating in the triode region. Thus we have

$$V_{DS} = 0.06 \text{ V}$$

### Set-3

- (i) Draw the I-V graph of a **MOSFET**. Identify all the regions. [You have to draw for at least three  $V_{GS}$  values and mark  $V_{ov}$  on the graph.]
- (ii) Draw the I-V graph of a **BJT**. Identify all the regions. [You have to draw for at least three  $I_B$  values on the graph.]
- (iii) Draw DTL and RTL inverter circuits. Why do we need these circuits? Explain.

**Solution:** See the class lecture.

### Set-4

 


Fig. 1

 


Fig. 2

- (i) **Derive** the expressions for y and q (separately).
- (ii) Consider y and p nodes to be shorted together. Now **find** the expression for q.
- (iii) Design a circuit using Op-Amp to implement the expression:

$$f = \exp\left(\frac{1}{4}x - 2y + \frac{d}{dt}z\right)$$

**Solution:**

- (i) See the class lecture (exponent and differentiator, respectively)

$$y = -I_s R \exp(x/V_T), \quad q = -RC (dp/dt)$$

- (ii)  $q = -RC dy/dt = -RC d(-I_s R \exp(x/V_T))/dt$

(iii)

