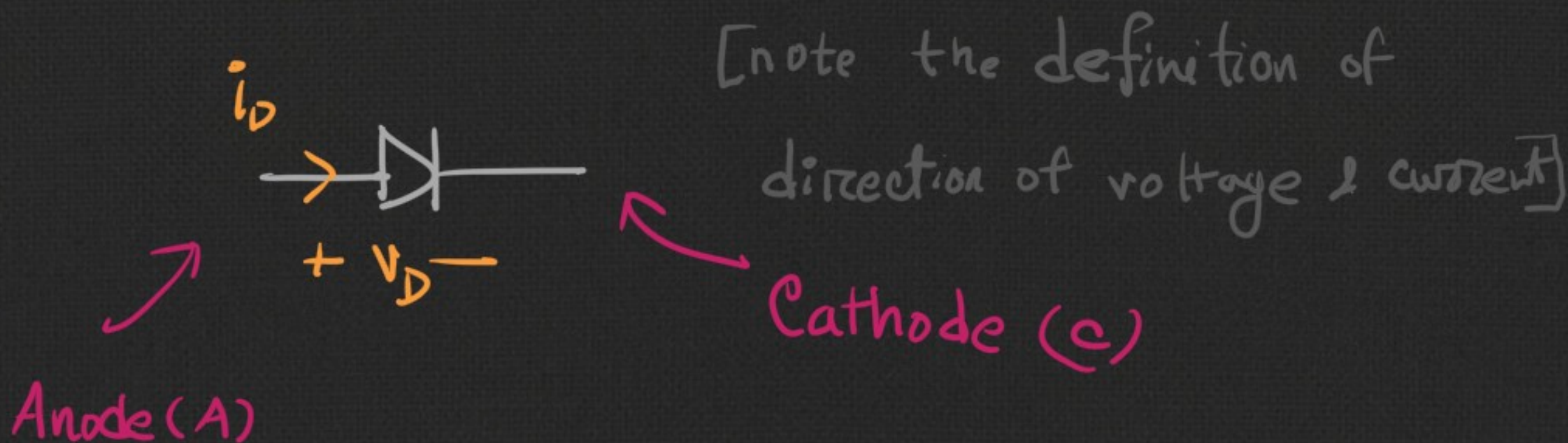


# Diode




$$V_D = V_A - V_C$$

$$i_D = \text{from A to C}$$

\* Diode is basically an electronic valve. It only allows current from A to C.

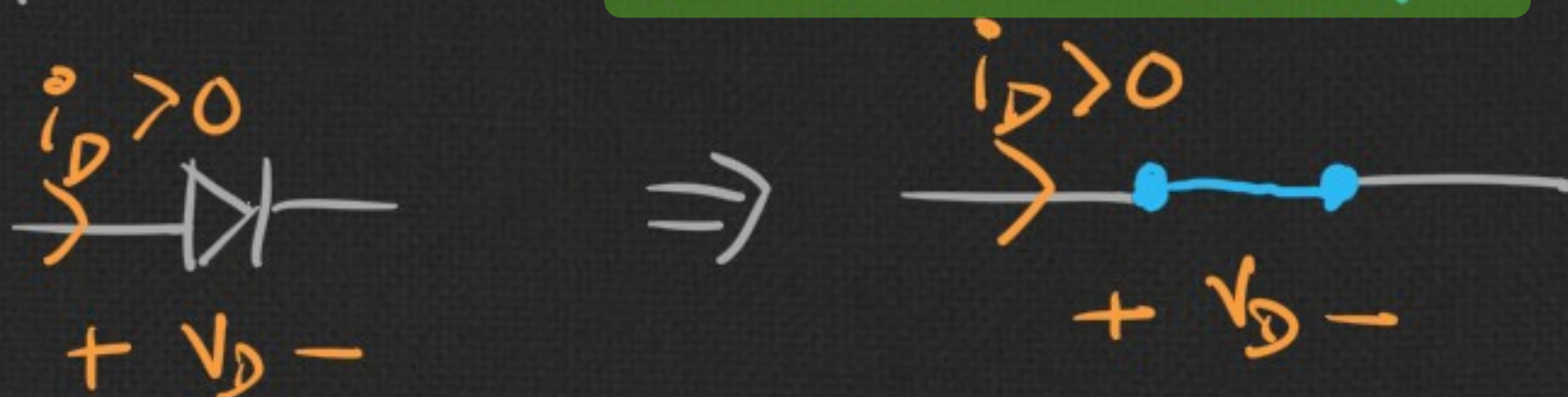\* So if current tries to flow from A to C [i.e. if  $i_D > 0$ ], the device will act like a short circuit



Hence  $V_D = 0$  in this condition. This is the FORWARD BIAS OR ON mode.

## Side note


For any circuit

this means  $V_1 = V_+ - V_-$   
 $\Rightarrow V_1 = V_a - V_b$


$V_2 = V_+ - V_-$   
 $\Rightarrow V_2 = V_b - V_a$



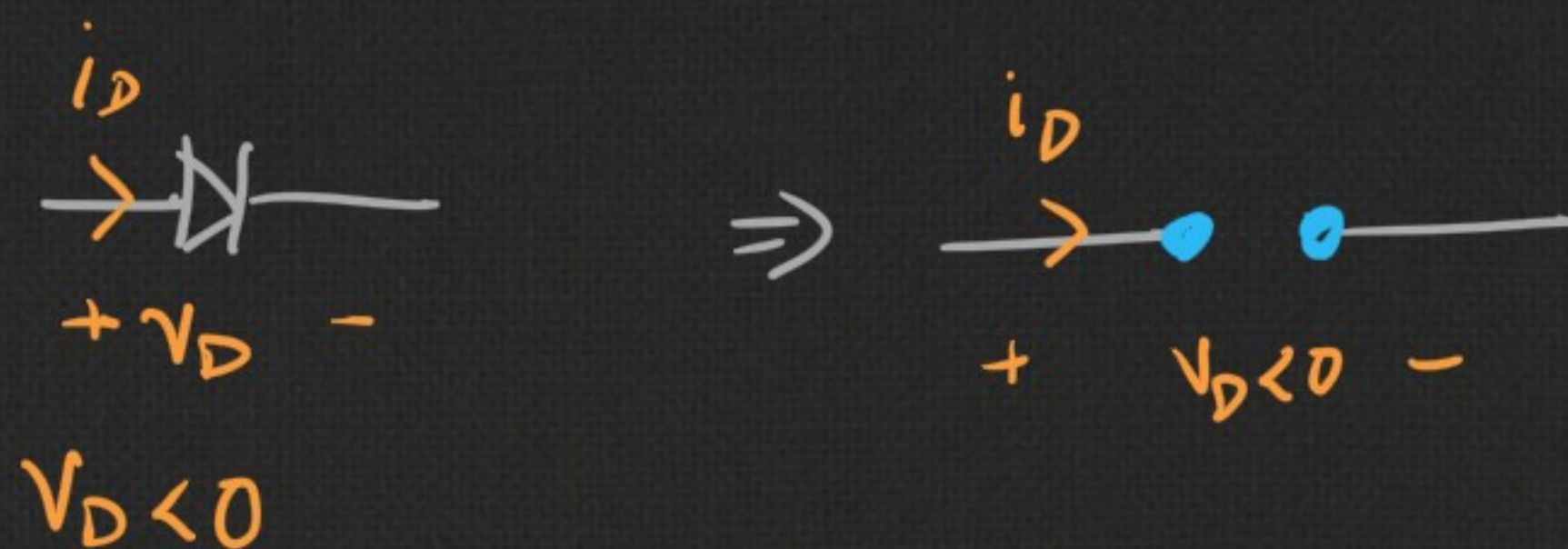\* On the other hand, if  $V_D < 0$ , the current will try to flow from C to A. But the diode won't allow such current, so it will act like an open circuit.




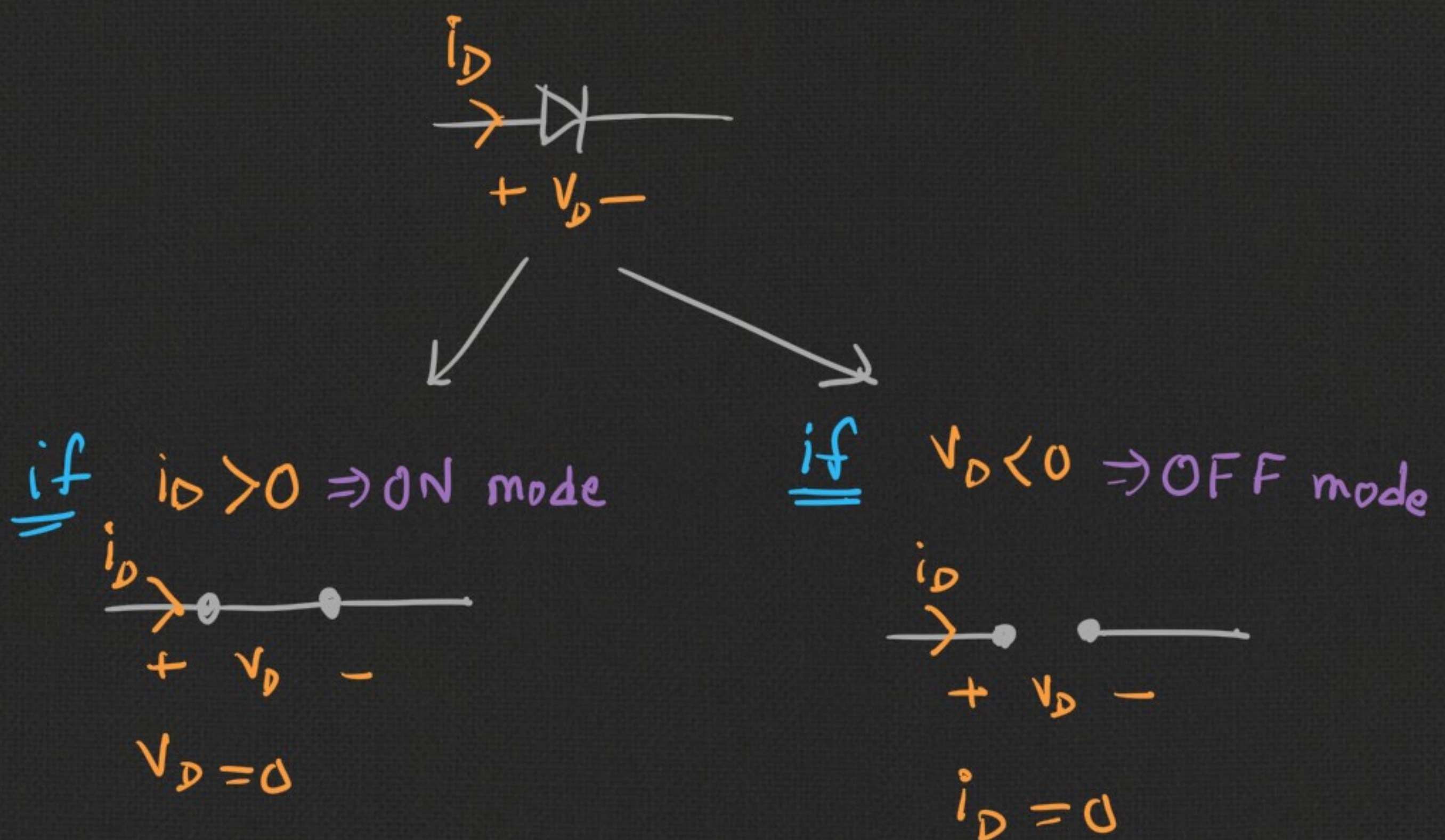Hence  $i_D = 0$  in this condition. This is called the **REVERSE BIAS** or **OFF** mode.




The corresponding IV curve:




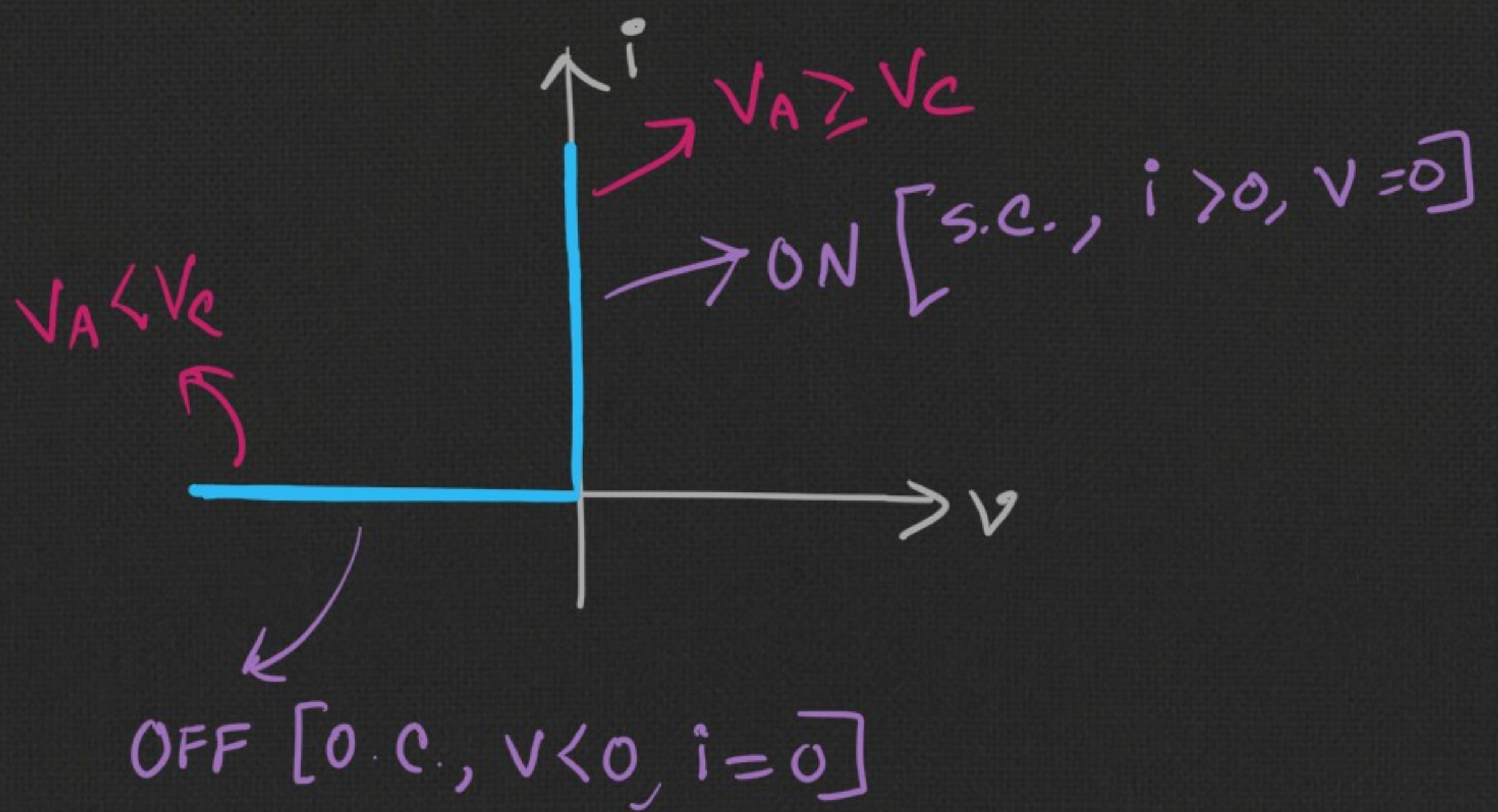

Circuit example [DC]

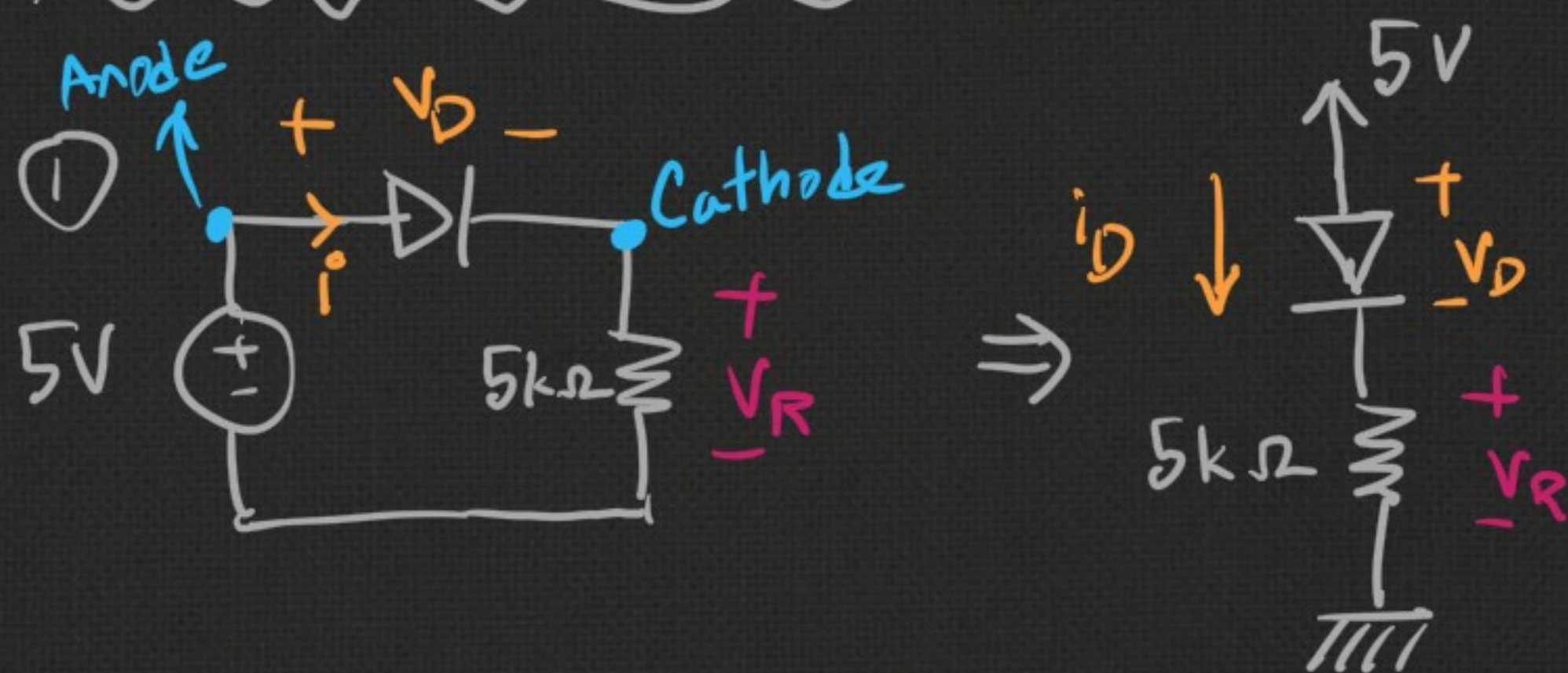

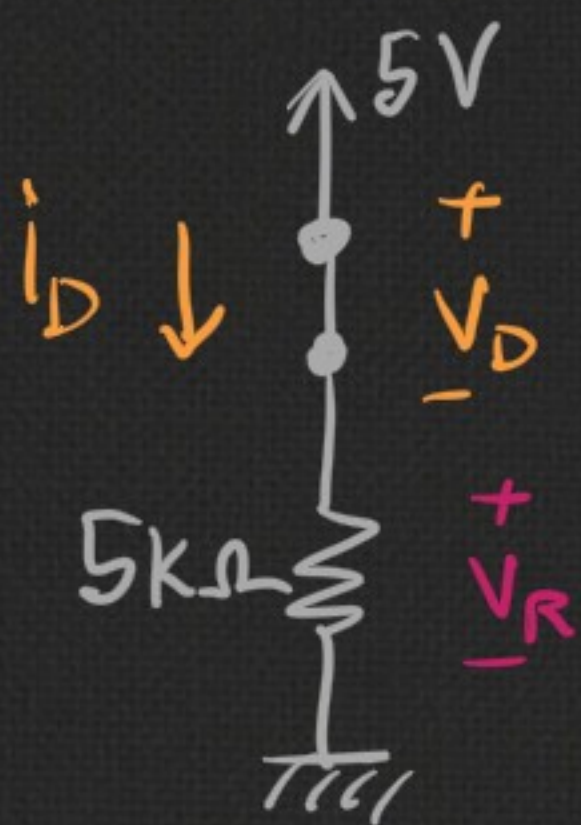Since  $5V > 0V \Rightarrow$  current will try to flow from A to C  $\Rightarrow i_D > 0 \Rightarrow$  Diode ON




$$V_D = 0 \text{ [short circuit]}$$

$$V_R = V_C - 0 = V_C = 5V$$


Potential of cathode  $\nwarrow$  Because cathode is shorted to 5V
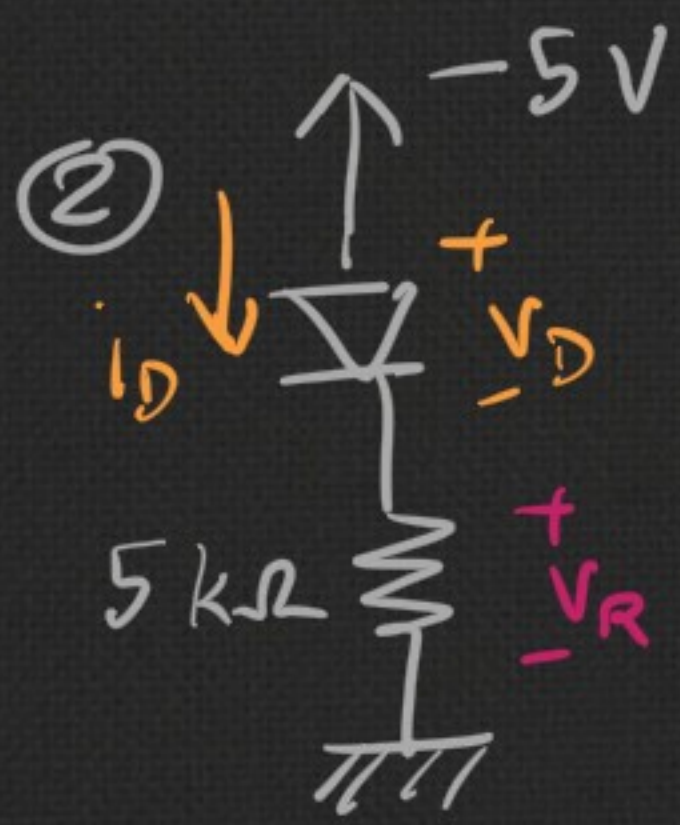
$$i_D = \frac{V_R}{R} = \frac{5V}{5k\Omega} = 1mA$$





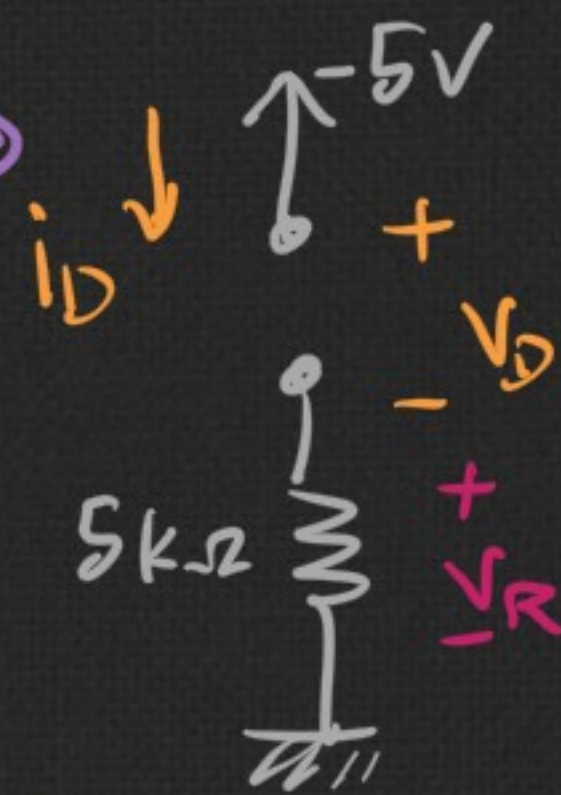Since  $V_A < V_C \Rightarrow V_D < 0 \Rightarrow \text{OFF mode}$   
 $\sim 0V$




$i_D = 0$  [open circuit]

$$V_R = iR = 0 \times 5k = 0$$

[Remember this!!!  
 if  $i$  through a  $R$  is 0,  
 the voltage across two  
 terminals will be equal]

$$V_D = V_A - V_C = -5V - 0V = -5V$$

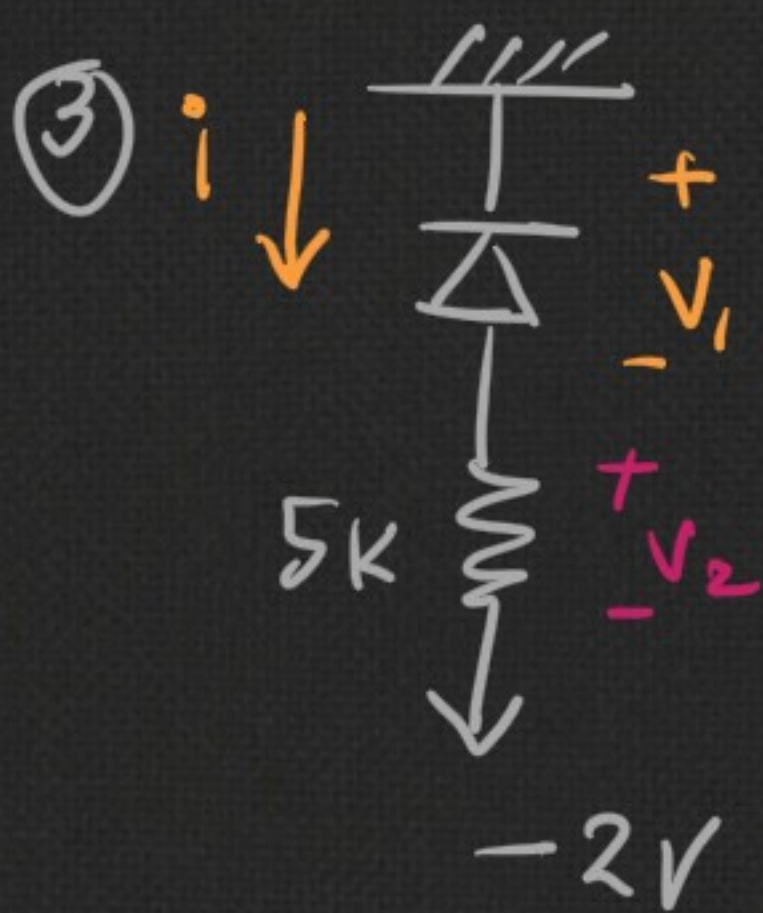
$\uparrow$  source       $\nwarrow$  Resistance



$V_A = 0V$  [Connected to GND]

$V_C \sim -2V$

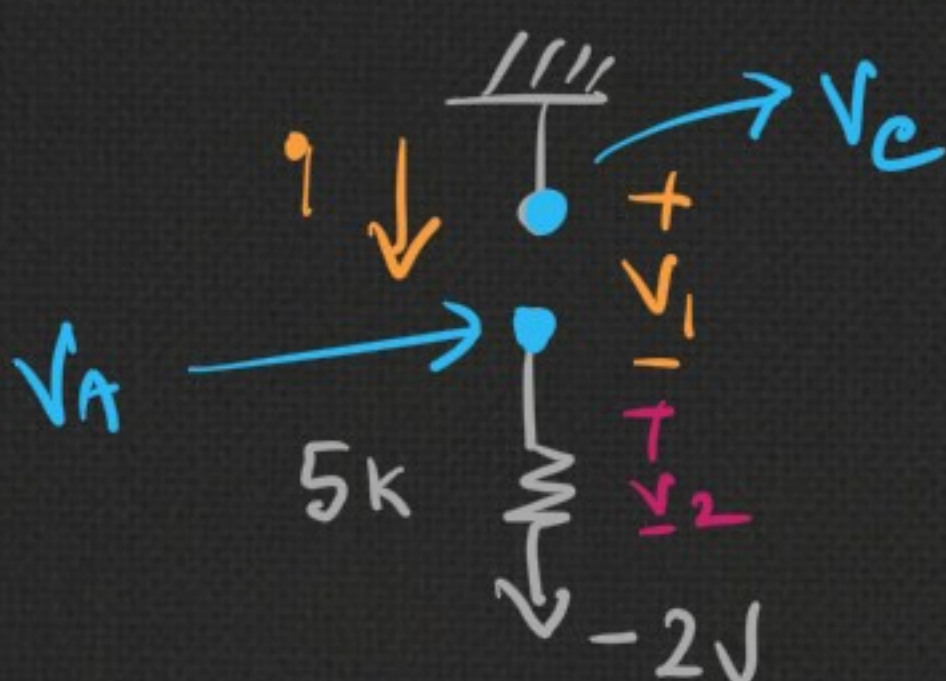So  $V_D < 0 \Rightarrow \text{OFF mode}$




$i = 0$  [open ckt]

Because the  $R$   
 is "shorted"

$$V_2 = i \times R = 0 \times 5k = 0 \Rightarrow V_A = -2V$$

$$V_1 = V_C - V_A = 0 - (-2) = 2V$$





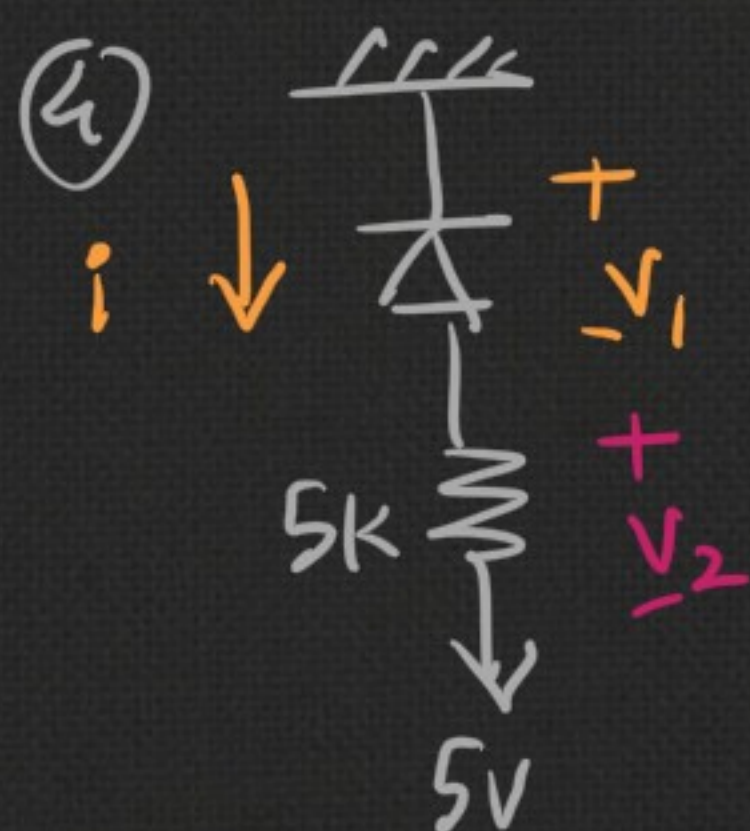


Find  $i$ ,  $V_1$ ,  $V_2$ . (Try yourself)

## Simple Application: Half-wave Rectifiers

First Step to Convert from AC to DC.

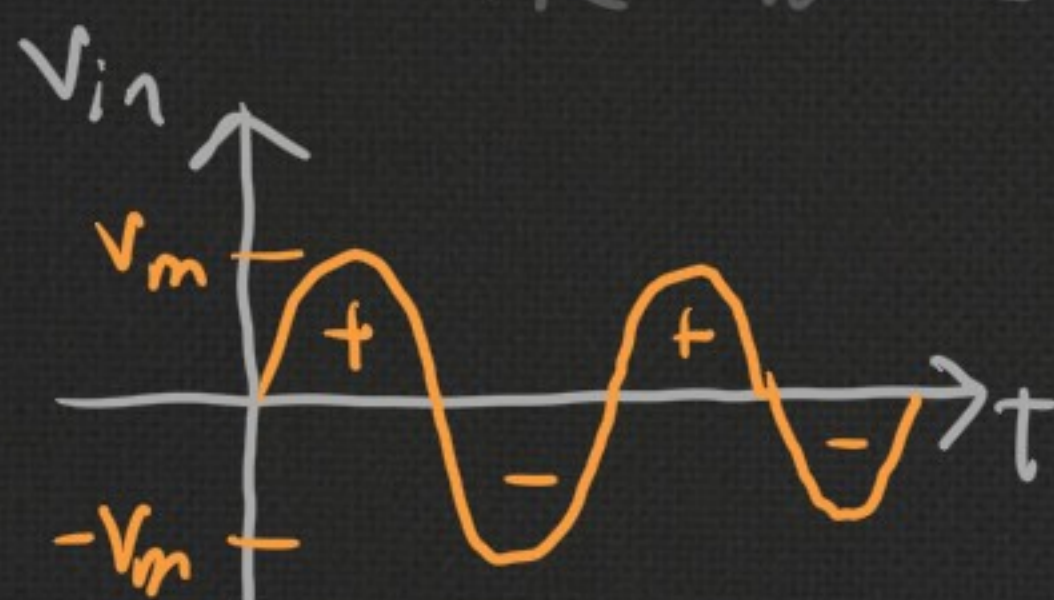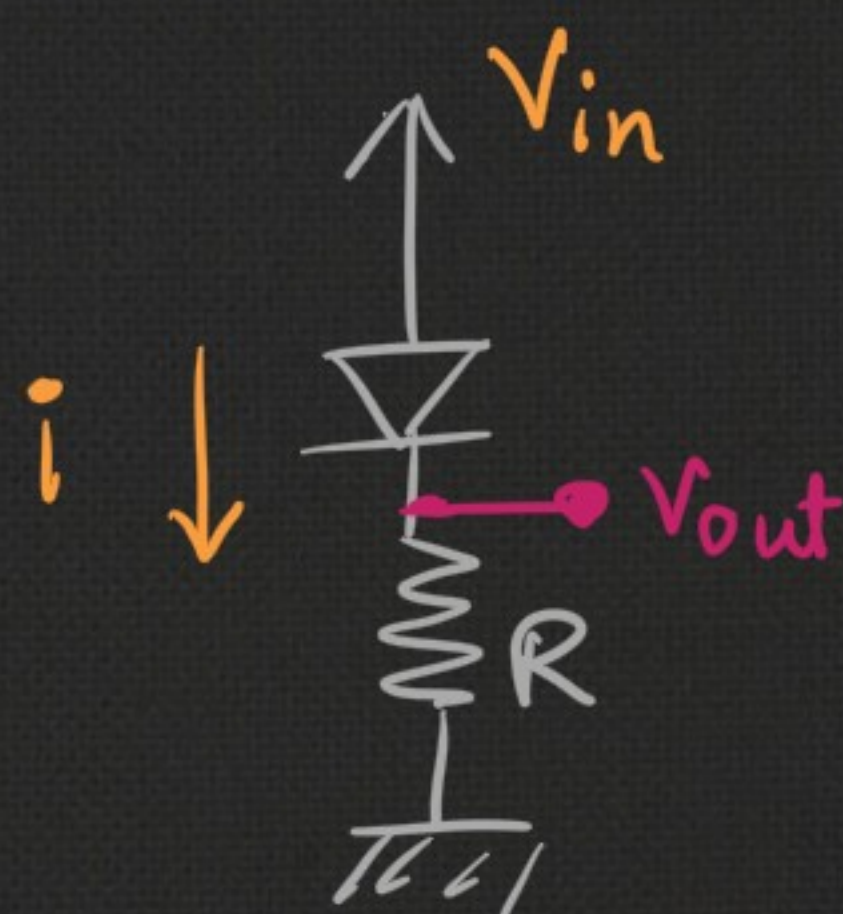

$V_{in} > 0$  [+ve half cycle]

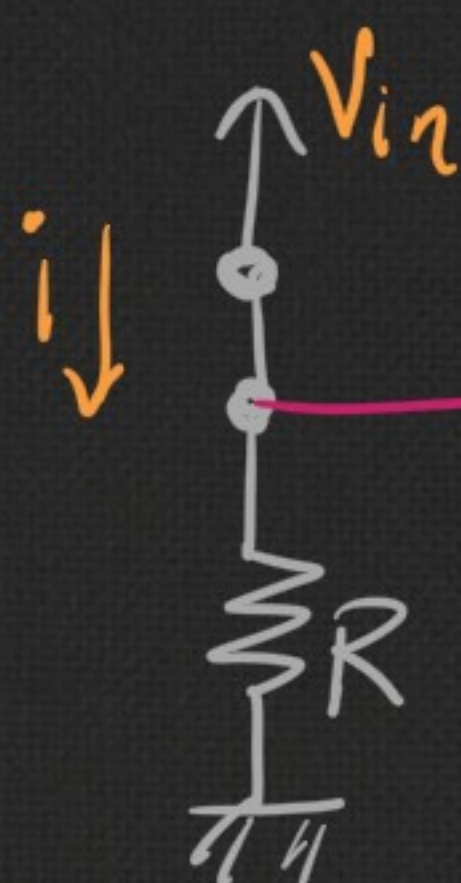

$$V_{out} = V_{in}$$

$$i = \frac{V_{in}}{R}$$

$y = x$ , st. line, going through origin,  $m=1$

$V_{in} < 0$  [-ve half cycle]



$$V_{out} = 0$$


$$i = 0$$

Diode is conducting

Diode is not conducting



## waveforms

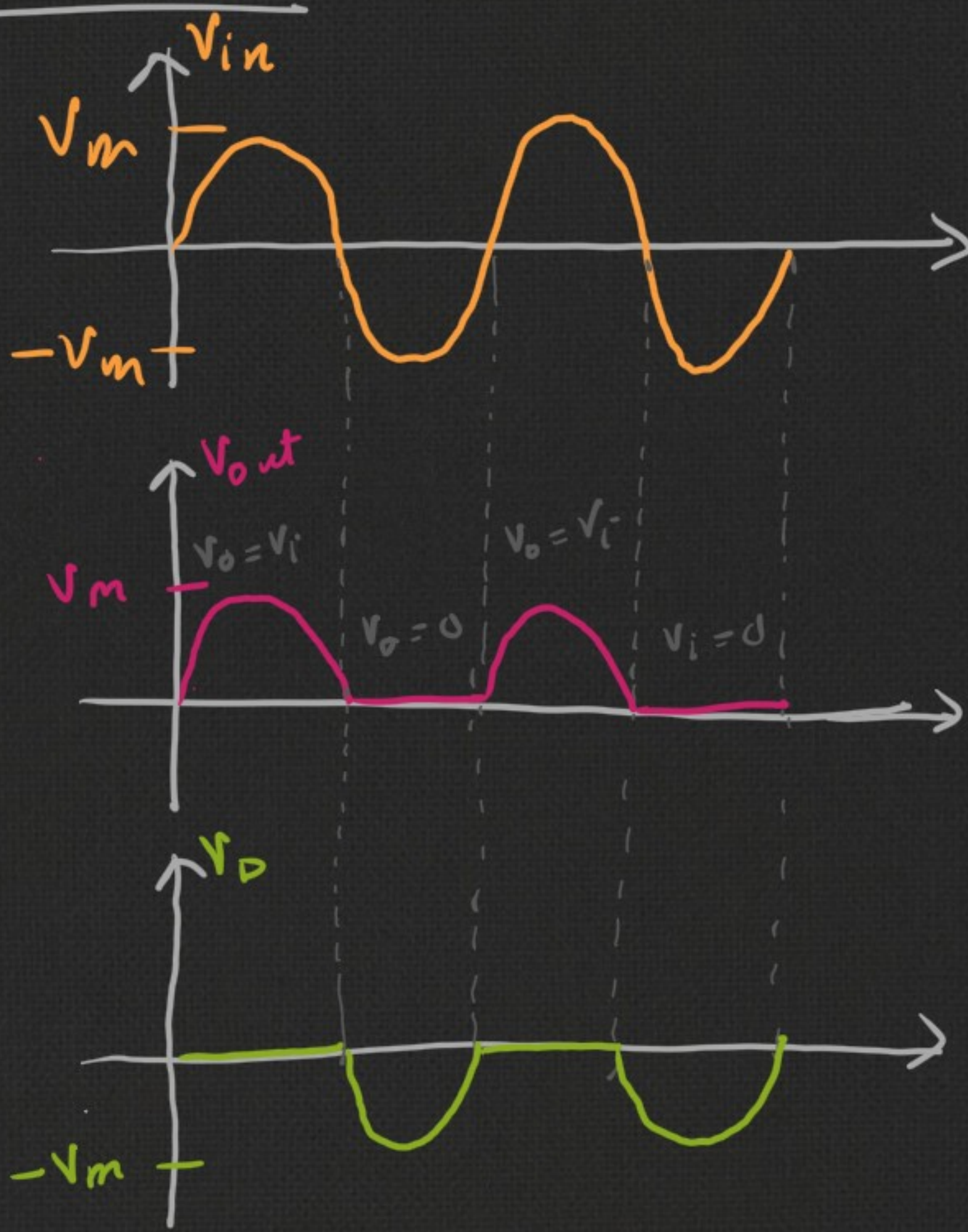

$$V_{in} = V_{out} + V_D$$

$$\Rightarrow V_D = V_{in} - V_{out}$$

## Transfer Characteristics

$\Rightarrow$  x axis  $\rightarrow$  input

$\Rightarrow$  y axis  $\rightarrow$  output

