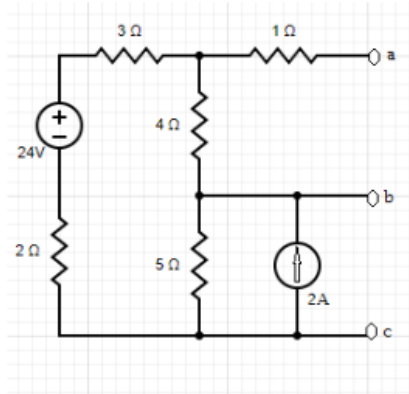


### Step 1

1 of 13

Solving for a:



### Step 2

2 of 13

To get  $R_{th}$ , we need to:

1. Turn off all the **independent sources**

So in our circuit:

**We put the 2A current source to zero.**


**We put the 24V voltage source to zero.**

2. Determine the  $R_{th}$  at the terminals a-b of the open circuit.

The input resistance is equal to the thevenin equivalent resistance

**Step 3**

3 of 13

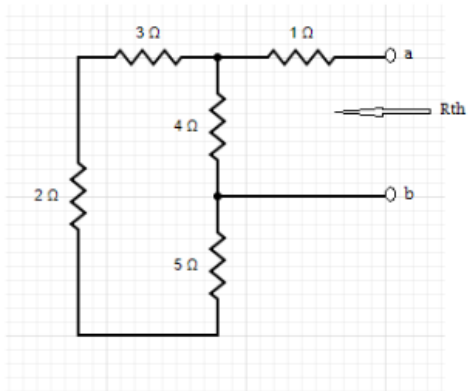**Step 4**

4 of 13

From the last figure:

The resistors  $5\ \Omega$  and  $3\ \Omega$  and  $2\ \Omega$  are in series and both are in parallel with the resistor  $4\ \Omega$ :


So the equivalent resistance of the three resistor is:

$$R_{eq} = (5 + 3 + 2) \parallel 4 = 10 \parallel 4 = \frac{10 \times 4}{10 + 4} = \frac{40}{14}\ \Omega$$

$$R_{th} = \frac{40}{14} + 1 = \frac{54}{14} = 3.857\ \Omega$$

### Step 5

5 of 13

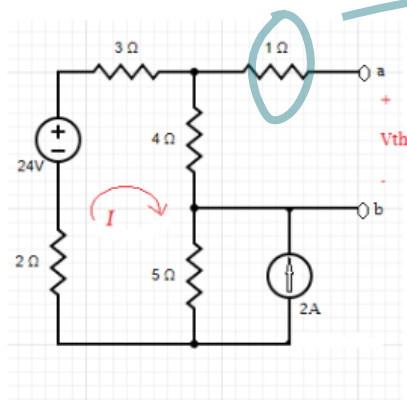

what about considering voltage across this 1 ohm resistance

### Step 6

6 of 13

Apply mesh analysis:

Apply KVL to the last circuit :

$$2I + 3I + 4I + 5(I + 2) - 24 = 0$$

$$14I + 10 - 24 = 0$$

$$14I = 14$$


$$I = 1A$$

$$V_{th} = 4I = 4 \times 1 = 4V$$

### Step 7

7 of 13

Thevenin equivalent circuit at a-b:

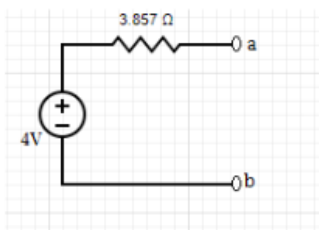


C - B / B - C ?

### Step 8

8 of 13

Solving for b:

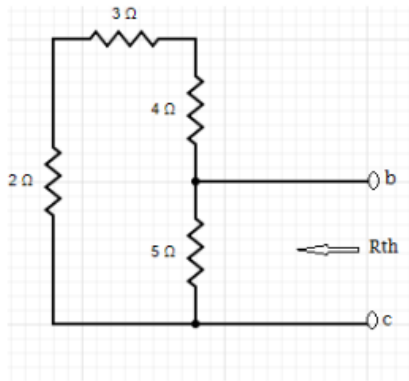

### Step 9

9 of 13

From the last figure:

The resistors  $4\Omega$  and  $3\Omega$  and  $2\Omega$  are in series and both are in parallel with the resistor  $5\Omega$ :

So the equivalent resistance of the three resistor is:


$$R_{eq} = (4 + 3 + 2) \parallel 5 = 9 \parallel 5 = \frac{9 \times 5}{9 + 5} = \frac{45}{14} \Omega$$

$$R_{th} = \frac{45}{14} = 3.214 \Omega$$

### Step 10

10 of 13

To get  $V_{th}$  at b-c:

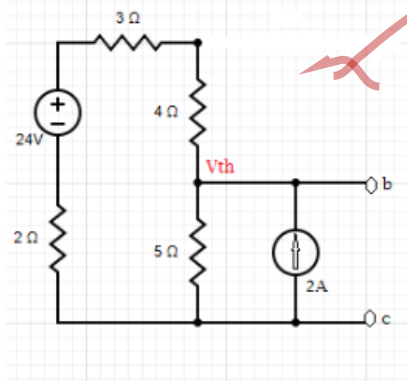

$1 \Omega$   
??

### Step 11

11 of 13

Apply nodal analysis to the previous circuit:

Apply KCL at the node  $V_{th}$ :

$\{\text{\color{#4257b2}}\}$

$$\frac{V_{th} - 24}{4 + 3 + 2} + \frac{V_{th}}{5} - 2 = 0$$

$$\frac{V_{th} - 24}{9} + \frac{V_{th}}{5} = 2 \quad \text{multiply by 45}$$

$$5V_{th} - 120 + 9V_{th} = 90$$

$$14V_{th} = 210$$

$$V_{th} = 15V$$

### Step 12

12 of 13

Thevenin equivalent circuit at b-c:

