

# Department of Computer Science and Engineering (CSE) BRAC University

Summer 2022

CSE250 – Circuits and Electronics

Open circuit, Short circuit, Nodal analysis




Purbayan Das, C. Lecturer  
Department of Computer Science and Engineering (CSE)  
BRAC University
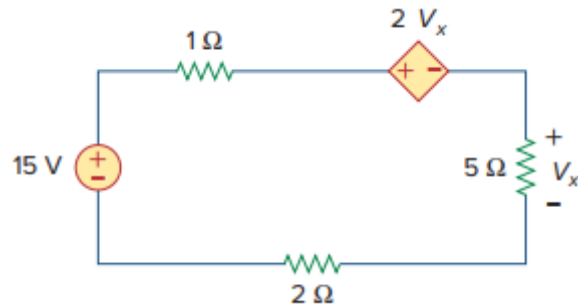
# Ground

- Except for a few special cases, electrical and electronic systems are grounded for reference and safety purposes.




- In general, the placement of the ground connection will not affect the magnitude or polarity of the voltage across an element but it may have a significant impact on the voltage from any point in the network to ground.*



# Example 1

For the series network shown below, determine

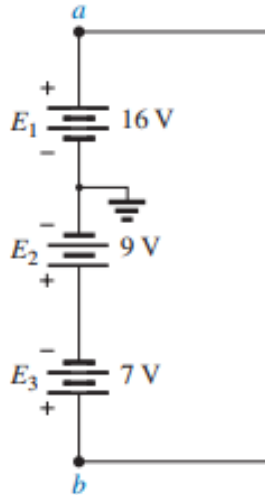- i) The voltage  $V_a$ .
- ii) The voltage  $V_b$ .
- iii) The voltage  $V_{ab}$




Ans: (i)  $V_a = 16 \text{ V}$   
(ii)  $V_b = 16 \text{ V}$   
(iii)  $V_{ab} = 0 \text{ V}$

# Example 2

For the series network shown below, determine


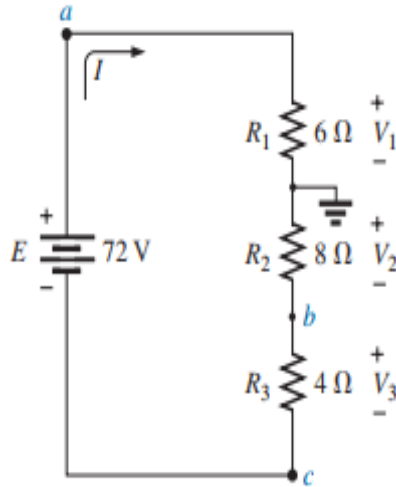
- i) The voltage  $V_a$ .
- ii) The voltages  $V_b$  and  $V_c$ .
- iii) The voltage  $V_{ab}$



Ans: (i)  $V_a = 24 \text{ V}$   
(ii)  $V_b = -32 \text{ V}$ ;  $V_c = -48 \text{ V}$   
(iii)  $V_{ab} = 56 \text{ V}$

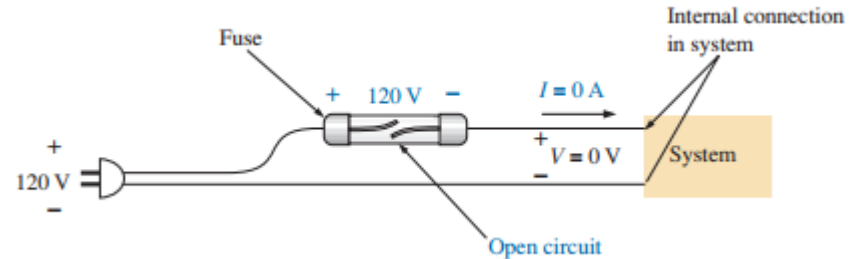
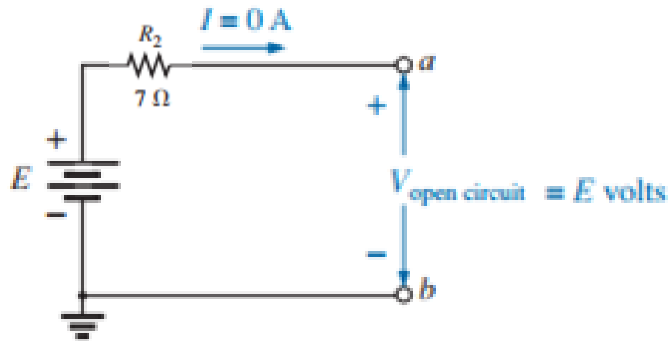
# Open circuit

- An **open circuit** is two isolated terminals not connected by an element of any kind
- *An open circuit can have a potential difference (voltage) across its terminals, but the current is always zero amperes*







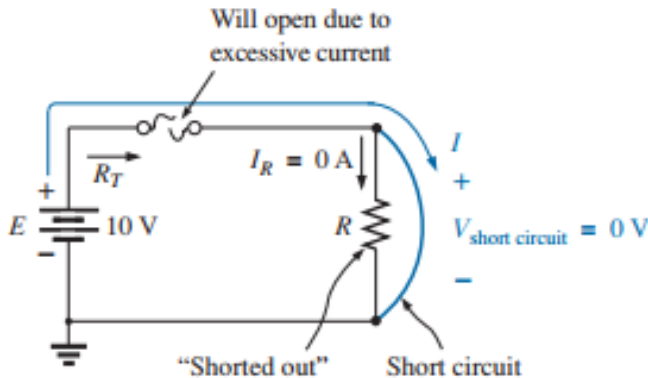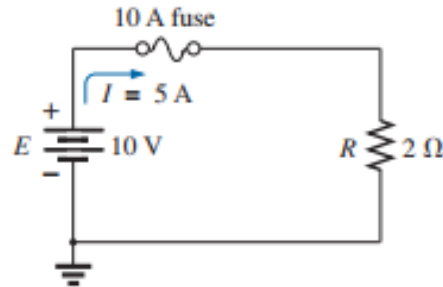
# Short circuit

- A **short circuit** is a very low resistance, direct connection between two terminals of a network
- *A short circuit can carry a current of a level determined by the external circuit, but the potential difference (voltage) across its terminals is always zero volts.*



# I-V characteristics

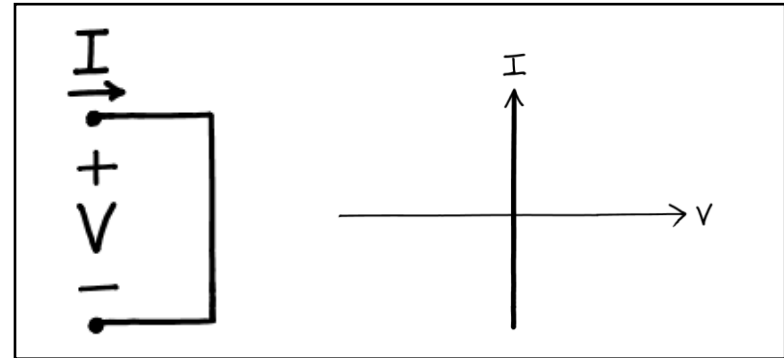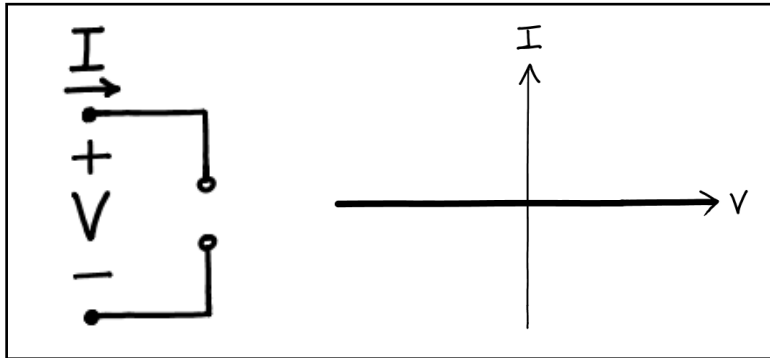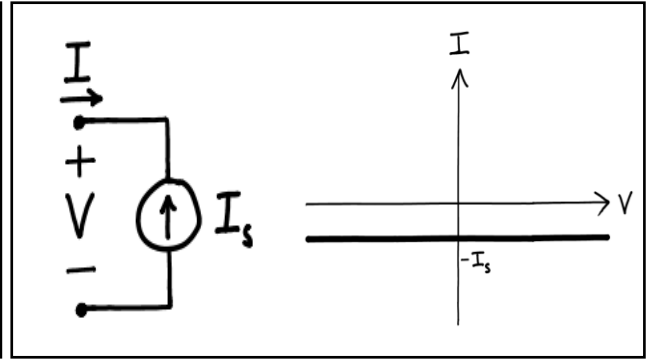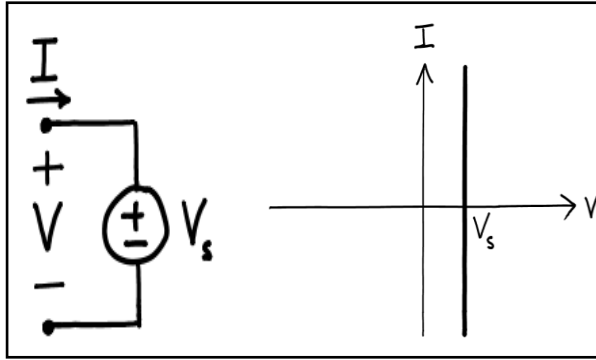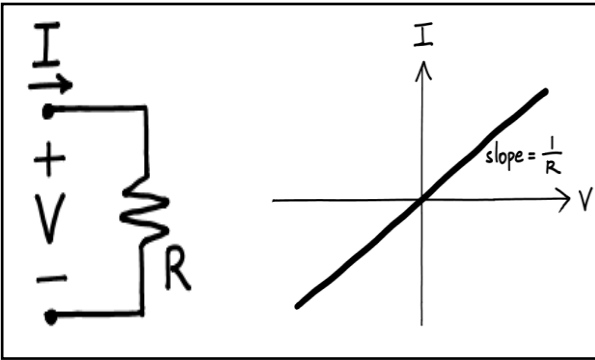

# Circuit laws, method of analysis, & theorems

## Laws

- Ohm's Law
- Kirchhoff's current law
- Kirchhoff's voltage law

## Method of analysis

- Nodal analysis
- Mesh analysis

## Theorems

- Superposition theorem
- Source transformation
- Thevenin's theorem
- Norton's theorem
- Maximum power transfer theorem



# Nodal analysis


- Nodal analysis provides a general procedure for analyzing circuits using node voltages as the circuit variables

## Steps to Determine Node Voltages:

1. Select a node as the reference node. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n - 1$  nodes. The voltages are referenced with respect to the reference node.
2. Apply KCL to each of the  $n - 1$  nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.

# Example 3


- Find all the node voltages

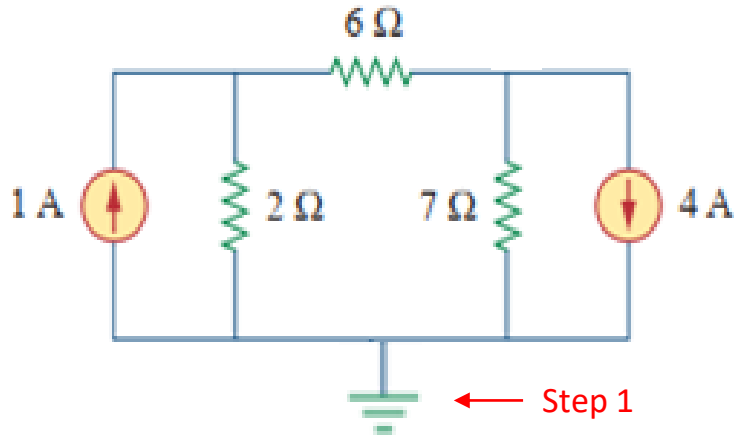

Ans: - 2 V; - 14 V; 0 V

# Example 4


- Find  $V_a$  using nodal analysis

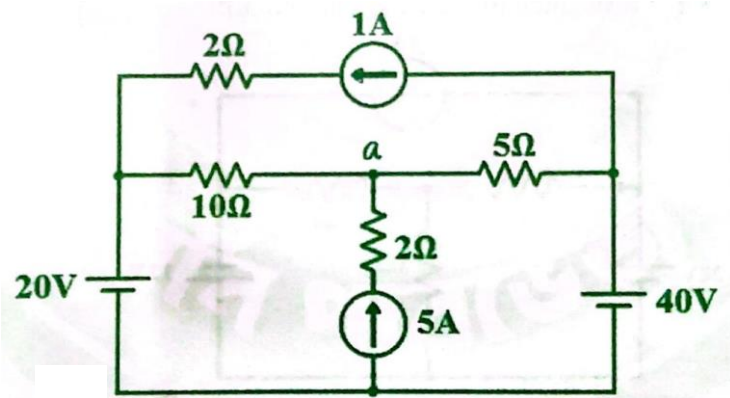

Ans:  $V_a = 50 \text{ V}$

# Example 5


- Find  $i_0$  using nodal analysis

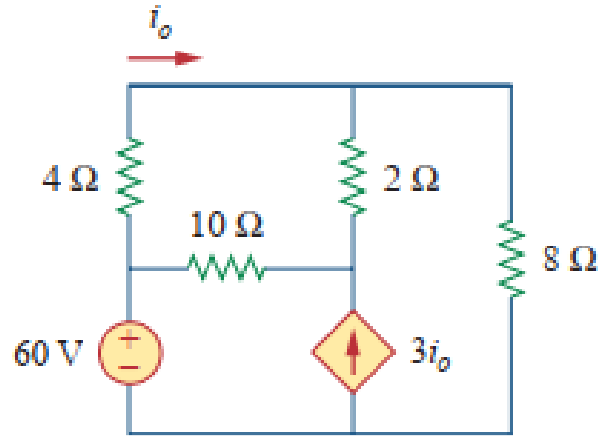

Ans:  $i_0 = 1.73\text{ A}$
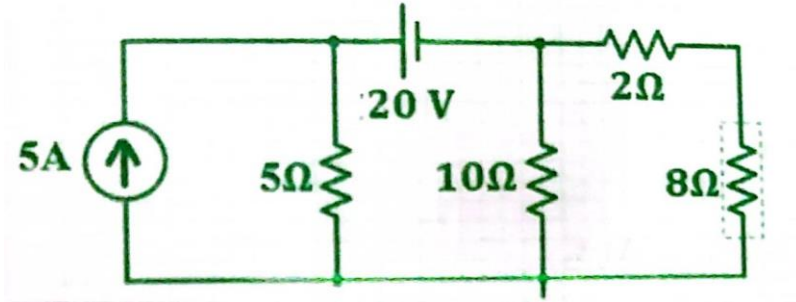
## Example 6


- Find voltages across the current source and across the  $8\ \Omega$  resistor using nodal analysis



Ans:  $22.5\text{ V}$ ;  $2\text{ V}$

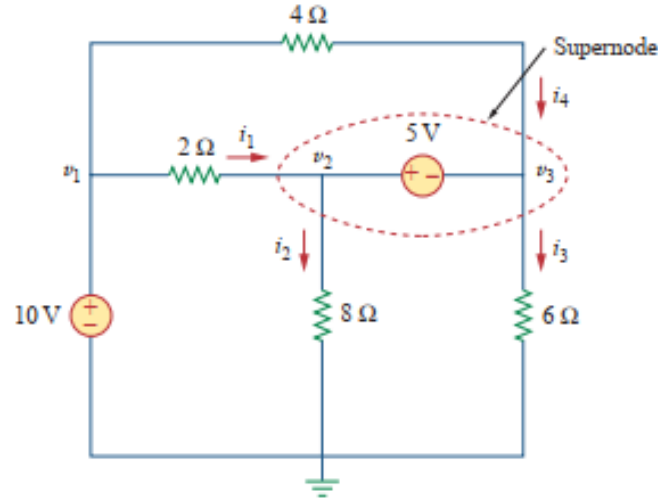
# Supernode

- A **supernode** is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.



# Example 7


- Find  $i_0$  using nodal analysis

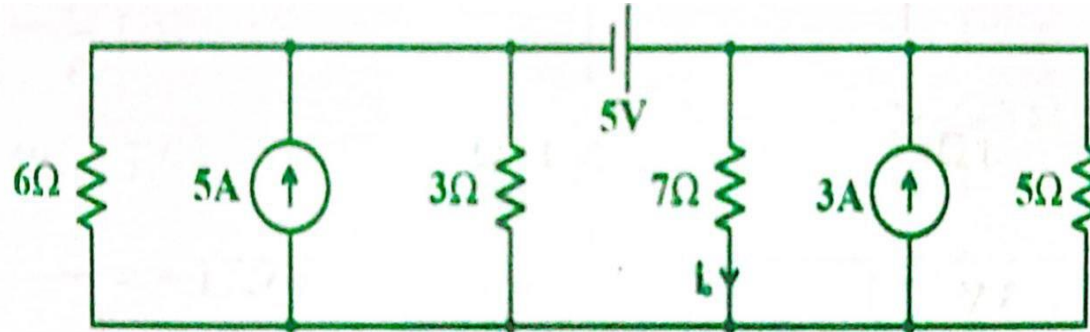

Ans:  $i_0 = 1.78\text{ A}$
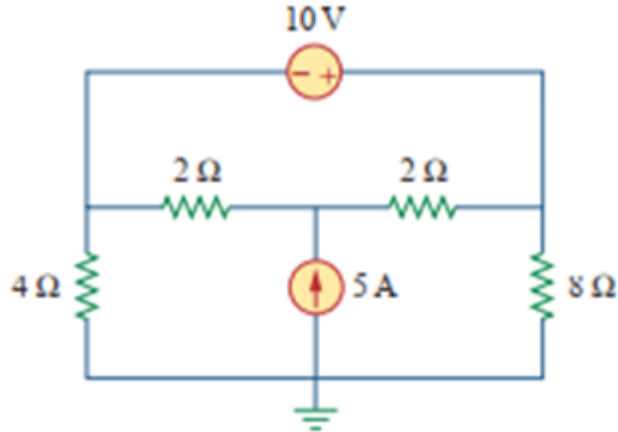
# Example 8

- Determine the node voltages using nodal analysis




Ans: 10 V; 20 V; 20 V; 0 V



# Example 9

- Find  $v_1$ ,  $v_2$ ,  $v_3$

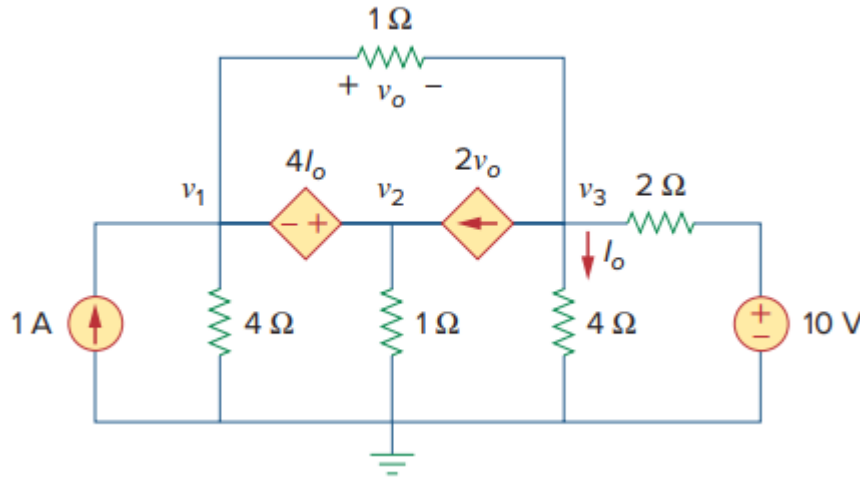


Ans:  $v_1 = 2.61 \text{ V}$ ;  $v_2 = 2.78 \text{ V}$ ;  $v_3 = 0.17 \text{ V}$
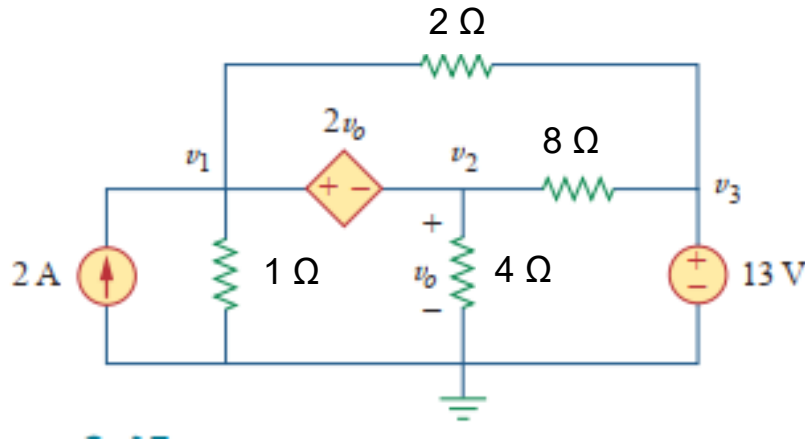
# Example 10




- Determine voltages through in the circuit using nodal analysis.



Ans:  $v_1 = 6.23 \text{ V}$ ;  $v_2 = 2.08 \text{ V}$ ;  $v_3 = 13 \text{ V}$
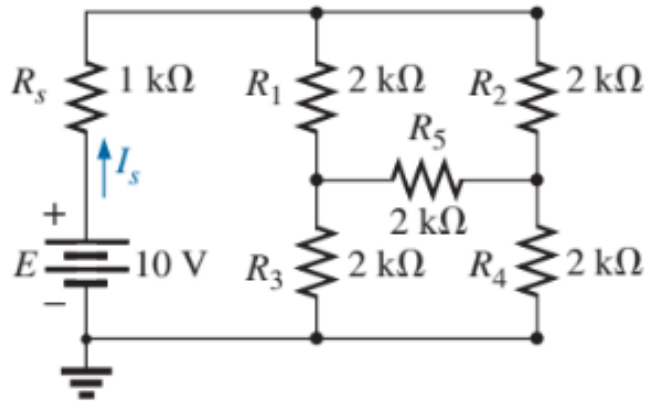
# Example 11


- Determine the current through the source resistor  $R_s$  using nodal analysis



Ans:  $i_s = 3.33\text{ mA}$
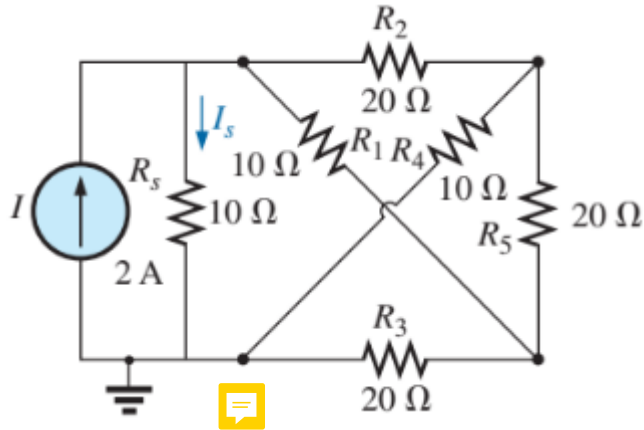
# Example 12

- Determine the current through the source resistor  $R_s$  using nodal analysis



Ans:  $i_s = 1.18 \text{ A}$

# Thank you for your attention