

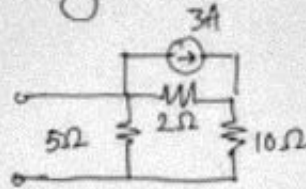
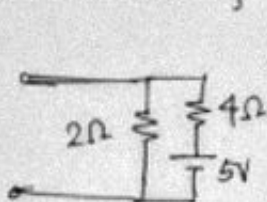
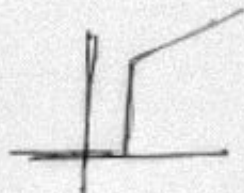
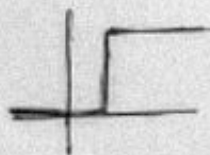


I-V characteristics (Practice Problems)

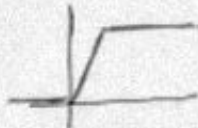1. Find the I-V of the following circuits:



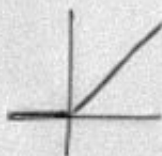2. For the following I-V graphs, which region behaves like which circuit?



3. For the given circuits, the region AB behaves like a Voltage Source + Resistance (or, Current Source + Resistance). Find the value of Voltage Source/Current Source and Resistance.

