

Time Domain is a time quantity

Real quantity

Phasor-domain is independent of time

Complex quantity

- Transform sinusoids to phasors \Rightarrow For a particular circuit we either sin or cos for all the conversions in that circuit, Not both.

In AC circuits, current $\neq 0$ (I) even if capacitors connected

So, $i = C \frac{dV}{dt}$ \rightarrow V is not constant, so capacitor is not open nor the i.

$$\# \int V(t) dt = \frac{V_m \angle \phi}{j\omega}$$

$$\frac{dV(t)}{dt} = j\omega \cdot V_m \angle \phi$$

Integrating means in phasor domain dividing by $j\omega$ and diff means multiplying by $j\omega$.

DC circuits

- 1) Resistance (R)
- 2) Capacitor has ∞
- 3) Inductor has 0

AC circuits
Impedance (Z)

- 2) $Z_C = \frac{1}{j\omega C}$
- 3) $Z_L = j\omega L$
- 4) $Z_R = R$

Example (capacitor's Z_C) :

Calculation

$$2 - j 1.06 \times 10^{-3}$$

My answer:

$$\textcircled{1} 2.000 \angle -5.299 \times 10^{-4}$$

$$\textcircled{2} 2 \angle -0.03^\circ$$

write
1j/i instead
of just j/i

$$(0.5 + j)$$

$$C = (0.5 + 1j)$$

$$\# (j.05)^{-1}$$

impedance is also a c.
 $2 - j 1.06 \times 10^{-3}$
Polar form
 $2 \angle -0.03^\circ$
① Shift +2
② option 2
③ (=)

addition using calculator
 $V_1 + V_2 = 20 \angle 45^\circ + 10 \angle 0^\circ$
 $\square + j \square$
 $\square \angle \square$

$$\# \frac{1}{j \times 100 \pi \times 3}$$

$$\textcircled{2} Z_L = j \omega L = j \times 100 \pi \times$$

$$\textcircled{3} Z_C = \frac{1}{j \omega C}$$

complex form: $(j200\pi + \frac{1}{j200\pi}) \parallel (\frac{1}{j300\pi}) + 2$

- ① complex mode
- ② shift + ENTER (i) = j
- ③ write j at the end (200 x π x j)

\rightarrow radian form
 \rightarrow $\frac{1}{j300\pi}$
 \rightarrow why minus
 $2 = j200\pi$
 $\frac{1}{j200\pi} \times 2 = \frac{1}{j200\pi}$

$\pi = 3.1416$
 Normal
 calculation
 \rightarrow still
 valid for
 later comparison

$$Q \quad \frac{102.67 \angle -65.33^\circ}{1.06 \angle -135^\circ}$$

$$= 96.86 \angle 67.67^\circ$$

$$Q \quad \frac{-1.25j}{8 - 1.25j} \times 75 \angle 0^\circ$$

$$\dots \rightarrow -81.11^\circ$$

* $\begin{pmatrix} + \\ - \end{pmatrix}$ $\begin{pmatrix} 1 \end{pmatrix}$
source short
vs gm, open


Example (Capacitors Z_C)



$$Z_C = \frac{1}{j\omega C}$$

$$Z_{eq} = \frac{1}{j\omega C} + R \quad \left[\text{As } Z_C \text{ and } R \text{ in series} \right]$$

for induction

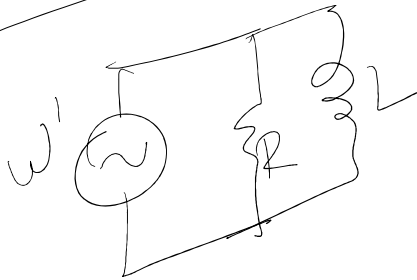

$$Z_{eq} = (Z_R \parallel Z_L)$$

$$Z_R = R$$

$$Z_L = j\omega L$$

Nodal Analysis: Hacks

① Divide by each denominator after forming the eq.

$$\frac{V_1 - 75\angle 0^\circ}{4} + \frac{V_1}{j4} + \frac{V_2}{-j1} + \frac{V_2}{2} = 0$$

$$0.25V_1 - 18.75\angle 0^\circ - j0.25V_1 + jV_2 + 0.5V_2 = 0$$

use brackets while
inverting a complex num

$$\#_-(-10 \angle 0^\circ)$$

mins mid ⁹⁰
cal/s for error
to correct by adding

$$= 11.58 \angle -81.11^\circ$$

$$Q \ 0.53 \angle -86.24^\circ \times 6 \angle$$

$$= 3.18 \angle -86.24^\circ$$

$$Q) \ 11.58 \angle -81.11 - 90^\circ +$$

$$\Rightarrow 12.28 \angle -156.11^\circ$$

$$12.28 \cos(5t - 156.11^\circ)$$

$+ 180^\circ$

0° air gap open
no check
(Therm in res
ap ✓ check)

3.18 -86.24°

6°
5.16°)

$\therefore 0.25 V_1 - 15.75 V_2 = 0$
 2 For solving equations: Cramer's Rule

Superposition:

(a) $\underbrace{11.58 \angle -81.11^\circ}_{\sin} + \underbrace{3.18 \angle -86.24^\circ}_{\cos}$

$\omega = 5$

$\omega = 2$

$\neq \omega_1 \neq$

So not

→ can not

+ (b) $11.58 \sin(5t - 81.11^\circ) + 3.18 \cos(2t)$


4

ω_2
valid

add them if $\omega_1 \neq \omega_2$

-86240/

5

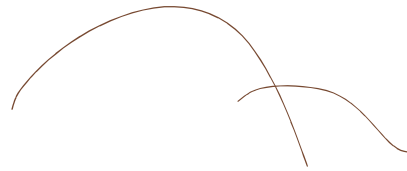

$$= 12.28 \cos(30^\circ)$$

$$Q = -50 \angle 30^\circ - 60$$

$$\Rightarrow -106.28 \angle$$

90°


13.6°

$$y(t) = 11.58 \sin(5t - 81^\circ) + 3.18 \cos(\omega t)$$

$$\text{if } \omega_1 = \omega_2 \quad \circ$$

bring them in the same function first

-86.240/

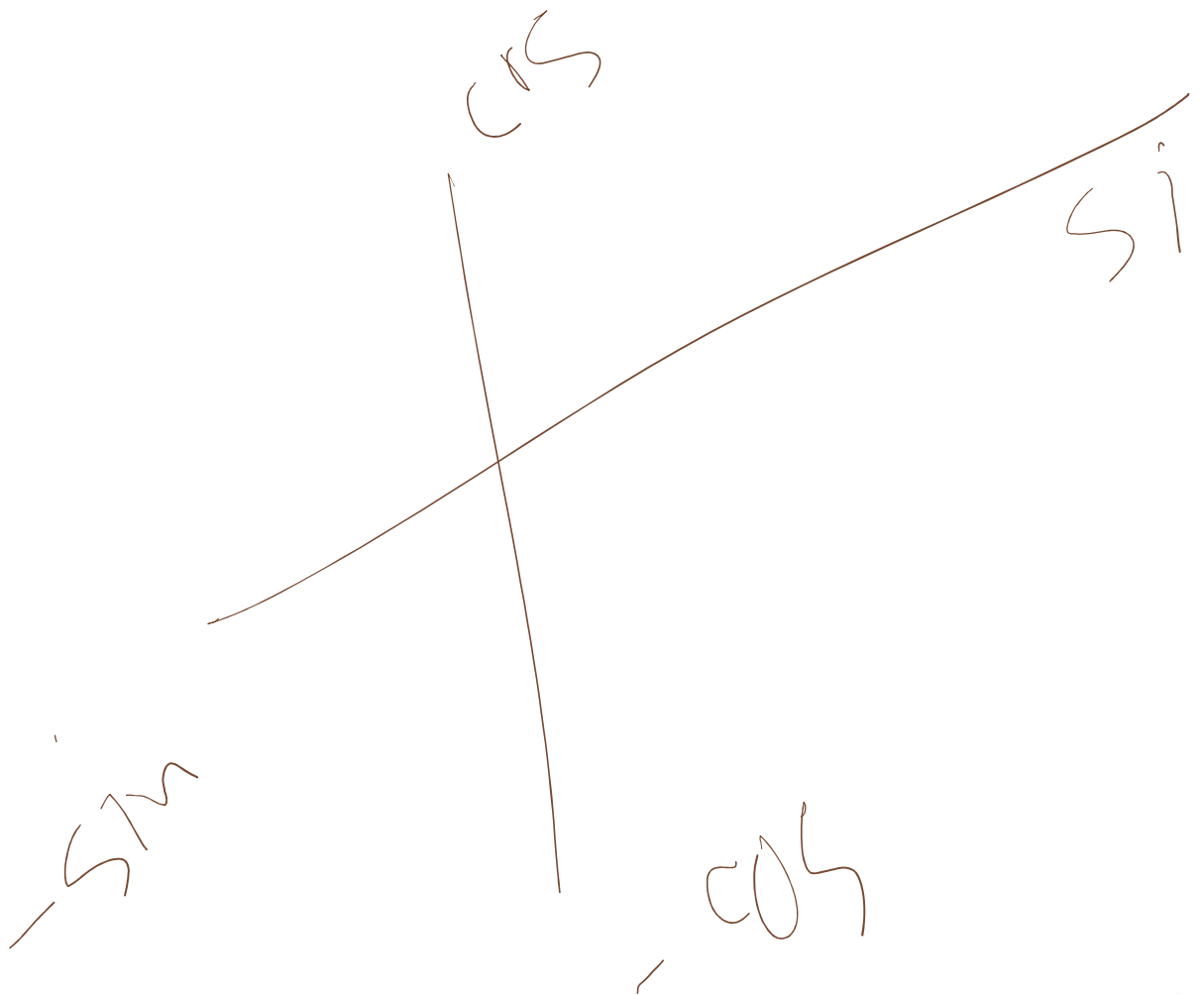

in (67-20

W

9

2

$$11 \sin \theta$$

$$= 11 \cos \theta$$



