

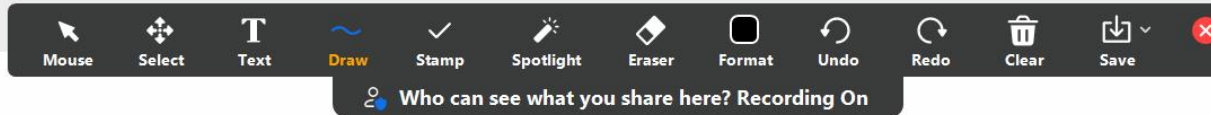


Lecture 8: Method of assumed state

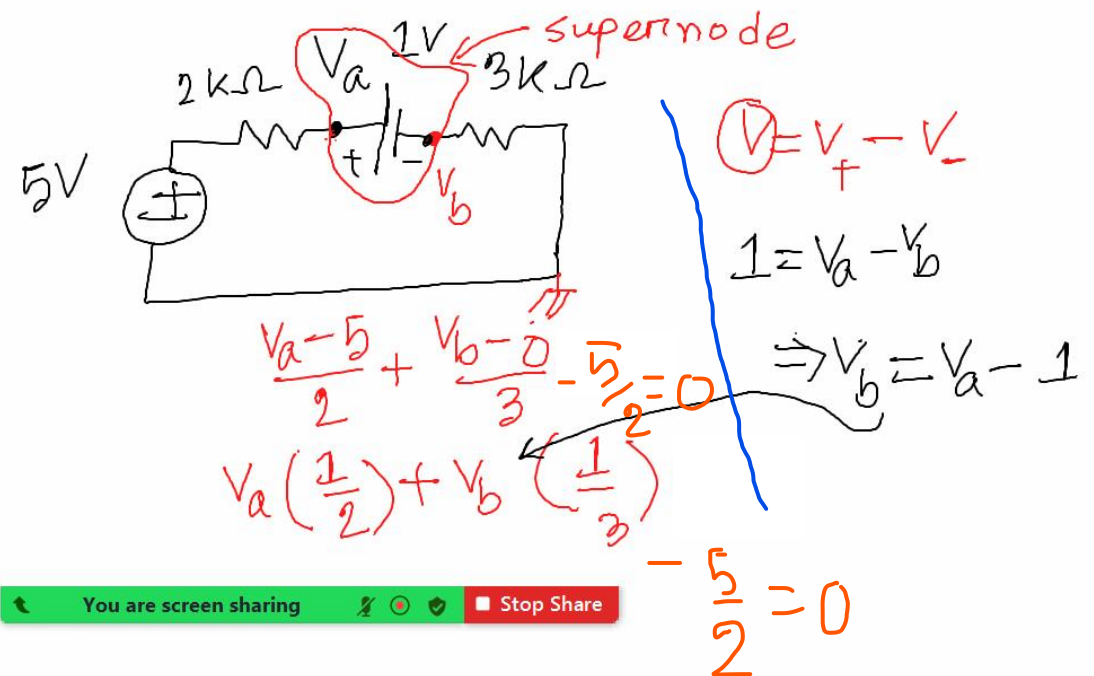


Review:

When should we consider a 'supernode' in nodal analysis?

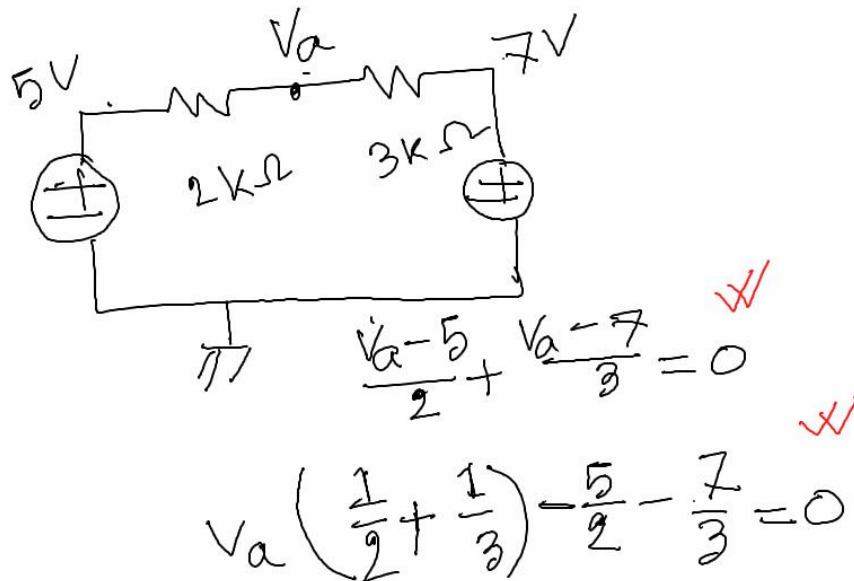


Lecture 8: Method of assumed state

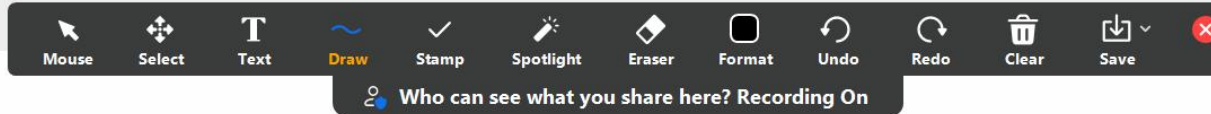



Review:

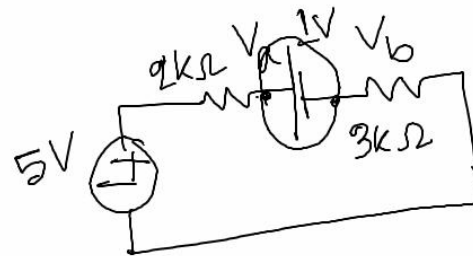When should we consider a 'supernode' in nodal analysis?



$$V_a \left(\frac{1}{2} \right) + V_b \left(\frac{1}{3} \right) - \frac{5}{2} = 0$$
$$V_a - V_b = 1$$

Lecture 8: Method of assumed state

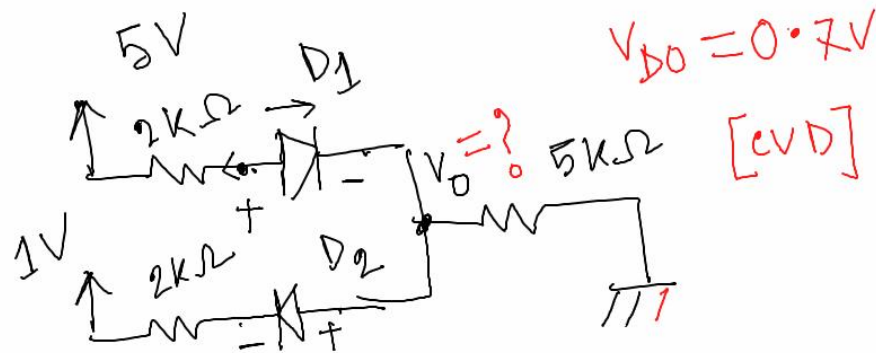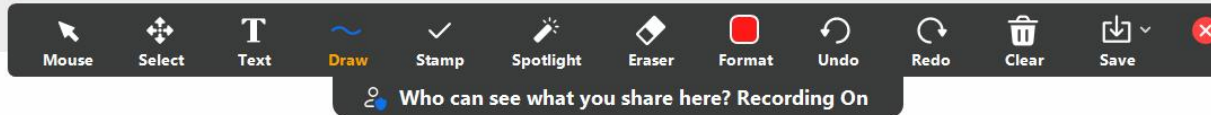

$$0.7 = V_+ - V_-$$

$$\Rightarrow 0.7 = V_a - V_0 \Rightarrow V_0 = V_a - 0.7$$

at V_a ,

$$\frac{V_a - 5}{2} + \frac{V_0 - 0}{5} = 0$$


$$V_a \left(\frac{1}{2} \right) + V_0 \left(\frac{1}{5} \right) - \frac{5}{2} - \frac{0}{5} = 0$$

$$\Rightarrow V_a \left(\frac{1}{2} \right) + (V_a - 0.7) \frac{1}{5} - \frac{5}{2} = 0$$

$$\begin{cases} V_a = 3.77V \\ V_0 = V_a - 0.7 = 3.07V \end{cases}$$

Step 1: D_1 ON, D_2 OFF

Step 2:

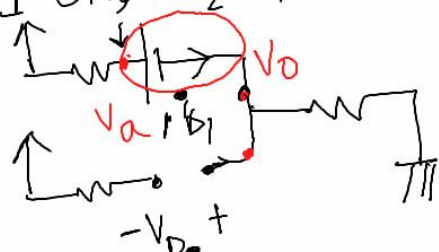

Step 3: $i_{D1} = \frac{5 - V_a}{2} = \frac{5 - 3.77}{2} > 0$

$$V_{D2} = V_a - V_c = V_0 - 1 = 3.07 - 1 = 2.07 < 0.7$$


\therefore assumption wrong

Lecture 8: Method of assumed state



Who can see what you share here? Recording On

S + 1: D_1 ON, D_2 ON

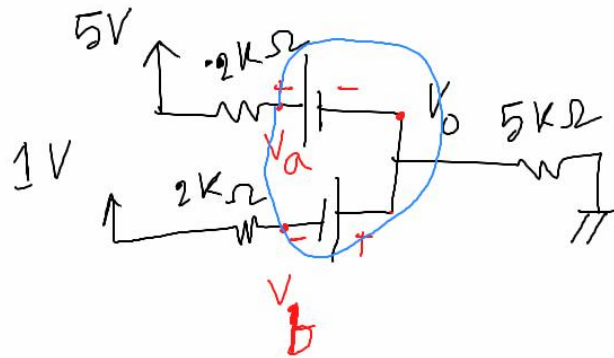

$$V_a - V_o = 0.7$$

$$V_o - V_b = 0.7$$

$$V_b = V_o - 0.7$$

$$= V_a - 0.7 - 0.7$$

$$= V_a - 1.4$$

$$V_o = V_a - 0.7$$

$$= 2V$$

$$V_b = V_o - 0.7$$

$$= 1.3V$$

$$i_{D1} = \frac{5 - V_a}{2} = 1.15 > 0$$

$$i_{D2} = \frac{V_b - 1}{2} = 0.15 > 0$$

$$\frac{V_a - 5}{2} + \frac{V_o - 0}{5} + \frac{V_b - 1}{2} = 0$$

$$V_a \left(\frac{1}{2} \right) + V_o \left(\frac{1}{5} \right) + V_b \left(\frac{1}{2} \right) - \frac{5}{2} - \frac{1}{2} - \frac{0}{5} = 0$$


$$V_a \left(\frac{1}{2} \right) + (V_a - 0.7) \frac{1}{5} + (V_a - 1.4) \frac{1}{2} = \frac{5}{2} + \frac{1}{2}$$

$$V_a = 2.7V$$

You are screen sharing

Stop Share


Lecture 8: Method of assumed state

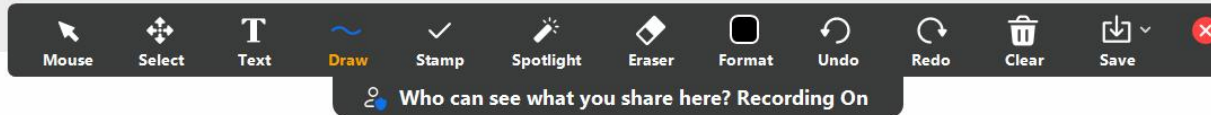

$$5 - V_a = 0.8 \Rightarrow V_a = 4.2 \text{ V}$$

$$V_b - (-5) = 0.8$$

$$\Rightarrow V_b = -4.2 \text{ V}$$

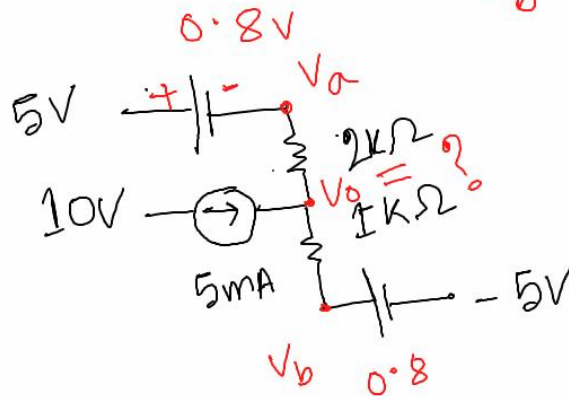

$$\Rightarrow V_b \frac{3}{2} - \frac{4.2}{2} - \frac{-4.2}{1} = 5$$

$$\Rightarrow V_b = 1.93 \text{ V}$$

$$i_{D1} = \frac{V_a - V_b}{2}$$

$$= \frac{4.2 - 1.93}{2} > 0$$



$$i_{D2} = \frac{V_b - V_b}{1}$$

$$= 1.93 - (-4.2) > 0$$

$$\text{at } V_0, \quad \frac{V_0 - V_a}{2} + \frac{V_0 - V_b}{1} - 5 = 0$$


$$\Rightarrow V_0 \left(\frac{1}{2} + \frac{1}{1} \right) - \frac{V_a}{2} - \frac{V_b}{1} - 5 = 0$$

Lecture : Half-wave rectifier

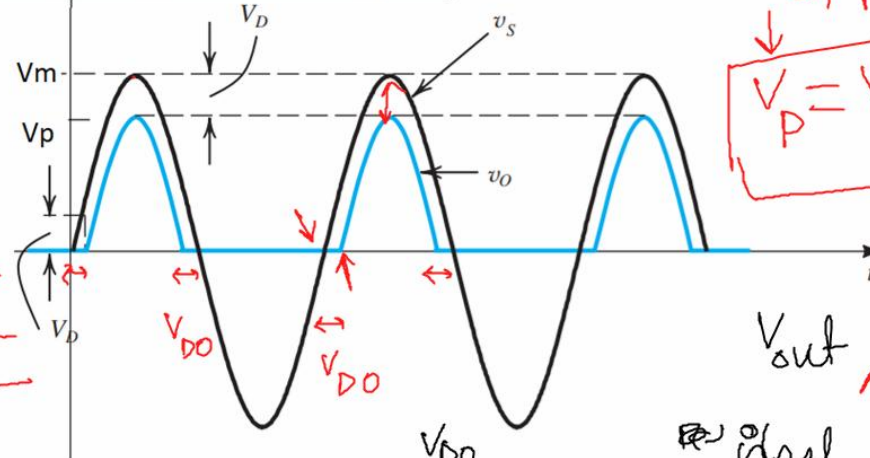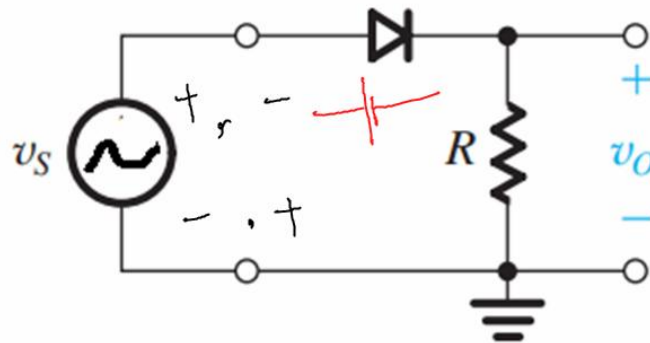

o/p q/p



$$V_p = V_m - V_{D0}$$

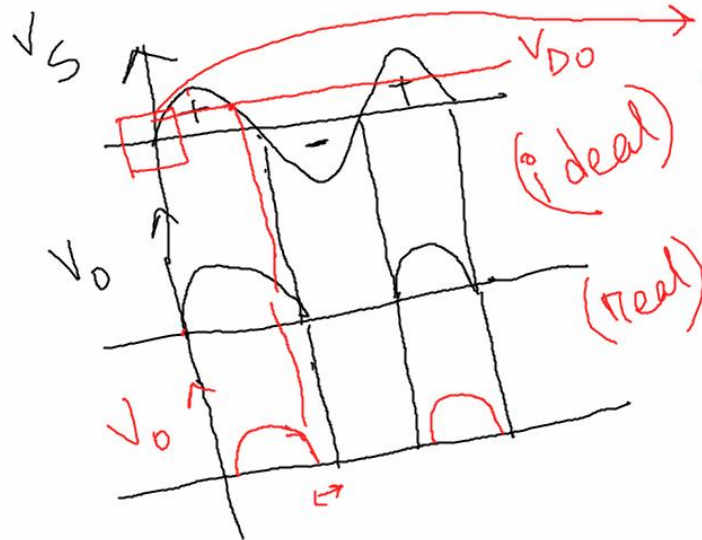



(+) half cycle

$$V_{D0} = V_s - v_o$$

$$\Rightarrow v_o = V_s - V_{D0}$$

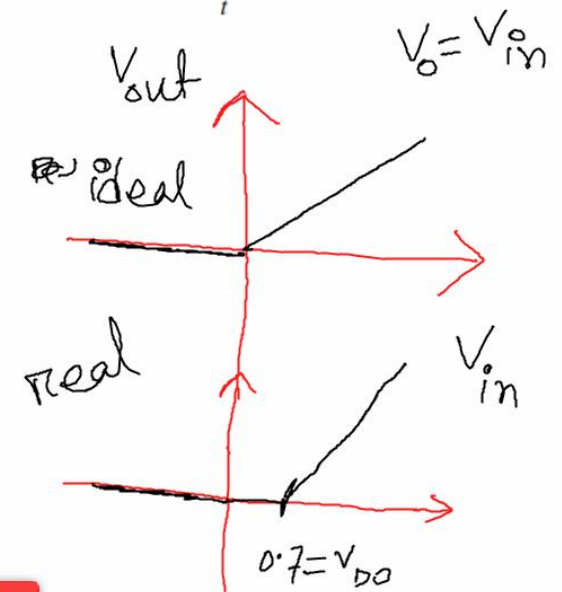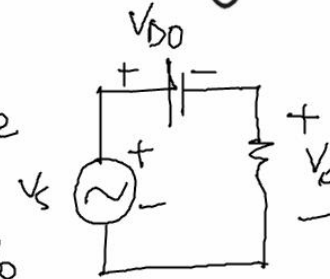


Lecture : Full-wave rectifier

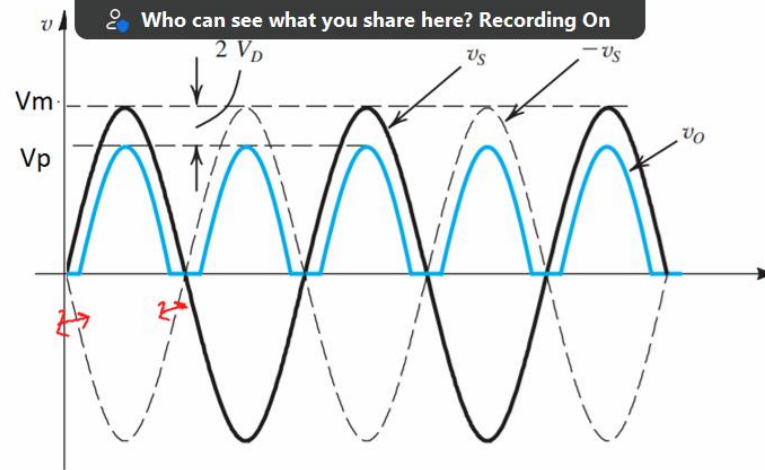
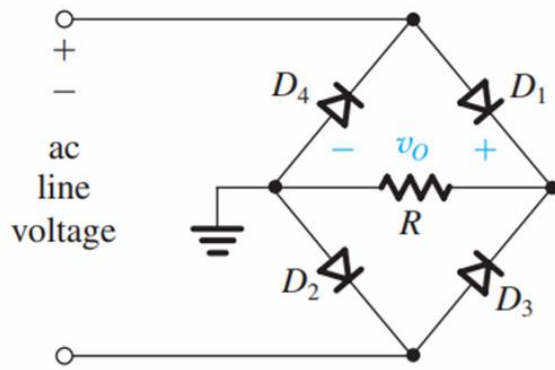


$$V_o = V_s - 2V_{DO}$$

$$V_P = V_m - 2V_{DO}$$

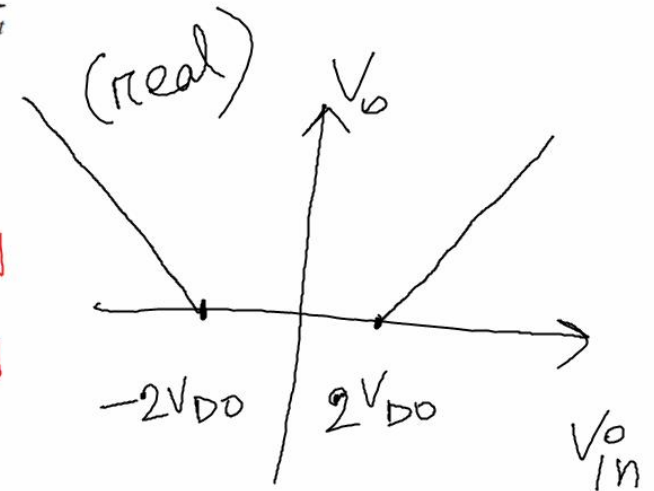

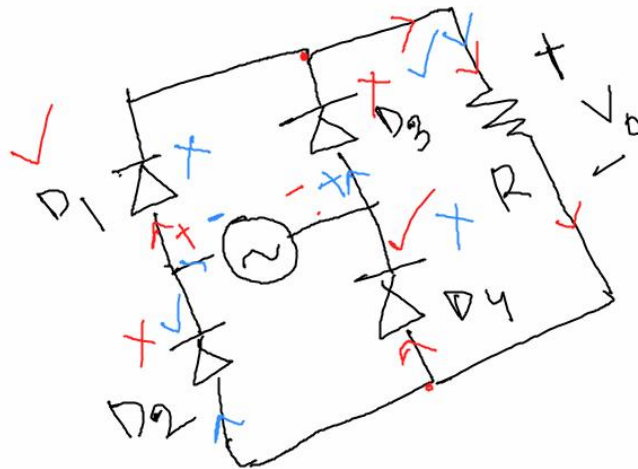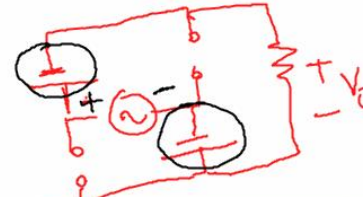(+) half-cycle D_1, D_4 ON
(-) D_2, D_3 ON



You are screen sharing Stop Share