

**BRAC University****Set: 01**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA



Midterm

Full Marks: 40



Time: 2 hours

Date: March 10, 2022

Answer all 4 questions. All the questions carry equal marks.

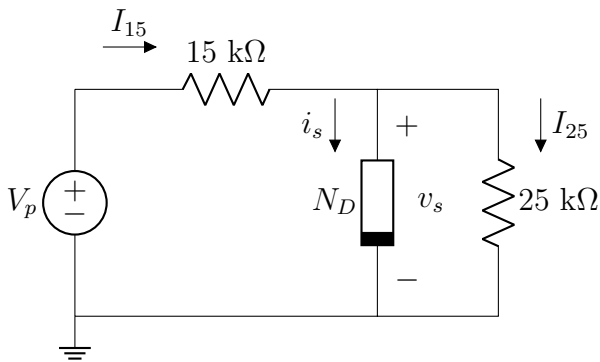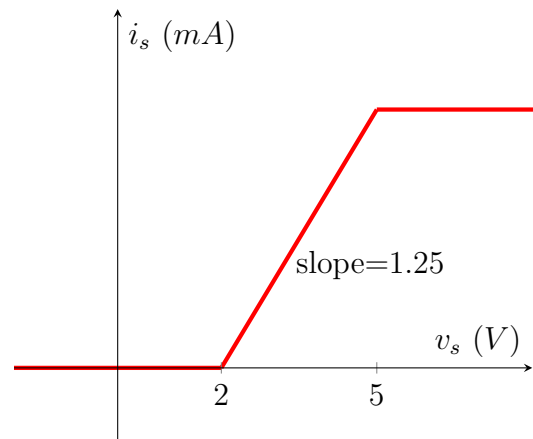**Question 1 [CO1]****10**(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

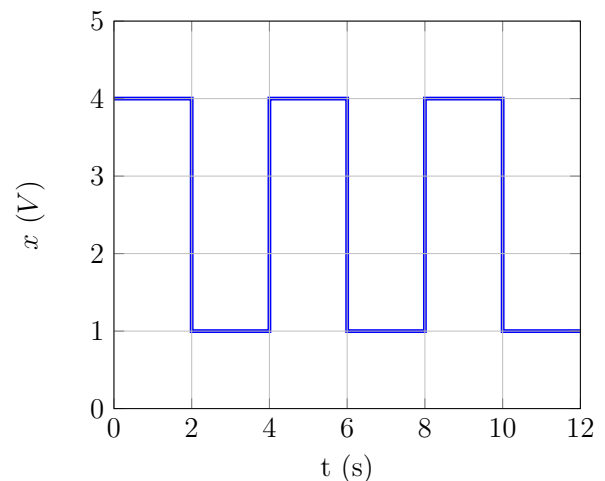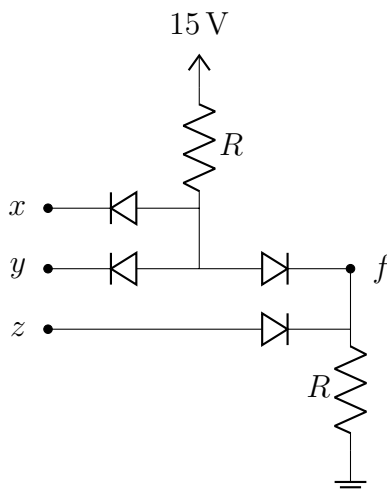**Question 2 [CO2]****10**

## Set: 01

For this question, all of the diodes are ideal.


- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x.y.z$ . Here “.” denotes logical AND. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

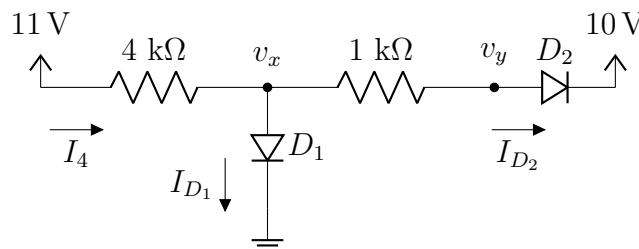- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

**BRAC University****Set: 02**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11



Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

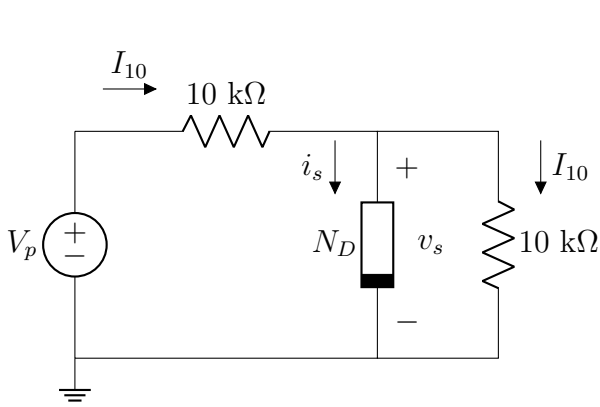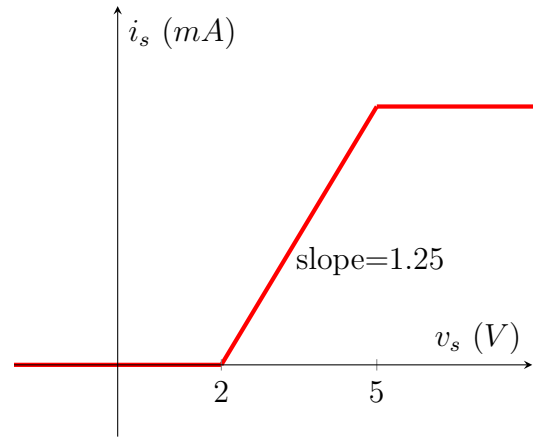**Question 1 [CO1]****10**(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

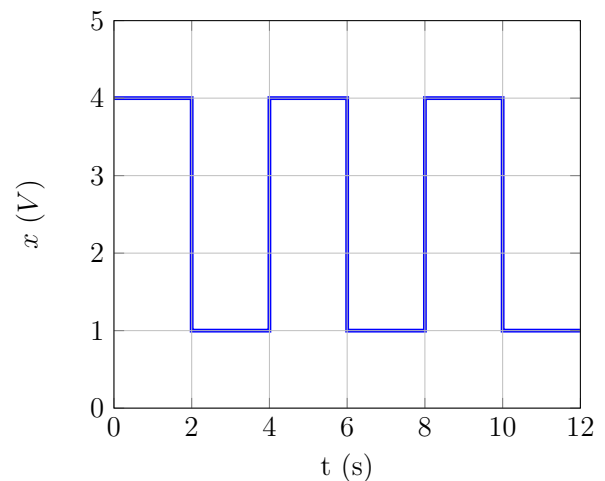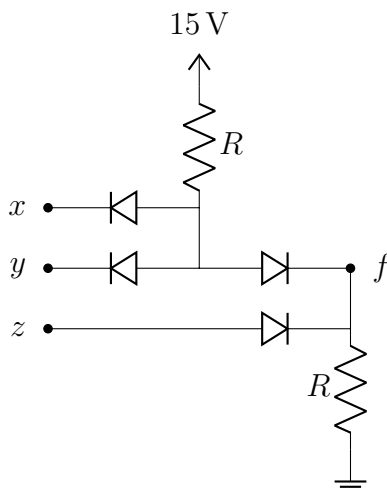**Question 2 [CO2]****10**

For this question, all of the diodes are ideal.

Set: 02


- 
- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x.y.z$ . Here “.” denotes logical AND. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

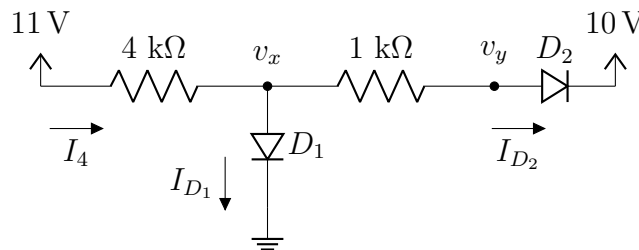- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

**BRAC University****Set: 03**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11



Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

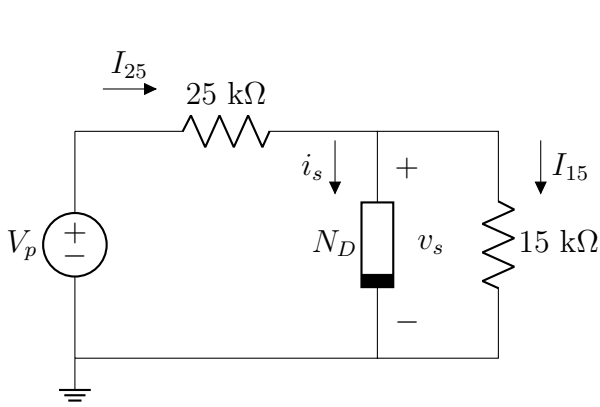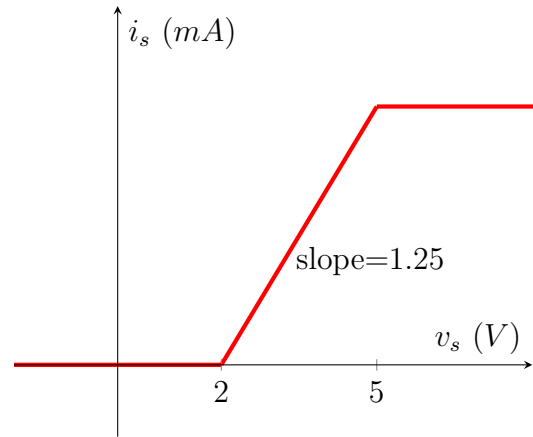**Question 1 [CO1]****10**(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

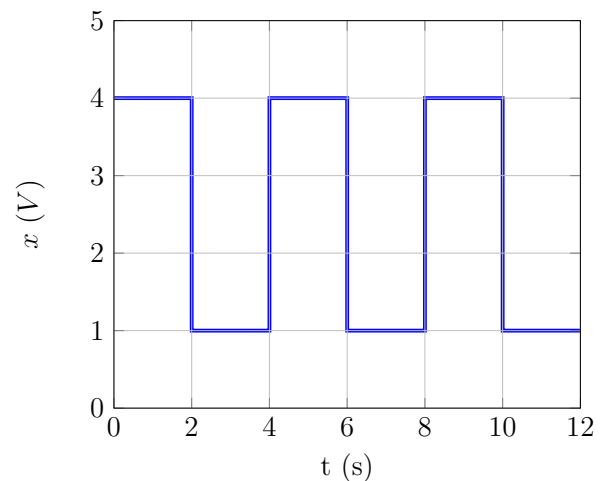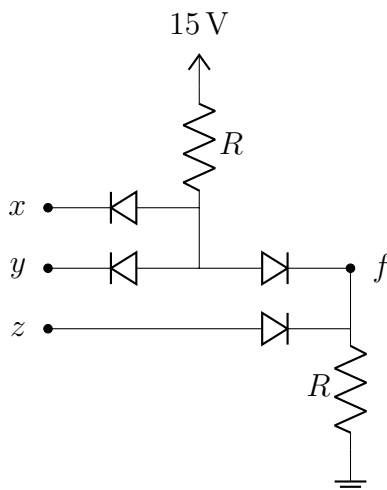**Question 2 [CO2]****10**

For this question, all of the diodes are ideal.

## Set: 03


- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

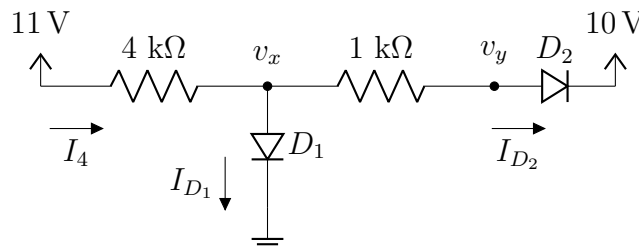- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

**BRAC University****Set: 04**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11



Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

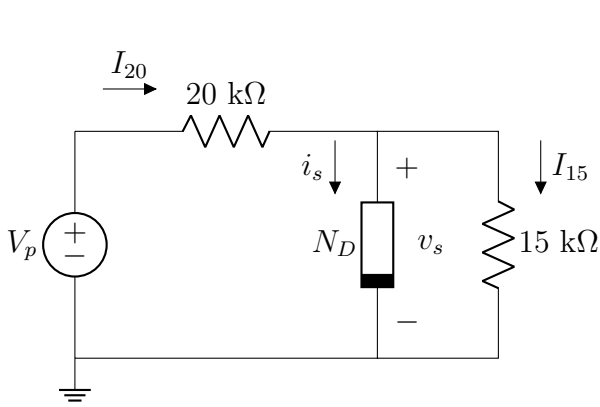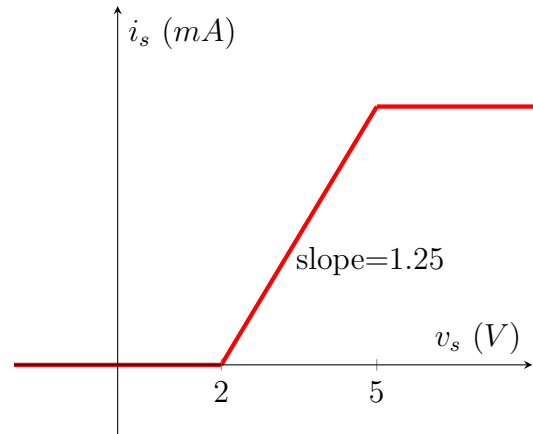**Question 1 [CO1]****10**(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

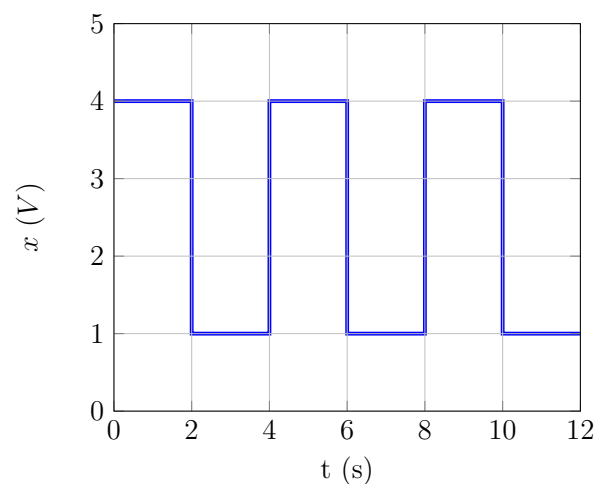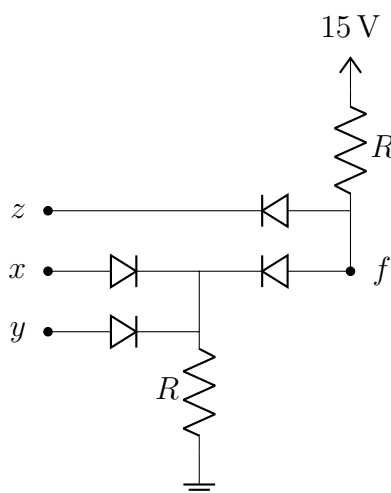**Question 2 [CO2]****10**

For this question, all of the diodes are ideal.

## Set: 04


- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

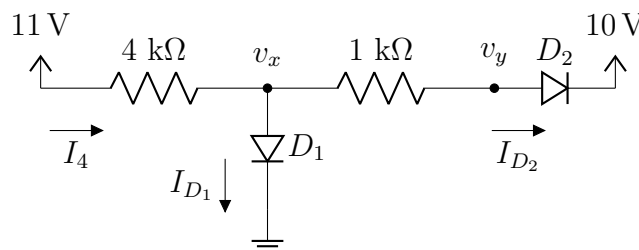- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]



# BRAC University

**Set: 05**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

## Question 1 [CO1]



10

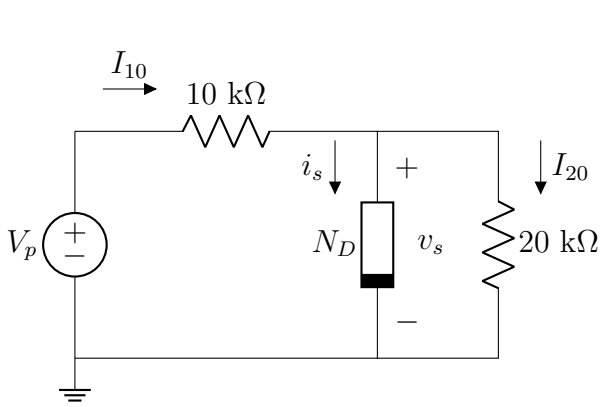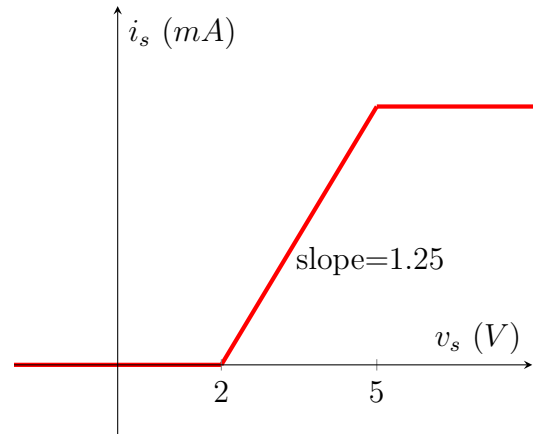(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

## Question 2 [CO2]

10

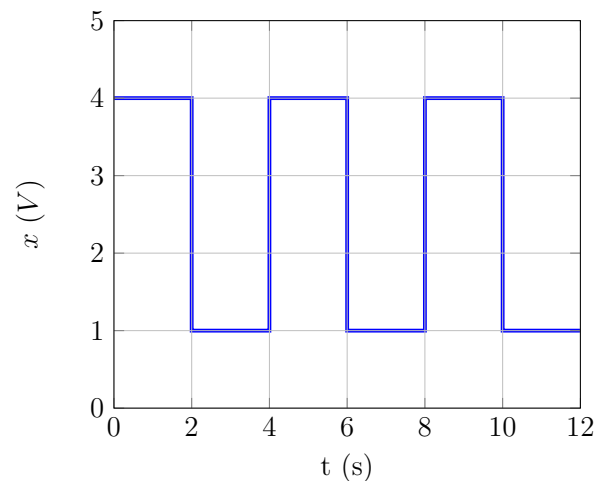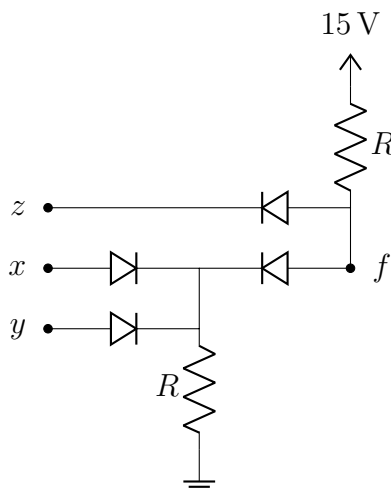

For this question, all of the diodes are ideal.

## Set: 05


- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

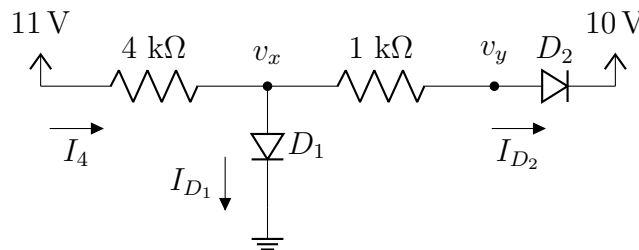- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

# BRAC University

**Set: 06**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

## Question 1 [CO1]



10

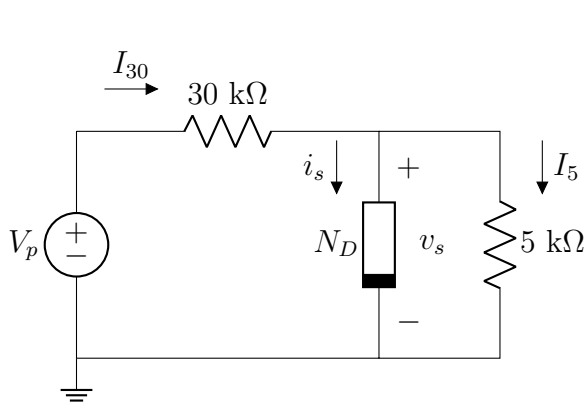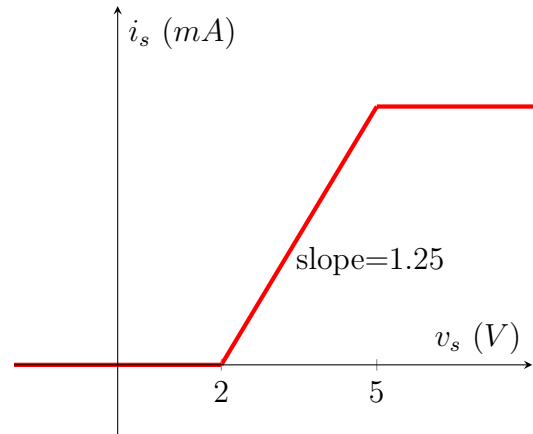(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

## Question 2 [CO2]

10

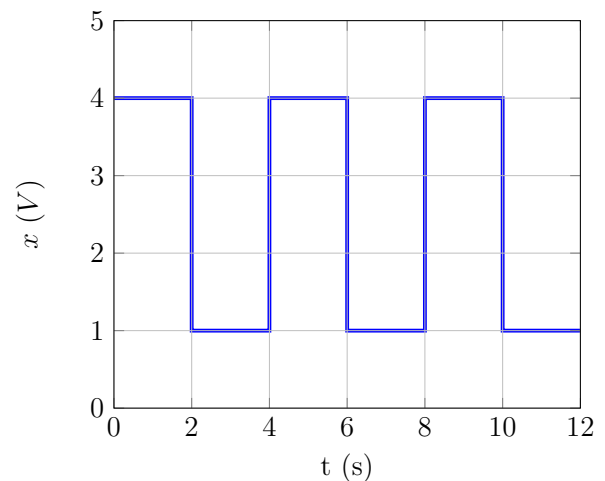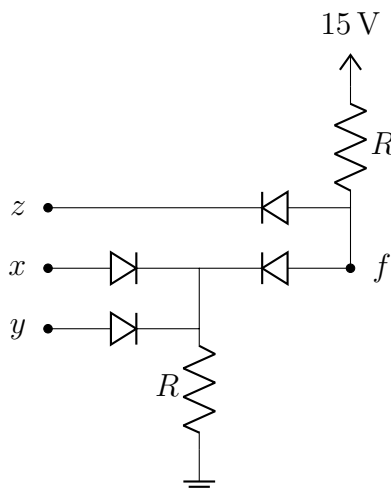

For this question, all of the diodes are ideal.

## Set: 06


- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

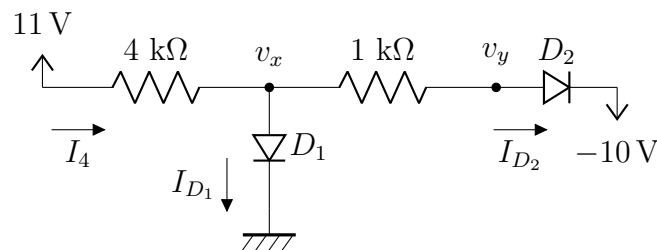- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

# BRAC University

**Set: 07**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

## Question 1 [CO1]



10

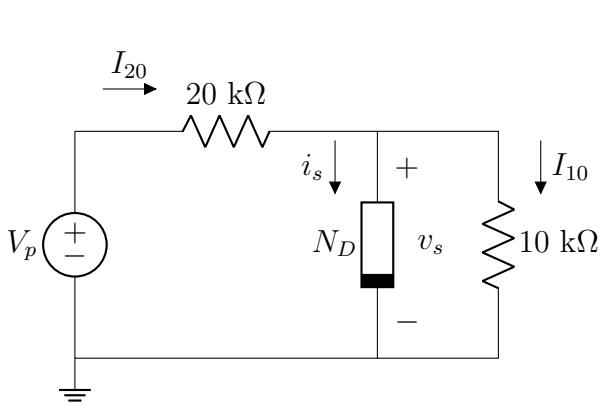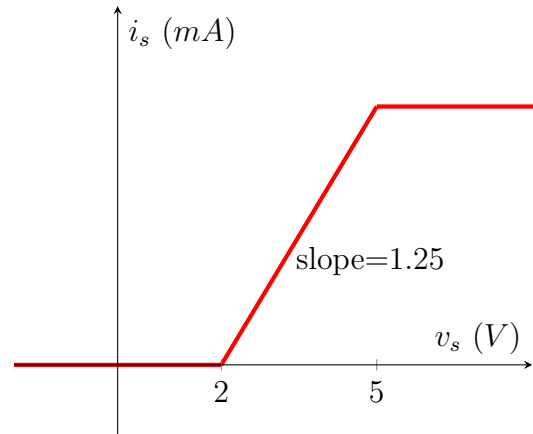(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

## Question 2 [CO2]

10

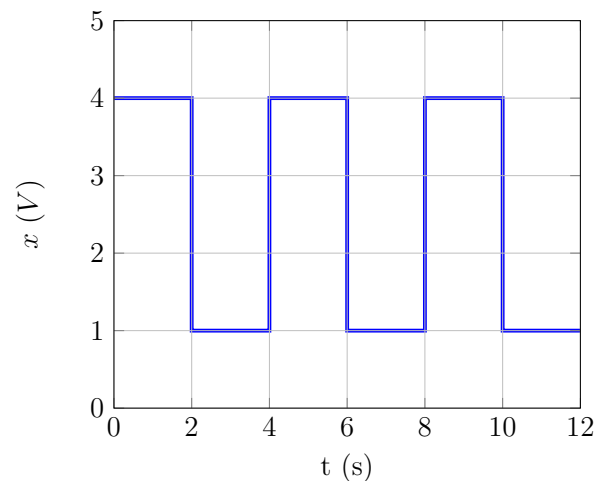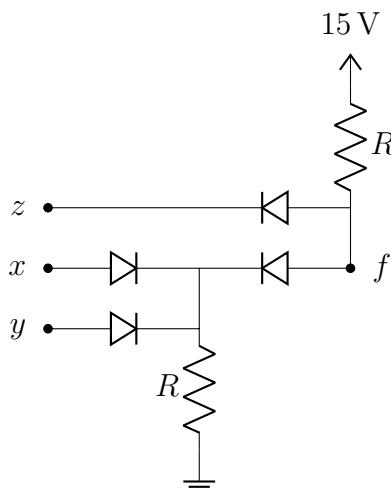

For this question, all of the diodes are ideal.

Set: 07


- 
- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

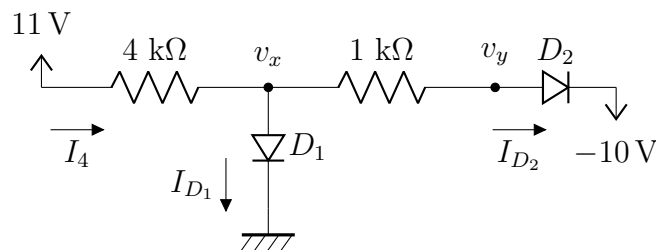- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

# BRAC University

**Set: 08**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

## Question 1 [CO1]



10

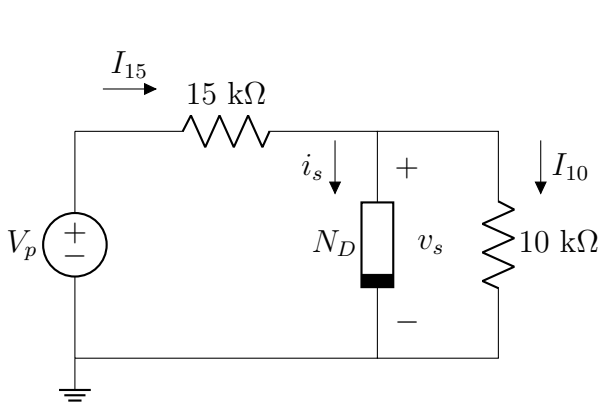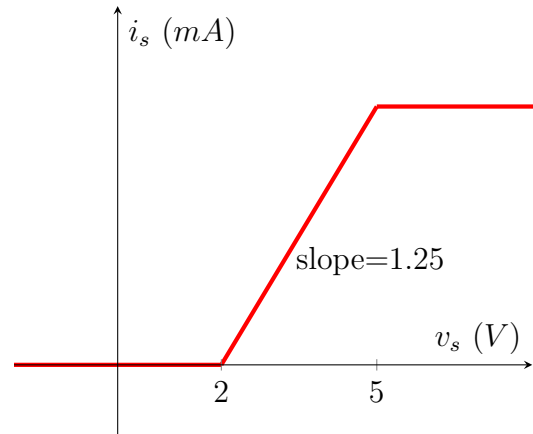(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

## Question 2 [CO2]

10

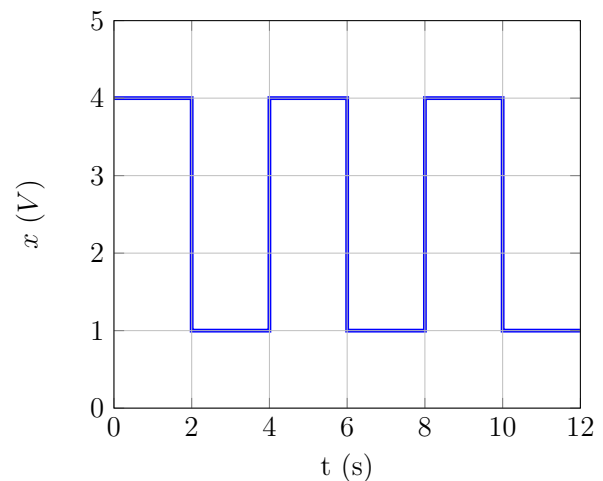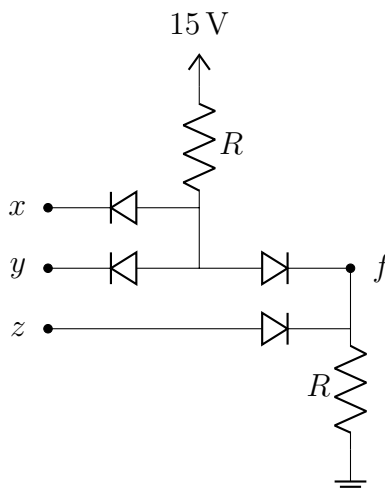

For this question, all of the diodes are ideal.

Set: 08


- 
- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

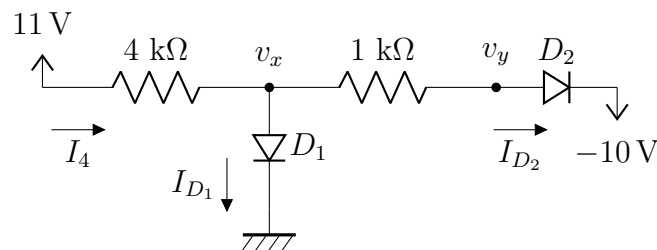- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]



# BRAC University

**Set: 09**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

## Question 1 [CO1]



10

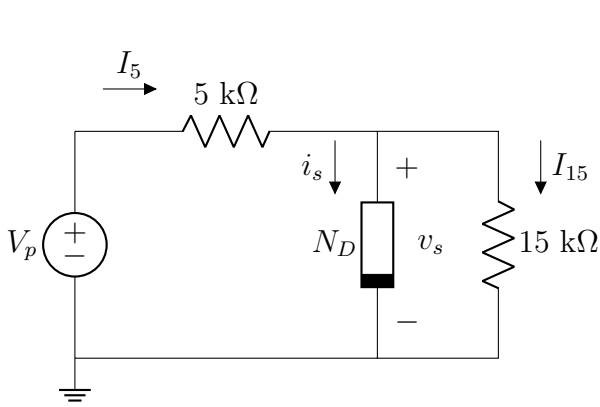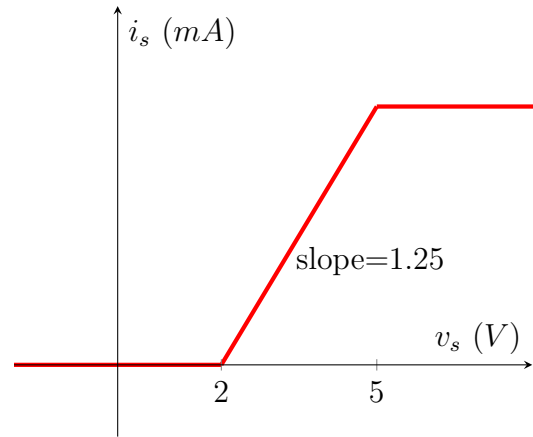(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

## Question 2 [CO2]

10

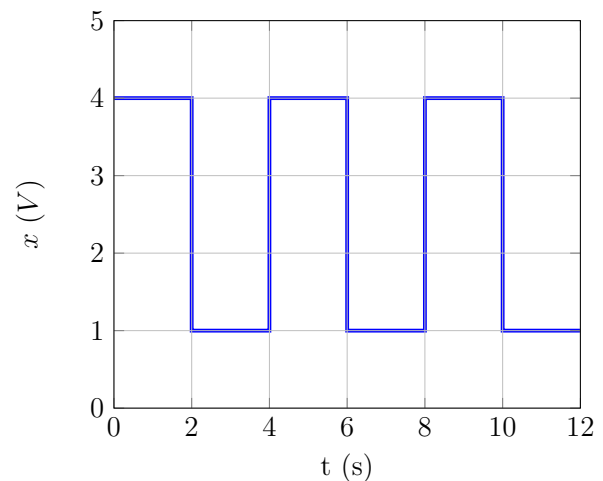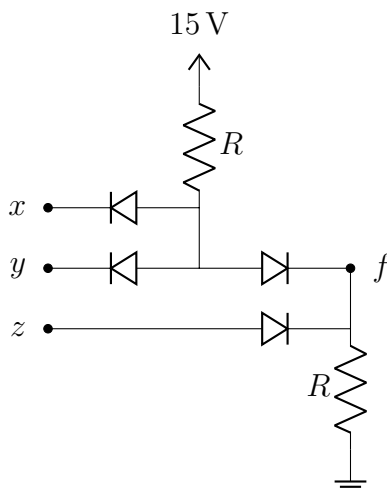

For this question, all of the diodes are ideal.

Set: 09


- 
- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

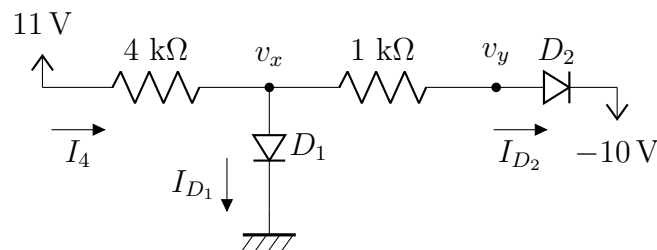- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]

# BRAC University

**Set: 10**

Semster: Spring 2020

Course No: CSE251

Course Title: ELECTRONIC DEVICES AND CIRCUITS

Section: 11

Faculty: ABA

Midterm



Full Marks: 40

Time: 2 hours

Date: March 10, 2022

## Question 1 [CO1]



10

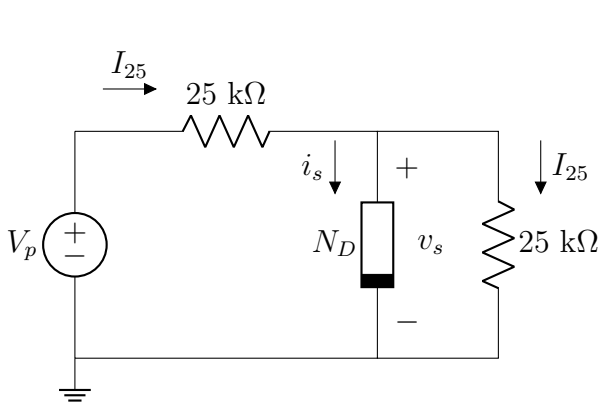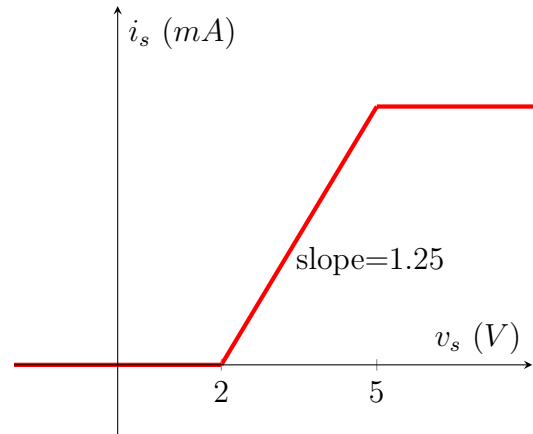(a) A circuit with a non-linear device  $N_D$ (b) IV Characteristics of the non-linear device  $N_D$ 

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device  $N_D$  and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when  $v_s = 3$  V and **calculate** the current through the device,  $i_s$ , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source  $V_p$  when  $v_s = 3$  V. [3]

## Question 2 [CO2]

10

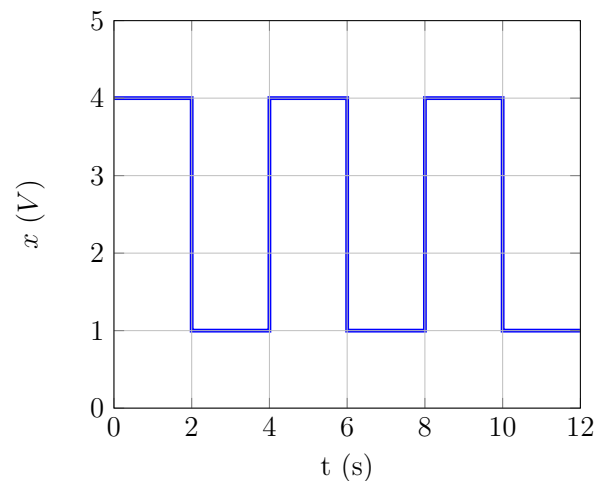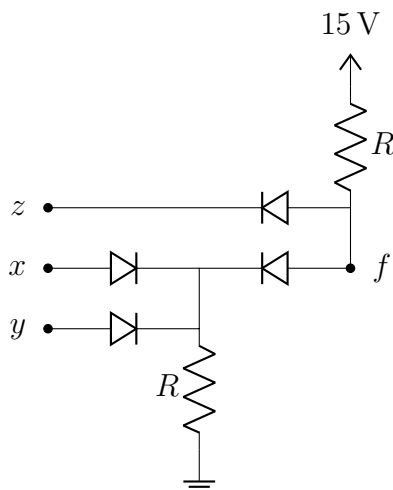

For this question, all of the diodes are ideal.

## Set: 10


- (a) Assuming  $x, y, z$  are boolean variables, **analyze** the circuit on the left to find an expression of  $f$  in terms of  $x, y$ , and  $z$ . [3]
- (b) **Analyze** the circuit on the left again to find the waveform (voltage vs time graph) of  $f$  assuming  $x, y, z$  are voltage signals, where  $y = 2\text{ V}$ ,  $z = 3\text{ V}$ , and  $x$  has a waveform as shown in the figure on the right. [5]
- (c) **Design** a circuit using ideal diodes to implement the logic function  $f = x + y + z$ . Here “+” denotes logical OR. [2]

**Bonus: Design** a circuit using ideal diodes to implement the XOR logic function between  $x$  and  $y$ , assuming you have access to  $x, \bar{x}, y$ , and  $\bar{y}$ . [3]

### Question 3 [CO1]

10

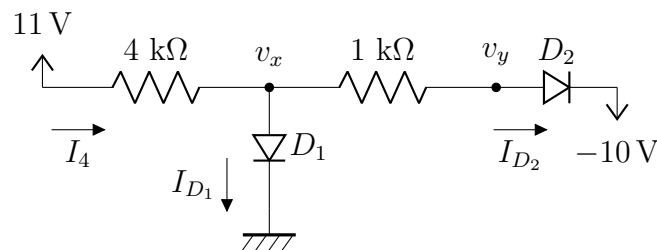- (a) **Analyze** the following circuit to find the values of  $I_{D1}$ ,  $I_{D2}$ ,  $v_x$ , and  $v_y$ . Here, **use** the Method of Assumed State using the CVD model of diode with  $V_{D0} = 0.5\text{ V}$ . [7]
- (b) **Validate** your assumptions about the states of the diodes. [3]



### Question 4 [CO2]

10

A voltage waveform  $v_i = 10 \sin(100\pi t)\text{ V}$  is input to a full-wave rectifier with a load resistance of  $R = 50\text{ k}\Omega$ . Silicon diodes are used in this circuit for which the forward drop is  $V_{D0} = 0.7\text{ V}$ .

- (a) **Show** the circuit of the rectifier. **Label** the input and output voltages properly. [2]
- (b) **Calculate** the DC value of the output voltage. [1]
- (c) **Contrast** the value found in part (b) with that when a  $5\text{ }\mu\text{F}$  capacitor is connected in parallel with the load. [2]
- (d) **Identify** the two diodes will be ON in the positive half cycle. [1]

Now the two diodes from part (d) are replaced with Germanium diodes [ $V_{D0} = 0.2\text{ V}$ ].

- (e) **Explain** the change in the voltage transfer characteristics and output voltage waveform of the circuit. Hence, calculate the peak of the output voltage in this case. [3+1]