

CSE 260

Assignment 04

Name: Shihab Muh tasim

ID: 21301610

sec: 1


Ans to the or no 1

Given, function, $F(a, b, c, d) = \sum (0, 1, 4, 7, 11, 15)$

a

Here, a is MSB and d is LSB.

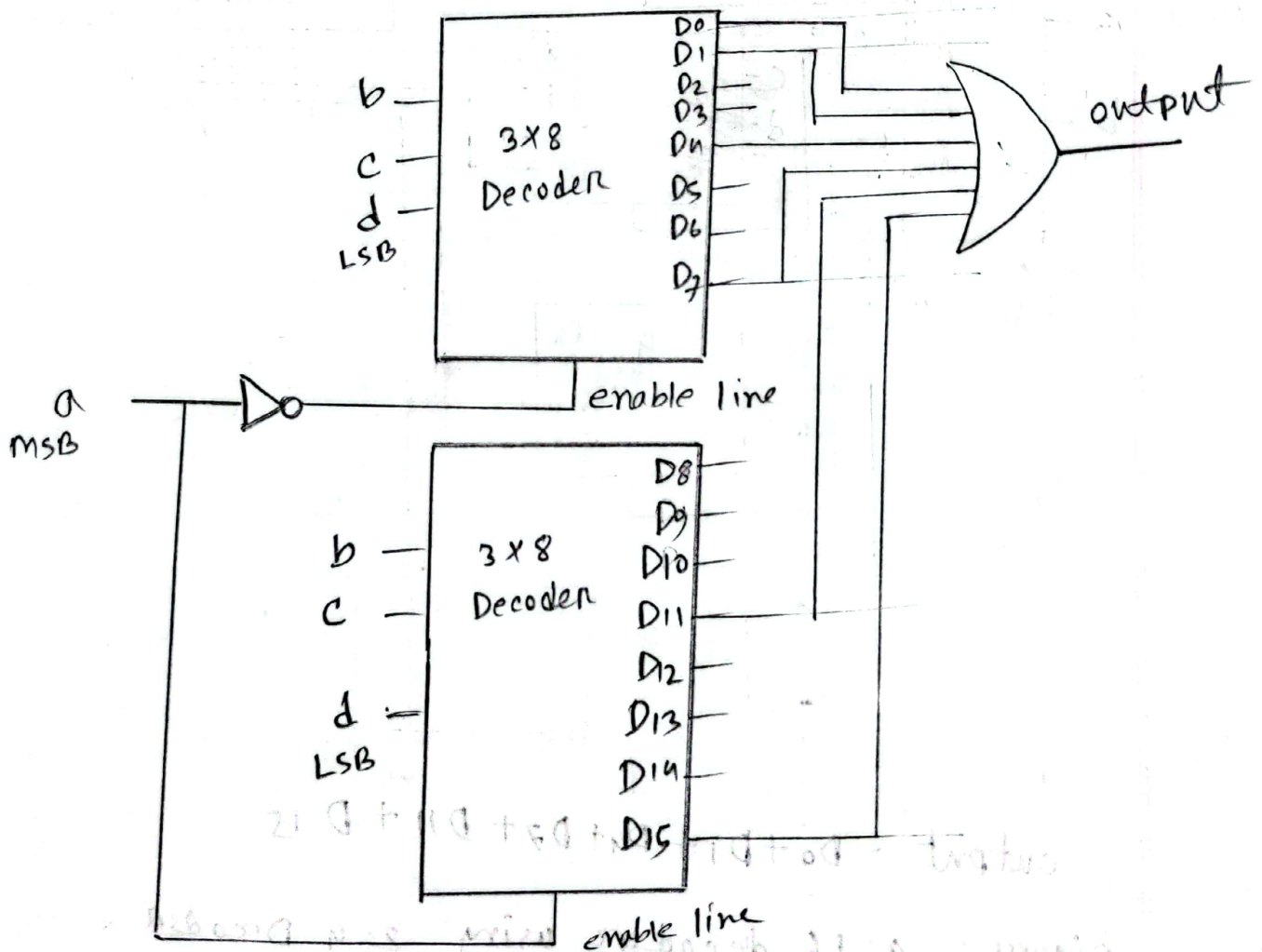
Implementing this circuit using 3:8 decoders,



(b)

Implementation of the boolean function,
 $F(a, b, c, d) = \sum(0, 1, 4, 7, 11, 15)$ using 2:4 Decoders.

Here, a is MSB and d is LSB.

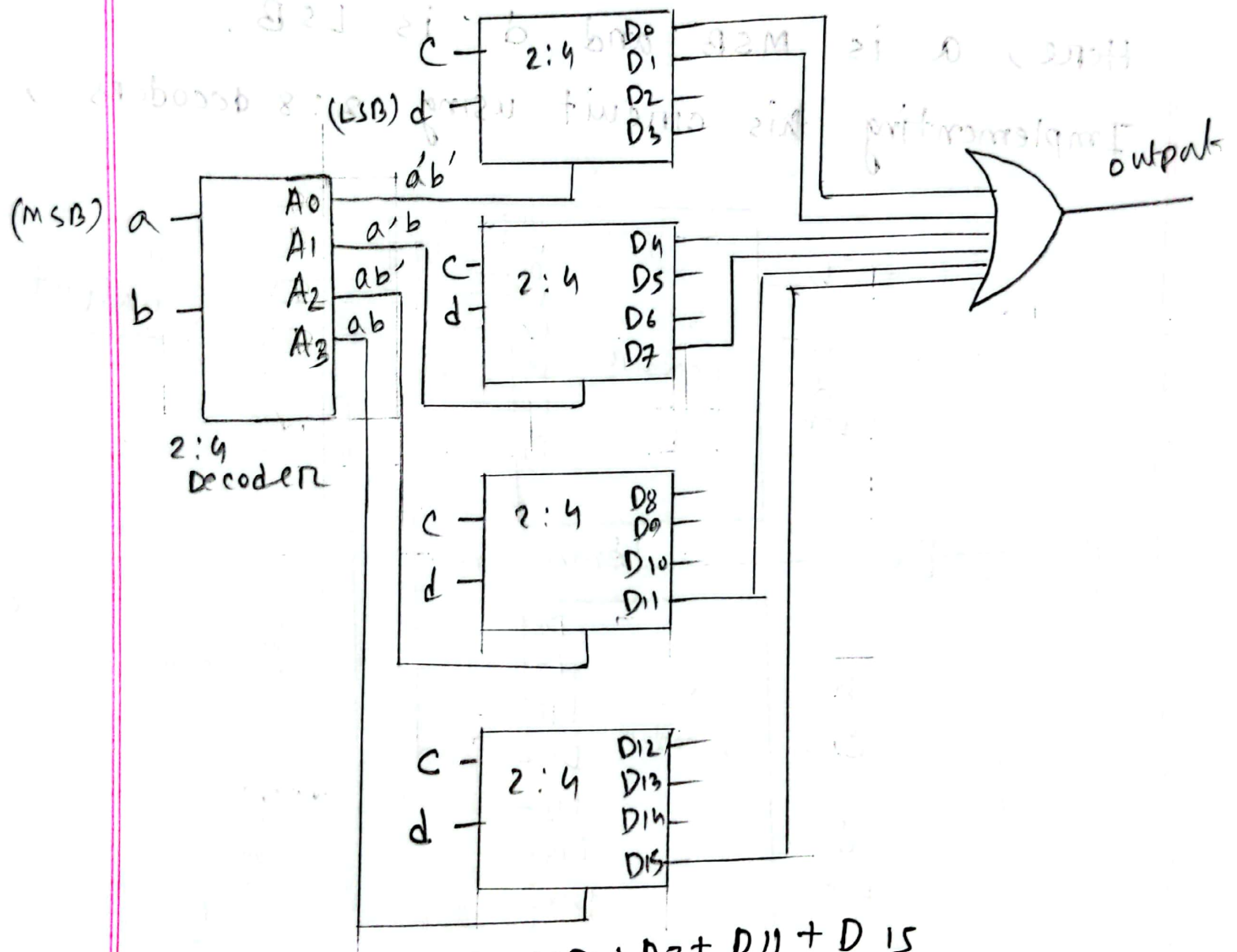

$$\therefore \text{output} = D_0 + D_1 + D_4 + D_7 + D_{11} + D_{15}$$

Figure: 4:16 decoder using 2:4 Decoder.


Ans to the or no 2

Given, $F(a, b, c, d) = \sum (0, 1, 3, 6, 10, 11, 14)$

a

Implementing the given function using 4:1 and 2:1 MUXs both in the same circuit.


Here, a is MSB and d is LSB.

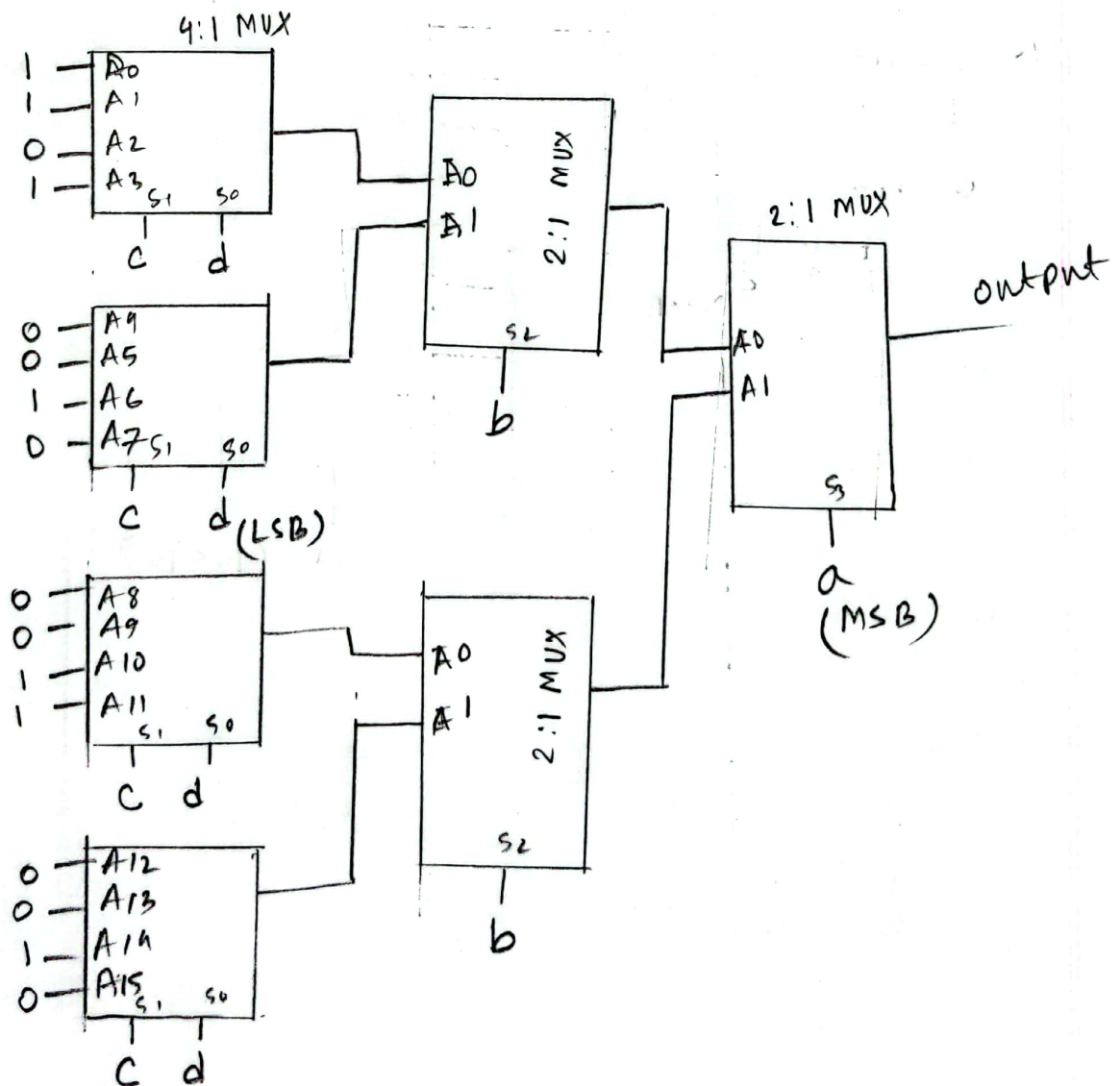

(b)

Implementing $F(a, b, c, d) = \sum (0, 1, 3, 6, 10, 11, 14)$
using only 8:1 MUX :

Here, a is MSB and d is LSB

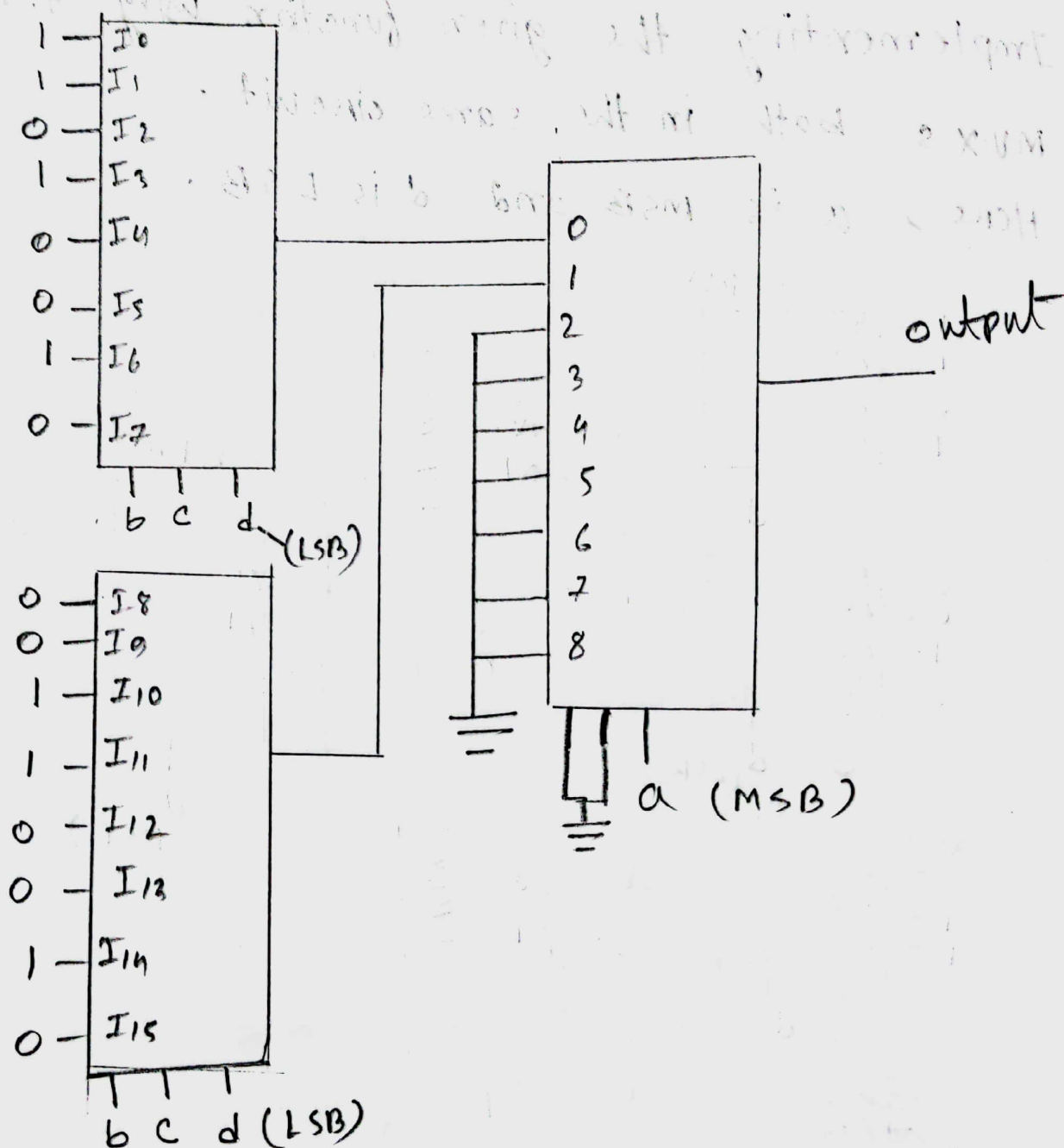


Ans to the or no 3

Truth table for 1's complement of 3 bit numbers using encoder and decoder.

Input				output			
min	A	B	C	min	X	Y	Z
0	0	0	0	7	1	1	1
1	0	0	1	6	1	1	0
2	0	1	0	5	1	0	1
3	0	1	1	4	1	0	0
4	1	0	0	3	0	1	1
5	1	0	1	2	0	1	0
6	1	1	0	1	0	0	1
7	1	1	1	0	0	0	0

Circuit diagram :

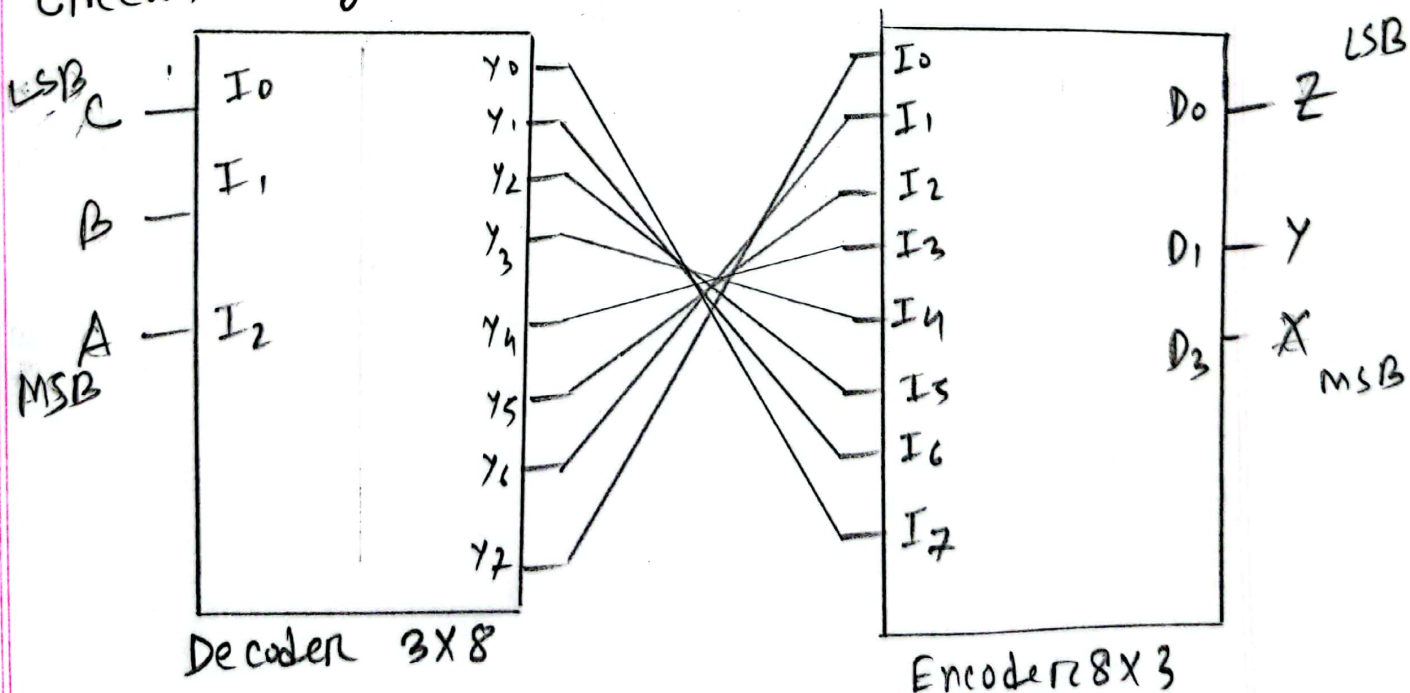

The given circuit takes 3 inputs in the decoder. Then as the decoder gives 1 in output according to given min terms 3 bit binary input, that corresponding pin to connected to the 1's complement value ~~binary~~ minterm $\text{pin}^{\text{in encoder}}$ so that it passes 1 through that pin and output is given in the encoder.