

CSE 260

Lab Report 8

Name : Shihab Muhtasim

ID : 21301410

sec : 1

1. Experiment Name : Design and Implementation of the following circuit: four 2 bit numbers A, B, C, D and two selection variables  $S_1$  and  $S_2$  are available.  $S_1$  will select either A or B and  $S_2$  will select either C or D. Depending on the two selection variables, the circuit will work in the following way.


$S_1$	$S_2$	Operation
0	0	A+C
0	1	A+D
1	0	B+C
1	1	B+D

2. Objective : i) To get familiarized with how mux works and to learn how to select certain numbers as required using mux.  
ii) Implementing parallel adder to add numbers after selecting using mux.


3. Required components and Equipments :

- i) LOGICSTATE (input)
- ii) LED - Green (output)
- iii) IC - MUX (74153)
- iv) Parallel Adder IC - 7483

#### 4. Experimental setup :

 

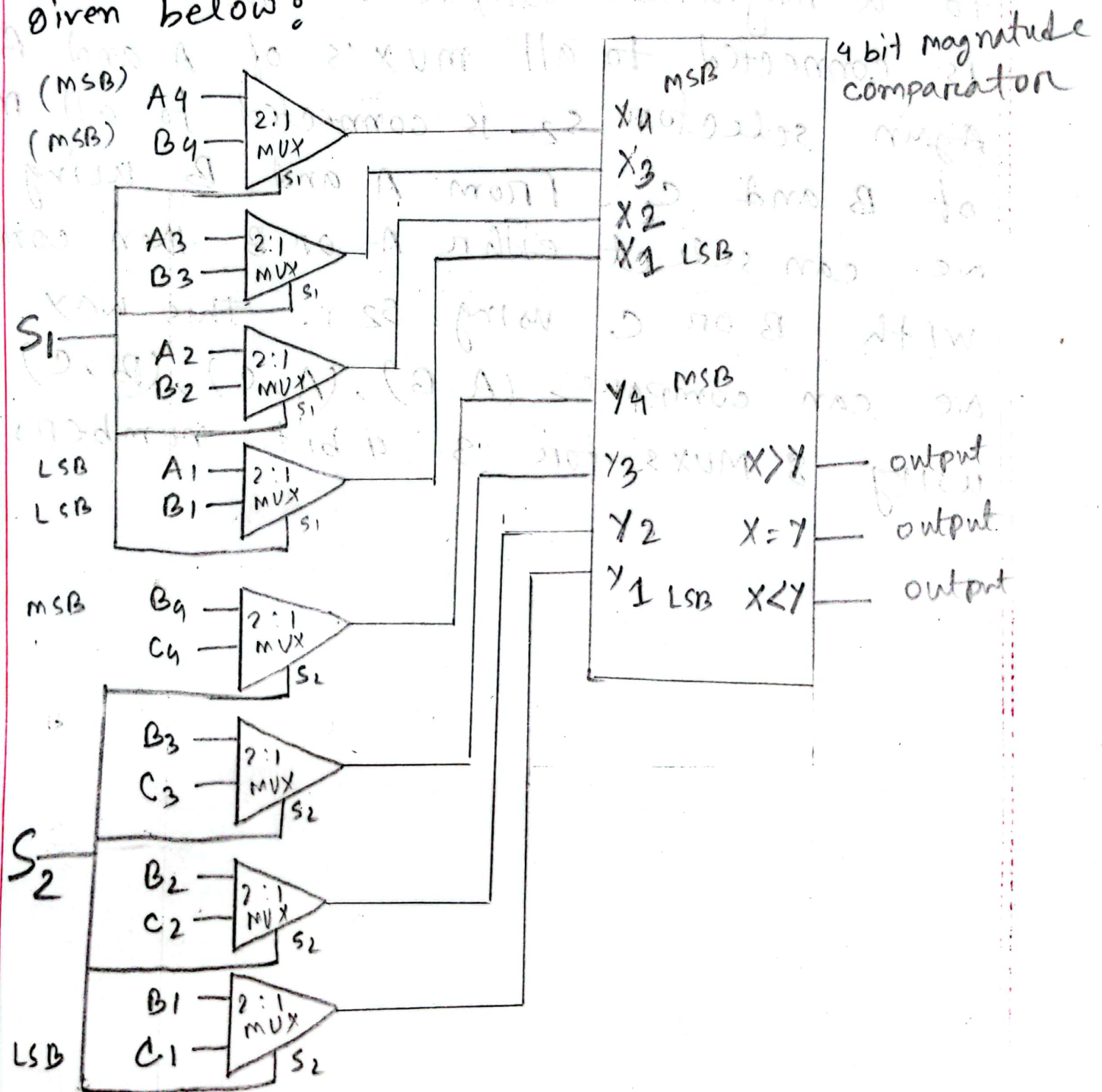5. Results and Discussion's : A circuit diagram which will compare three 4 bit numbers, using a magnitude comparator and 2:1 MUX's is given below:





In this circuit  $A = A_4 A_3 A_2 A_1$ ,  $B = B_4 B_3 B_2 B_1$ ,  
 $C = C_4 C_3 C_2 C_1$ . The input bits of this circuit  
are connected through 2:1 Mux then passed  
to a magnitude comparator. The selector  $S_1$   
is connected to all mux's of A and B.  
Again selector  $S_2$  is connected to all mux  
of B and C. From A and B using Mux  
we can select either A or B then compare  
with B or C using  $S_2$ . This way  
we can compare  $(A, B)$ ,  $(A, C)$ ,  $(B, C)$ .  
using 8 Muxs for 3 4 bit numbers.