

Assignment 1

CSE251

Fall 22

Name : Shihab Muhtasim

sec : 13

ID : 21301610

Ans to q no 1

(a)

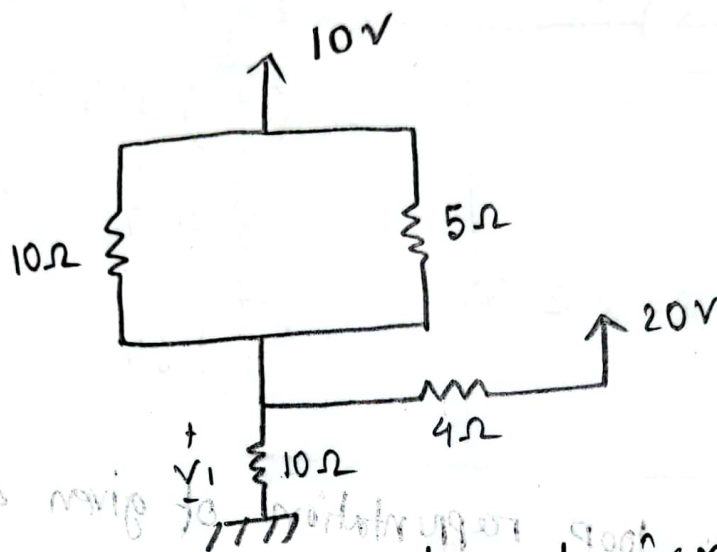


Fig: Alternate representation of given circuit

(b)

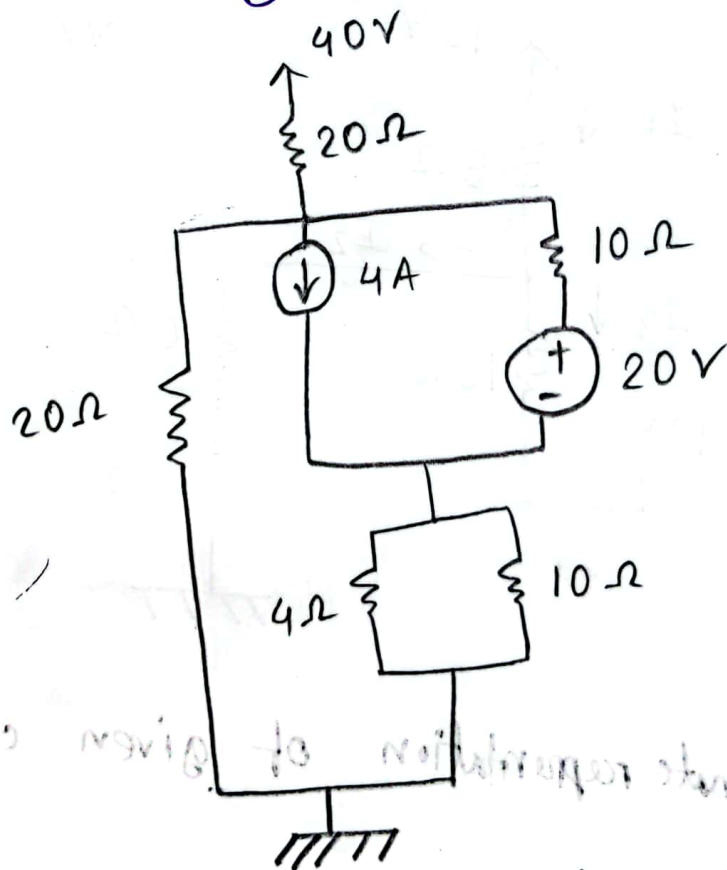


Fig: Alternate representation of given circuit.

Ans for q no 2


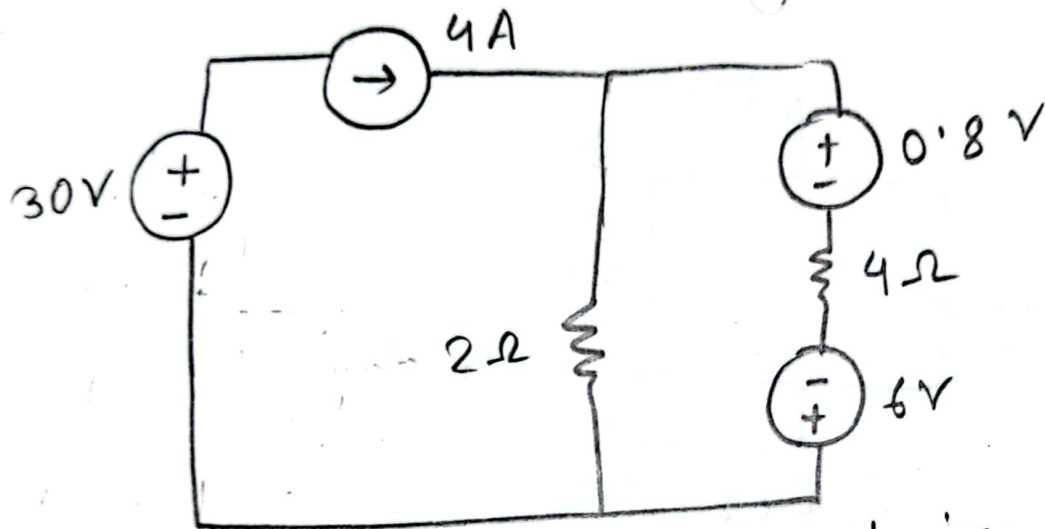


Fig: loop representation of given circuit

Ans to q no 3

i)

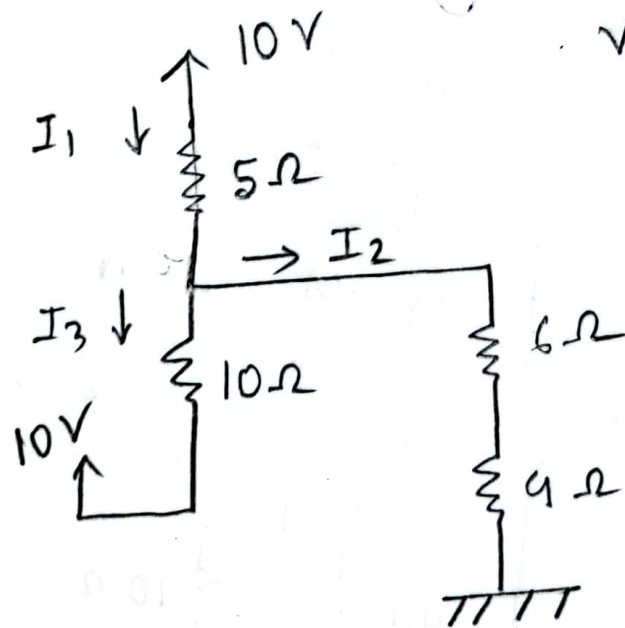

$$V_x = (10 + 0) = 10V$$

Fig: Alternate representation of given circuit

(ii) Applying KCL at node a:

$$-I_1 + I_2 + I_3 = 0 \quad \text{--- (1)}$$

Applying KVL in L1 path:

$$5I_1 + 10I_3 = 10 - 10$$

$$\Rightarrow 5I_1 + 10I_3 = 0 \quad \text{--- (2)}$$

Applying KVL in L2 path:

$$5I_1 + 10I_2 = 10 - 0 \quad [6 + 4 = 10 \text{ V}]$$

$$\Rightarrow 5I_1 + 10I_2 = 10 \quad \text{--- (3)}$$

Solving eq 1, 2, 3 we get,

$$I_1 = \frac{1}{2} \text{ A}$$

$$I_2 = \frac{3}{4} \text{ A}$$

$$I_3 = -\frac{1}{4} \text{ A}$$

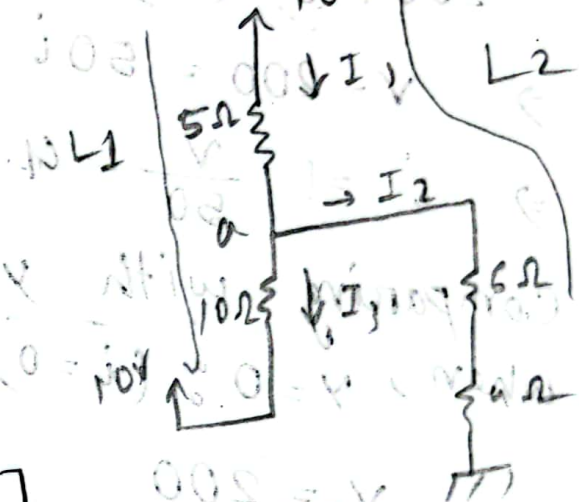
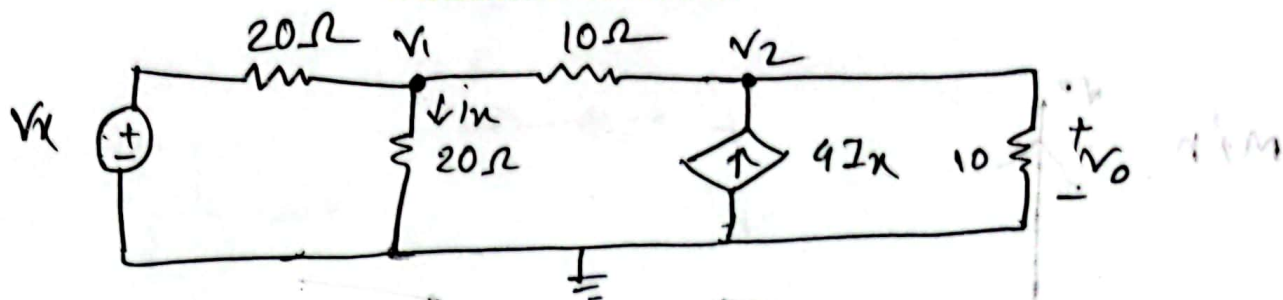


Fig. circuit + AR

(5)

Ans to q 4Applying KCL at node  $v_1$ :

$$\frac{v_1 - V_x}{20} + \frac{v_1}{20} + \frac{v_1 - v_2}{10} = 0$$

$$\Rightarrow v_1 - V_x + v_1 + 2v_1 - 2v_2 = 0$$

$$\Rightarrow 4v_1 - 2v_2 - V_x = 0$$

$$= 4v_1 - 2v_2 - 40 = 0$$

$$\Rightarrow 4v_1 - 2v_2 = 40 \quad \text{--- (1)}$$

$$i_x = \frac{v_1}{20}$$

$$V_x = 40 + 0 = 40 \text{ V}$$

Now, KCL at node  $v_2$ :

$$\frac{v_2 - v_1}{10} + \frac{v_2}{10} = 4I_x$$

$$\Rightarrow v_2 - v_1 + v_2 = \frac{40 \times v_1}{20}$$

$$\Rightarrow -3v_1 + 2v_2 = 0 \quad \text{--- (2)}$$

Solving eq 1 and 2:  $v_1 = 40 \text{ V}, v_2 = 60 \text{ V}$ 

$$\therefore v_0 = v_2 = 60 \text{ V}$$



(i)

Ans to the or no 5

Applying KVL on the right loop,

$$-200 + 50(-i) + v = 0$$

$$\Rightarrow v - 200 = 50i$$

$$\Rightarrow i = \frac{v}{50} - 4$$

Comparing with  $y = mx + c$ ,



when,  $v = 0$  ( $i = 0$ )

$$v = 200$$

Again,  $c = -4$

or, when,  $v = 0$ ,

$$i = -4 \text{ mA}$$

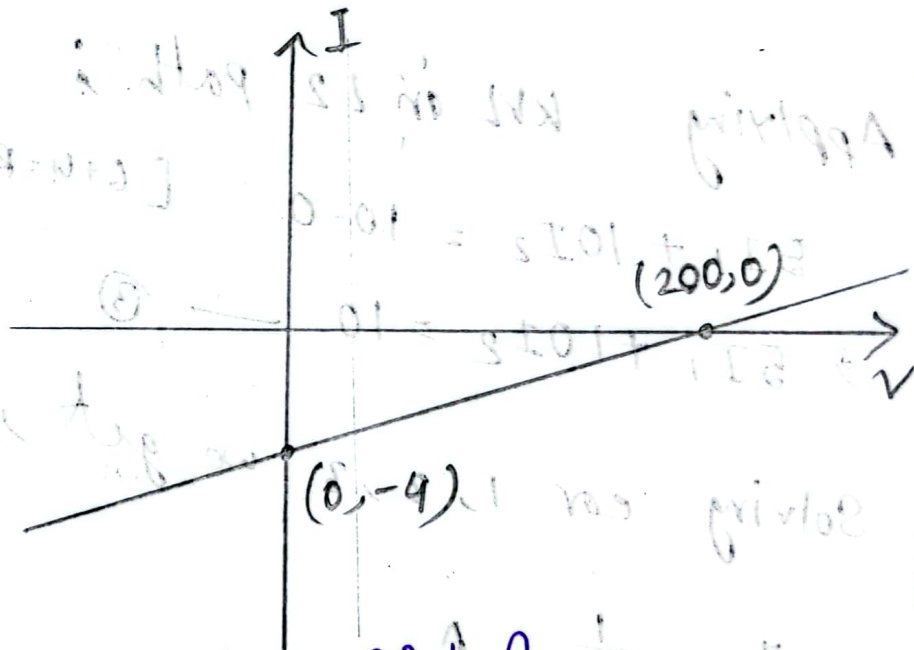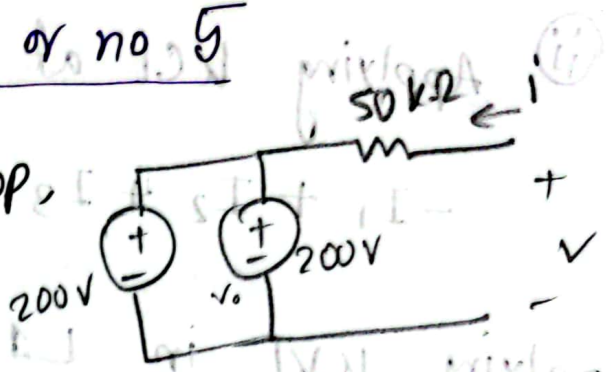

ii) (a)  $100 \text{ k}\Omega$

$$\text{Here, } i = \frac{v}{100} - \frac{v_0=200}{100}$$

$$\text{So, } c = -200/100 = -2$$

And when  $i = 0$ ,

$$v = 200 \text{ V}$$

(b)  $200 \text{ k}\Omega$


$$\text{Here, } i = \frac{v}{200} - \frac{200}{200}$$

$$c = -1$$

when  $i = 0$ ,

$$v = 200 \text{ V}$$

Plotting these cases in a graph

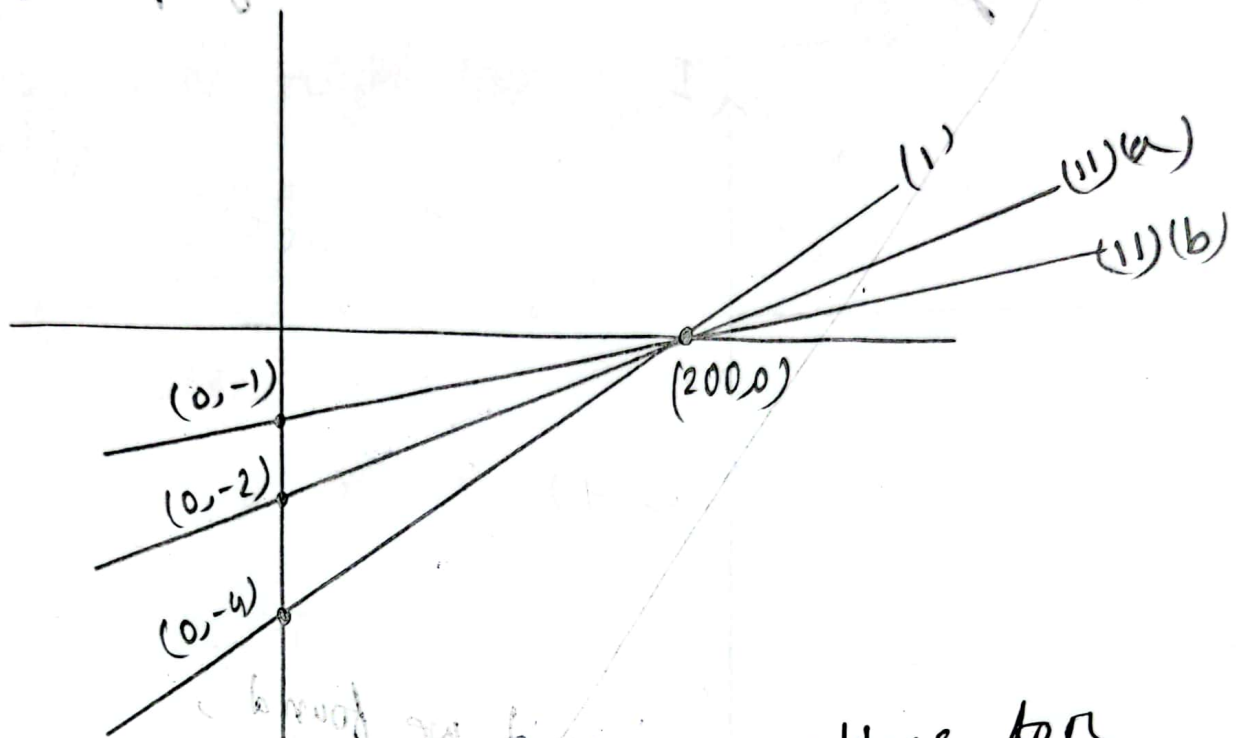

Here, we have found the same voltage for all the resistors. However, different points for current  $i$ . The reason is, from KVL we found,

$$V = V_0 + IR \quad \text{and} \quad i = \frac{V}{R} - \frac{V_0}{R}$$

So when we are finding  $V$  when  $y = x = 0$ ,  $V = V_0$ ; which shows it doesn't depend on resistance.

Again, when  $V = x = 0$ ,  $i = -\frac{V_0}{R}$  where  $i$  is clearly depended on resistance.

Again, in the results slopes  $m_1 > m_{11(a)} > m_{11(b)}$  and we know  $m = \frac{1}{R}$  which means this graph also portrays that,

$$\frac{1}{R_1} > \frac{1}{R_{11(a)}} > \frac{1}{R_{11(b)}} \Rightarrow R_1 < R_{11(a)} < R_{11(b)}$$

$$50 < 100 < 200 \, \Omega$$

which is true.

Ans to qno 6

(a)

Region AB : This device acts like a current source with constant  $-5 \text{ mA}$  current supply. ( $V \leq -5\text{V}$ ,  $I = -5 \text{ mA}$ )

Region BC : Here, the device acts like a resistor where,  $m = \frac{\Delta V}{\Delta I} = 1$

$$\therefore R = \frac{1}{1} = 1 \, \text{k}\Omega$$



CD region : It acts like a / This device can be modelled either as voltage source +  $R_s$  or Current source with parallel to Resistor.

In CD region,  $m = \frac{\Delta y}{\Delta x} = \frac{1}{3}$

$\therefore R = \frac{1}{\frac{1}{3}} = 3 \text{ k}\Omega$

$\therefore$  For (C ||  $R_p$ ) : [compared with  $y = mx + c$ ]

$i_D = \frac{V}{3} + I_0$

or,  $y = mx + c$

$\Rightarrow y = \frac{1}{3}x + c$

Now, putting point D(10, 6) in this eq,

$6 = \frac{10}{3} + c$

$\Rightarrow c = 2.67 \text{ V}$

Hence,  $y = \frac{1}{3}x + 2.67$

Now, when  $y = 0$

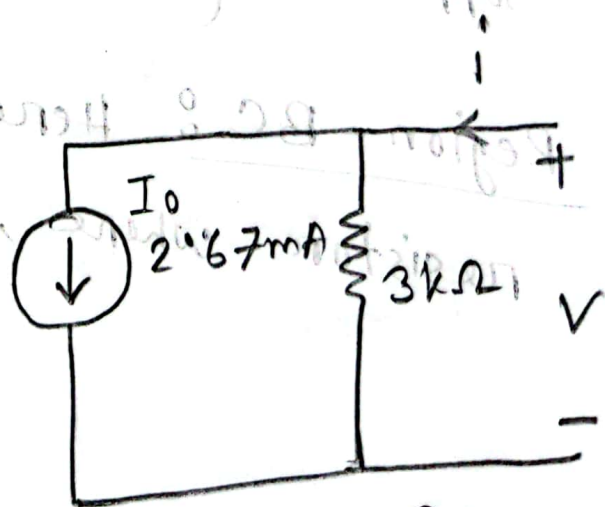


Figure : C.S +  $R_P$  model


(b)

when  $V_{BE} = 2V$ , the operating region is BC where: [It acts like a resistor]

$$m = \frac{48 - (-5)}{4 - (-5)} = 1 \quad \frac{V}{V} = m$$


$$\therefore R = 1 \text{ k}\Omega = 1000 \Omega$$
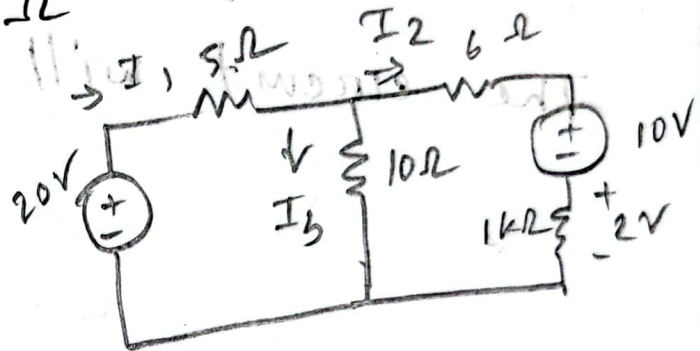
$$\begin{aligned} \text{value of } I_2 &= \frac{V}{R} \\ &= \frac{2}{1000} \\ &= 2 \times 10^{-3} \text{ A} \\ &= 2 \text{ mA} \end{aligned}$$



Alternative representation of the circuit shown in fig 1(a):

(c)

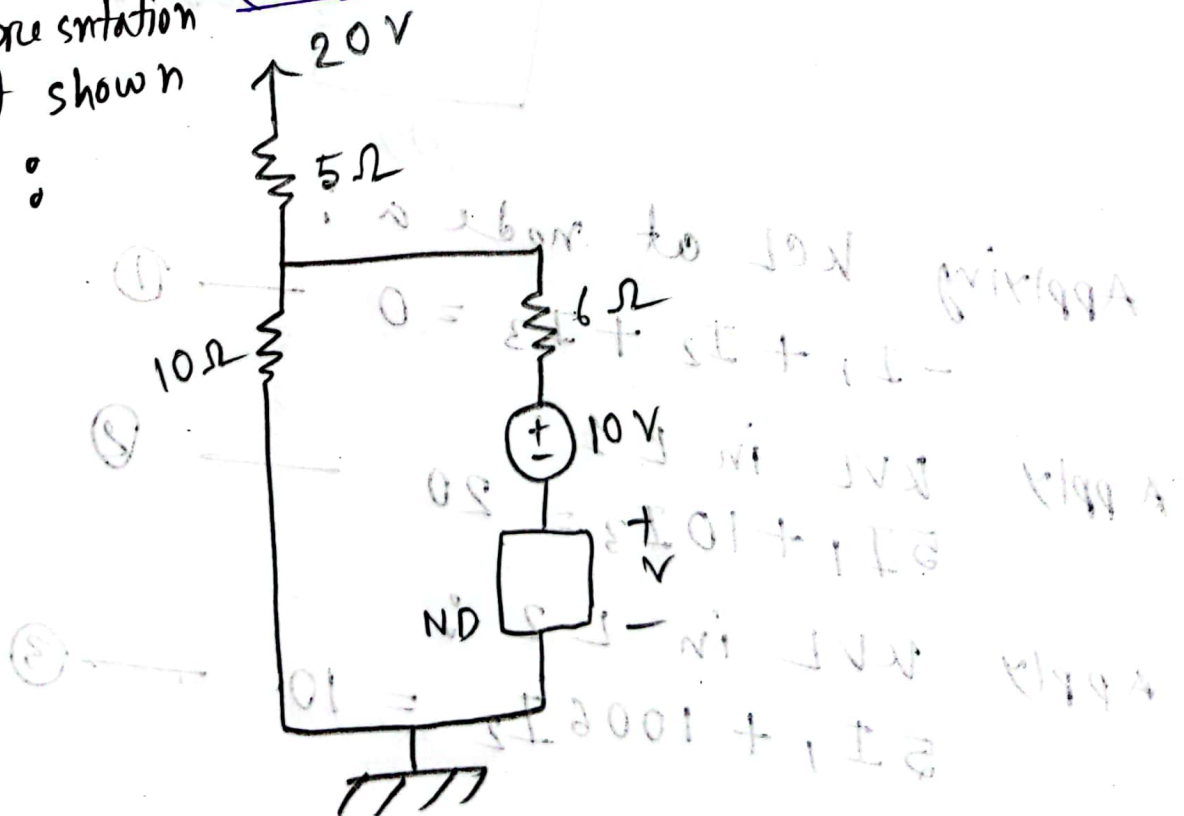


(d)

If ND acts like BC portion of graph which is a resistor, the circuit:

$$m = \frac{\Delta V}{\Delta u} = 1; R = 1 \text{ k}\Omega$$

The circuit will look like:

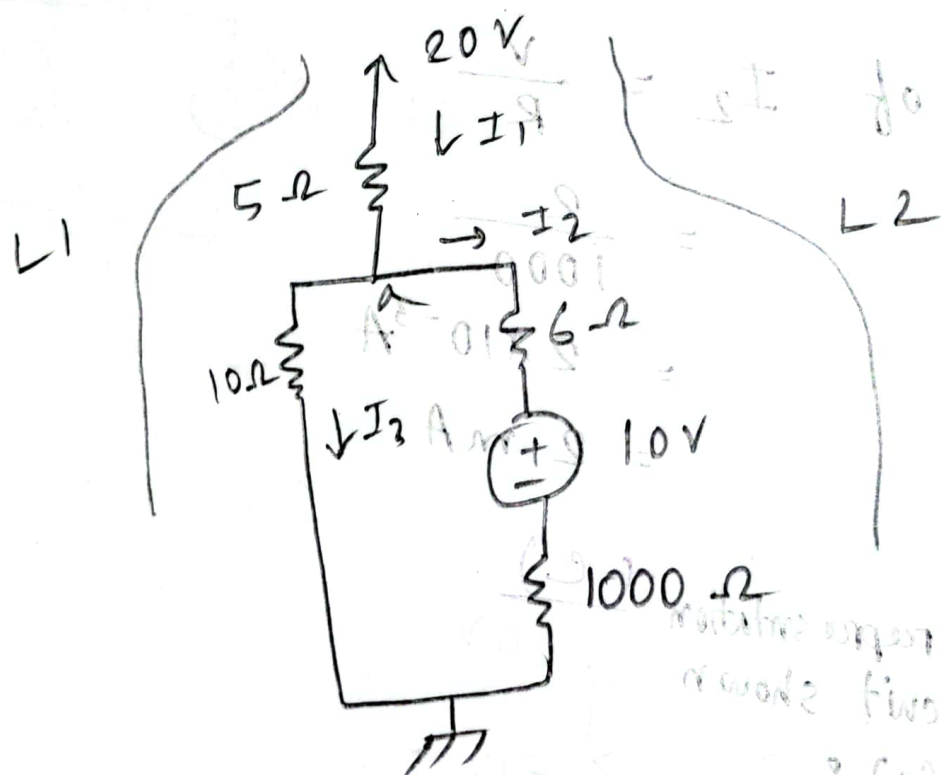

Applying KCL at node a:

$$-I_1 + I_2 + I_3 = 0 \quad \text{--- ①}$$

Apply KVL in L1:

$$5I_1 + 10I_3 = 20 \quad \text{--- ②}$$

Apply KVL in L2:

$$5I_1 + 1006I_2 = 10 \quad \text{--- ③}$$

Solving the equations:

$$I_1 = 1.335 \text{ A}, \quad I_2 = 3.302 \times 10^{-3} \text{ A}$$

$$I_3 = 1.332 \text{ A}.$$

microfilm dating : small

SI : 0.52

ID : 51301610