

BRAC University

Semester: Summer 22
Course No: CSE250
Course Title: CIRCUITS AND ELECTRONICS
Section: 19



Mid Assignment
Full Marks: 90
Release date: 28 June, 2022
Deadline: 17 July, 2022


Instructions

- This assignment contains 12 questions on various topics. You must respond to **9** of the 12 questions (see the section heading for instruction of how many to answer from each section).
- Each question is worth ten marks.
- Make an effort to solve and comprehend them.
- Turn in the hard copy of the assignment by **4:59 PM on July 17, 2022**.
- Your cover page must include your name, ID, course code, section, and submission date.
- Any form of copying will result in severe penalties. Best wishes.


Questions

Series-Parallel Configuration (Question 1 and 2 are mandatory)

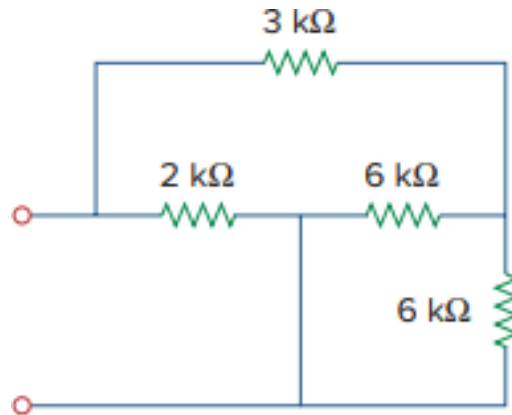1. Determine R_{eq} looking into the terminals.




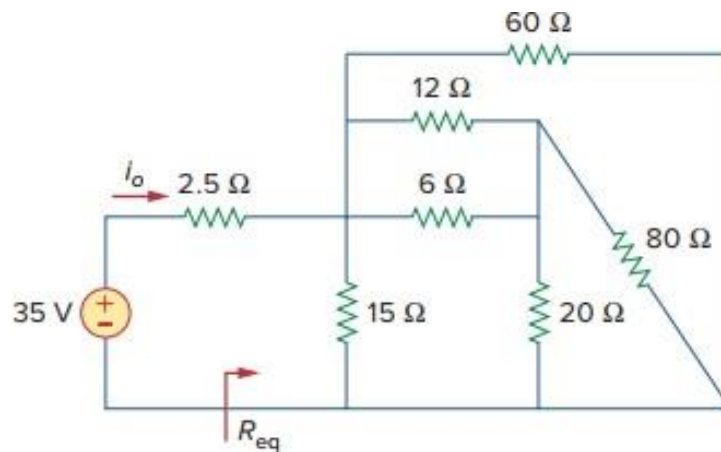2. Find R_{eq} and i_o for the following circuit.




Nodal Analysis (For questions 3–6, answer any 3)

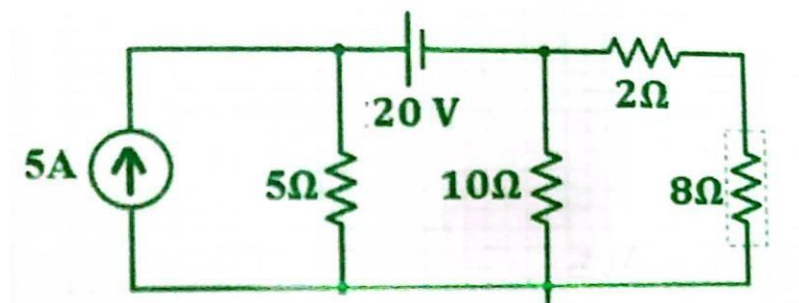
3. Find voltage across the 5 A current source using nodal analysis



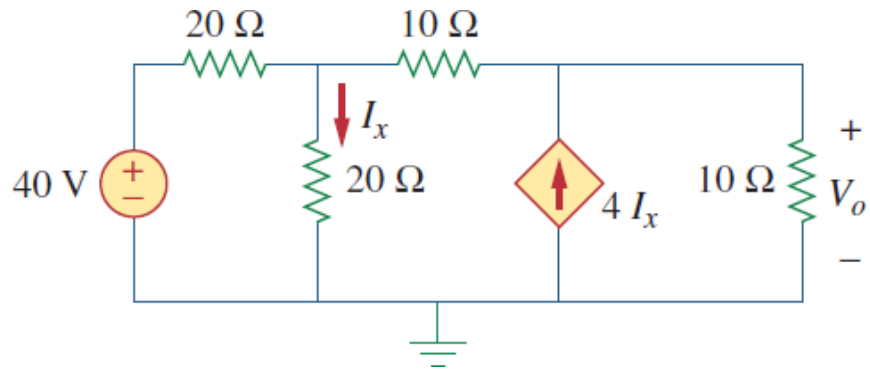
4. Using nodal analysis, determine $\mathbf{V_o}$ in the circuit below:



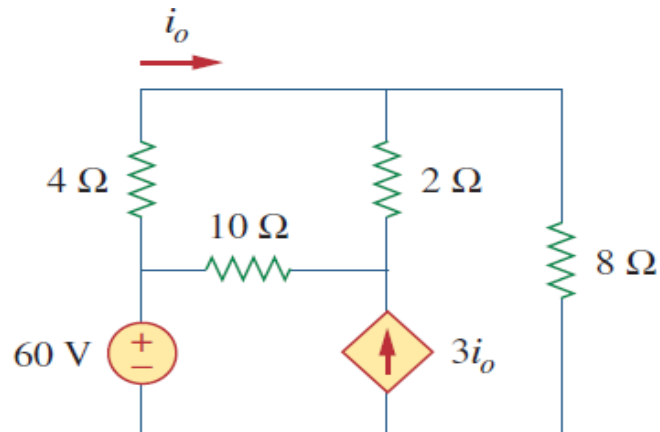5. Using nodal analysis, find current $\mathbf{i_o}$ in the circuit given below:




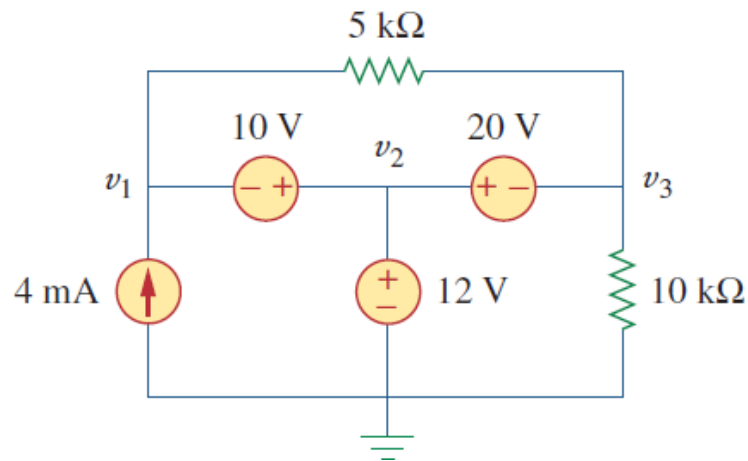6. Obtain the node voltages from the circuit shown below:




Mesh Analysis (For questions 7–9, answer any 2)

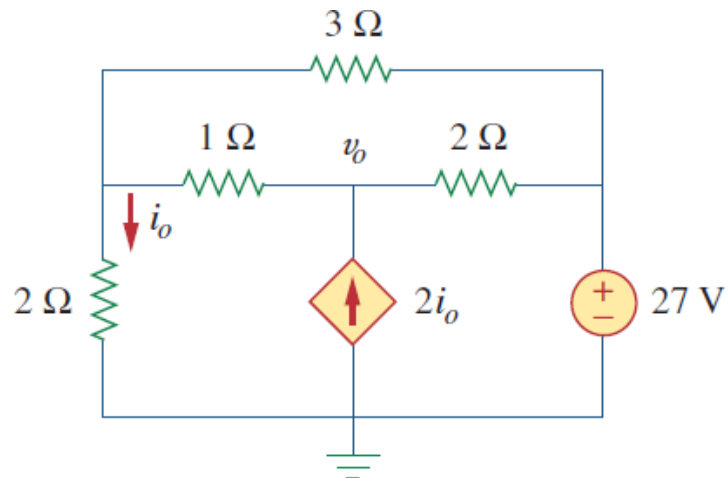
7. Find $\mathbf{v_o}$ and $\mathbf{i_o}$ in the circuit shown below:



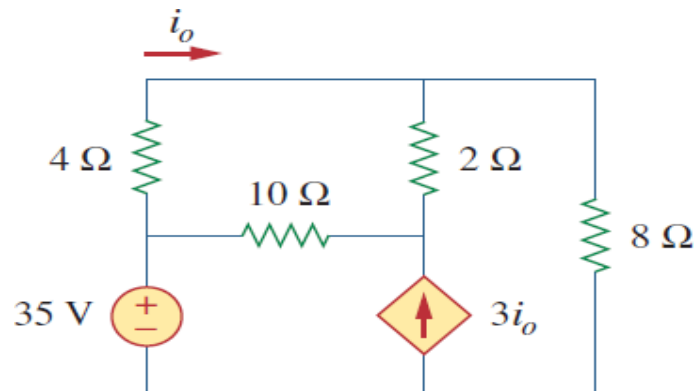8. Use mesh analysis to find the current $\mathbf{i_o}$ in the circuit given below:




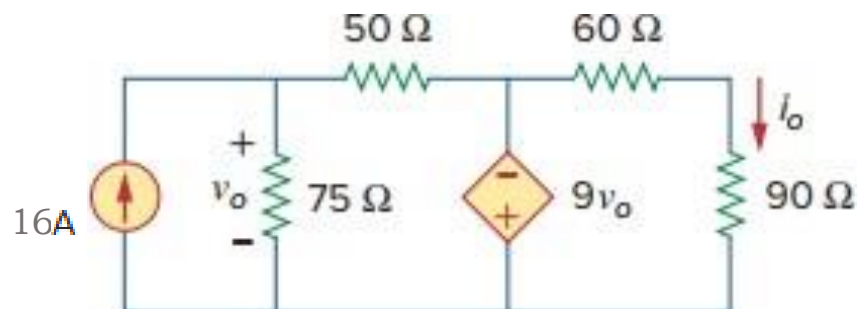9. Find $\mathbf{v_o}$ using mesh analysis.




Source Transformation (For questions 10–12, answer any 2)

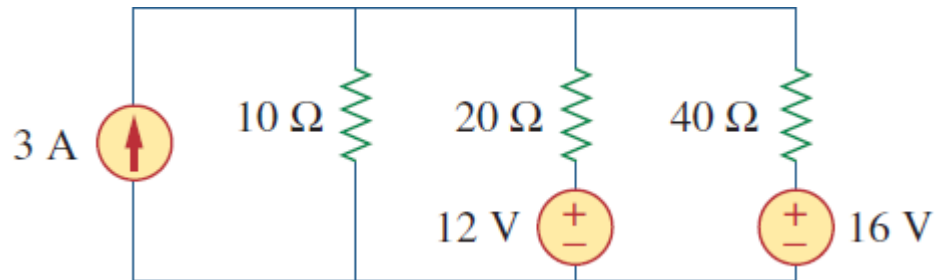10. Use source transformation to reduce the circuit in the figure below to a single voltage source in series with a single resistor.



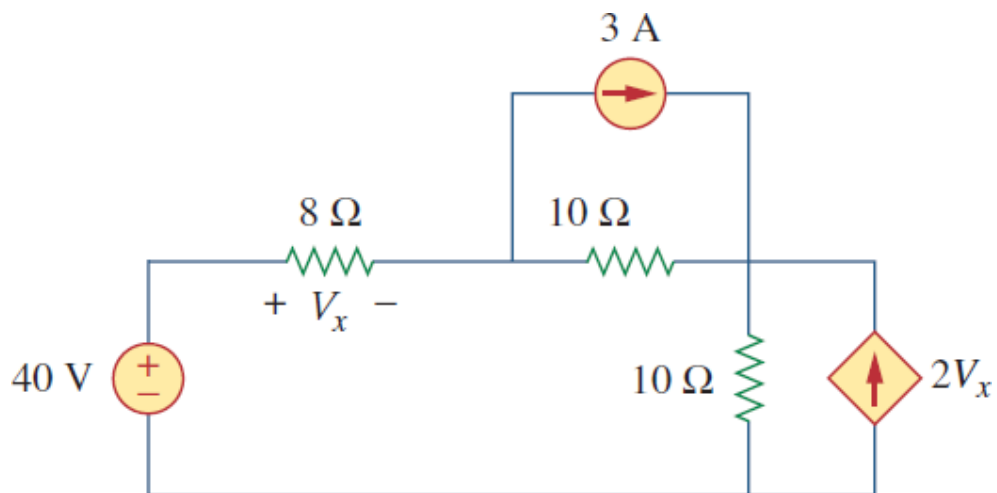11. Use source transformation to find the voltage V_x in the circuit below.



12. Obtain v_o in the circuit shown below using source transformation.

