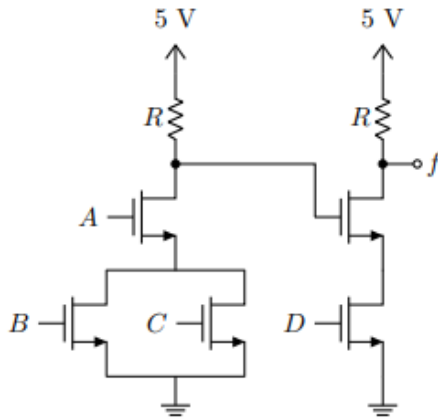



Name:**Student ID:**

1. Analyze the following circuit to find f in terms of boolean inputs A, B, C, and D. **[4.5]**



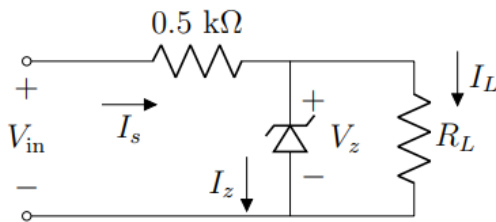2. In the circuit, the input voltage V_{in} has a nominal voltage of 10 V with a fluctuation of $\pm 10\%$. The Zener diode in the circuit is specified with parameter $V_z = 5.75$ V at $I_z = 5$ mA, $r_z = 0.05$ k Ω , and $I_{zk} = 0.3$ mA.

Identify the worst-case conditions and calculate the (i) Zener current (I_z), (ii) Zener voltage (V_z), and (iii) input voltage in this worst-case scenario. **[4.5]**




3. Design a circuit using Op-Amp to implement the expression:

[11]

$$f = -\frac{1}{3} \int x dt + 2 \ln y + 4z$$


Name:**Student ID:**

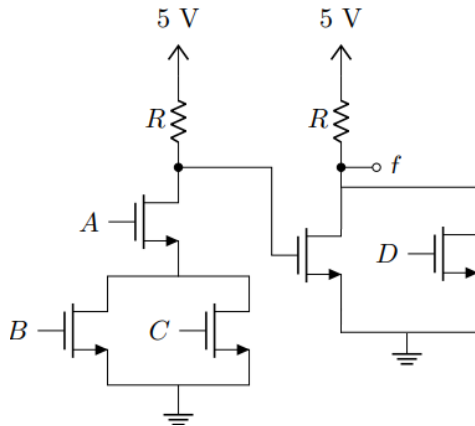1. Analyze the following circuit to find f in terms of boolean inputs A, B, C, and D. **[4.5]**



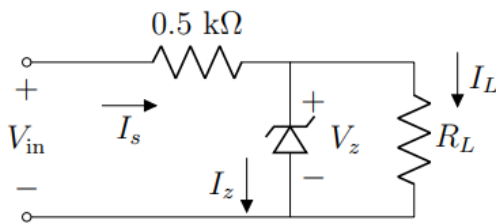2. In the circuit, the input voltage V_{in} has a nominal voltage of 10 V with a fluctuation of $\pm 5\%$. The Zener diode in the circuit is specified with parameter $V_z = 5.95$ V at $I_z = 4.5$ mA, $r_z = 0.05$ k Ω , and $I_{zk} = 0.27$ mA.

Identify the worst-case conditions and calculate the (i) Zener current (I_z), (ii) Zener voltage (V_z), and (iii) input voltage in this worst-case scenario. **[4.5]**




3. Design a circuit using Op-Amp to implement the expression:

[11]

$$f = -\frac{1}{3} \int x dt + 2 \ln y + 4z$$


Name:**Student ID:**

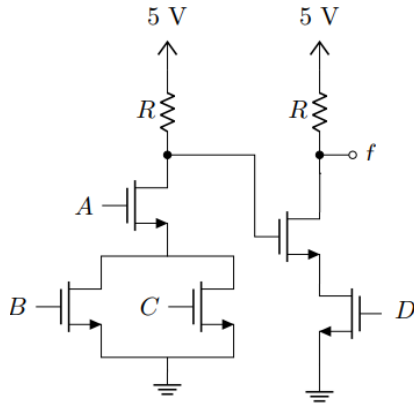1. Analyze the following circuit to find f in terms of boolean inputs A , B , C , and D . **[4.5]**



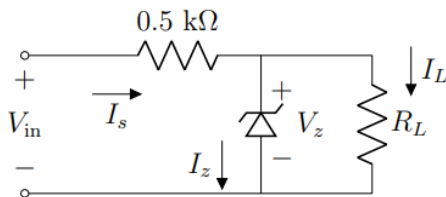2. In the circuit, the input voltage V_{in} has a nominal voltage of 10 V with a fluctuation of $\pm 2V$. The Zener diode in the circuit is specified with parameter $V_z = 5.95$ V at $I_z = 4.5$ mA, $r_z = 0.05$ k Ω , and $I_{zk} = 0.27$ mA.

Identify the worst-case conditions and calculate the (i) Zener current (I_z), (ii) Zener voltage (V_z), and (iii) input voltage in this worst-case scenario. **[4.5]**



3. Design a circuit using Op-Amp to implement the expression:

[11]

$$-\frac{1}{3} \int x dt + 2 \exp y + 4z$$