

CSE250
MID ASSIGNMENT
SUMMER 22

Name : Shihab Muhtasim

ID : 21301610

Sec : 19


Course : CSE250

Date : 18/07/2022



Series-Parallel Configuration

Ans to the or no 1

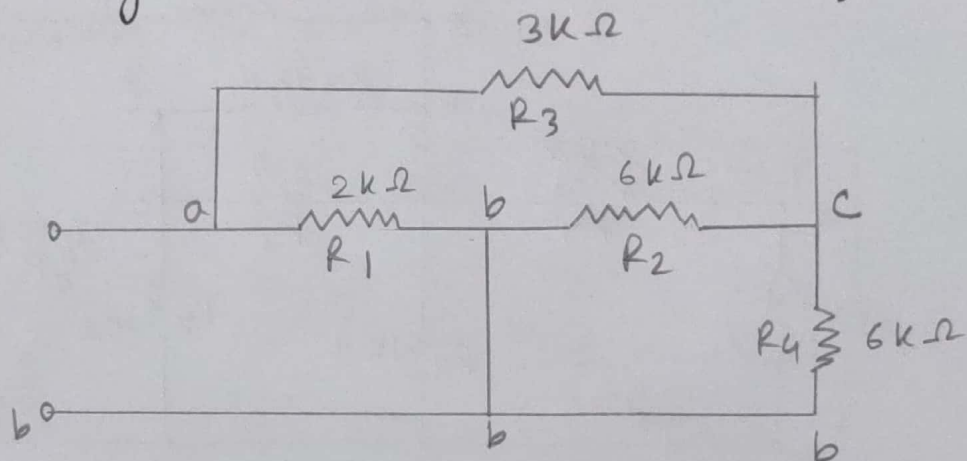Redrawing the given circuit and labeling it we get,




From the circuit above,

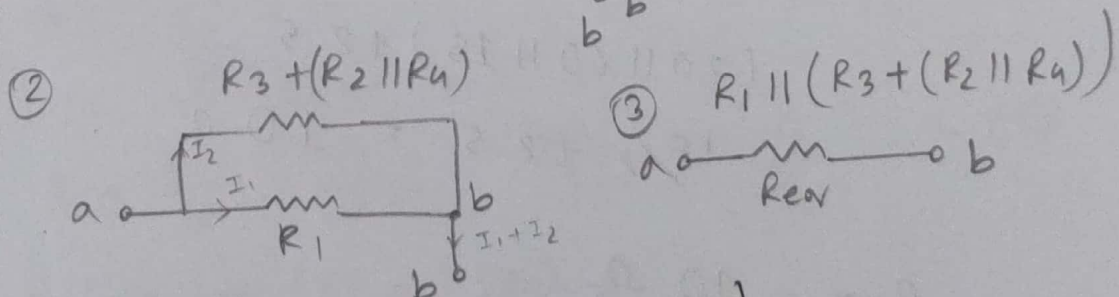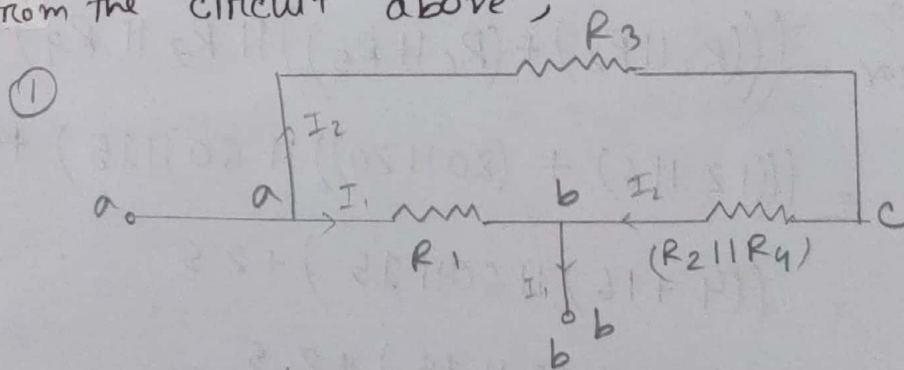

$$\begin{aligned}
 R_{eq} &= R_1 \parallel (R_3 + (R_2 \parallel R_4)) \\
 &= 2 \parallel (3 + (6 \parallel 6)) \\
 &= 2 \parallel (3 + 3) \\
 &= 2 \parallel 6 \\
 &= \frac{3}{2} \text{ k}\Omega
 \end{aligned}$$

Ans to the or no 2

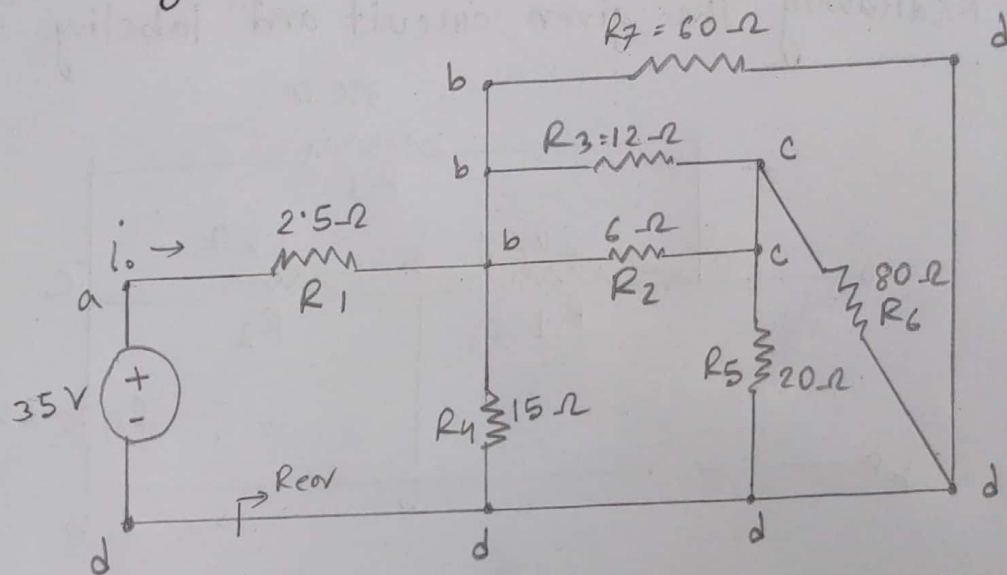Redrawing and labeling the given circuit,



$$\begin{aligned}
 \text{Here } R_{eq} &= \left(\left((R_3 \parallel R_2) + (R_6 \parallel R_5) \right) \parallel R_7 \parallel R_4 \right) + R_1 \\
 &= \left(((12 \parallel 6) + (80 \parallel 20)) \parallel 60 \parallel 15 \right) + 2.5 \\
 &= ((4 + 16) \parallel 60 \parallel 15) + 2.5 \\
 &= (20 \parallel 60 \parallel 15) + 2.5 \\
 &= 15/2 + 2.5 = 10 \Omega
 \end{aligned}$$


$$\therefore R_{eq} = 10 \Omega$$

$$\text{Now, } i_o = \frac{V}{R_{eq}} = \frac{35}{10} = 3.5 \text{ A}$$

Nodal Analysis

Ans to the or no 3

Redrawing the given circuit ,

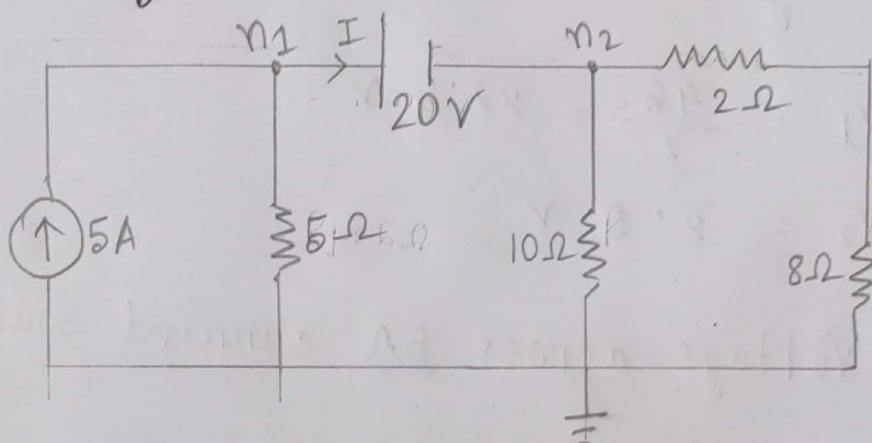

Let, current flow is I between node n_1 and n_2 because it is a supernode.

Now, KCL at node n_1 ,

$$5 = \frac{V_1}{5} + I \quad \dots (1)$$

KCL at node n_2 ,

$$I = \frac{V_2}{10} + \frac{V_2}{8+2} = \frac{2V_2}{10} = \frac{V_2}{5} \quad \dots (2)$$

Adding eq (1) and (2),

$$5 + I = \frac{V_1}{5} + \frac{V_2}{5} + I$$

$$\Rightarrow 5 = \frac{V_1 + V_2}{5}$$

$$\Rightarrow 25 = V_1 + V_2 \quad \dots (3)$$

KVL at supernode ,

$$-V_1 + 20V + V_2 = 0$$

$$\Rightarrow V_1 - V_2 = 20 \quad \dots (4)$$

Solving eq (3) and (4) ,


$$V_1 = \frac{45}{2} = 22.5 \text{ V}$$

$$V_2 = 2.5 \text{ V}$$

\therefore Voltage across 5A current source is

$$V_1 = 22.5 \text{ V}.$$

Ans to the q no 4

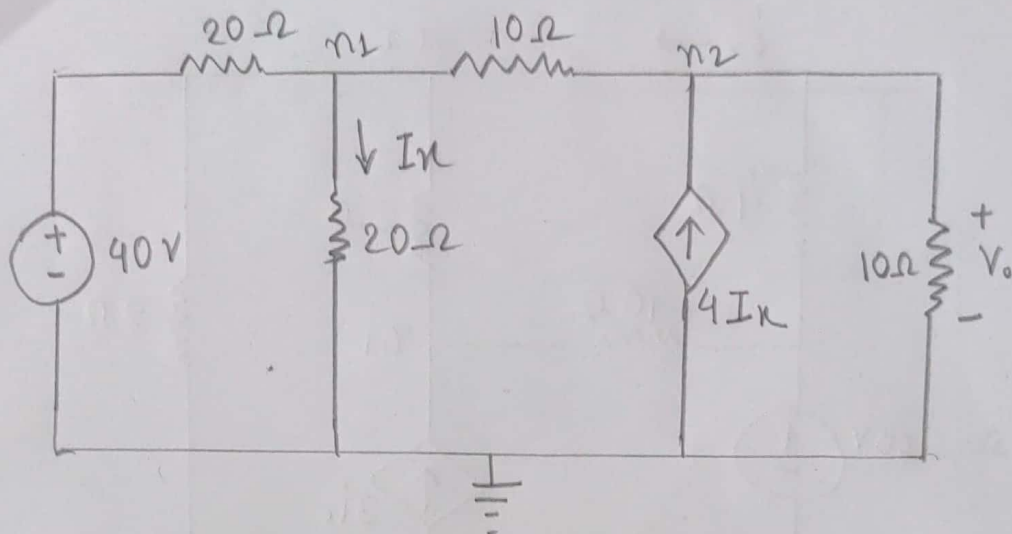

KCL at n_1 ,

$$\frac{v_1 - 40}{20} + \frac{v_1}{20} = \frac{v_2 - v_1}{10}$$

$$\Rightarrow 2v_1 - 40 = 2v_2 - 2v_1$$

$$\Rightarrow 4v_1 - 2v_2 = 40 \quad \text{--- (1)}$$

KCL at node n_2 ,

$$\frac{v_2 - v_1}{10} + \frac{v_2}{10} = 4I_n$$

$$\Rightarrow \frac{2v_2 - v_1}{10} = 4 \times \frac{v_1}{20} \quad \left[\because I_n = \frac{v_1}{20} \right]$$

$$\Rightarrow 2v_2 - v_1 = 2v_1$$


$$\Rightarrow 2v_2 - 3v_1 = 0 \quad \text{--- (2)}$$

Solving eq (1) and (2),

$$v_2 = 60 \text{ V}$$

$\therefore v_o$ in the circuit is $v_2 = v_o = 60 \text{ V}$

Ans to the or no 5

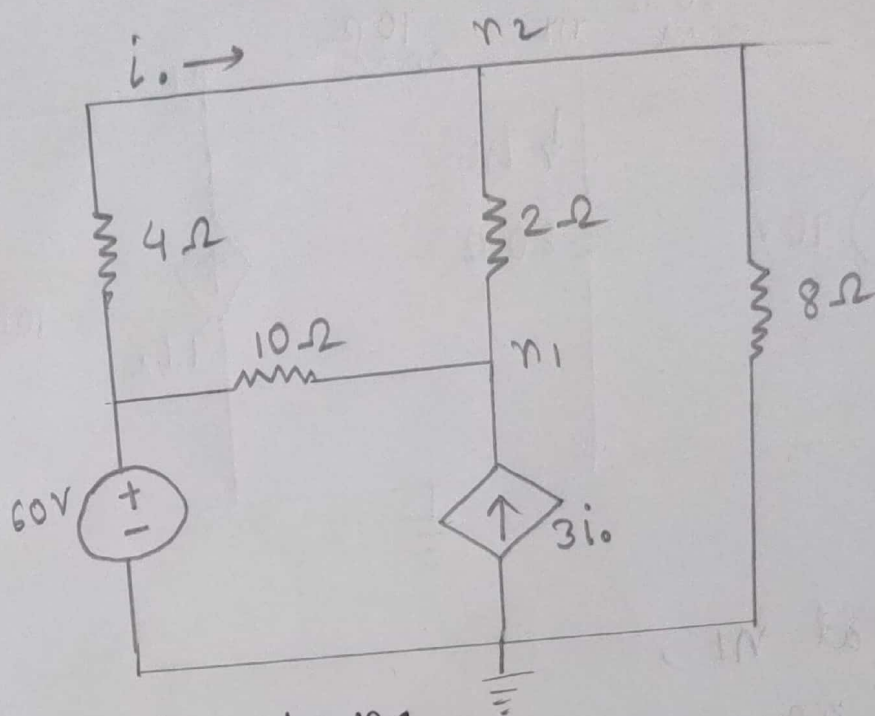

KCL at node n_1 ,

$$3i_o = \frac{v_1 - 60}{10} + \frac{v_1 - v_2}{2}$$

$$\Rightarrow 3\left(\frac{60 - v_2}{4}\right) = \frac{v_1 - 60 + 5v_1 - 5v_2}{10} \quad \left[\because i_o = \frac{60 - v_2}{4}\right]$$

$$\Rightarrow \frac{180 - 3v_2}{4} = \frac{6v_1 - 5v_2 - 60}{10}$$

$$\Rightarrow 24v_1 + 10v_2 = 2040 \quad (1)$$

KCL at node n_2 ,

$$\frac{60 - v_2}{4} + \frac{v_1 - v_2}{2} - \frac{v_2}{8} = 0$$

$$\Rightarrow \frac{120 - 2v_2 + 4v_1 - 4v_2 - v_2}{8} = 0$$

$$\Rightarrow 4v_1 - 7v_2 = -120 = 0 \quad (2)$$


Solving eq (1) and (2),

$$v_2 = \frac{690}{13} = 53.07 \text{ V}$$

$$\text{Current } i_o \text{ in the circuit, } i_o = \frac{60 - v_2}{4} = \frac{60 - 53.07}{4}$$

$$i_o = 1.73 \text{ A}$$

Ans to the q no 6

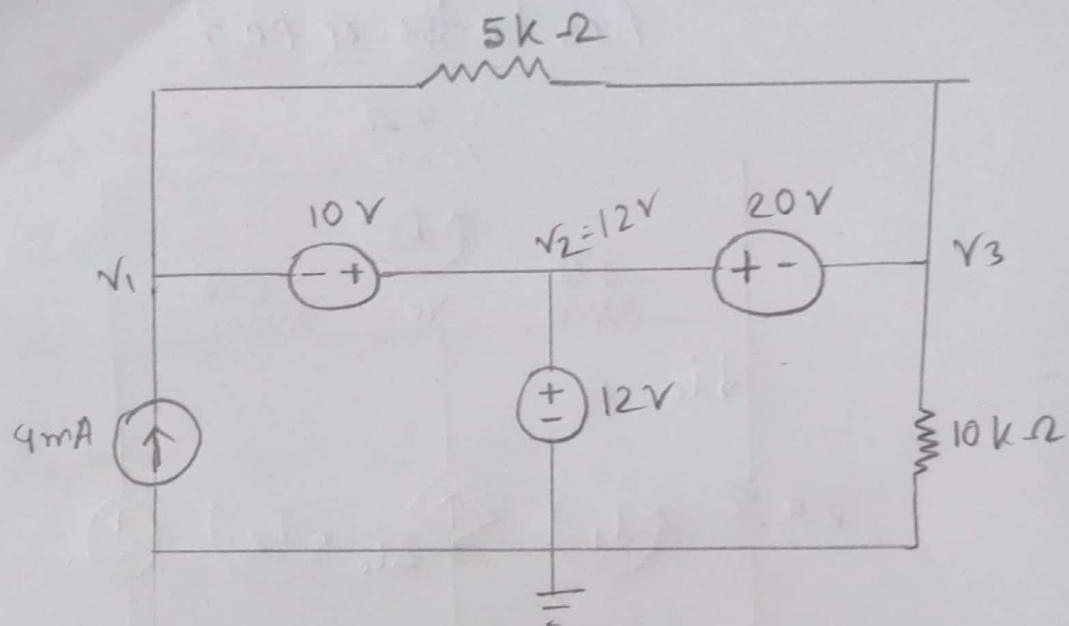

Since node v_2 is shorted with 12V voltage,

$$v_2 = 12\text{V}$$

Again,

$$v_1 - v_2 = -10$$

$$\Rightarrow v_1 = v_2 - 10$$

$$\Rightarrow v_1 = 12 - 10 = 2$$

$$\therefore v_1 = 2\text{V}$$

$$\text{Now, } v_2 - v_3 = 20$$

$$\Rightarrow v_3 = -20 + v_2$$

$$\Rightarrow v_3 = 12 - 20$$


$$\Rightarrow v_3 = -8\text{V}$$

The node voltages of the circuit,

$$v_1 = 2\text{V}, v_2 = 12\text{V}, v_3 = -8\text{V}$$

Mesh Analysis

Ans to the or no 7

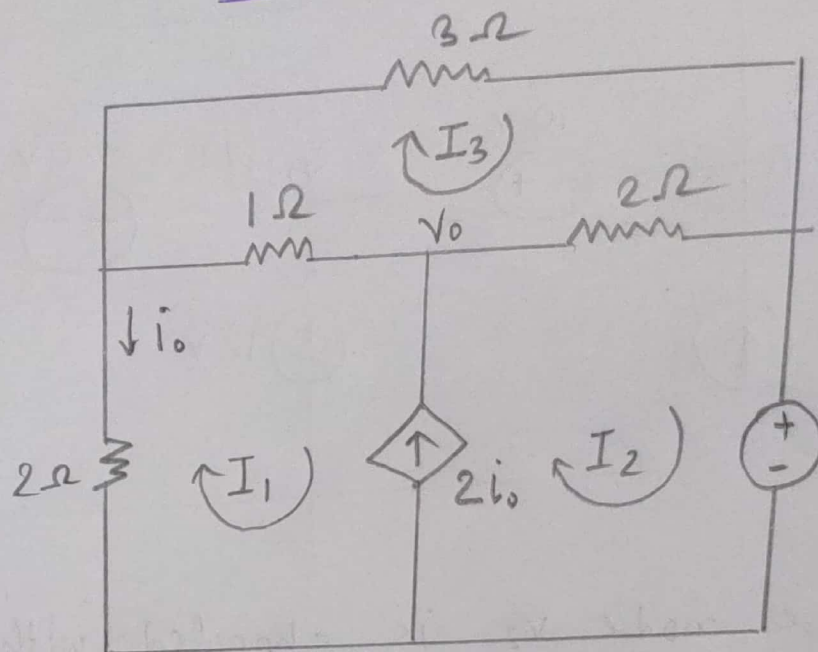

KVL at loop (1+2) due to supermesh,

$$2I_1 + I_1 - I_3 + 2I_2 - 2I_3 + 27 = 0$$

$$\Rightarrow 3I_1 + 2I_2 - 3I_3 = -27 \quad \text{--- (1)}$$

At the dependent source,

$$I_2 - I_1 = 2i_o$$

$$\Rightarrow I_2 - I_1 + 2I_1 = 0 \quad [\because i_o = -I_1]$$

$$\Rightarrow I_1 + I_2 = 0 \quad \text{--- (2)}$$

KVL at loop 3,

$$3I_3 + 2I_3 - 2I_2 + I_3 - I_1 = 0$$

$$\Rightarrow -I_1 - 2I_2 + 6I_3 = 0 \quad \text{--- (3)}$$

Solving eq 1, 2, 3 we get ,

$$I_1 = -18 ,$$

$$I_2 = 18 ,$$

$$I_3 = 3 .$$

$$\text{Now, } i_o = -I_1 = 18 \text{ A}$$

Applying KVL at loop 2 ,

$$-V_o + 2I_2 - 2I_3 + 27 = 0$$


$$\Rightarrow V_o = 2(18) - 2(3) + 27$$

$$\Rightarrow V_o = 57 \text{ V}$$

$$\therefore V_o = 57 \text{ V}$$

$$i_o = 18 \text{ A}$$

Ans to the or no 8

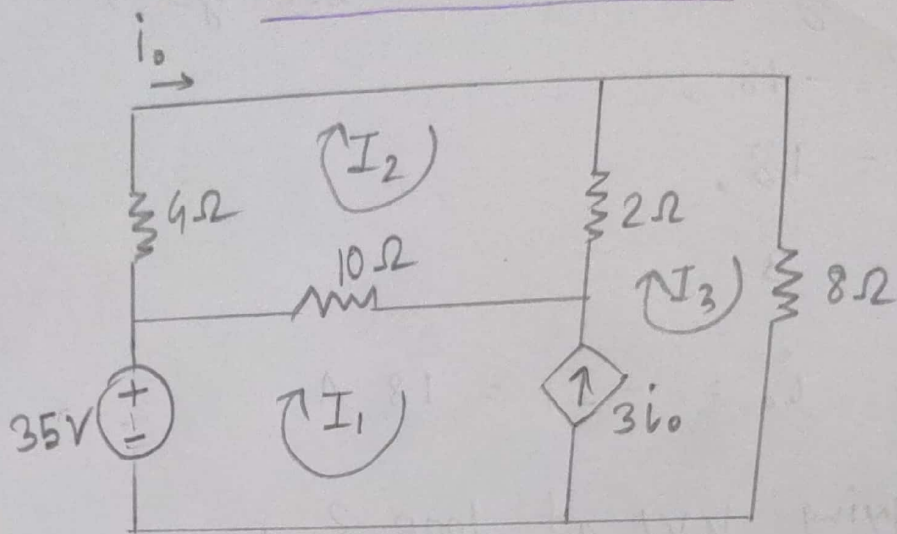

KVL at loop (1+3) due to supermesh,

$$-35 + 10I_1 - 10I_2 + 2I_3 - 2I_2 + 8I_3 = 0$$

$$\Rightarrow 10I_1 - 12I_2 + 10I_3 = 35 \quad \text{--- (1)}$$

Again, at the dependent source,

$$I_3 - I_1 = 3i_o$$

$$\Rightarrow -I_1 - 3I_2 + I_3 = 0 \quad \text{--- (2)} \quad [\because i_o = I_2]$$

Now, KVL at loop 2,

$$10I_2 - 10I_1 + 4I_2 + 2I_2 - 2I_3 = 0$$

$$\Rightarrow -10I_1 + 16I_2 - 2I_3 = 0 \quad \text{--- (3)}$$


Solving eq 1, 2, 3 we get,

$$I_1 = 0.841 \text{ A}, \quad I_2 = 1.009 \text{ A}, \quad I_3 = 3.8701 \text{ A}$$

$$\therefore i_o = I_2 = 1.009 \text{ A}$$

\therefore Current i_o is 1.009 A.

Ans to the or no 9

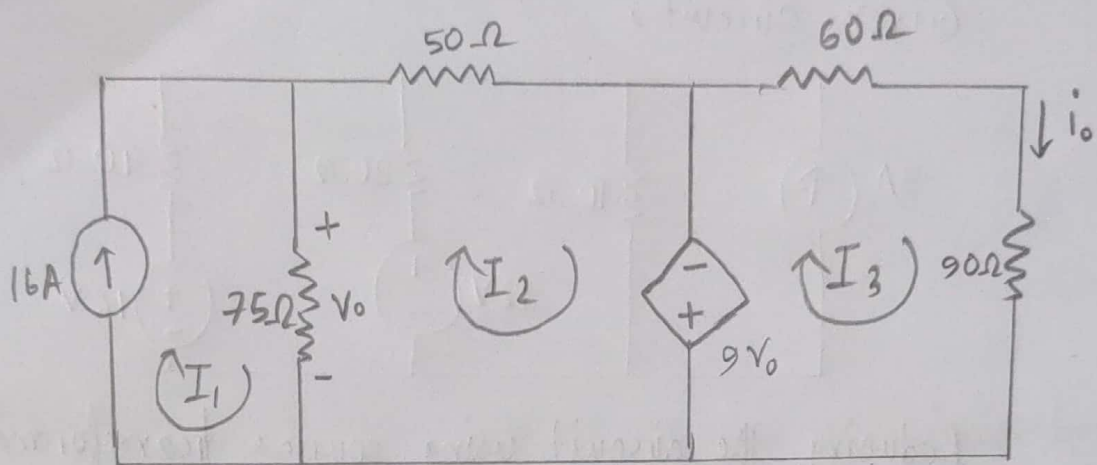

from loop 1 ,

$$I_1 = 16 \text{ A}$$

KVL at loop 2 ,

$$75 I_2 - 75 I_1 + 50 I_2 - 9 V_0 = 0$$

$$\Rightarrow 125 I_2 - 75 I_1 = 9 V_0$$

$$75 = \frac{V_0}{I_1 - I_2}$$

$$\Rightarrow 125 I_2 - 75 I_1 = 9 \times \{75 (I_1 - I_2)\} \Rightarrow V_0 = 75 (I_1 - I_2)$$

$$\Rightarrow -750 I_1 + 800 I_2 = 0$$

$$\Rightarrow I_2 = \frac{750 \times 16}{800}$$

$$\Rightarrow I_2 = 15 \text{ A}$$

$$\text{Now, } V_0 = 75 (I_1 - I_2)$$

$$\Rightarrow V_0 = 75 (16 - 15)$$


$$\Rightarrow V_0 = 75 \text{ V}$$

$\therefore V_0$ in this circuit is 75 V.


Source Transformation

Ans to the or no 10


Given circuit,

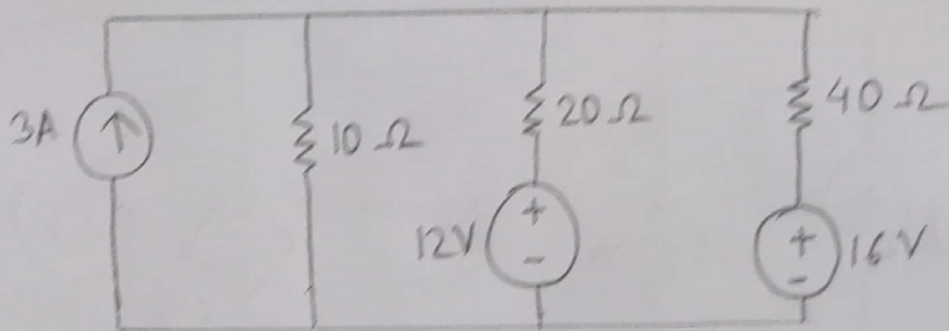

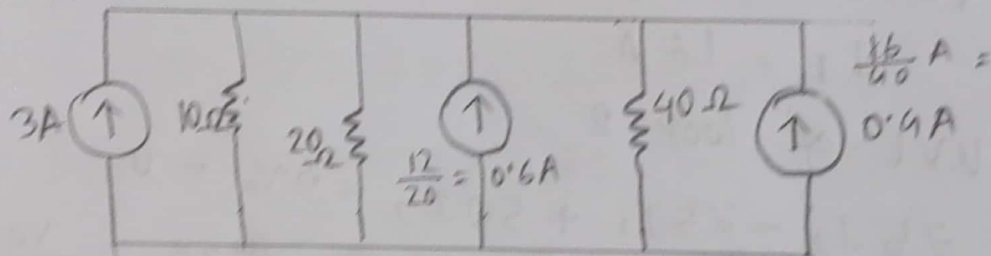Reducing the circuit using source transformation,
step 1 :



step 2 :

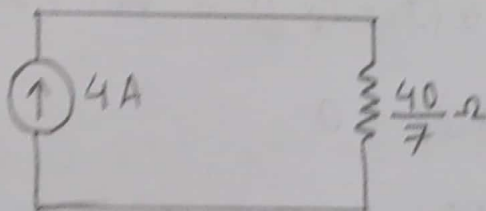


Here,

$$① \uparrow 4A = (3 + 0.6 + 0.4) A$$


$$② \frac{40}{7} \Omega = (10 \parallel 20 \parallel 40) \Omega$$

step 3 :

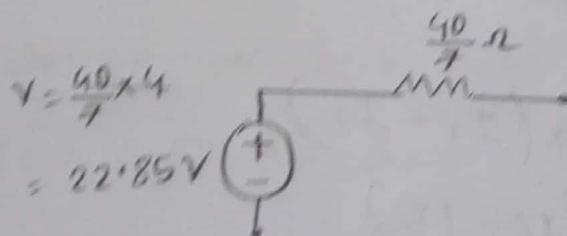


Ans to the or no 11


Given circuit,

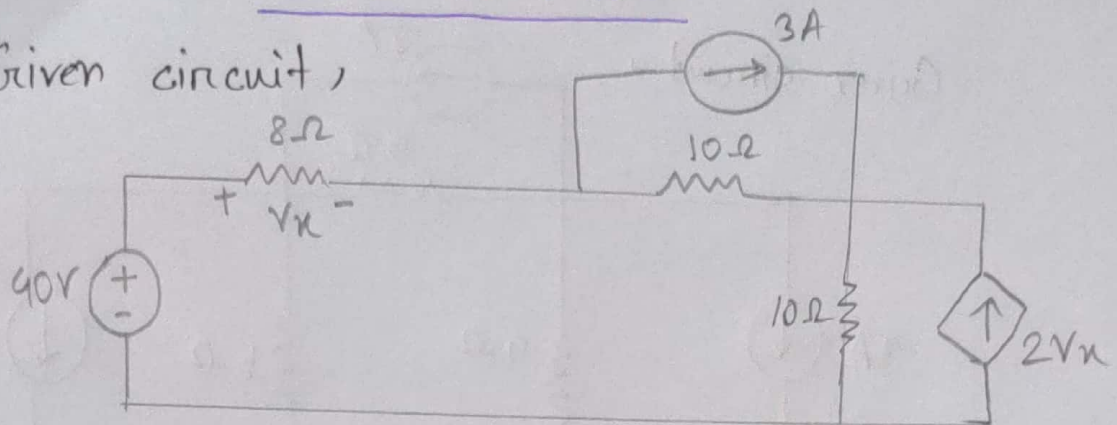

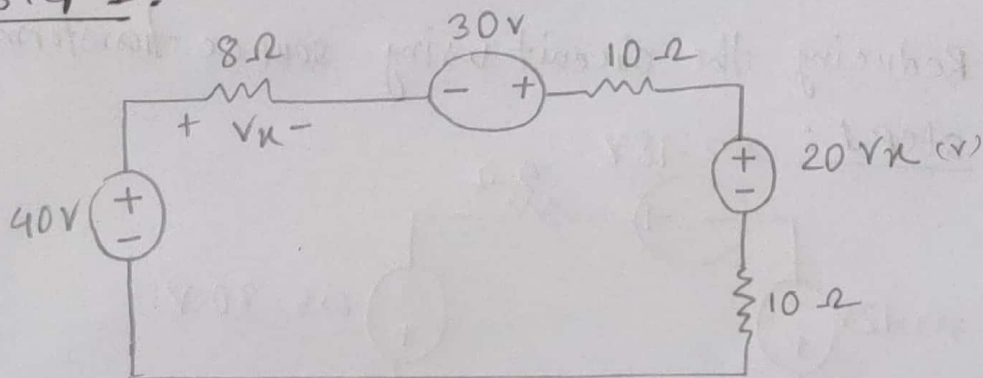Reducing the circuit using source transformation,
step 1:



step 2 :

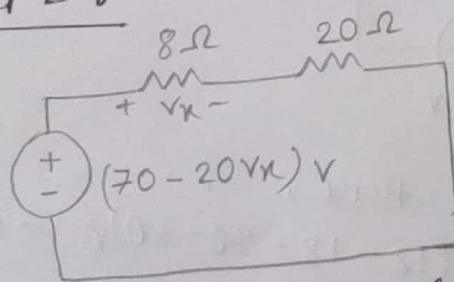

Here,

$$(40 + 30 - 20V_x)V = (70 - 20V_x)V$$

$$\text{Now, current, } I = \frac{V}{R_{\text{eq}}} = \frac{70 - 20V_x}{28}$$

$$\text{Again, } V_x = IR_8$$

$$\Rightarrow V_x = \frac{70 - 20V_x}{28} \times 8$$


$$\Rightarrow 23.5V_x = 70$$

$$\Rightarrow V_x = 2.98 \text{ V}$$

\therefore Voltage V_x in the circuit is 2.98 V


Ans to the or no 12

Given circuit,

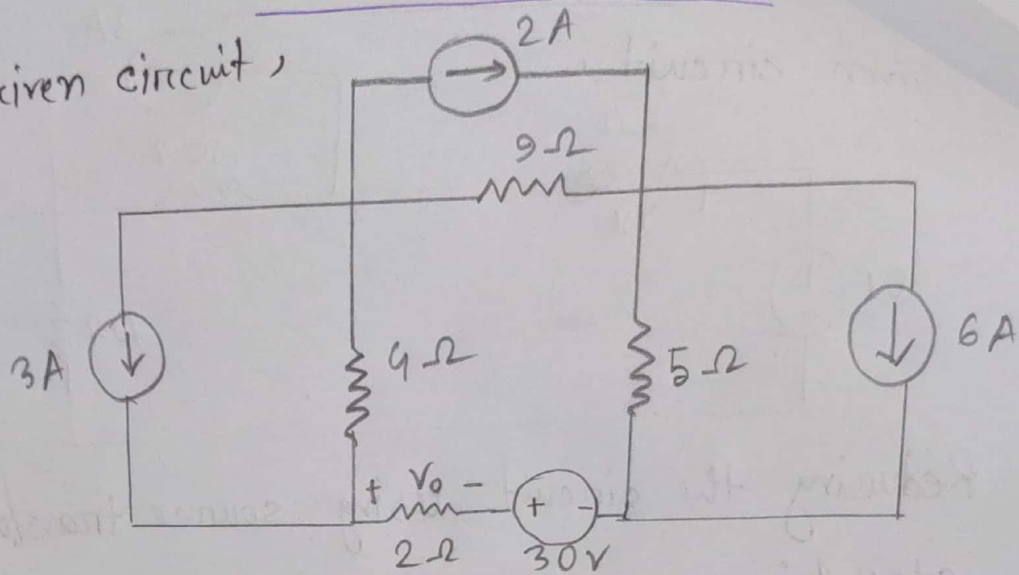


Reducing the circuit using source transformation,

step 1: $9 \times 2 = 18V$

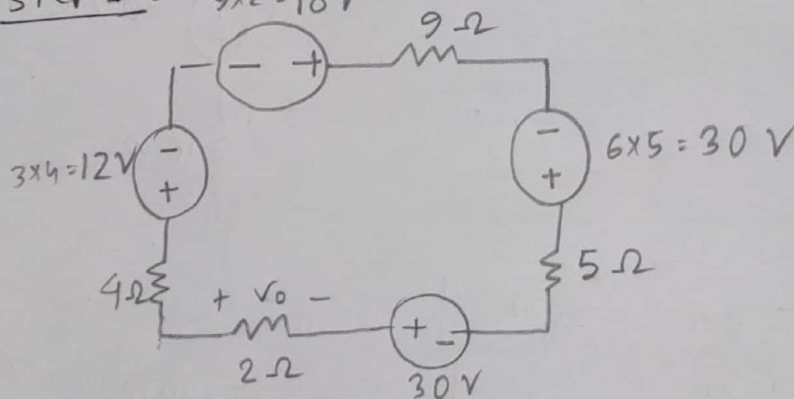

step 2:

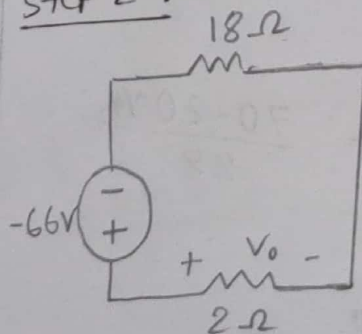

Here,
 $(12 - 18 - 30 - 30)V = -66V$

Now,

$$\text{Current, } I = \frac{V}{R_{\text{eq}}} = \frac{-66}{20}$$

$$V_o = IR_2 = \frac{-66}{20} \times 2$$
$$= -6.6V$$

$\therefore V_o$ in the circuit is $-6.6V$