

1.



CSE251

Electronic Devices and Circuits

Exp-02: Study of Half-Wave and Full-Wave Diode Rectifier Circuit

Submitted By:

Name: Fardeen Bin Ibrahim

ID: 20201066

Group: 05

Semester: Fall 22

Cooperated by:

ID: 21301610

ID: 21301611

ID: 20101443

Date of Performance: 10/10/22

Date of Submission: 16/10/22

2.

Average RMS for HW= $V_m/\pi = 1.579V$

Effective RMS for HW= $V_m/2 = 2.480V$

The values are similar to those obtained in the multimeter.

Average RMS for FW= $2V_m/\pi = 3.158V$

Effective RMS for FW= $V_m/\sqrt{2} = 3.507V$

The values are larger than those obtained in the multimeter.

3. Data Table

		Experimental Observation			Theoretical Calculation		
	C(uF)	Vr-rms (V)	Vdc (V)	Ripple Factor	Vr-rms (V)	Vdc (V)	Ripple Factor
HW	1	0.690	3.20	0.216	0.647	3.28	0.197
	4.7	0.224	3.93	0.0570	0.208	3.96	0.0525
FW	1	0.328	3.36	0.0976	0.323	3.40	0.0950
	4.7	0.091	3.63	0.0251	0.104	3.62	0.0287

4. Circuit Diagrams:

Sub: _____

SAT SUN MON TUE WED THU FRI
☐ ☐ ☐ ☐ ☐ ☐ ☐

DATE: / /

Circuit Diagrams:

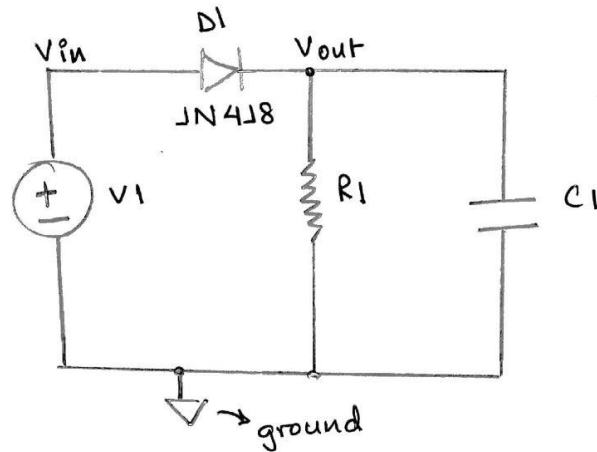


Figure: Half Wave Rectifier Circuit




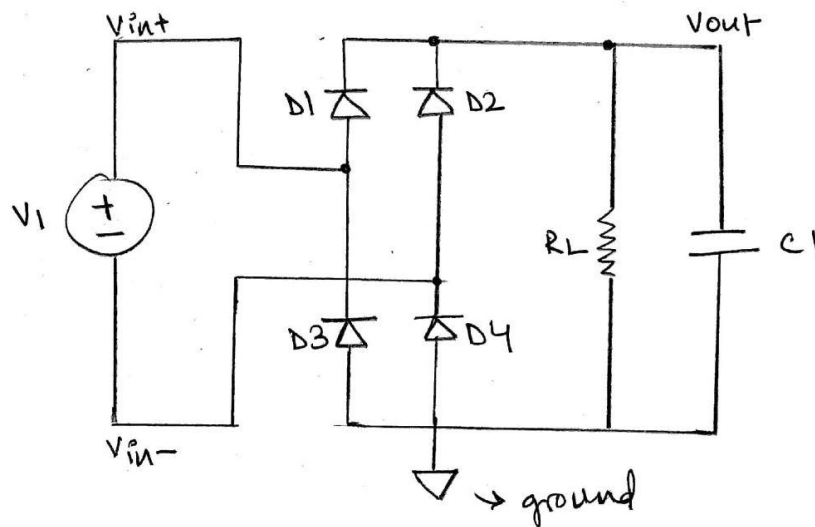
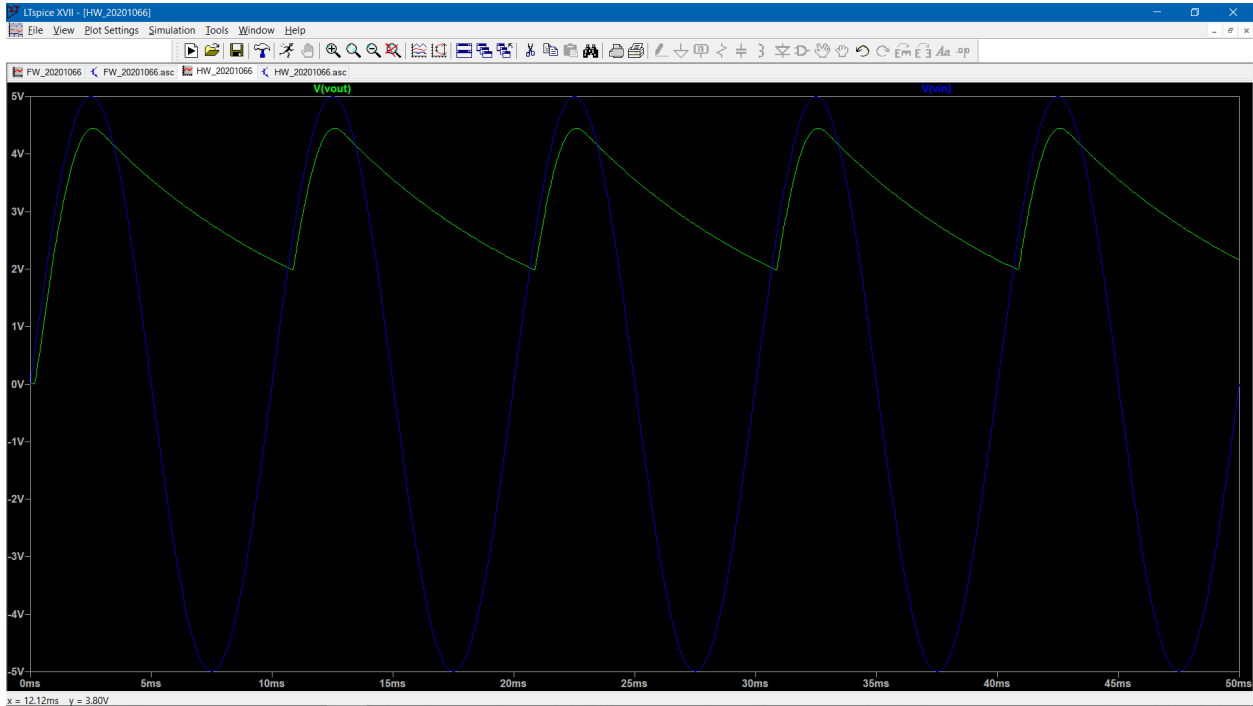
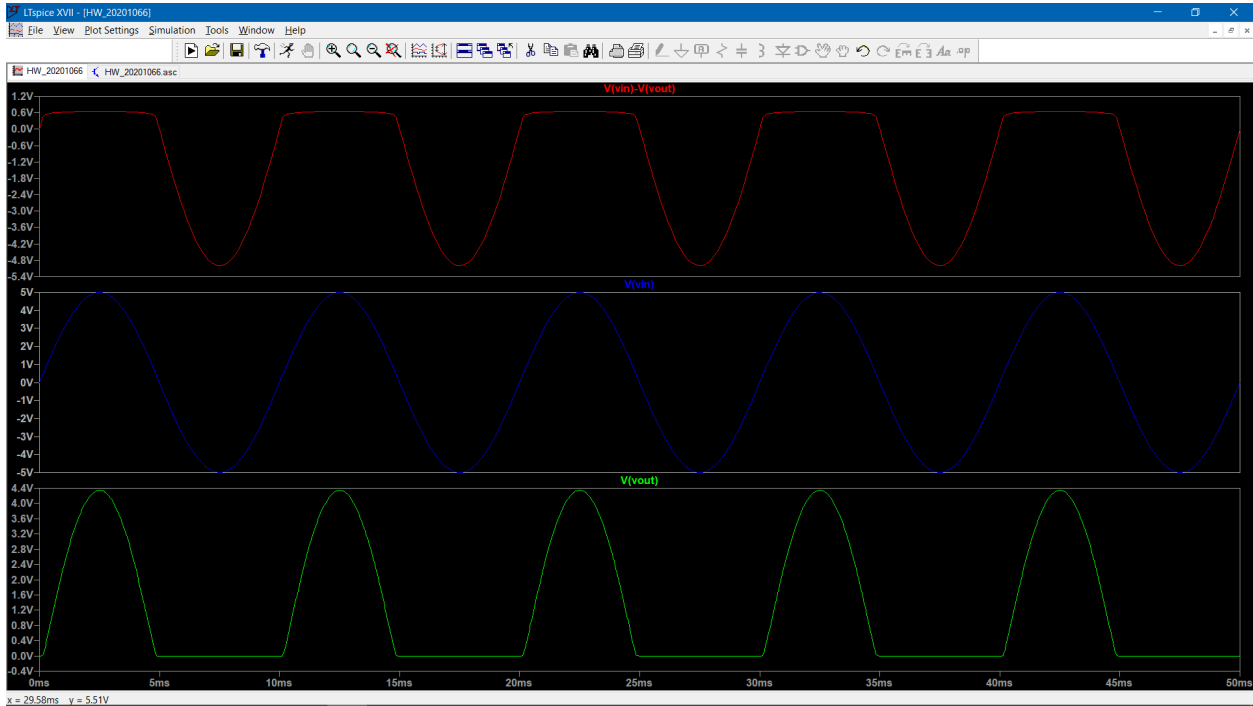
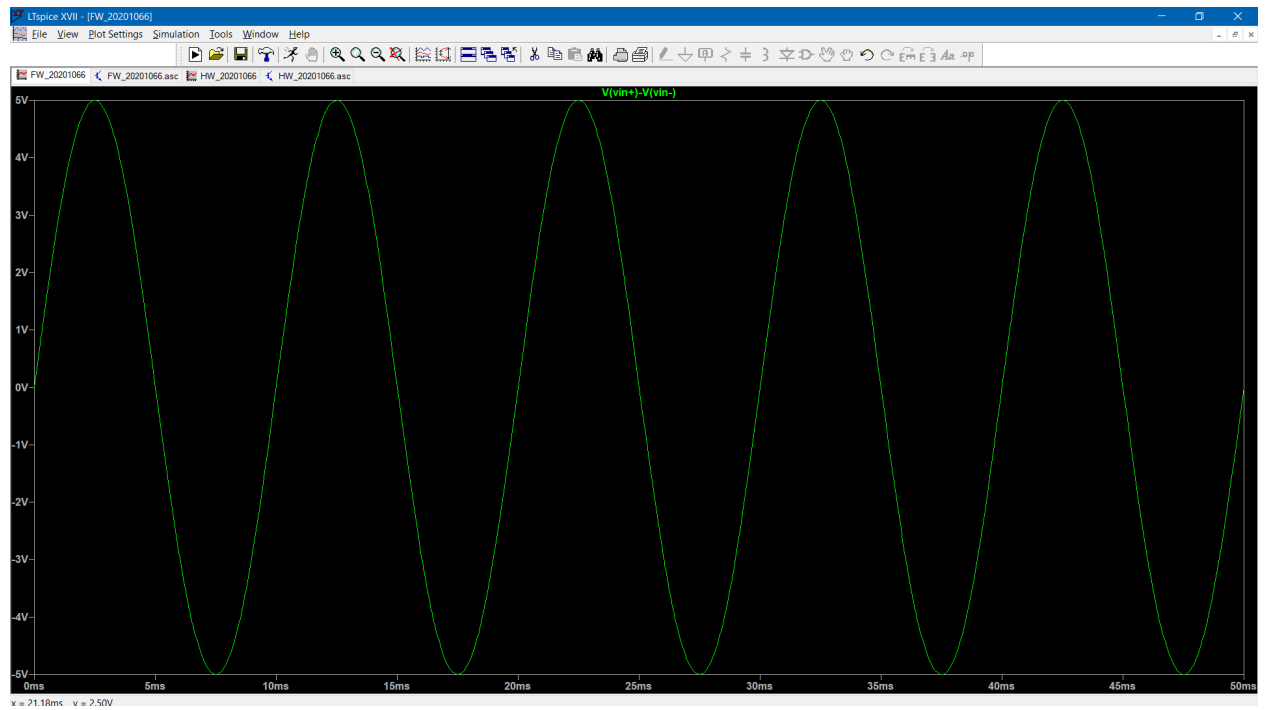


Figure: Full Wave Rectifier Circuit

5. Waveform Traces

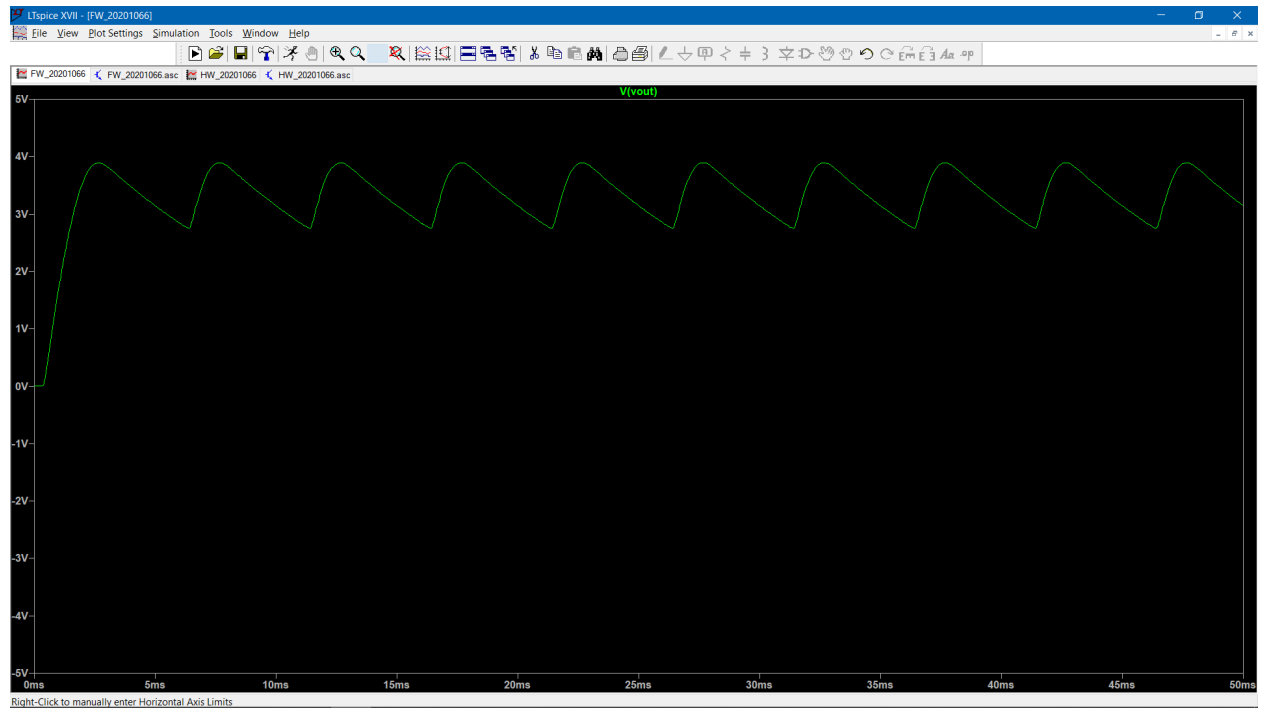

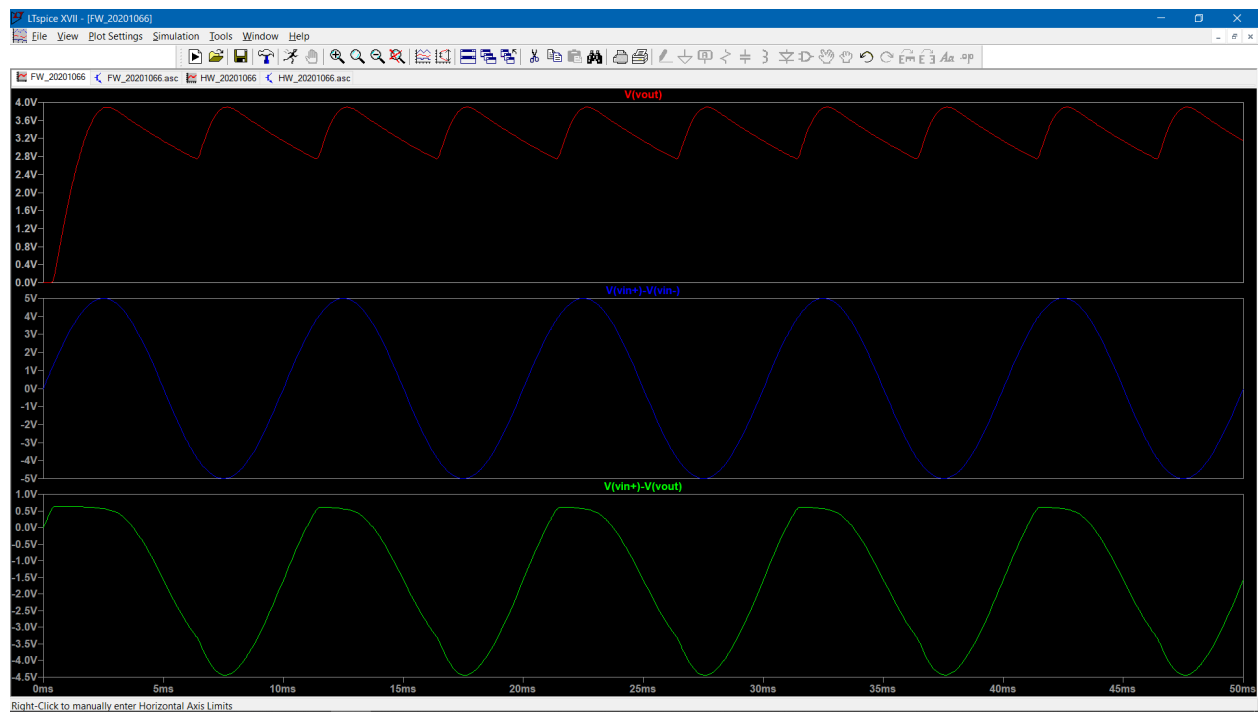

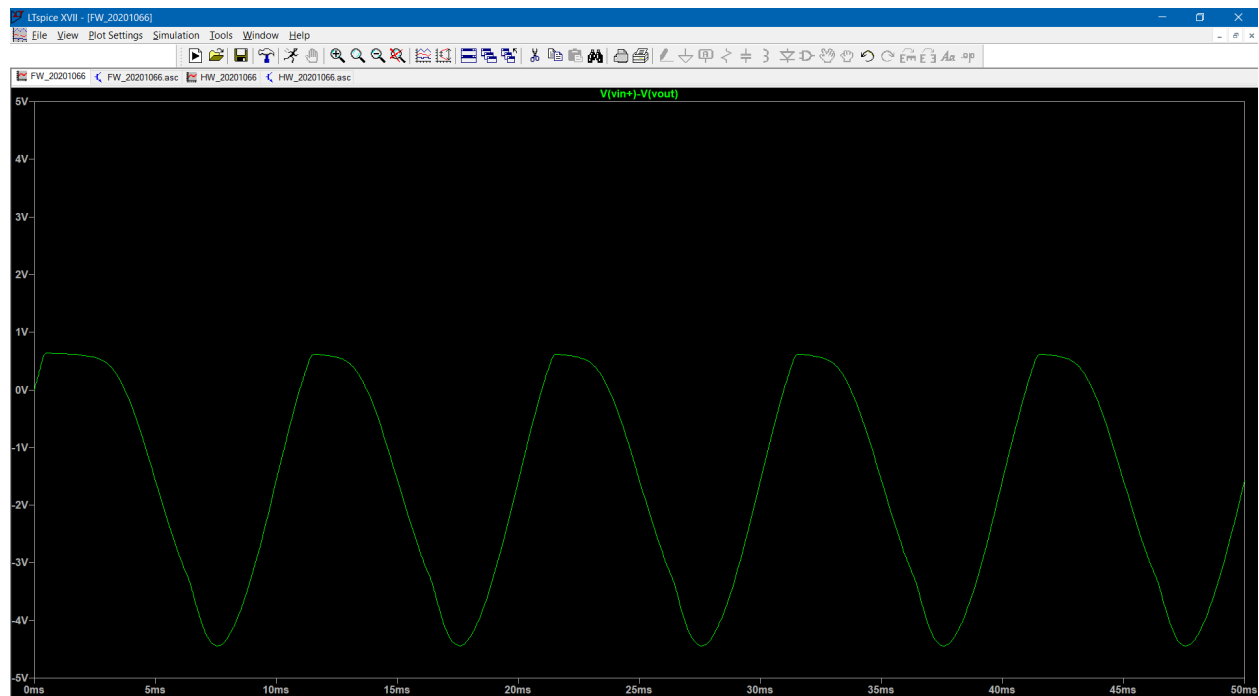

6. Data Sheet

Lab Group: 05

Student ID: 20201066, 20101443, 21301610, 21301611

Experimental Observation

- HW Rectifier without Capacitor:**
 Peak output voltage, V_p (oscilloscope) = 4.96V
 Average or DC output voltage, V_{dc} (multimeter in DC mode) = 1.31V
 RMS or AC output voltage, V_{r-rms} (multimeter in AC mode) = 1.70V
- HW Rectifier with 1μF Capacitor:**
 Peak output voltage, V_p (oscilloscope) = 4.40V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 2.24V
 Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 3.20V
 RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.690V
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.216$
- HW Rectifier with 4.7μF Capacitor:**
 Peak output voltage, V_p (oscilloscope) = 4.32V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 0.72V
 Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 3.93V
 RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.224V
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.0570$

Theoretical Calculation (Homework)

- HW Rectifier Without Capacitor:**
 Peak output voltage, V_p (see the experimental observation) = 4.96V
 Peak input voltage, $V_m = 4.96V$
 Diode voltage, $V_{D0} = 0.7V$
 DC output voltage of the rectifier, $V_{dc} = \frac{V_m}{\pi} - \frac{V_{D0}}{2} = 1.229V$
 RMS or AC output voltage, $V_{r-rms} = \frac{V_p}{2} = 2.48V$
- HW Rectifier With 1μF Capacitor:**
 Peak output voltage, V_p (see the experimental observation) = 4.40V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (see the experimental observation) = 2.24V
 DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.28V$
 RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.647V$
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.197$
- HW Rectifier with 4.7μF Capacitor:**
 Peak output voltage, V_p (see the experimental observation) = 4.32V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (see the experimental observation) = 0.72V
 DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.96V$
 RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.208V$
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.0525$

Task-02: FW Rectifier

Procedure

- Construct circuit of Figure 6 without the capacitor. Observe V_s and V_o separately on the oscilloscope [i.e. use only one channel].
- Save the input and output waveforms in your memory stick, or sketch the waveforms on a tracing paper.
- Measure V_o with a multimeter in dc and ac mode.
- Connect 1μF capacitor across the load resistor, R_L (BE CAREFUL about the polarity of the capacitor).
- Save the output waveform in your memory stick, or sketch the waveform on a tracing paper.
- Measure the peak voltage of the output, V_p and peak-to-peak ripple voltage $V_{r(p-p)}$ from the oscilloscope (To measure the peak and the ripple voltages, go to the "measure" tab of the oscilloscope or switch on the cursors of the oscilloscope. This allows you to level your cursor horizontally with the peak or the ripple voltage and measure the values).

7. Also measure V_o with a multimeter in dc and ac mode and calculate the ripple factor.
8. Replace $1\mu\text{F}$ Capacitor with $4.7\mu\text{F}$ and repeat steps 4-7.

Experimental Observation

1. **FW Rectifier without Capacitor:**
 Peak output voltage, V_p (oscilloscope) = 4.0V
 Average or DC output voltage, V_{dc} (multimeter in DC mode) = 2.26V
 RMS or AC output voltage, V_{r-rms} (multimeter in AC mode) = 1.36V
2. **FW Rectifier with $1\mu\text{F}$ Capacitor:**
 Peak output voltage, V_p (oscilloscope) = 3.96V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 1.12V
 Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 3.36V
 RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.328V
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.0976$
3. **FW Rectifier with $4.7\mu\text{F}$ Capacitor:**
 Peak output voltage, V_p (oscilloscope) = 3.80V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (oscilloscope) = 0.36V
 Average or DC value of the ripple voltage, V_{dc} (multimeter in DC mode) = 3.63V
 RMS or AC value of the ripple voltage, V_{r-rms} (multimeter in AC mode) = 0.091V
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.0251$


Theoretical Calculation (Homework)



1. **FW Rectifier without Capacitor:**
 Peak output voltage, V_p (see the experimental observation) = 4.0V
 Peak input voltage, $V_m = 4.96\text{V}$
 Diode voltage, $V_{D0} = 0.7\text{V}$
 DC output voltage of the rectifier, $V_{dc} = \frac{2V_m}{\pi} - 2V_{D0} = 1.758\text{V}$
 RMS or AC output voltage, $V_{r-rms} = \frac{V_p}{\sqrt{2}} = 2.828\text{V}$
2. **FW Rectifier with $1\mu\text{F}$ Capacitor:**
 Peak output voltage, V_p (see the experimental observation) = 3.96V
 Peak to peak ripple voltage, $V_{r(p-p)}$ (see the experimental observation) = 1.12V
 DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.40\text{V}$
 RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.323\text{V}$
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.0950$
3. **FW Rectifier with $4.7\mu\text{F}$ Capacitor:**
 Peak output voltage, V_p (see the experimental observation) = 3.80V
 Peak to peak ripple voltage, V_p (see the experimental observation) = 0.36V
 DC value of the ripple voltage, $V_{dc} = V_p - \frac{V_{r(p-p)}}{2} = 3.62\text{V}$
 RMS value of the ripple voltage, $V_{r-rms} = \frac{V_{r(p-p)}}{2\sqrt{3}} = 0.104\text{V}$
 Ripple factor, $r = V_{r-rms}/V_{dc} = 0.0287$


10-10-22


7.



Schematic Diagram for HW:

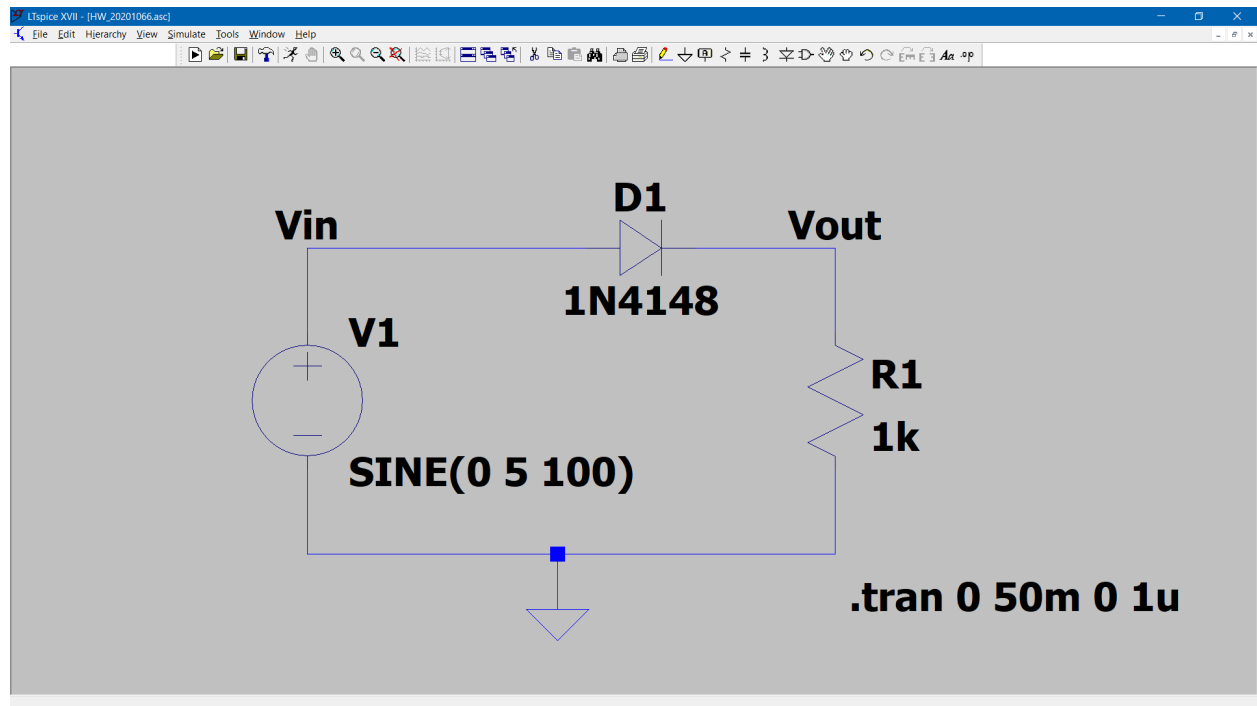

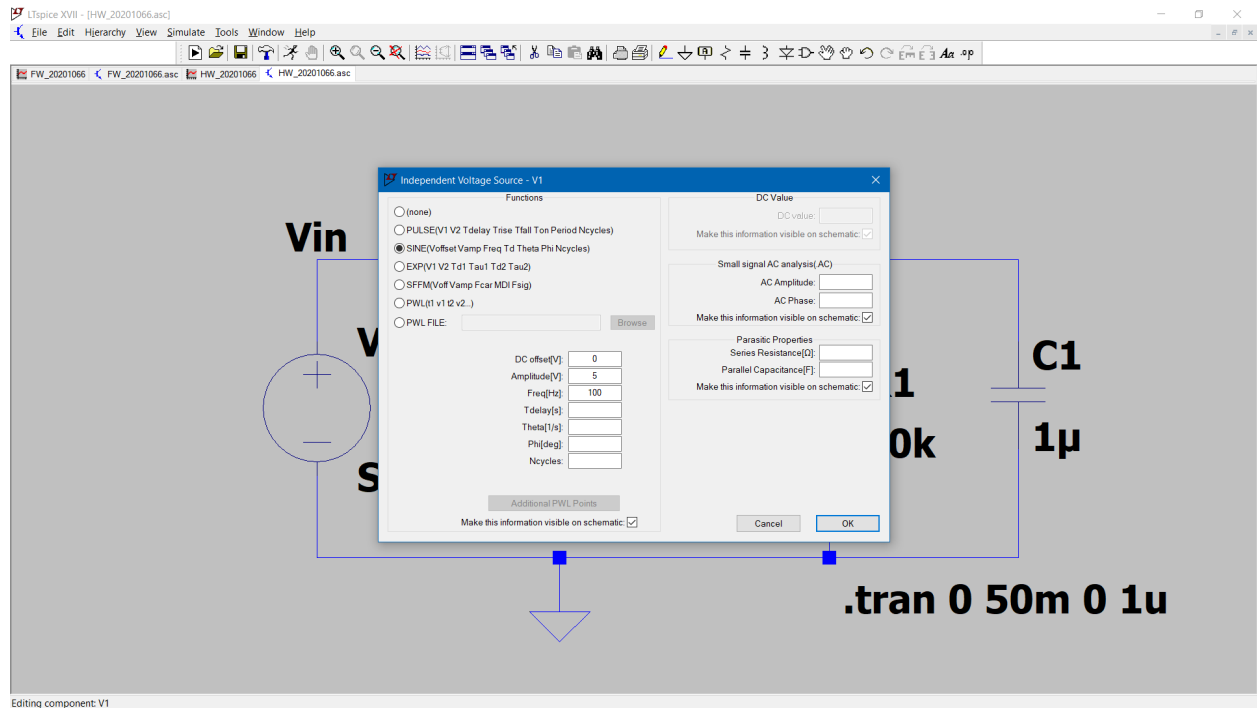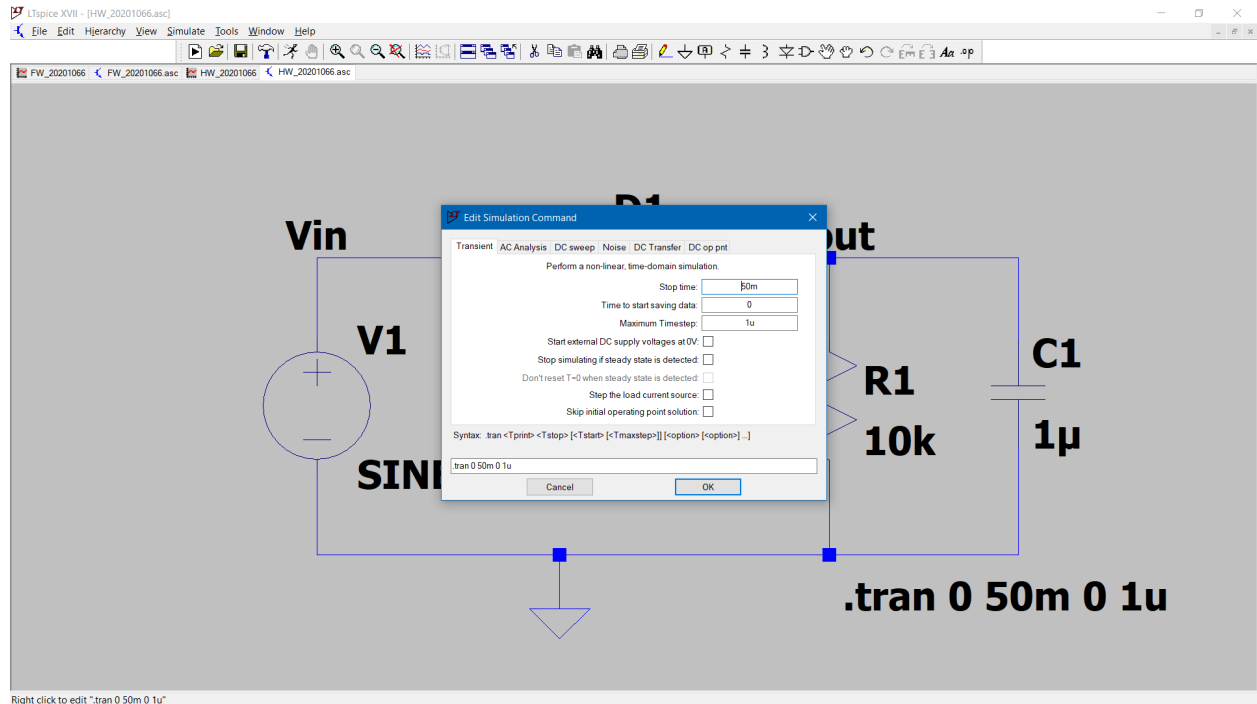

Schematic Diagram for FW:

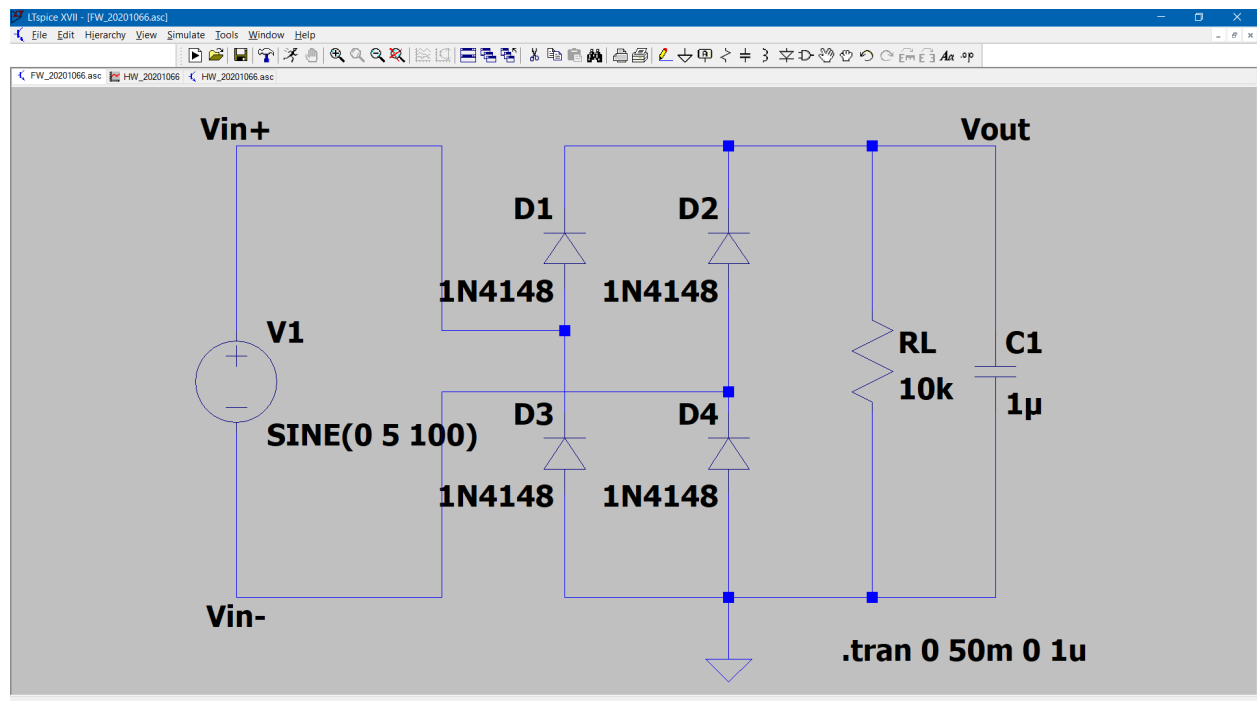

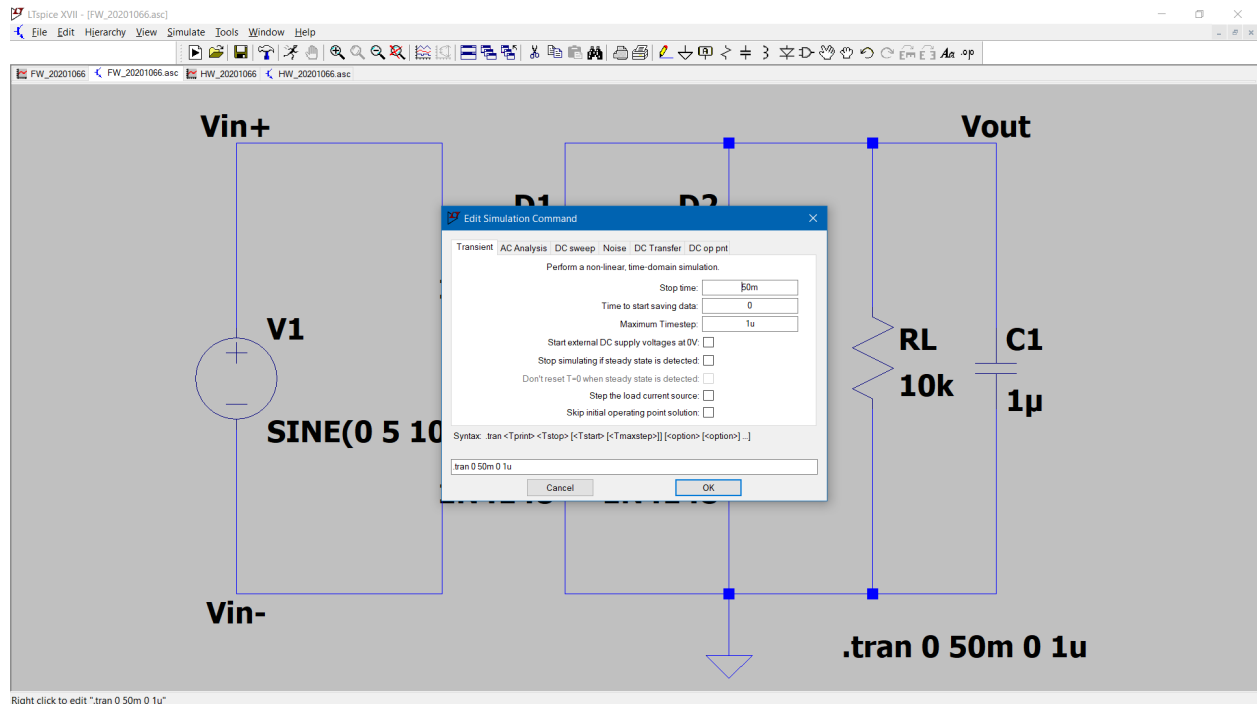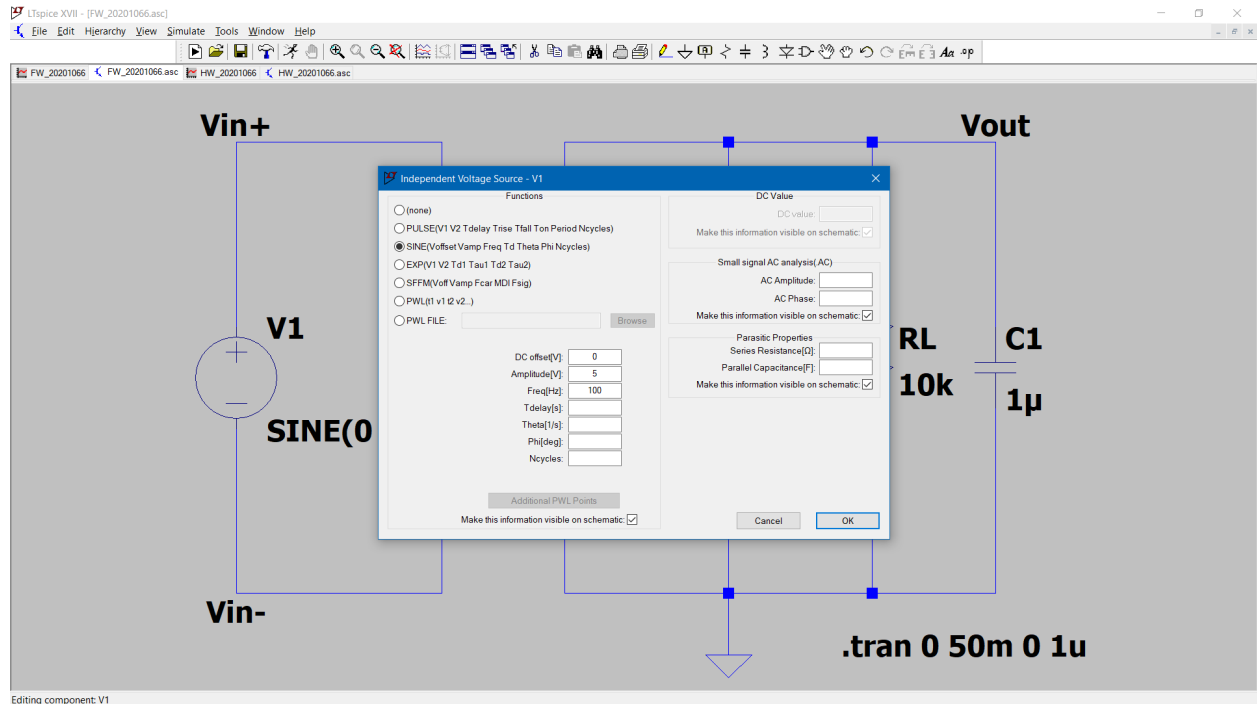

8. Discussion

The 4.7μF capacitor acts as a better filter as ripple voltage is lower and DC voltage is higher. Ripple factor is also very low.

The Full-Wave Rectifier is better than the Half-Wave Rectifier because the average output voltage is higher in a Full-Wave Rectifier, there is less ripple voltage produced in the Full-Wave Rectifier when compared to the Half-Wave Rectifier.

Both channels were not used simultaneously because an oscilloscope has ground inputs inside, and connecting both channels directly would short out some parts of the rectifier bridge.

Challenges faced during the experiment was primarily arranging the circuit on the breadboard properly for the FW Rectifier and calibrating the oscilloscope to generate the correct waveform for the voltages,