

Assignment 2

CSE251

Fall 22

Name : Shihab Muhtasim


sec : 13

ID : 21301610

Ans to or 1

(i)

Assuming D_1 as OFF and D_2 as ON :

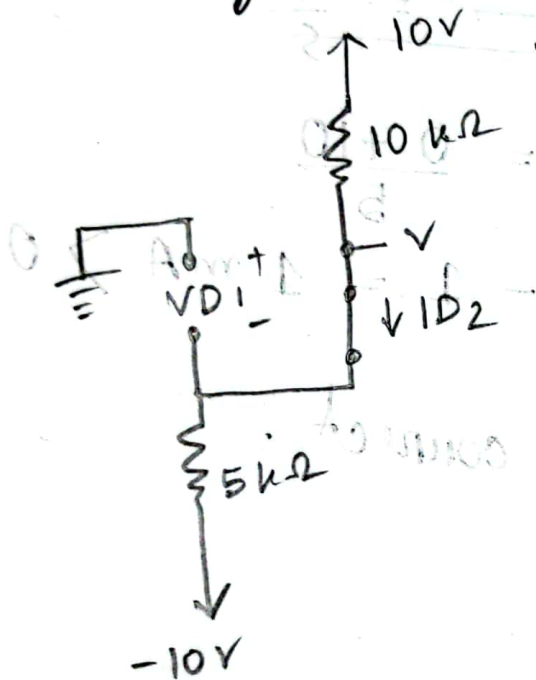

Here, $I_{D2} = \frac{10 - (-10)}{10 + 5} \text{ mA}$

$= 1.33 \text{ mA}$ which is greater than zero.

Assump is correct.

Again,

Nodal at V,

$$\frac{V - 10}{10} + \frac{V + 10}{5} = 0$$

$$\Rightarrow V - 10 + 2V + 20 = 0$$


$$\Rightarrow V = -\frac{10}{3}$$

$$\therefore V_{D1} = 0 - \left(-\frac{10}{3}\right)$$

$$= \frac{10}{3} \neq 0$$

This assumption is wrong.

Assuming Both D_1 and D_2 are ON:

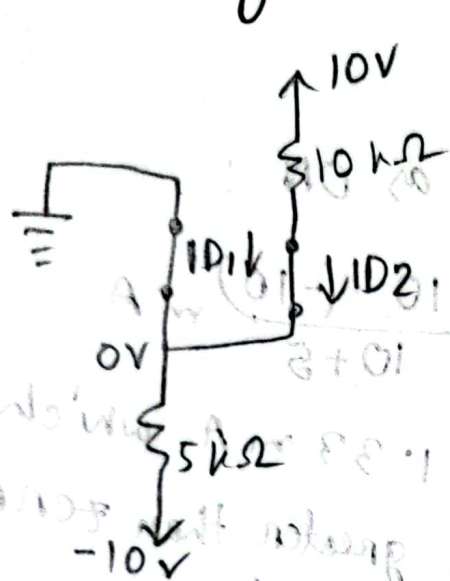

Here, $I_{D2} = \frac{10 - 0}{10} = 1\text{mA} > 0$

$I_{D1} = \frac{0 - (-10)}{5} = \frac{10}{5}$

KCL:

$I_{D1} + I_{D2} = \frac{0 + 10}{5}$


$\Rightarrow I_{D1} = 2 - 1 = 1\text{mA} > 0$

\therefore Our both assumptions are correct.

(ii)

Given, $V_{D0} = 0.7\text{V}$

Assuming both D_1 and D_2 are ON.

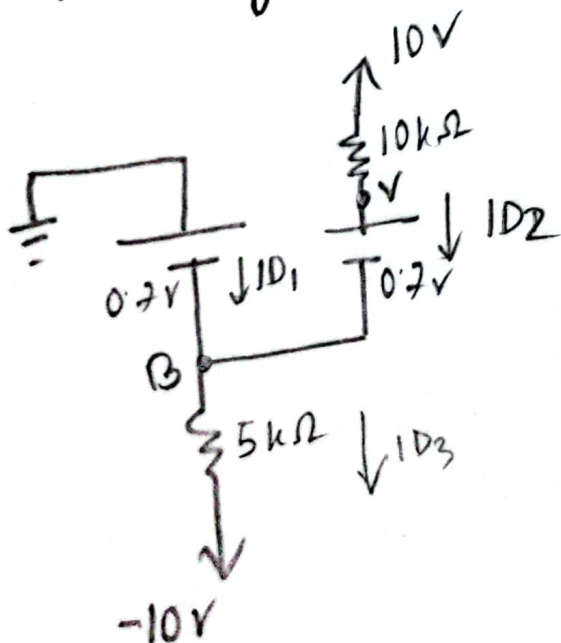

① At D_2 : $0.7 = V - B$

② At D_1 : $0.7 = 0 - B$

$\Rightarrow B = -0.7$

Supernode KCL:

$\frac{V - 10}{5} = \frac{V - 0.7}{10}$ Now,

From ① $V = 0.7 + B$

$\Rightarrow V = 0$

Now, $I_{D2} = \frac{10 - 0}{10} = 1 \text{ mA} > 0$


KCL: $I_{D1} + I_{D2} = \frac{0 + 10}{5} I_{D3}$

$\Rightarrow I_{D1} = I_{D3} - I_{D2}$
 $= \frac{-0.7 + 10}{5} - 1$

$= 1.86 - 1 = 0.86 \text{ mA} > 0$

\therefore Both assumptions are correct.

Assuming both ON:

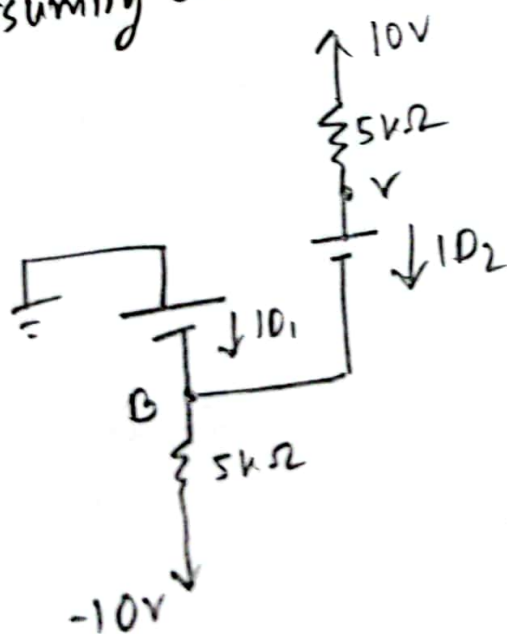

(iii)

At $D1$,
 $0.7 = 0 - B$

$\therefore B = -0.7$

At $D2$,
 $0.7 = V - B$

$\therefore V = 0$

Now, $I_{D2} = \frac{10}{5} = 2 \text{ mA} > 0$

Again,


$I_{D1} + I_{D2} = I_{D3}$

$\Rightarrow I_{D1} = \frac{-0.7 + 10}{5} - 2$

$= -0.14 < 0$

\therefore This assumption is wrong.

Assuming D_1 OFF and D_2 ON:

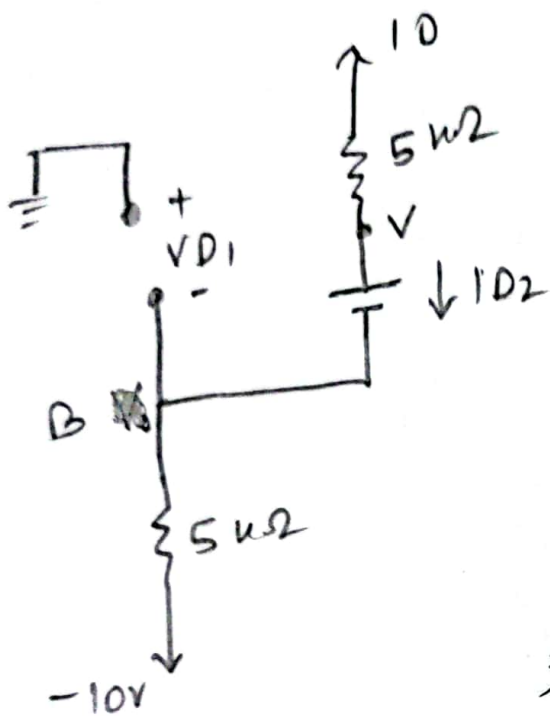

Here,

$$0.7 = V - B$$

$$B = V - 0.7$$

At V ,

$$\frac{V - 10}{5} + \frac{B + 10}{5} = 0$$

$$\Rightarrow V - 10 + V - 0.7 + 10 = 0$$

$$\Rightarrow V = 0.35 \text{ V}$$

$$B = -0.35 \text{ V}$$

$$\text{Now, } I_{D2} = \frac{10 - 0.35}{5} = 1.93 \text{ mA} > 0$$

$$V_{D1} = 0 - B = 0 - (-0.35) = 0.35 \text{ V} < 0.7$$

Both assumptions are correct.

[correct assumption]



Ans to or 2

10! 21301610

(a)

$$V_1 = (5 + 0 \times 10^{-2}) = 5V$$

Assuming D_1, D_2 are ON!

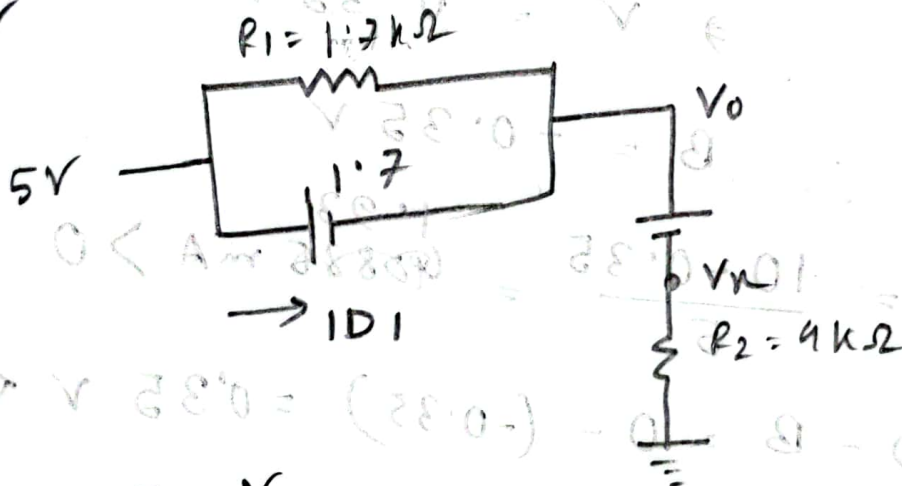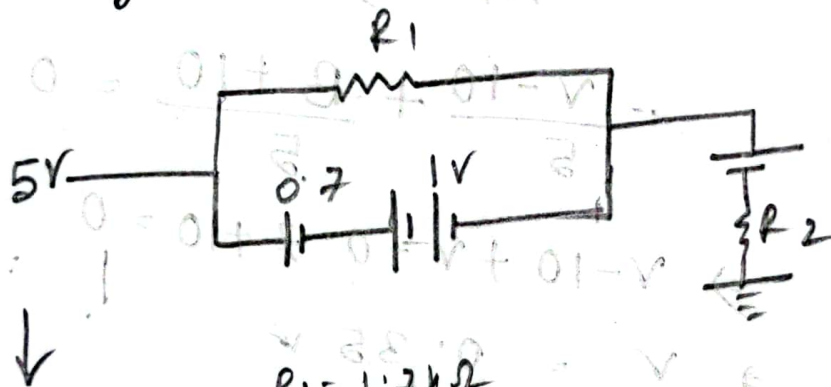

$$\textcircled{1} \quad 1.7 = 5 - V_0$$

$$V_0 = 5 - 1.7 = 3.3V$$

$$\textcircled{2} \quad I_{R1} = \frac{5 - 3.3}{1.7} = 1mA$$

$$\textcircled{3} \quad 0.7 = V_0 - V_R$$

$$\therefore V_R = 3.3 - 0.7 = 2.6V$$

$$\textcircled{4} \quad I_{D2} = \frac{2.6 - 0}{4} = 0.65mA > 0$$


[correct assumption]

$$\textcircled{5} \text{ KCL: } I_{D1} + I_{R1} = I_{D2}$$

$$\Rightarrow I_{D1} = 0.65 - 1 = -0.35 \text{ mA} \not> 0$$

\therefore This assumption is wrong.

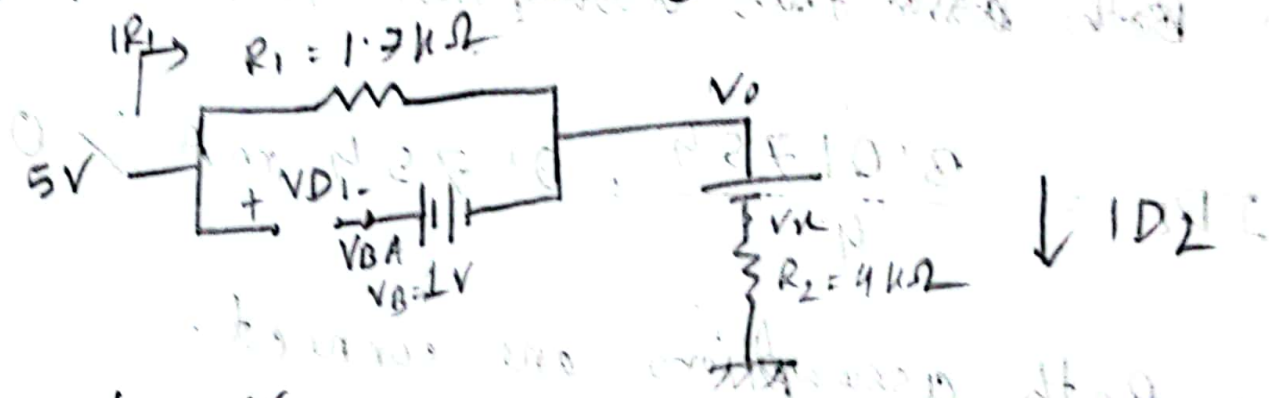Second Assumption: Assuming D_1 OFF, D_2 ON:



$$\textcircled{1} 1 = V_{BA} - V_0$$

$$\textcircled{2} 0.7 = V_0 - V_K$$

$$\textcircled{3} V_{D1} = 5 - V_{BA}$$

$$\textcircled{4} \text{ KCL: } I_{R1} = I_{D2}$$

$$\Rightarrow \frac{5 - V_0}{1.7} = \frac{V_K - 0}{4}$$

$$\Rightarrow 20 - 4V_0 = 1.7V_K$$

$$\Rightarrow 20 - 4V_0 = 1.7(V_0 - 0.7) \quad [\text{From eqn 2}]$$

$$\Rightarrow -5.7V_0 = -21.19$$

$$\Rightarrow V_0 = 3.7175 \text{ V}$$

$$\Rightarrow V_K = 3.01754 \text{ V}$$

$$\therefore V_K = 3.01754 \text{ V} \quad \therefore I_{R1} = \frac{5 - 3.7175}{1.7} = 0.754 \text{ mA}$$

from eq 1,

$$V_{BA} = 1 + V_0 = 1 + 3.717 = 4.7175 \text{ V}$$

from 3,

$$V_{D1} = 5 - 4.7175 = 0.2825 < 0.7$$

~~Both~~ This assumption is correct.


$$I_{D2} = \frac{3.01754}{4} = 0.754 \text{ mA} > 0$$


Both assumptions are correct.

Ans to or 3

Part a

(ii)

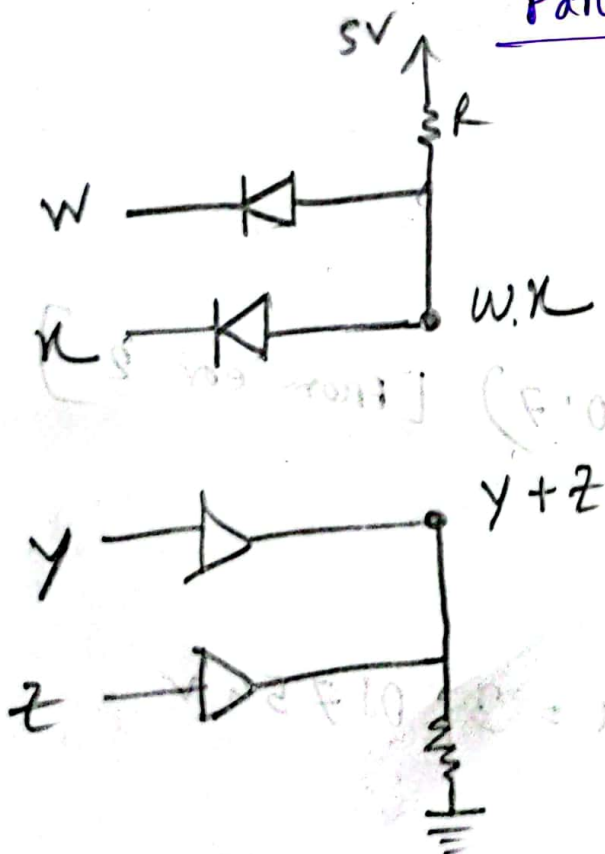

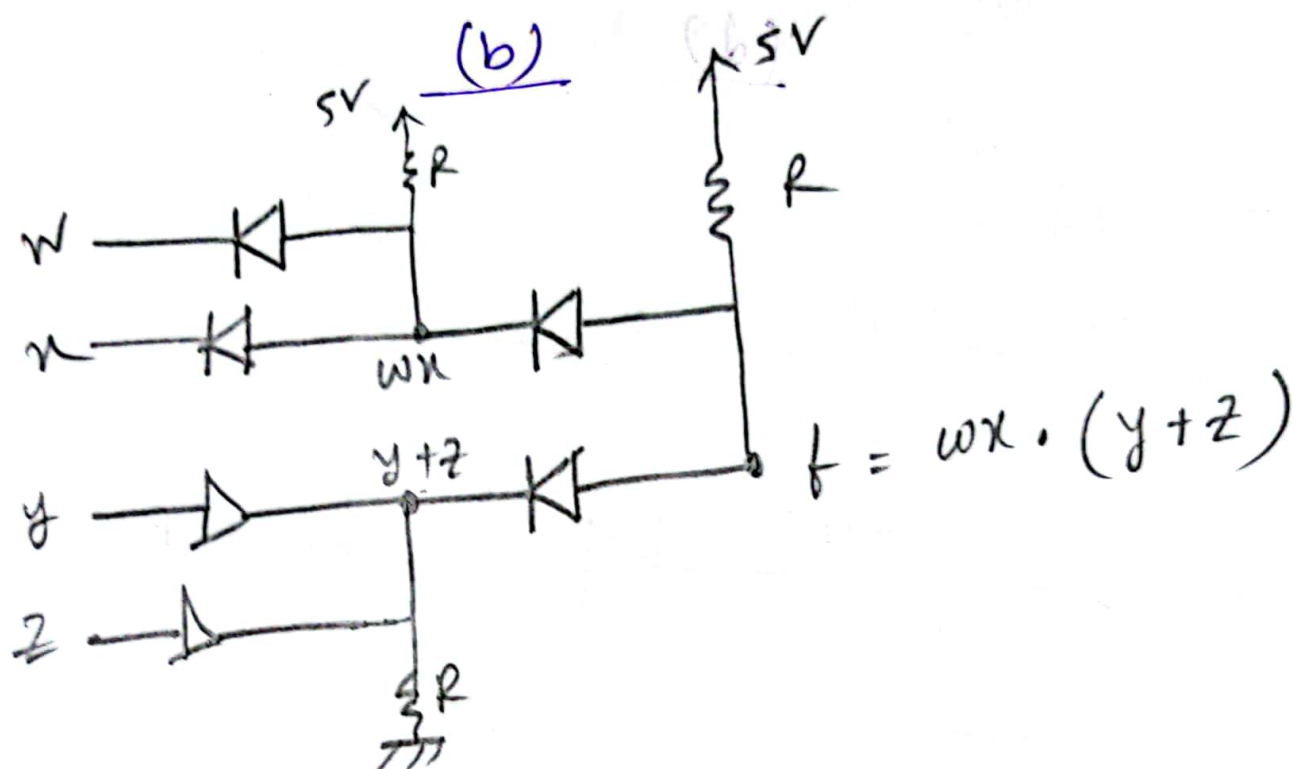

Part b

© Boolean signals F, R, G, N

Condition: ① $\rightarrow F$

② $\rightarrow R$

③ $\rightarrow G$

④ $\rightarrow N$


Both 1, 2 has to be satisfied.

\therefore So we take the MIN / AND operation. So if any is not satisfied it won't work. (F, R)

Again, Either 3 or 4 has to be satisfied

So we take $(G+N)$

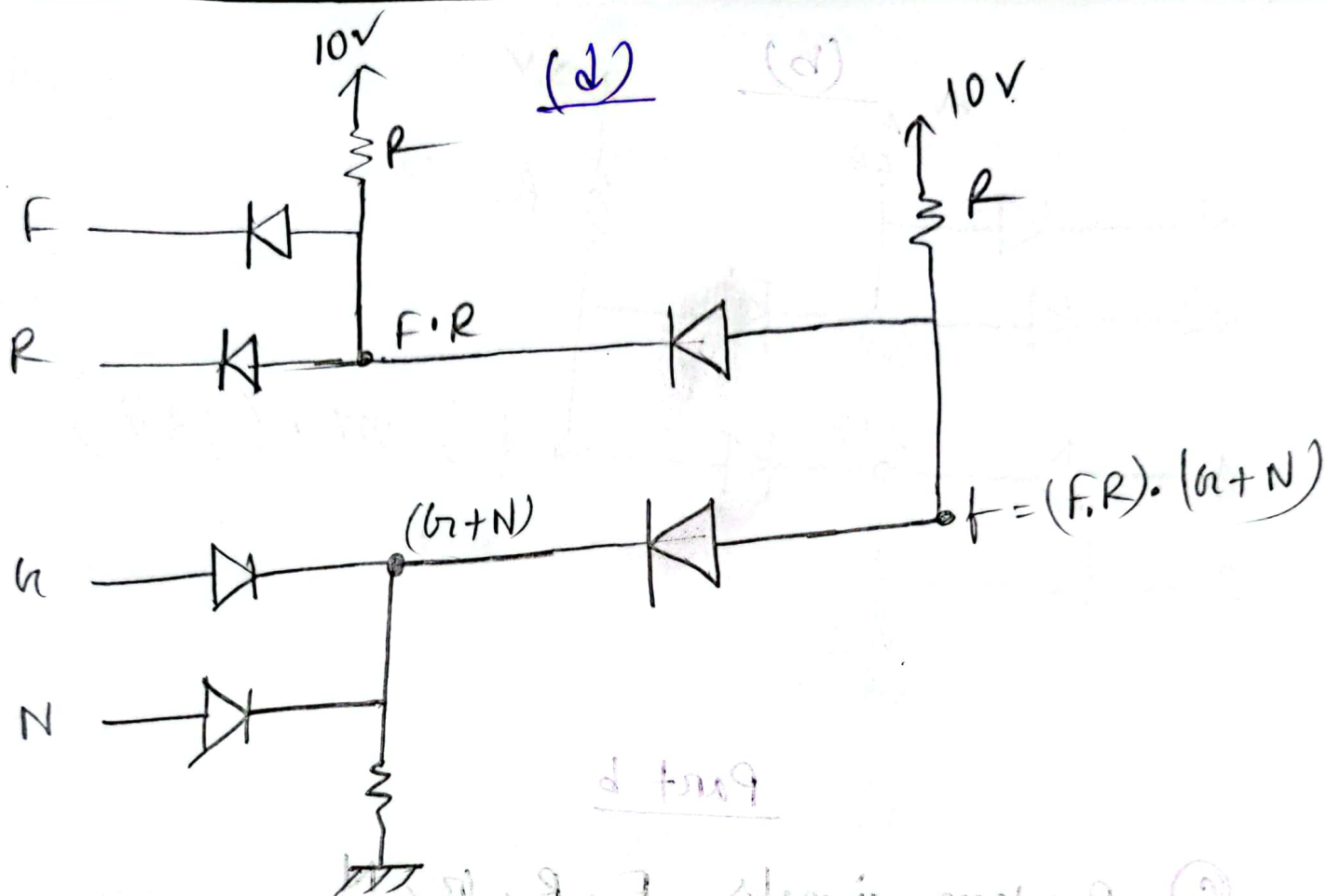
\therefore Final output = $(F \cdot R) \cdot (G+N)$



Ans to or 4

$$V_{D0} = 0.5 \text{ V}$$

Assuming D_1 OFF and D_2 ON :

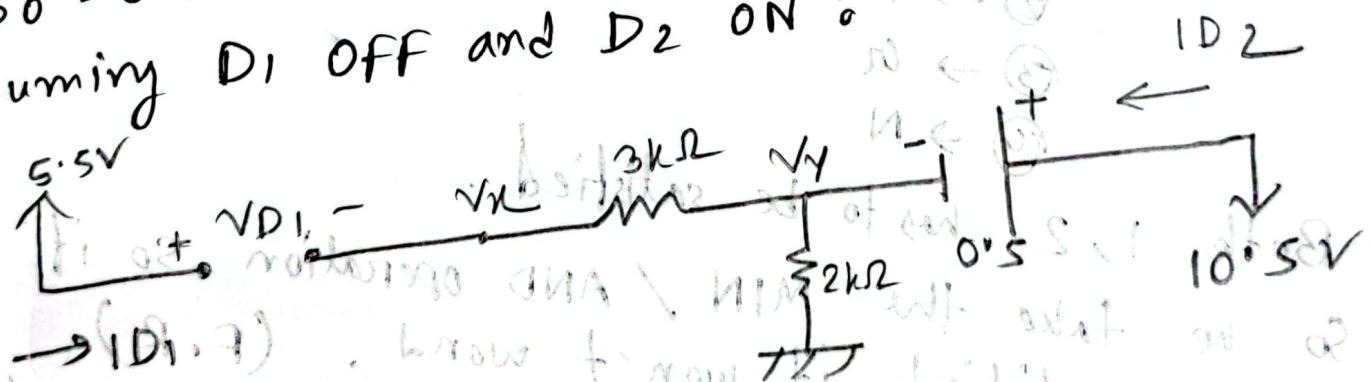

$$\textcircled{1} \quad 0.5 = 10.5 - V_{D1}$$

$$\therefore V_{D1} = 10$$

$$\textcircled{2} \quad I_{D2} = \frac{10}{2} = 5 \text{ A} > 0$$

[correct assumption]

$$\textcircled{3} \quad I_{D1} = 0 \quad [\text{short circuit}]$$

$$\textcircled{4} \quad \frac{V_x - V_y}{3} = 0$$

$$\Rightarrow V_x = V_y = 10$$

$$\textcircled{5} \quad V_{D1} = 5.5 - 10 = -4.5 \text{ V} < 0.7$$

\therefore Both assumptions correct.