

Assignment 2



BRAC University

Semester: Fall 2022

Course No: CSE251

Course Title: Electronic Devices and Circuits

Full Marks: 100

Deadline: **2 November 2022**


1. Find the values of I and V in the circuit shown below for the following cases:

(i) Assuming the diodes to be ideal.

(ii) Assuming the diodes to be non-ideal *[Hints: use constant voltage drop model with $V_{D0}=0.7\text{ V}$].*

(iii) Assuming the diodes to be non-ideal and use $5\text{ k}\Omega$ instead of $10\text{ k}\Omega$ *[Hints: use constant voltage drop model with $V_{D0}=0.7\text{ V}$].*


[10×3=30]

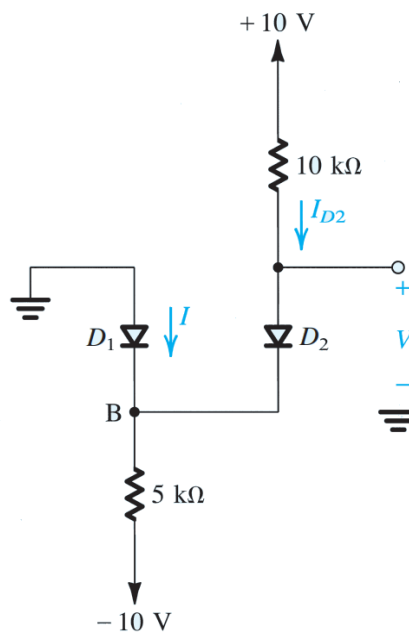

2. Consider the circuit shown in the following Figure. The cut-in voltage of each diode is $V_{D0} = 0.7$ V.

(a) Let $v_1 = (5 + \text{last digit of your ID} \times 10^{-2})$ V. Assume both diodes are conducting. Is this a correct assumption? Why or why not? Determine I_{R1} , I_{D1} , I_{D2} , and v_O (**if necessary, modify the assumption and calculate the values for the correct one**).

[20]

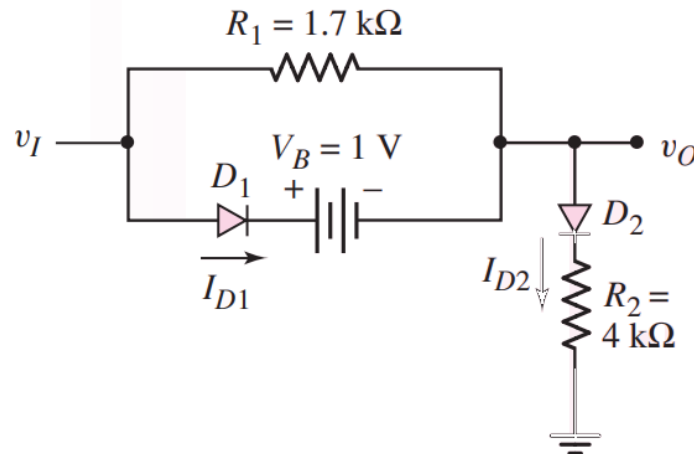

3. Analyze the circuit shown below. Assume all the diodes to be ideal.

Part a:

(ii) Assuming w , x , y , z are boolean variables, **analyze** the circuit to find an expression of ckt-1 (the dotted ... rectangle) in terms of w and x , and an expression of ckt-2 (the dashed - - - rectangle) in terms of y and z .

[5+5]

(b) **Analyze** the circuit again to find an expression of f in terms of w , x , y , z . Use results from (a).

[5]


Part b: Jawad has created a new ride-sharing app: **Juber**. When you request a Juber ride, Juber's algorithm generates 4 signals to determine whether it will be forwarded to a rider. (1) Signal F determines if the rider is free. (2) Signal R determines if the rider is within close proximity. (3) Signal G determines if the rider has a good rating. (4) Signal N determines if the rider is new. If both conditions 1 and 2 are satisfied, and either condition 3 or condition 4 are satisfied, the request will be connected.

(c) Deduce the logic function using boolean signals F , R , G , and N to implement Juber's algorithm.

[10]

(d) Design a circuit using ideal diode logic gates to implement this function.

[15]

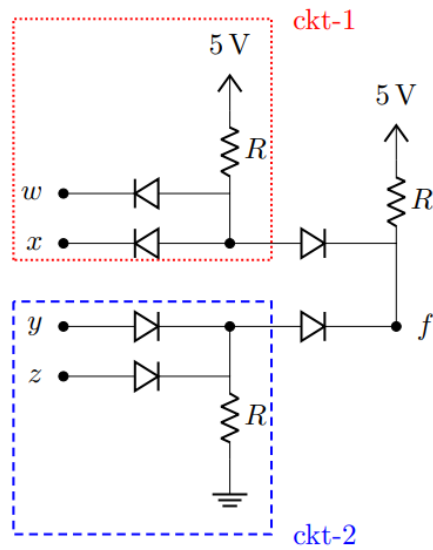

4. Analyze the circuit to find the values of I_{D1} , I_{D2} , v_x , and v_y [$V_{D0} = 0.5 \text{ V}$]. You must **validate** your assumptions.

[10]

