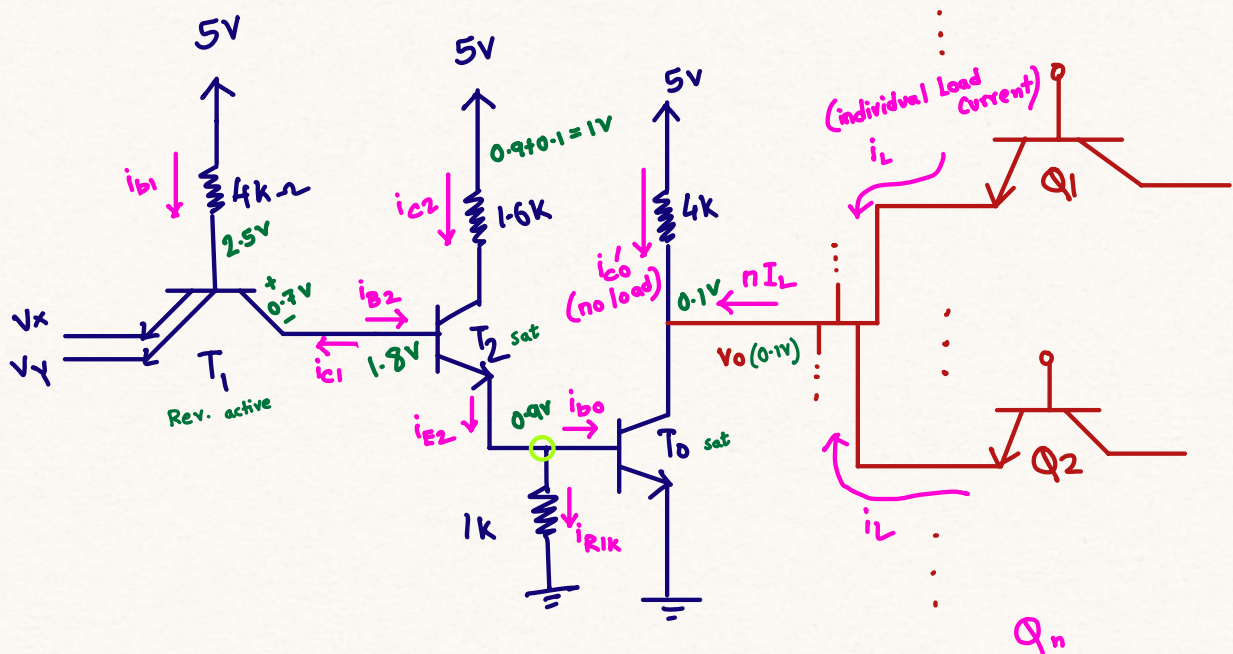


Q. Find maximum fanout for this ckt.

Case ①: output of driver low ( $V_o = 0.1$ )

Given:  $V_{CE(sat)} = 0.1 \text{ V}$        $\beta_R = 0.1$   
 $\beta_{FWD} = 25$        $V_{OH} = 3.4 \text{ V}$

Case I: output low



main eqn. :  $I_{C_{o_{max}}} = I_{C_o'} + n_{max} I_L$  — ①

②  $I_{C_{o_{max}}} = \beta_{FWD} \cdot I_{b_o} ; @ sat$

③  $I_{b_o} = I_{E2} - I_{R1k}$

④  $I_{R1k} = \frac{0.9 - 0}{1k}$

⑤  $I_{E2} = I_{B2} + I_{C2}$

⑥  $I_{C2} = \frac{5 - 1}{1.6k}$


$I_{b1} = \frac{5 - 2.5}{4k}$  ⑦

$I_{C1} = \beta_{REV} \cdot I$  ⑧

$|I_{B2}| = |I_{C1}|$  ⑨

## Load condition in this case ...

$Q_1$  load is at saturation

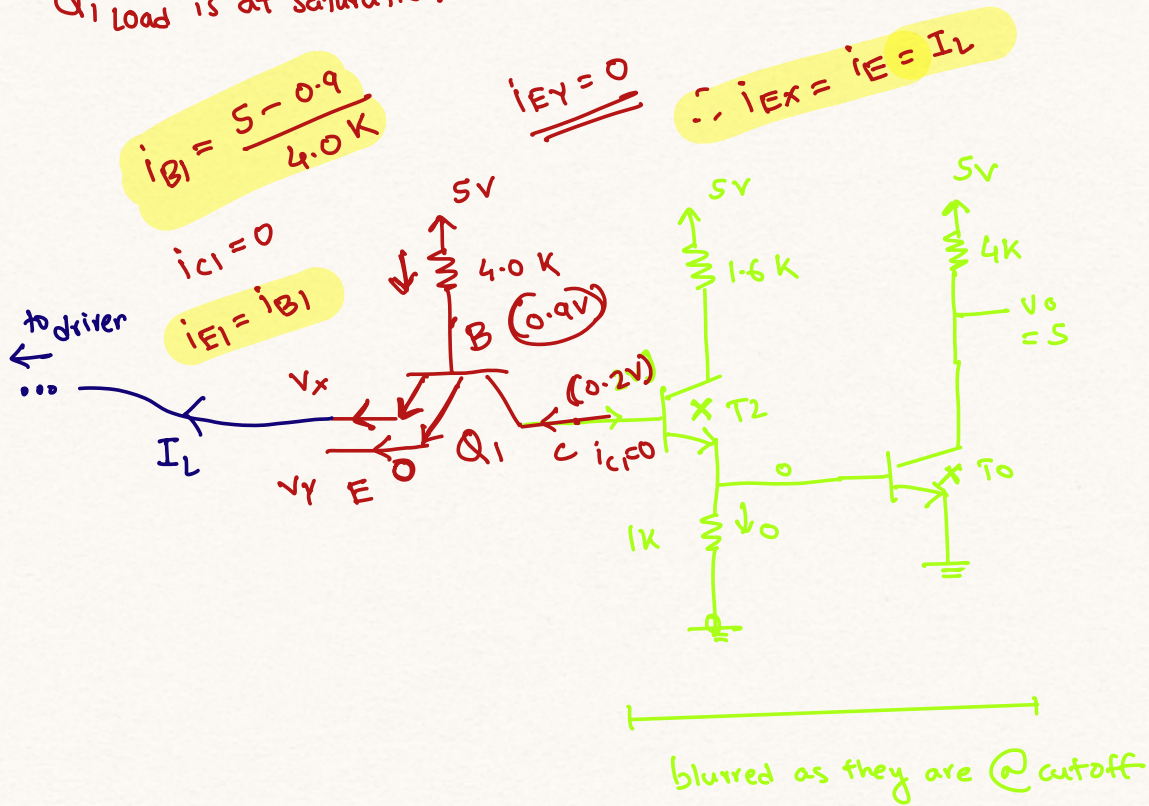



$T_0, T_2$  sat ;  $T_1$  R.A. (driver ckt)

$Q_1 \rightarrow$  saturation (Load) as output low

$$i_c' = \text{no load current} = \frac{5-0.1}{4k}$$


$$i_L = \text{individual load current} = \frac{5-0.9}{4k} \quad \text{see load diagram}$$

$$i_{B0} = \text{base current of } T_0 = 2.5725 \text{ mA}$$


$$i_{c, \max} = \beta_{Fwd} \times i_{B0} = i_L \times n_{\max} + i_c'$$

$$\max = \lfloor 61.35 \rfloor = 61$$

Case 02 : The output of driver is high

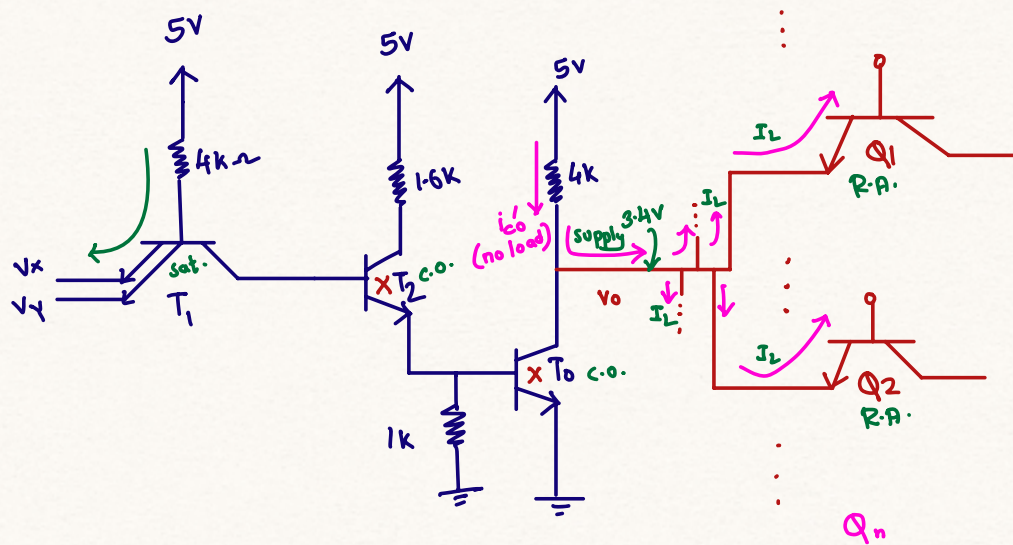

Load condition for this case

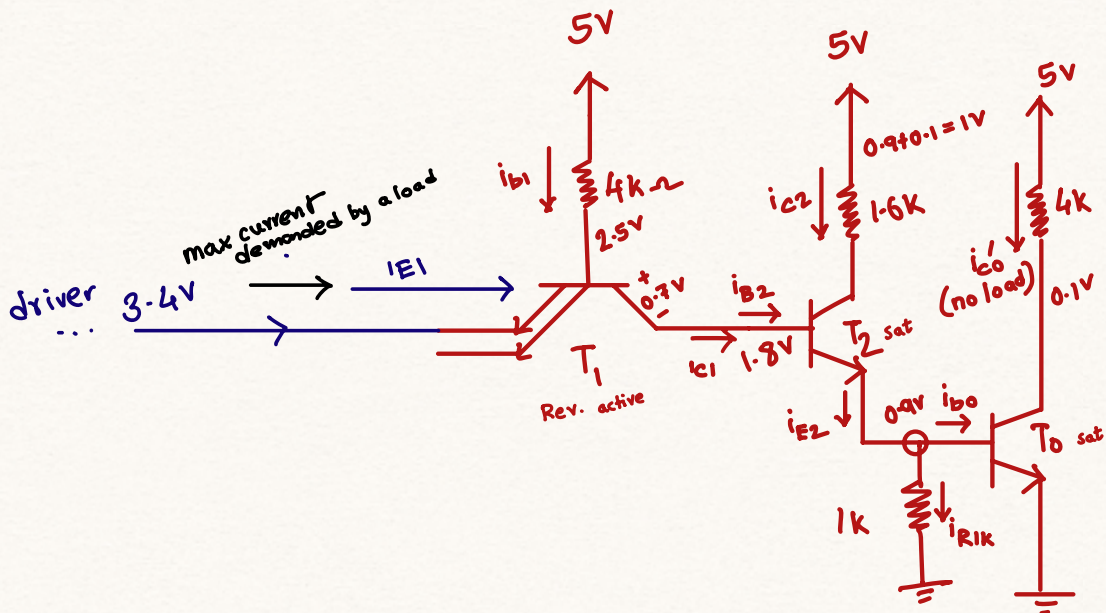



For Load

$$I_{E1} = \beta_{Rev} \cdot I_{B1}$$

$$I_{B1} = \frac{5 - 2.5}{4k}$$

max current demanded by a load =  $I_{E1}$

For driver

$$\text{max supply current} = \frac{5 - 3.4}{4k}$$

$$\text{max Fanout} = \frac{\text{supply}}{\text{demand}} = \frac{0.4}{0.0675} = \lfloor 5.92 \rfloor = 5$$

$$\text{Finally max fanout} = \min(5, 61) = 5 //$$