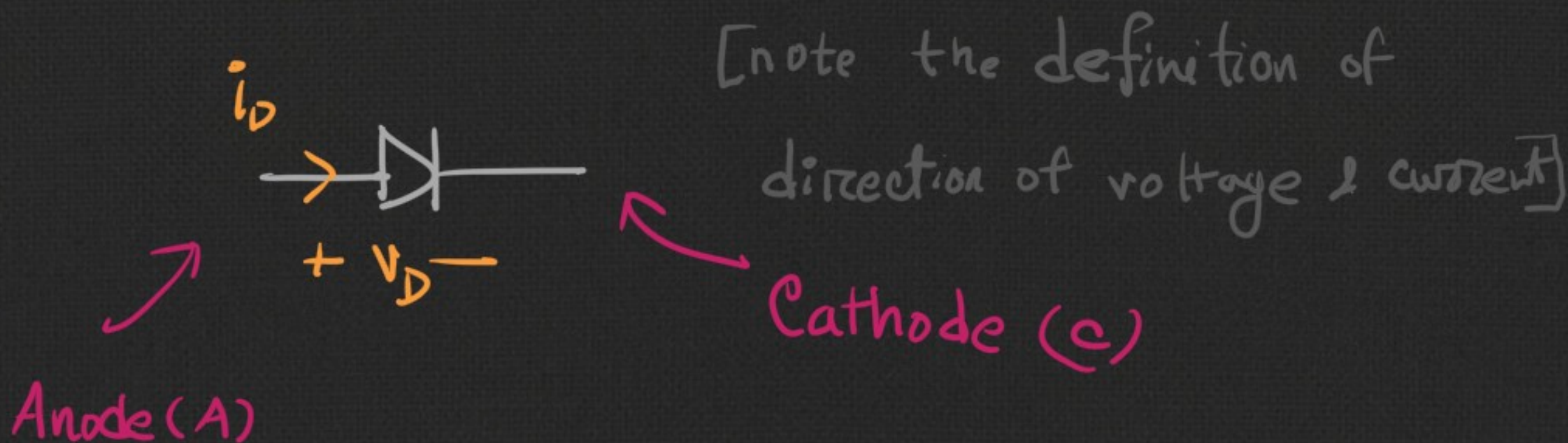


Diode



$$V_D = V_A - V_C$$

$$i_D = \text{from A to C}$$

* Diode is basically an electronic valve. It only allows current from A to C.

* So if current tries to flow from A to C [i.e. if $i_D > 0$], the device will act like a short circuit



Hence $V_D = 0$ in this condition. This is the FORWARD BIAS OR ON mode.


Side note

For any circuit


this means $V_1 = V_+ - V_-$
 $\Rightarrow V_1 = V_a - V_b$

$V_2 = V_+ - V_-$
 $\Rightarrow V_2 = V_b - V_a$

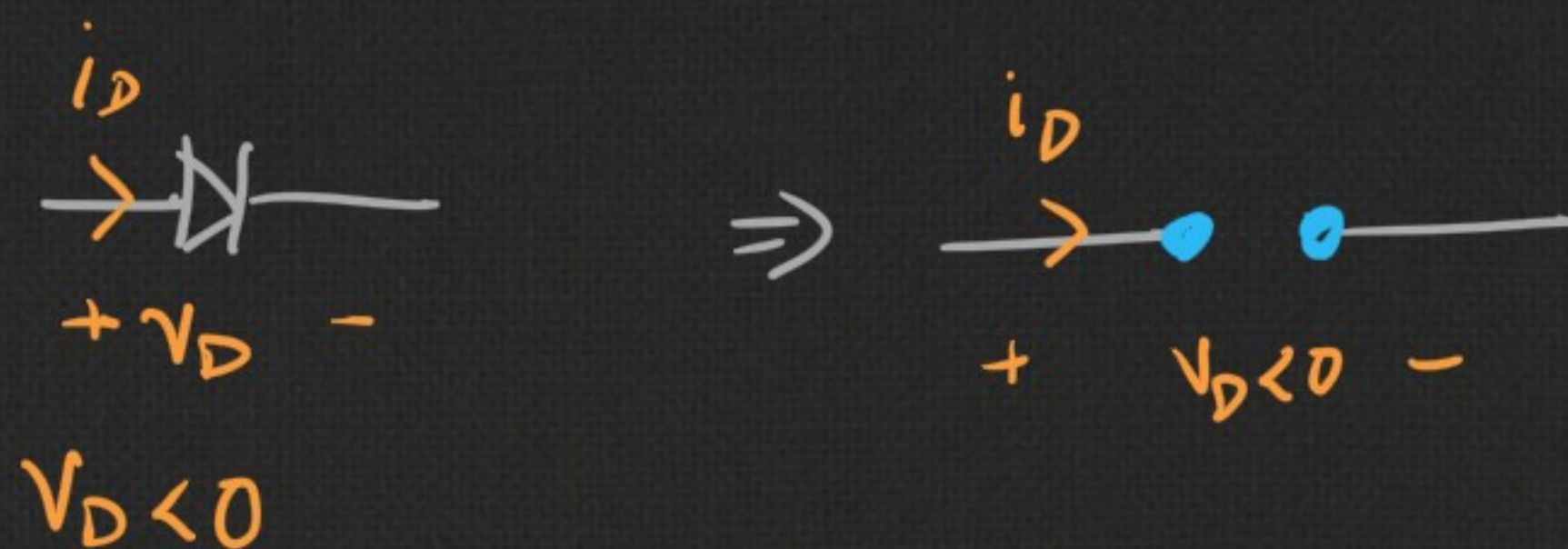
* On the other hand, if $V_D < 0$, the current will try to flow from C to A. But the diode won't allow such current, so it will act like an open circuit.



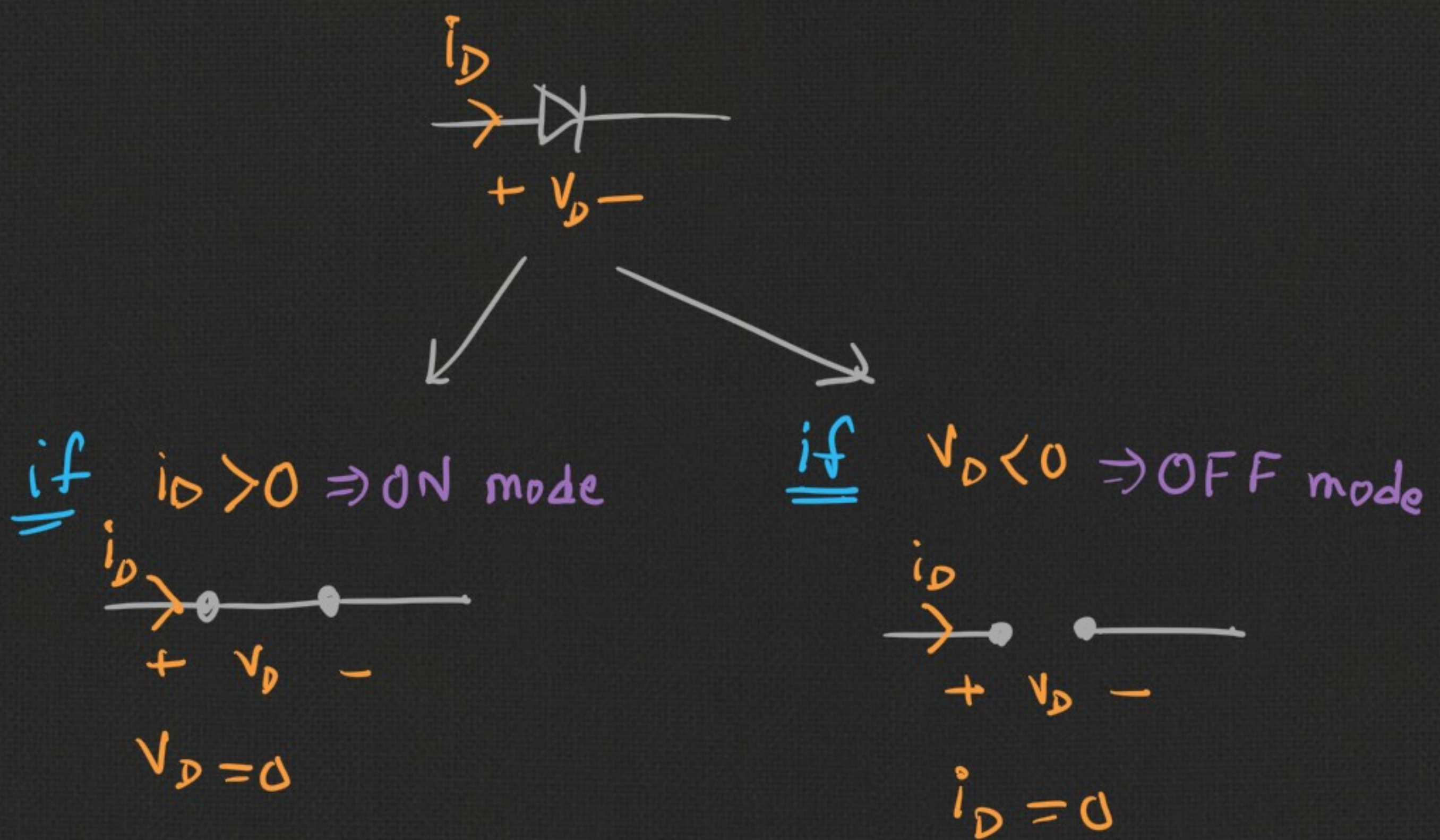
Hence $i_D = 0$ in this condition. This is called the REVERSE BIAS or OFF mode.




The corresponding IV curve:

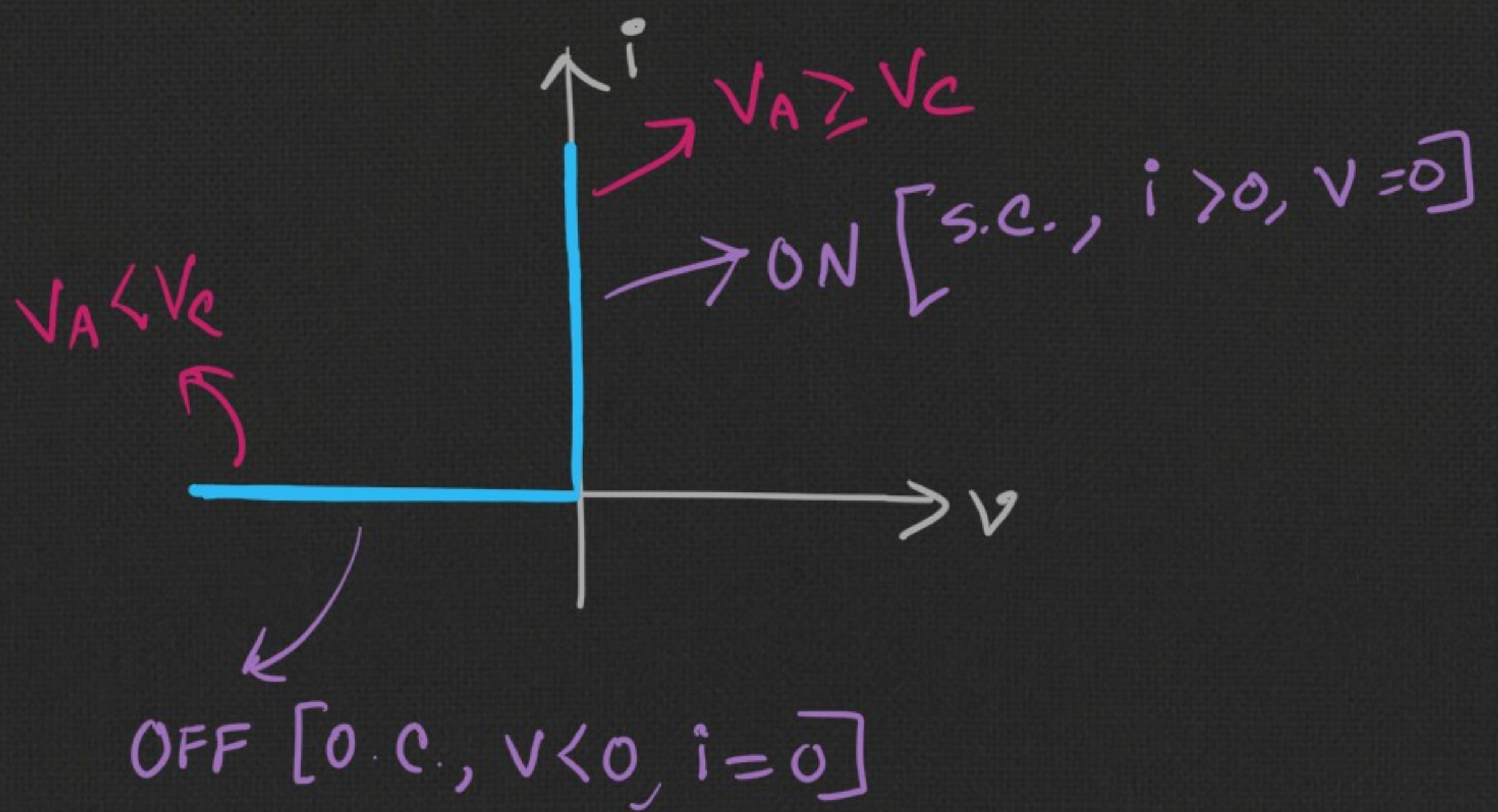

Circuit example [DC]

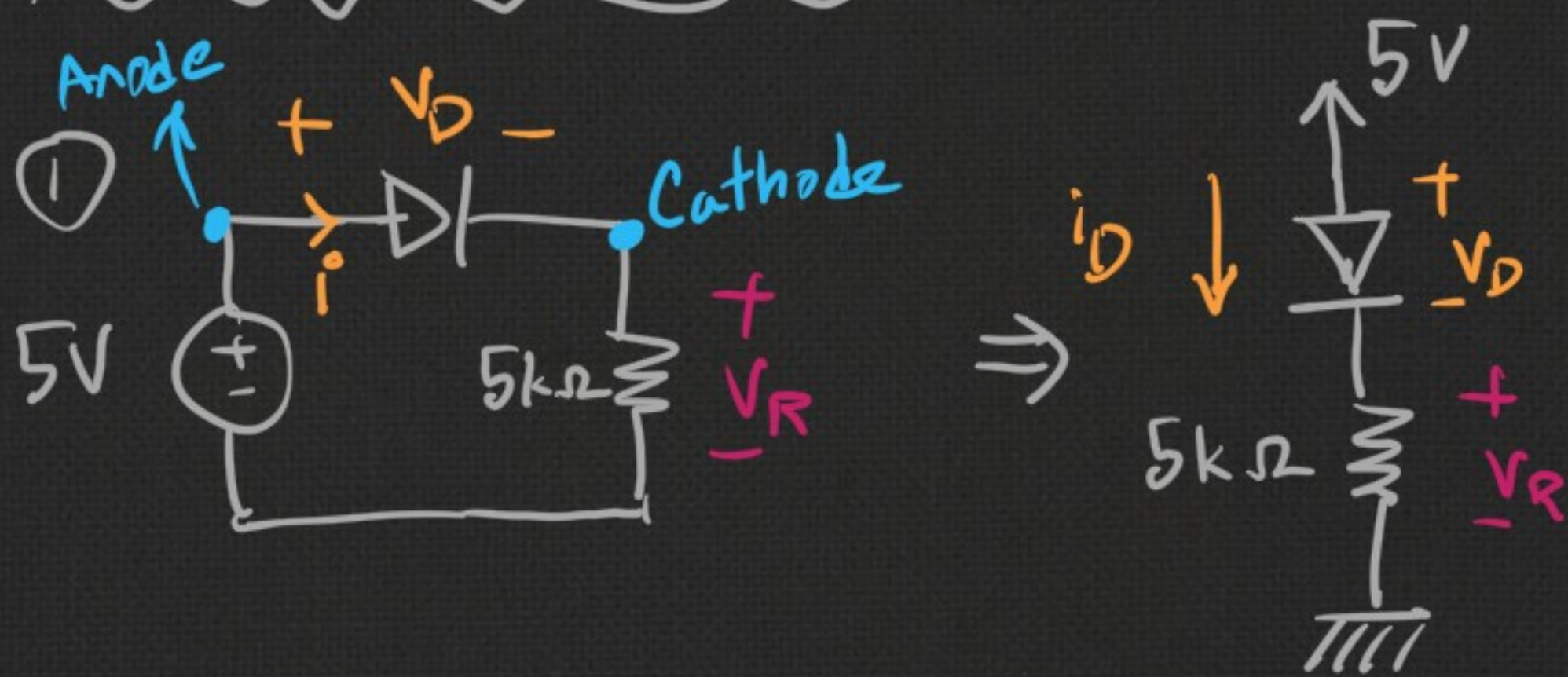

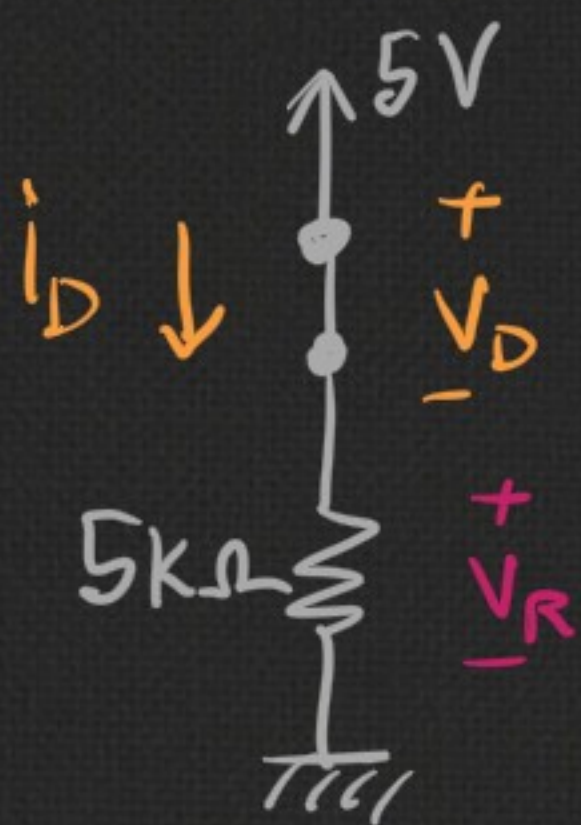Since $5V > 0V \Rightarrow$ current will try to flow from A to C $\Rightarrow i_D > 0 \Rightarrow$ Diode ON




$$v_D = 0 \text{ [short circuit]}$$


$$v_R = v_C - 0 = v_C = 5V$$

Potential of cathode \swarrow Because cathode is shorted to 5V
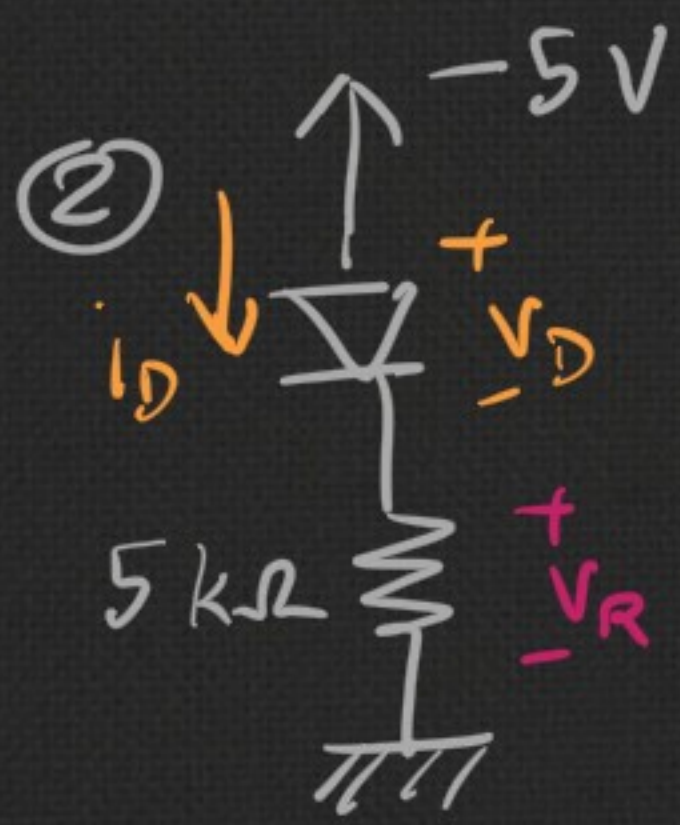
$$i_D = \frac{v_R}{R} = \frac{5V}{5k\Omega} = 1mA$$



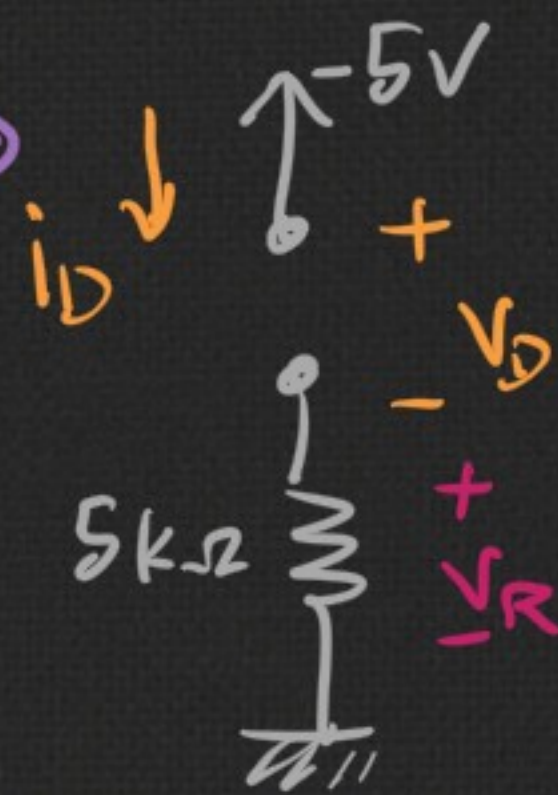Since $V_A < V_C \Rightarrow V_D < 0 \Rightarrow \text{OFF mode}$
 $\sim 0V$



$$i_D = 0 \text{ [open circuit]}$$


$$V_R = iR = 0 \times 5k = 0$$

[Remember this!!!]

if i through a R is 0, the voltage across two terminals will be equal

$$V_D = V_A - V_C = -5V - 0V = -5V$$


\uparrow source \nwarrow Resistance

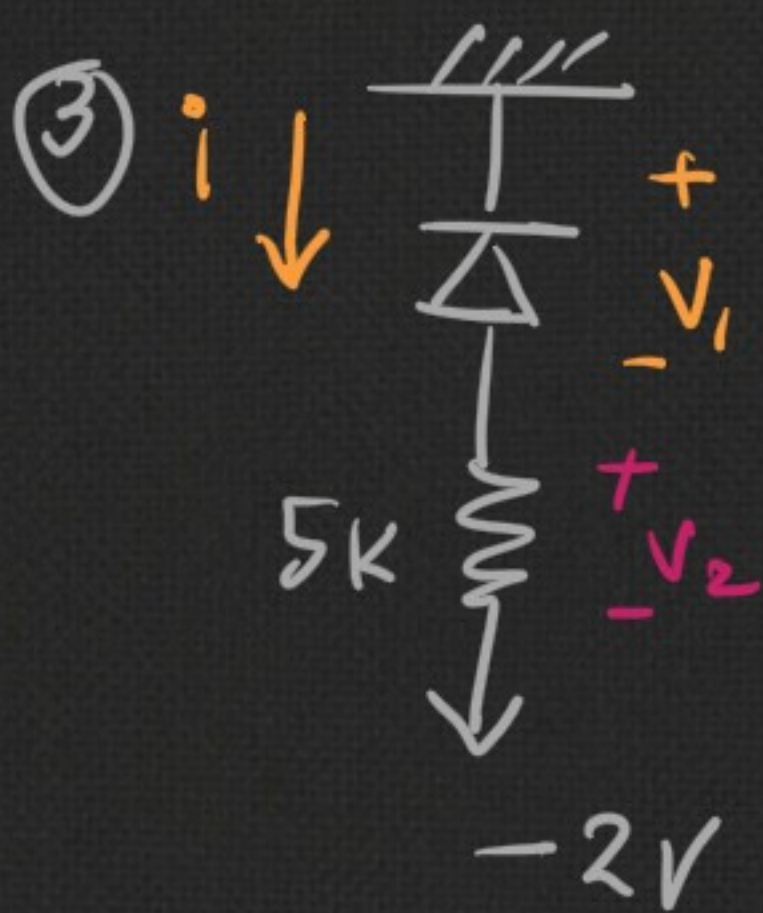

$$V_A = 0V \text{ [Connected to GND]}$$

$$V_C \sim -2V$$
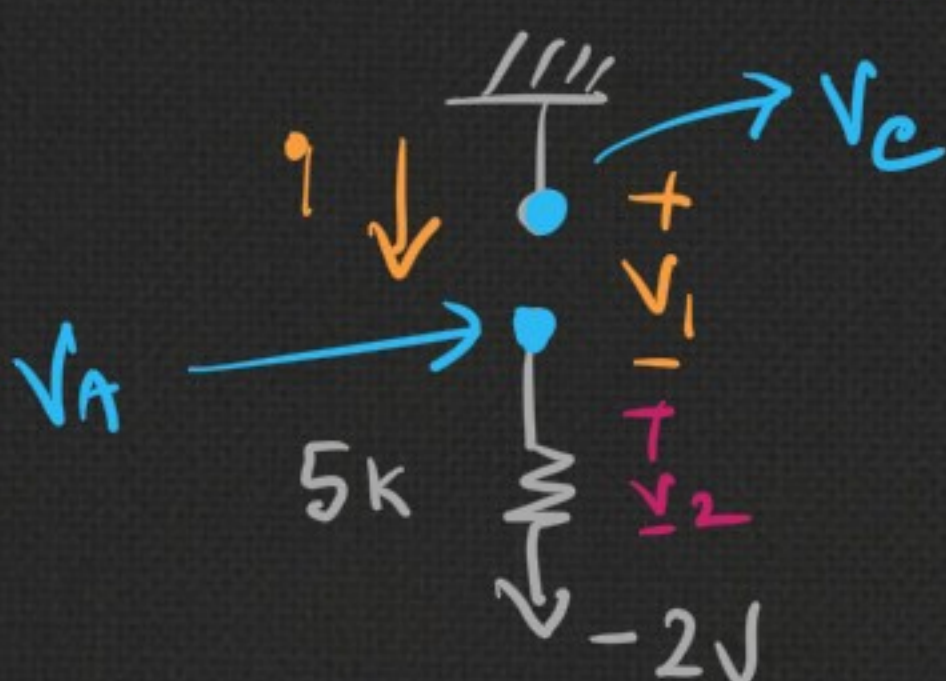
$$\text{So } V_D < 0 \Rightarrow \text{OFF mode}$$




$$i = 0 \text{ [open ckt]}$$

Because the R is "shorted"

$$V_2 = i \times R = 0 \times 5k = 0 \Rightarrow V_A = -2V$$



$$V_1 = V_C - V_A = 0 - (-2) = 2V$$

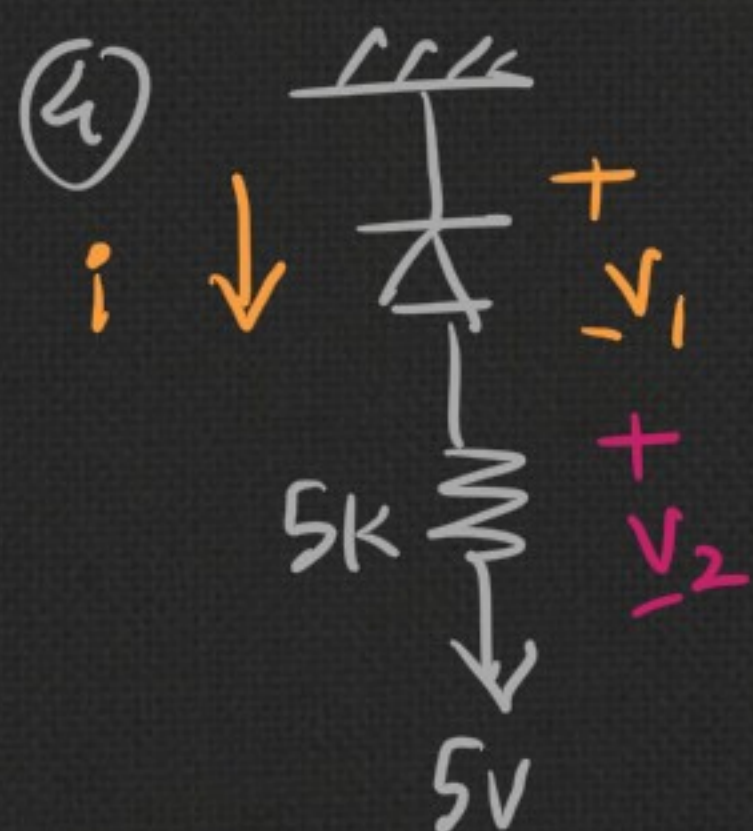


Find i , V_1 , V_2 . (Try yourself)

Simple Application: Half-wave Rectifiers

First Step to Convert from AC to DC.

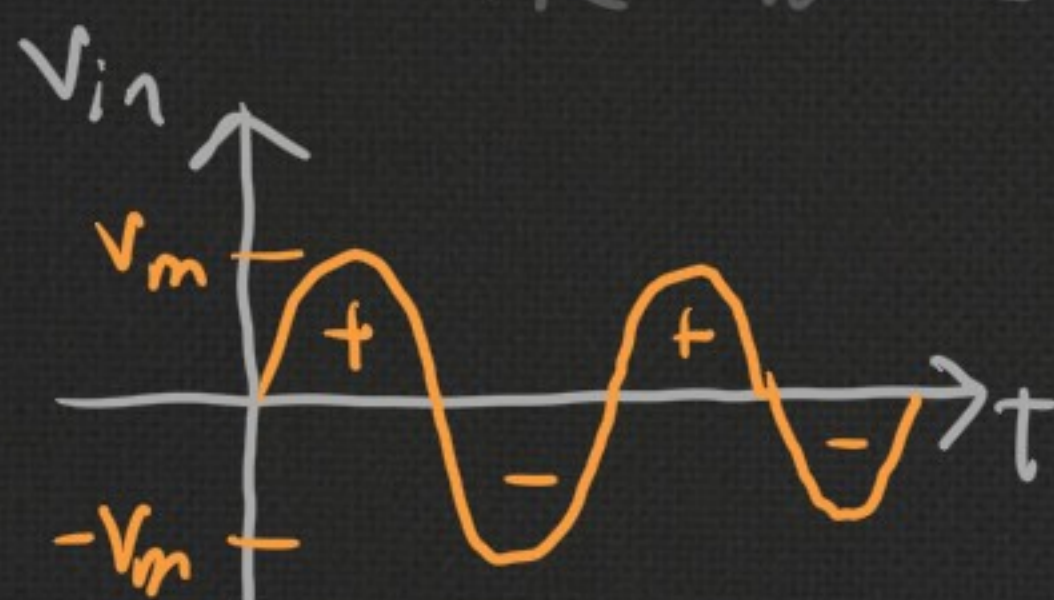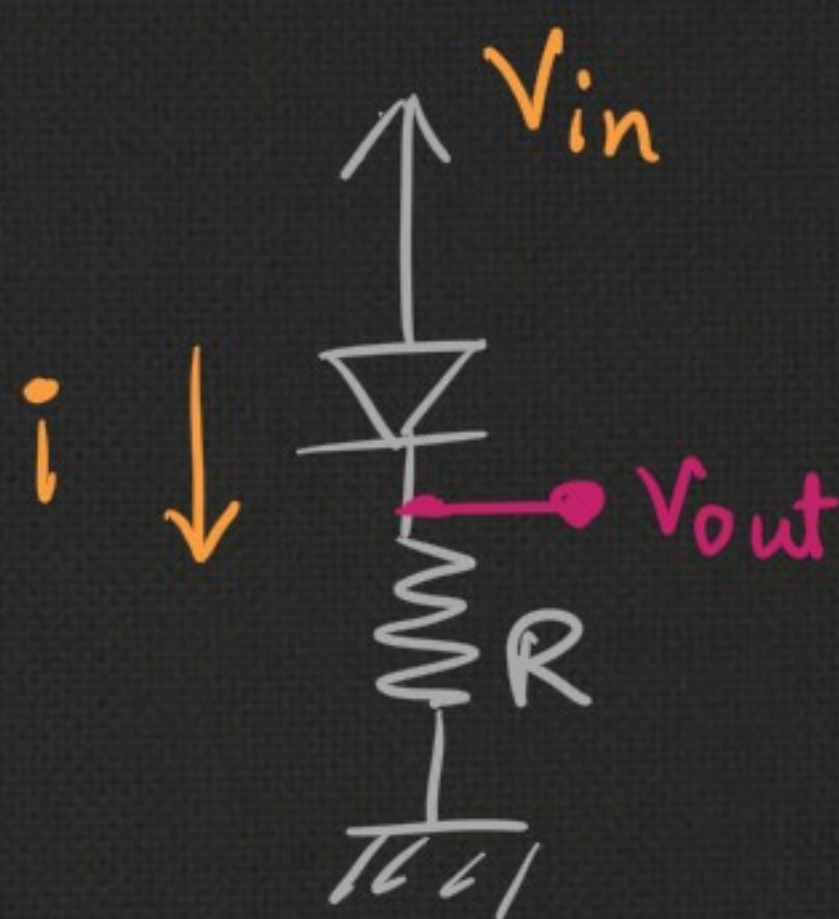

$V_{in} > 0$ [+ve half cycle]

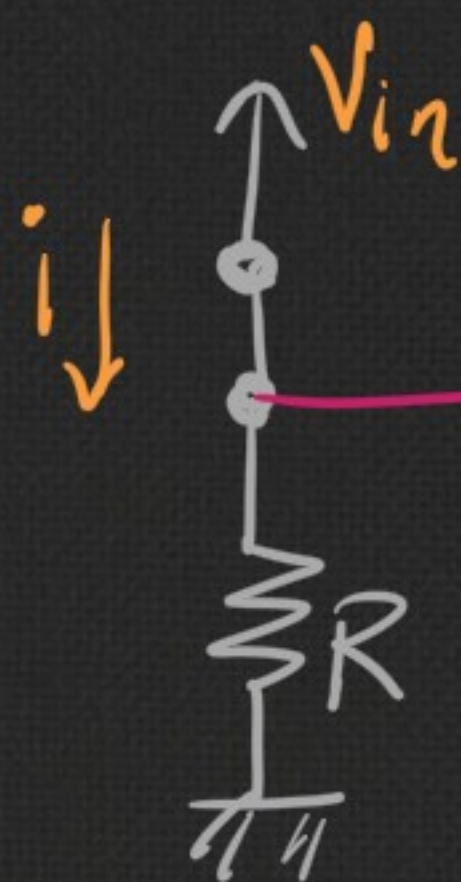

$y = x$, st. line, going through origin, $m=1$

$$V_{out} = V_{in}$$

$$i = \frac{V_{in}}{R}$$

$V_{in} < 0$ [-ve half cycle]




$$V_{out} = 0$$

$$i = 0$$

Diode is conducting

Diode is not conducting

waveforms

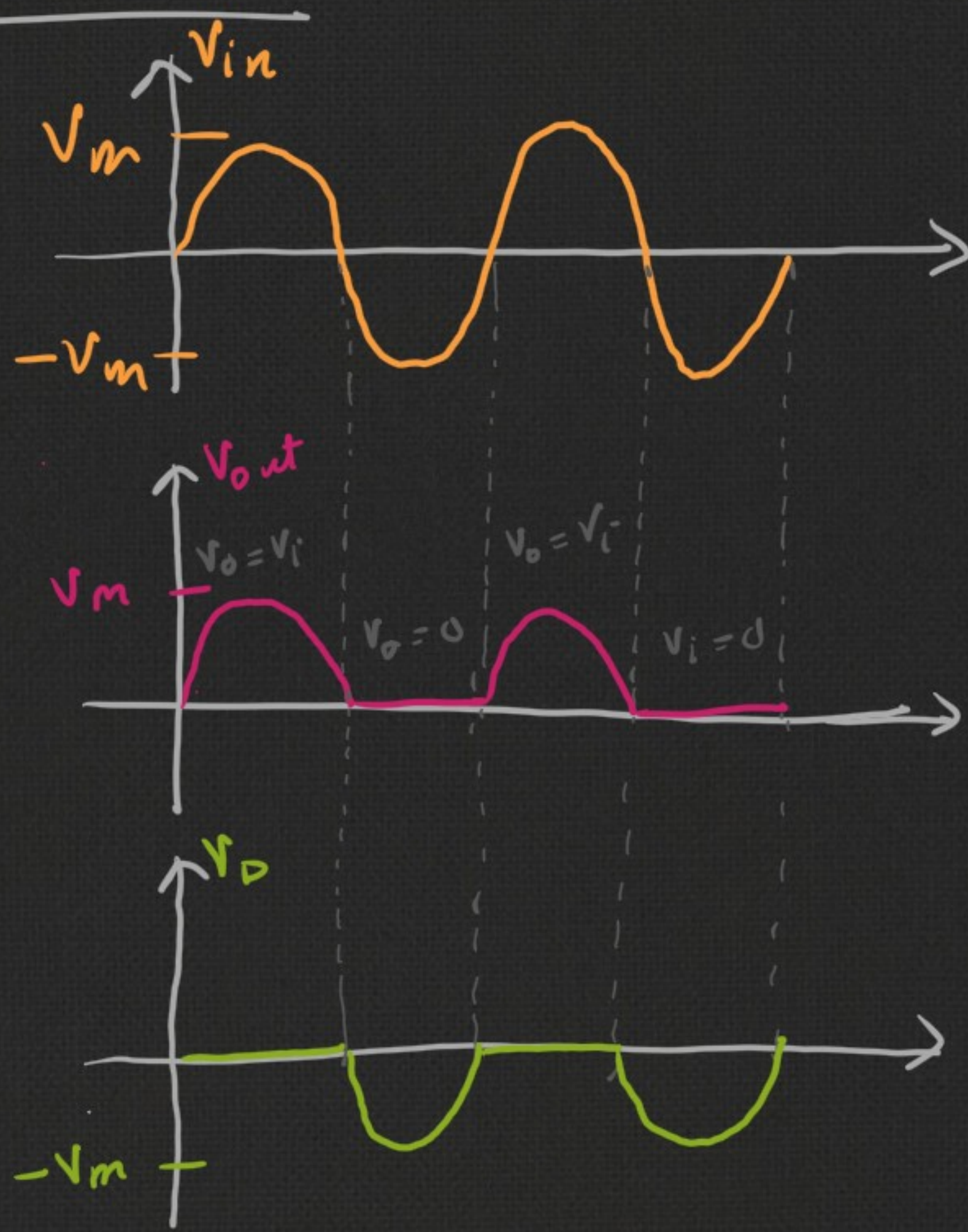

$$V_{in} = V_{out} + V_D$$

$$\Rightarrow V_D = V_{in} - V_{out}$$

Transfer Characteristics

\Rightarrow x axis \rightarrow input

\Rightarrow y axis \rightarrow output

