



CSE 251

Electronic Devices and Circuits

Lecture 1-10 Overview




Inspiring Excellence

Course instructor:

Ankan Ghosh Dastider (AGD)

Lecturer, Department of Computer Science and Engineering,
School of Data and Sciences, Brac University

Email: ankan.ghosh@bracu.ac.bd




- High Level Programming** → **Assembly language** → **Machine language** → **Architecture...**
- (C, C++, etc.) (x86, ARM, CUDA, etc.) (100110) (RISC, CISC, etc.)


(Register, Mux)	(AND, OR, etc.)
-----------------	-----------------

Lecture 1: Introduction

- **Vacuum tube**

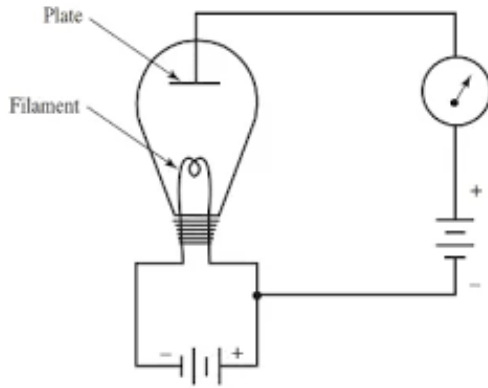


Diode

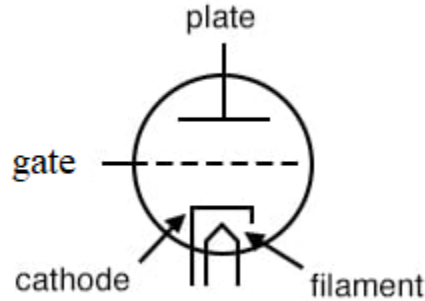


Triode

- To ensure current passes along one direction and stops flowing in the other direction
- Gate allows us to control this is a more robust way

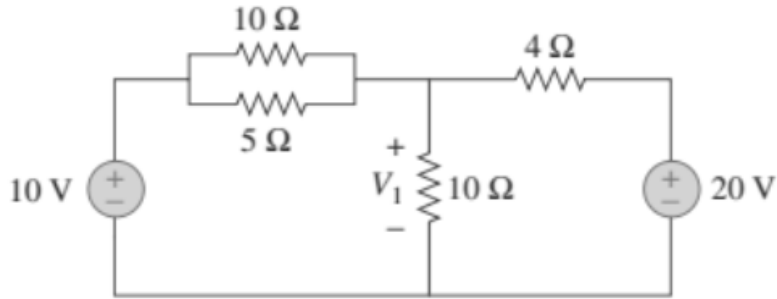Lecture 2: Alternate circuit representation









Loop representation




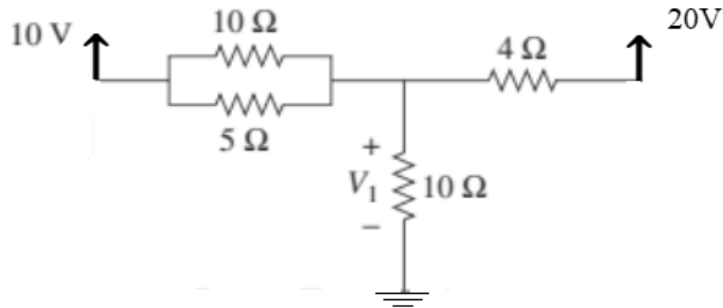


Alternate representation


- We shall try to use a common ground for all the sources, minimizing the number of floating sources
- KCL remains the same in both types of representations. KVL works along a line in the alternate representation, not in a loop

Lecture 3: I-V characteristics

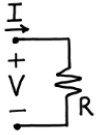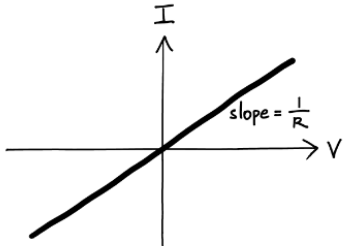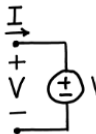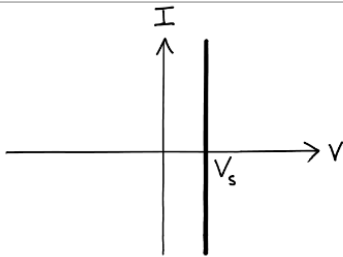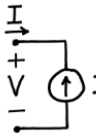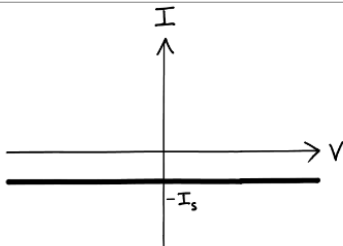
Element	Diagram	I-V Characteristic	Explanation
Resistor			A resistor R satisfies Ohm's law $I = V/R$ so its I-V characteristic goes through the origin and has slope $1/R$.
Voltage Source			A voltage source V_s maintains a fixed voltage drop and can allow any current, so its I-V characteristic is a vertical line at $V = V_s$.
Current Source			A current source I_s maintains a fixed current and can allow any voltage drop, so its I-V characteristic is a horizontal line at $I = -I_s$. Note that there is a negative sign because the current arrow labels on I and I_s are in opposite directions.

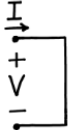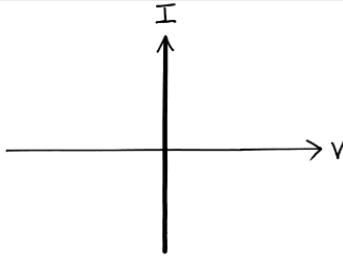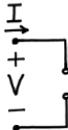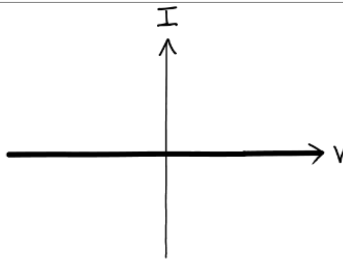Short Circuit			A short circuit is a direct connection between two terminals. The short circuit maintains zero voltage drop and can allow any current, so its I-V characteristic is a vertical line at $V = 0$. Notice that a short circuit behaves identically to a zero voltage source with $V_s = 0$ V.
Open Circuit			An open circuit is the absence of a connection between two terminals. The open circuit maintains zero current and can allow any voltage drop, so its I-V characteristic is a horizontal line at $I = 0$. Notice that an open circuit behaves identically to a zero current source with $I_s = 0$ A.

Lecture 3: I-V characteristics

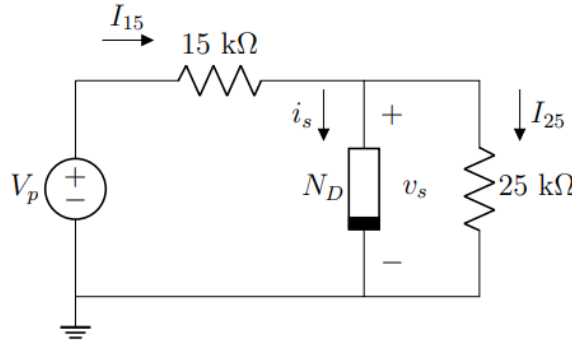

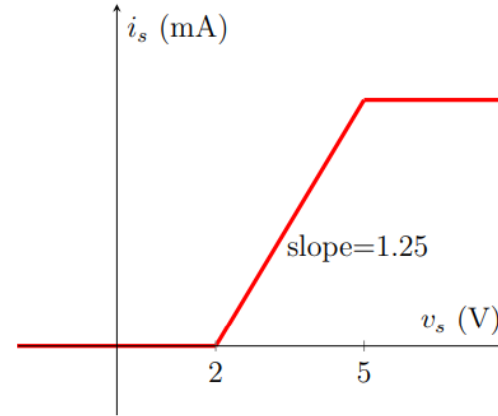(a) A circuit with a non-linear device N_D



(b) IV Characteristics of the non-linear device N_D

- Identify** the equivalent linear circuit models for the 3 linear segments in the IV characteristics of the non-linear device N_D and **calculate** the model parameters. [3]
- Show** the alternative representation of the circuit in Figure (a). [2]
- Detect** the operating region for the device when $v_s = 3\text{ V}$ and **calculate** the current through the device, i_s , for this voltage. [2]
- Apply** KVL and KCL to calculate the value of voltage source V_p when $v_s = 3\text{ V}$. [3]

Lecture 4: Introduction to diodes

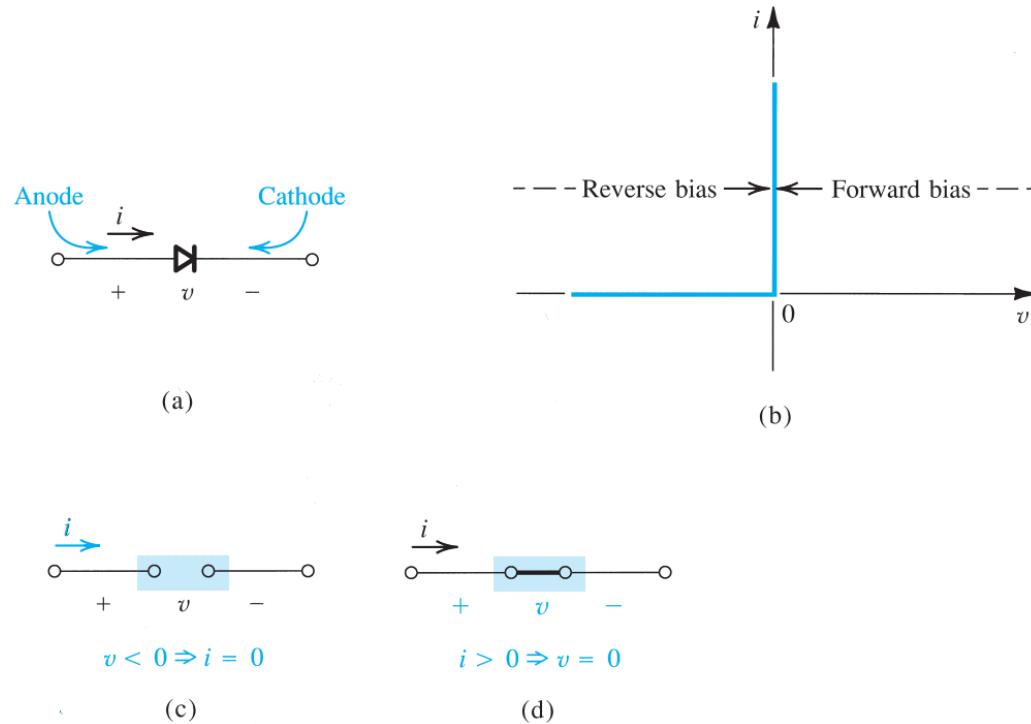


Figure 4.1 The ideal diode: (a) diode circuit symbol; (b) $i-v$ characteristic; (c) equivalent circuit in the reverse direction; (d) equivalent circuit in the forward direction.

Lecture 5: AC to DC conversion

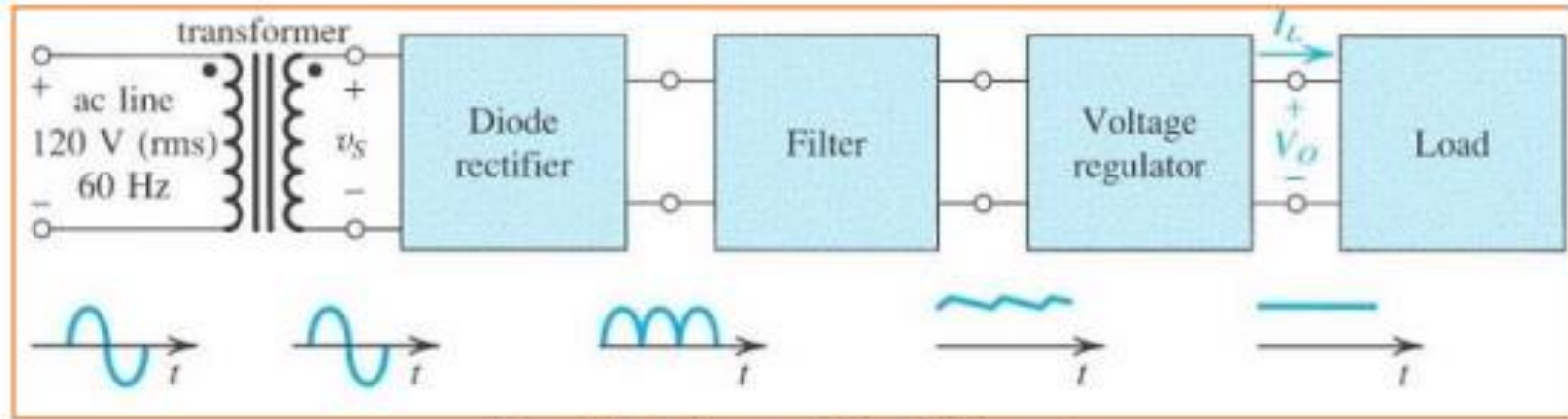


Figure 4 Block diagram of AC to DC Converter

NOTE: V_i can be sinusoidal (generally), triangular, rectangular, etc. Read the question carefully.

Lecture 5: AC to DC conversion

The Ideal-Diode Model

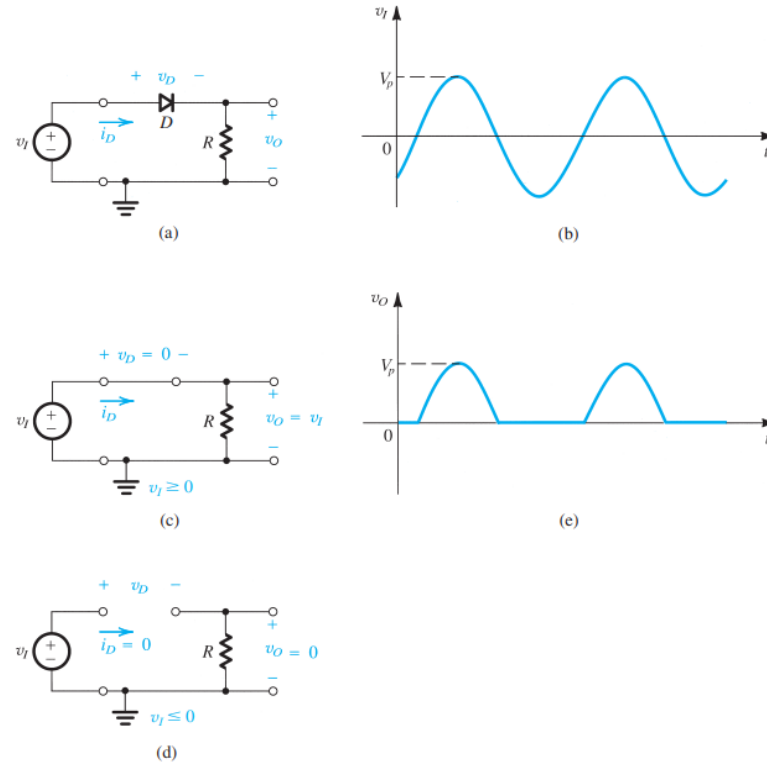


Figure 4.3 (a) Rectifier circuit. (b) Input waveform. (c) Equivalent circuit when $v_I \geq 0$. (d) Equivalent circuit when $v_I \leq 0$. (e) Output waveform.

Lecture 6: Ideal diodes and building logic gates


- **Max/OR and Min/AND**

operation:


(remember the conditions when they are applicable)

- Learn to implement AND, OR logics using them

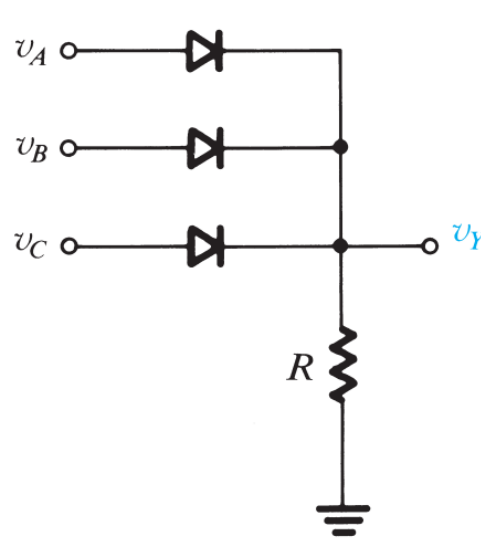(like implement $y=a+bx$ using ideal diodes)



(a)

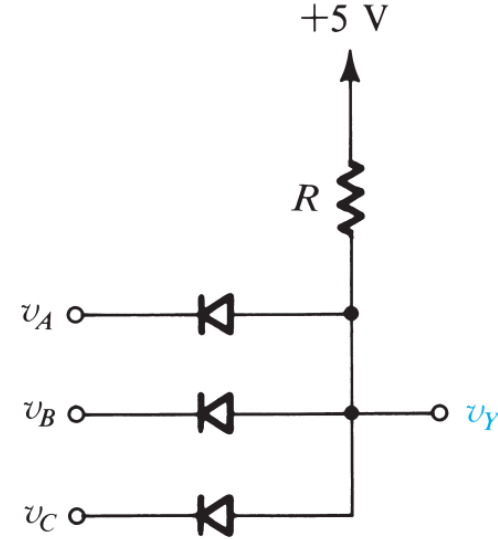

(b)

Figure 4.5 Diode logic gates: (a) OR gate; (b) AND gate (in a positive-logic system).

Lecture 7: p-n junction, 3 models of diode


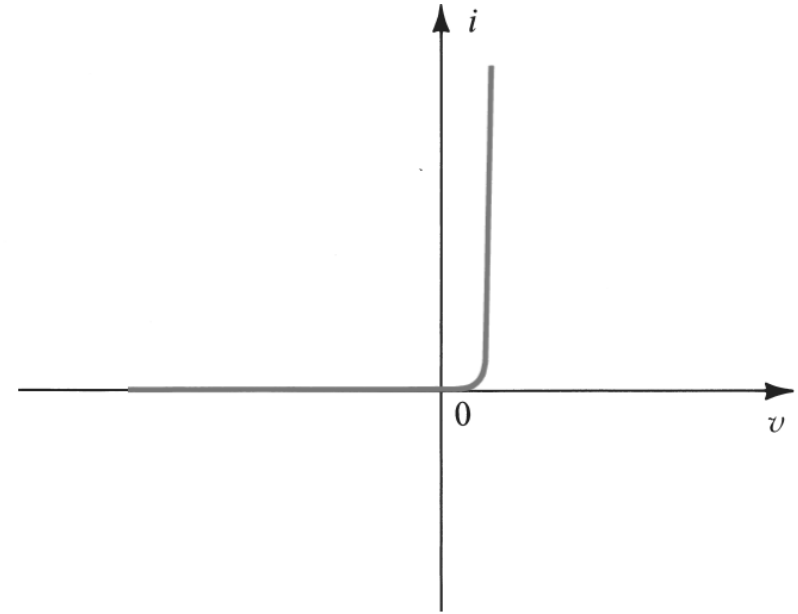
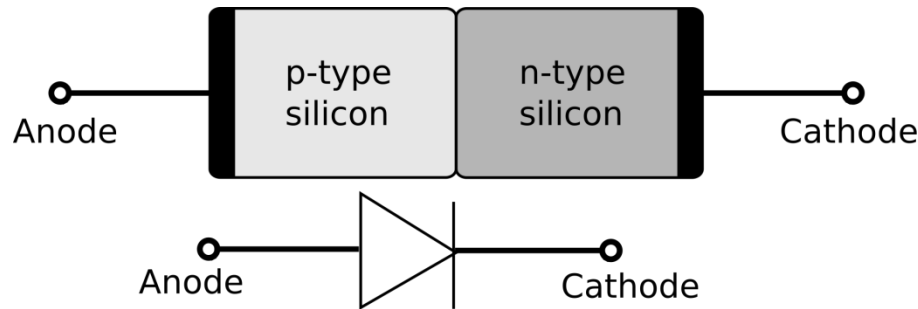


Figure 4.7 The $i-v$ characteristic of a silicon junction diode.

Lecture 7: p-n junction, 3 models of diode

The Constant-Voltage-Drop Model

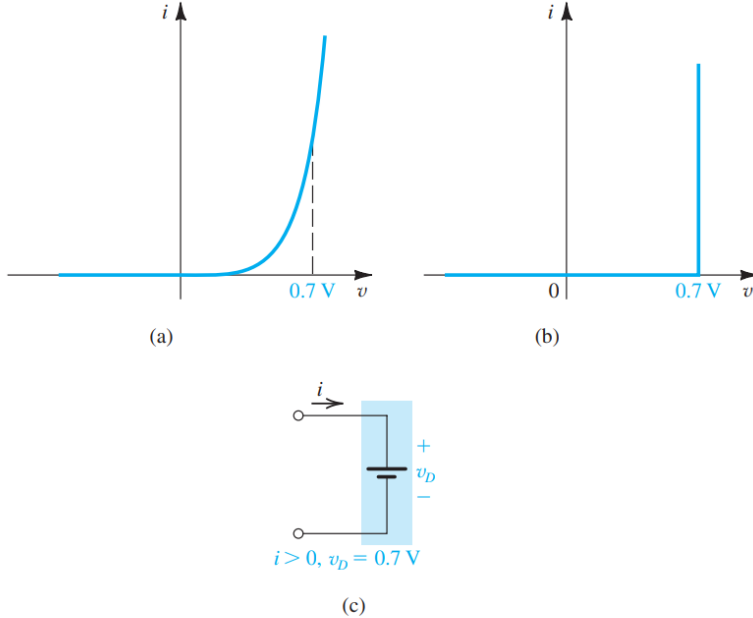

The Constant-Voltage-Drop+R Model

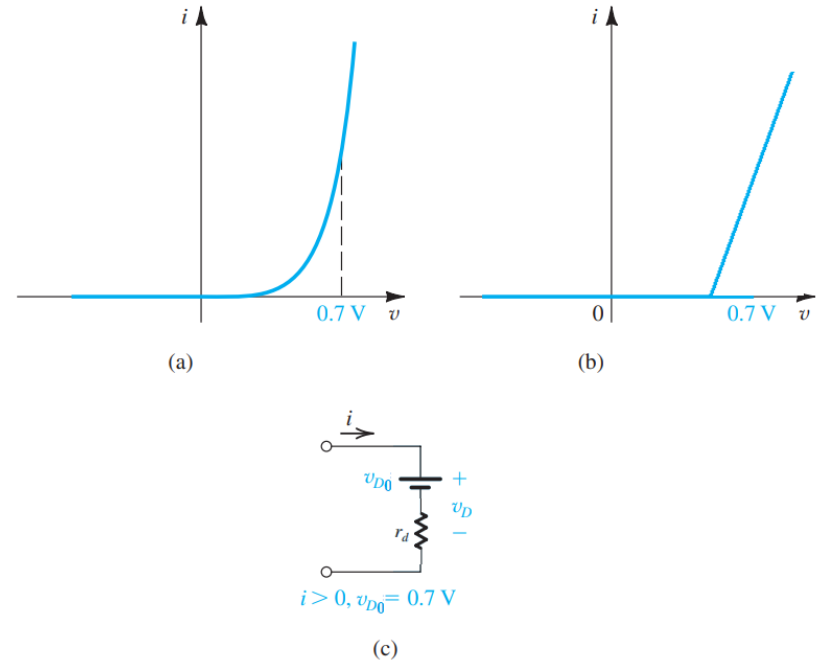


Figure 4.12 Development of the diode constant-voltage-drop model: (a) the exponential characteristic; (b) approximating the exponential characteristic by a constant voltage, usually about 0.7 V ; (c) the resulting model of the forward-conducting diodes.

Lecture 7: p-n junction, 3 models of diode

Example 4.2

Assuming the diodes to be ideal, find the values of I and V in the circuits of Fig. 4.6.

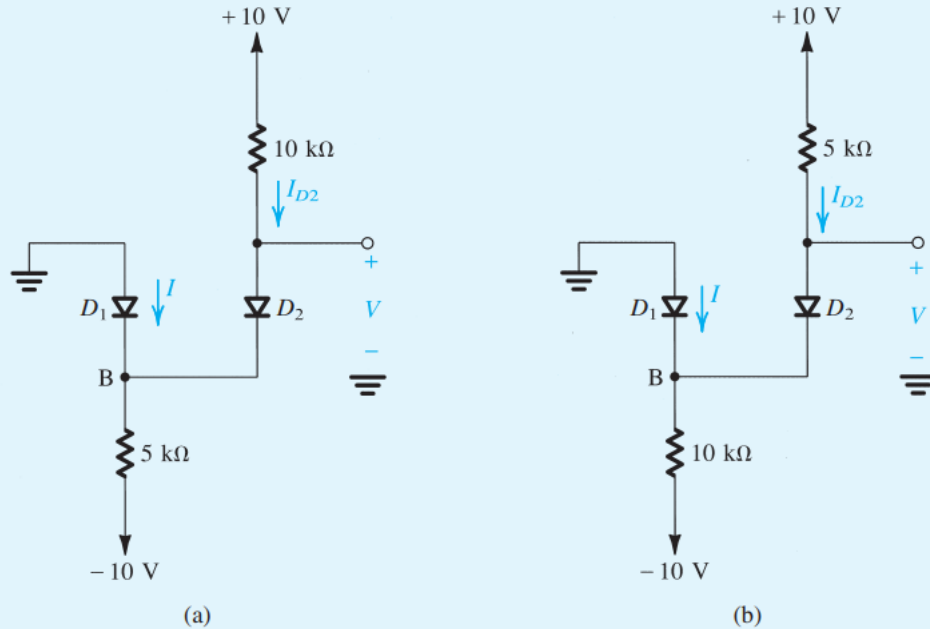


Figure 4.6 Circuits for Example 4.2.

Lecture 8: Method of assumed state

EXAMPLE 2.9

Objective: Determine the output voltage and diode currents for the circuit shown in Figure 2.35, for two values of input voltage.

Assume the circuit parameters are $R_1 = 5 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $V_\gamma = 0.7 \text{ V}$, $V^+ = +5 \text{ V}$, and $V^- = -5 \text{ V}$. Determine v_O , i_{D1} , and i_{D2} for $v_I = 0$ and $v_I = 4 \text{ V}$.


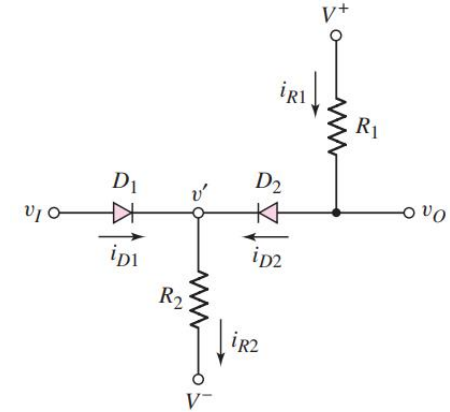
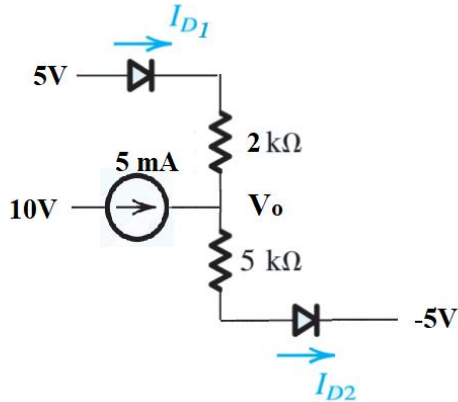


Figure 2.35 A two-diode circuit

Example: Find the values of I_{D1} , I_{D2} , and V_O in the circuit shown below assuming the diodes to be non-ideal [*Hints: use constant voltage drop model with $V_{D0}=0.7 \text{ V}$*]




Lecture 8: Method of assumed state

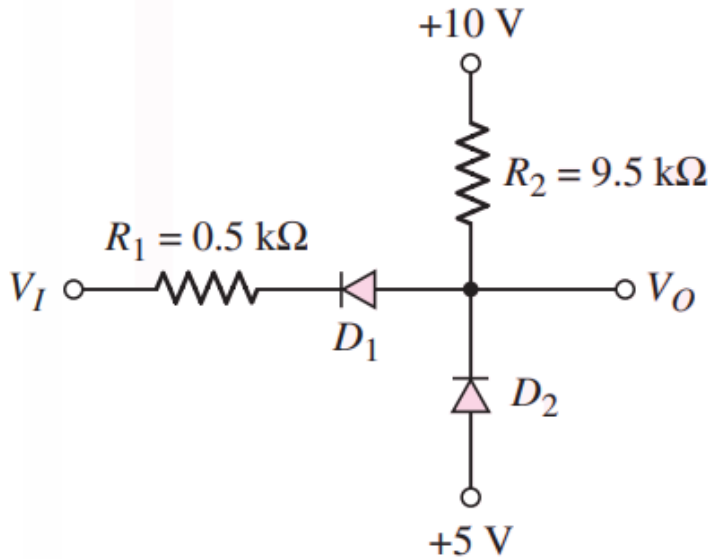

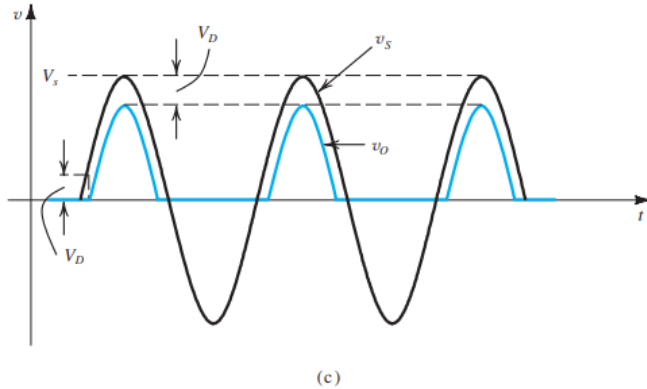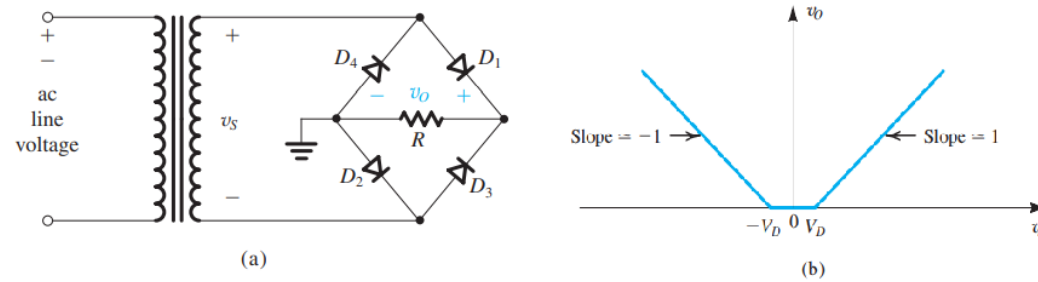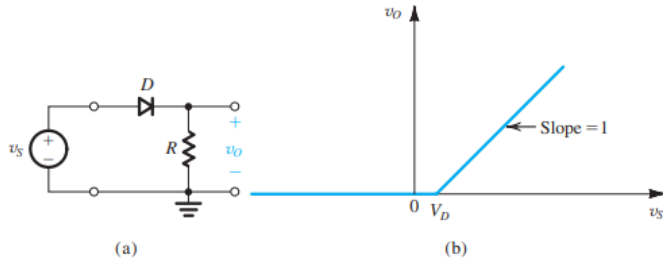
Example: Find the values of I_{D1} , I_{D2} , and V_O in the circuit shown below assuming the diodes to be Non-ideal. Here $V_i=2\text{V}$. *[Hints: use constant voltage drop model with $V_{D0}=0.7 \text{ V}$].*

NOTE: Changing the values of R or V_i may change the condition of diodes being ON or OFF

Lecture 9: Half-wave and Full-wave rectifier





Half-wave

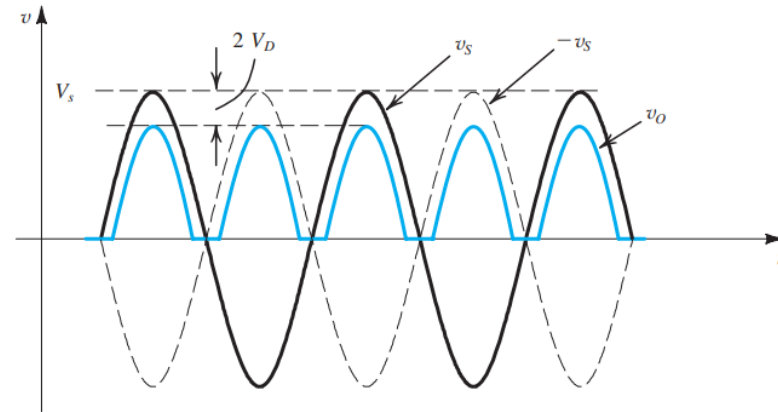

Full-wave

Lecture 10: Filtering and calculating ripple values

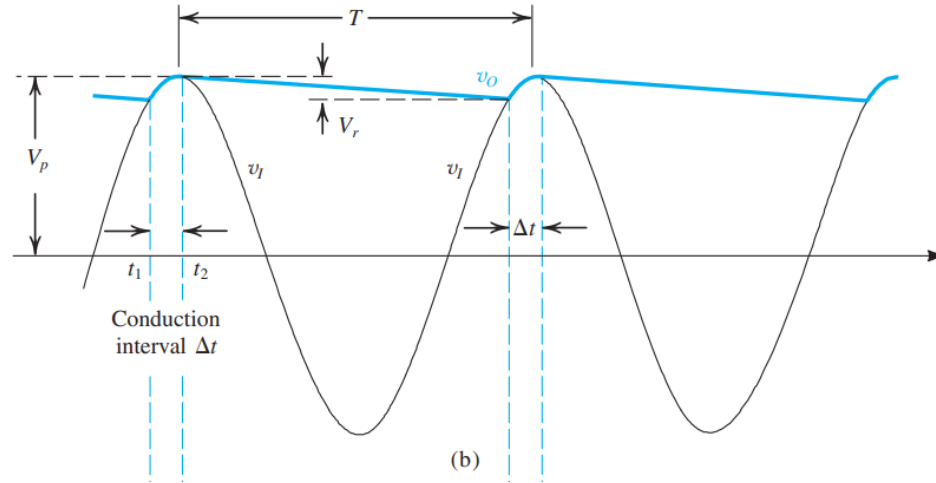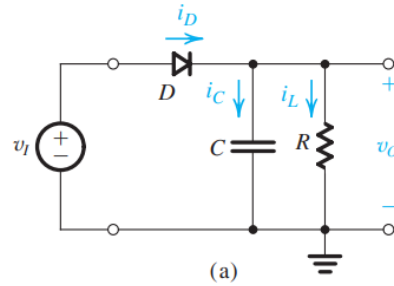

Lecture 10: Filtering and calculating ripple values

Without capacitor

Rectifier	i/p peak	o/p peak	average
H/W	V_M	V_P	$V_{avg}=V_{DC}=\frac{1}{\pi}V_M-\frac{1}{2}V_{Do}$
F/W	V_M	V_P	$V_{avg}=V_{DC}=\frac{2}{\pi}V_M-2V_{Do}$

With capacitor

Rectifier	i/p peak	o/p peak	frequency	Ripple voltage	average
H/W	V_M	$V_P=V_M-V_{Do}$	$f_r=f_i$	$V_r=\frac{V_P}{f_rRC}$	$V_{avg}=V_{DC}=V_P-\frac{1}{2}V_r$
F/W	V_M	$V_P=V_M-2V_{Do}$	$f_r=2f_i$	$V_r=\frac{V_P}{f_rRC}$	$V_{avg}=V_{DC}=V_P-\frac{1}{2}V_r$

$$I_{o,avg}=V_{o,avg}/R, V_{rms}=V_p/\sqrt{2}$$