
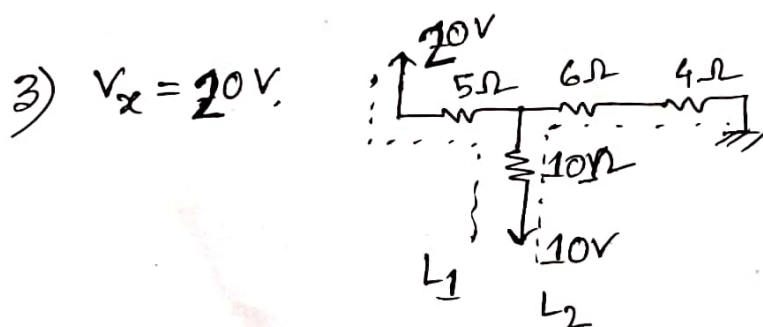
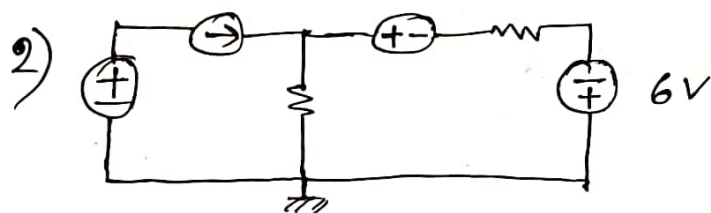
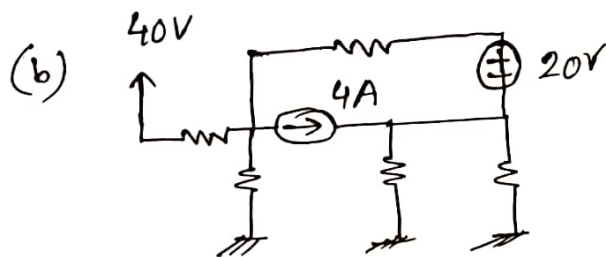


or,

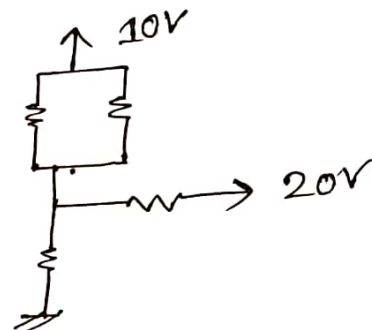

[KCL]

$$I_1 = I_2 + I_3 \dots \dots (i)$$

along L_1 , [KVL]

$$5I_1 + 10I_3 = 20 - 10 = 10 \dots \dots (ii)$$


along L_2 , [KVL]

$$-10I_3 + 10I_2 = 10 - 0 \dots \dots (iii)$$

\therefore solving (i), (ii), and (iii),

$$I_1 = 1.5A, I_2 = 1.25A, I_3 = 0.25A$$

(values may change — follow the steps)

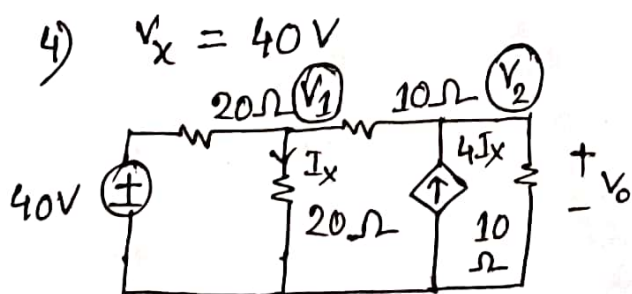

$$\text{Here, } I_x = \frac{V_1}{20} \Rightarrow 4I_x = \frac{V_1}{5}$$

at node V_1 , [nodal analysis]

$$\frac{V_1 - 40}{20} + \frac{V_1}{20} + \frac{V_1 - V_2}{10} = 0$$

$$\Rightarrow V_1 \left(\frac{1}{20} + \frac{1}{20} + \frac{1}{10} \right) - V_2 \left(\frac{1}{10} \right) - \frac{40}{20} = 0 \dots \dots (i)$$


at node V_2 , $\frac{V_2 - V_1}{10} + \frac{V_2}{10} - 4I_x = 0$

$$\Rightarrow V_2 \left(\frac{1}{10} + \frac{1}{10} \right) - V_1 \left(\frac{1}{10} \right) - \frac{V_1}{5} = 0$$

$$\Rightarrow V_2 \left(\frac{1}{5} \right) - V_1 \left(\frac{1}{10} + \frac{1}{5} \right) = 0 \quad \dots \dots (11)$$

solving (i) and (ii), $V_1 = 40V$, $V_2 = V_0 = 60V$.


5) The given circuit is equivalent to:

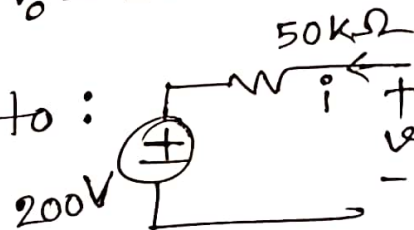

$$v = 50i + 200$$

$$\Rightarrow i = \frac{v}{50} - \frac{200}{50}$$

$$= \frac{v}{50} - 4 \quad \dots (i)$$

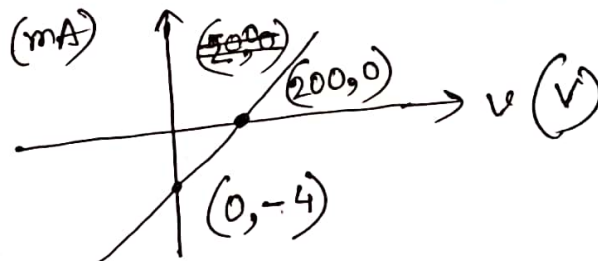


\therefore y intersecting point: $(0, -4)$.

for x-intersecting point, $i=0$ at that point. $\therefore (i) \Rightarrow v=200$


\therefore the point: $(200, 0)$

if $R = 100k\Omega$, $i = \frac{v}{100} - 2$, when $R = 200k\Omega$, $i = \frac{v}{200} - 1$

x-intersecting point will be fixed.

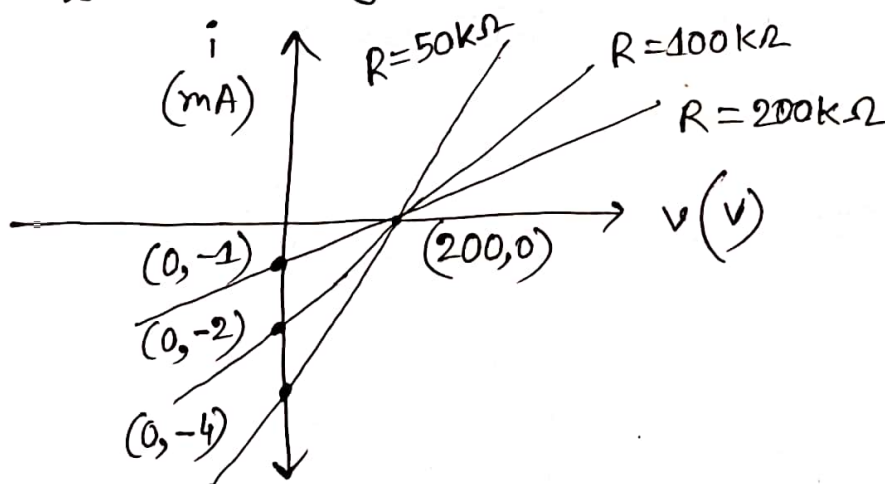

Note:

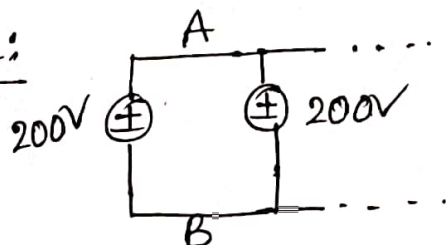

placing a voltmeter across A-B node will always provide 200V

6) a. AB: current source, $I_2 = -5 \text{ mA}$

BC: resistor, $R_{BC} = \frac{1}{\text{slope}} = \frac{1}{\frac{4 - (-5)}{4 - (-5)}} = 1 \text{ k}\Omega$

CD: (i) current source in parallel to a resistor
(ii) or, voltage source in series with " "

$$R_{CD} = \frac{1}{\text{slope}} = \frac{1}{\frac{.6 - 4}{10 - 4}} = \frac{1}{\frac{2}{6}} = 3 \text{ k}\Omega$$



(i) $\boxed{i = \frac{V}{R} + I_0}$ or, $i = \frac{V}{3} + I_0$

at point C, $i = 4 \text{ mA}$, $V = 4 \text{ V}$

$$\therefore 4 = \frac{4}{3} + I_0 \Rightarrow I_0 = \left(4 - \frac{4}{3}\right) = 2.67 \text{ mA}$$

similarly for (ii). You need to solve either in 1st or 2nd method.

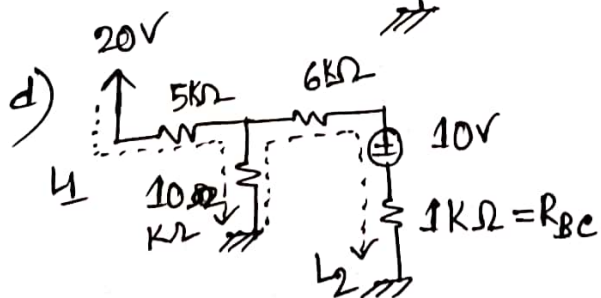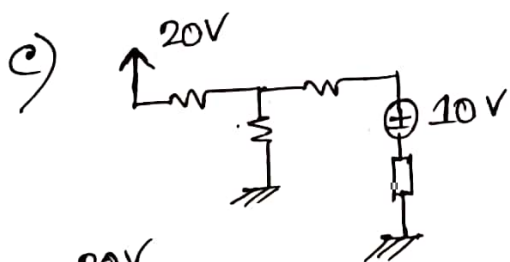b) $V = 2 \text{ V}$ is within BC region. It is represented by a resistor. So, $I_2 = \frac{V}{R} = \frac{2}{1} = 2 \text{ mA}$.



$$I_1 = I_2 + I_3 \quad [\text{KCL}]$$

KVL at L_1 ,

$$5I_1 + 10I_3 = 20 - 0$$

KVL at L_2 ,

$$-10I_3 + 6I_2 + 1I_2 = 0 - 10 - 0$$

$$\therefore I_1 = 1.55 \text{ mA}$$

$$I_2 = 0.32 \text{ mA}$$

$$I_3 = 1.22 \text{ mA}$$

[in question, some values were in Ω ; so answers may change.]