

ID:

Sec:

Name:

**Brac University****Set: 02**

Semester: Summer 2022

Course No: CSE251

Course Title: Electronic Devices and Circuits



Section: 1 to 13

Final Exam


Full Marks: 30

Time: 1 hour 45 minutes

Date: September 9, 2022

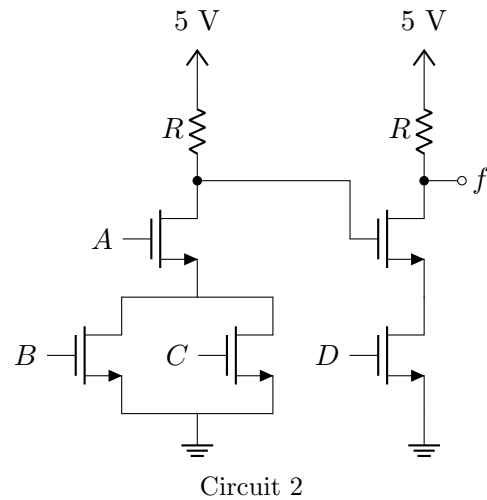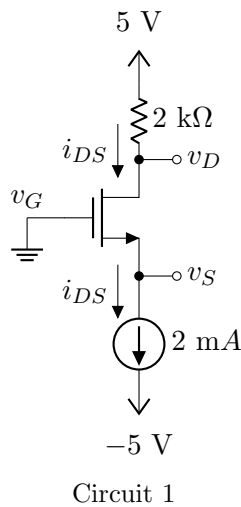Answer **any 3 questions**. All the questions carry equal marks.**Question 1 [CO1, CO2]****10****Part a:** Refer to the **Circuit 1** above. For the MOSFET, $V_T = 1\text{ V}$ and $k = k'_n \frac{W}{L} = 4\text{ mA/V}^2$.

- Identify** the value of the gate voltage v_G and the drain-source current i_{DS} . [0.5+0.5]
- Calculate** the value of the drain voltage v_D using the $2\text{ k}\Omega$ resistor. [1]
- Analyze** the circuit to find v_S . Here, **use** the Method of Assumed State. You must **validate** your assumptions. [Hint: assume $v_S = x$] [3+2]

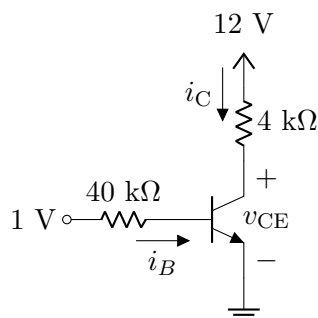Part b: Analyze the **Circuit 2** above to find f in terms of *boolean* inputs A , B , C , and D . [3]**Question 2 [CO3, CO4]****10****Part a:** Analyze the circuit below to find i_C and v_{CE} . Here, **use** the Method of Assumed State. You must **validate** your assumptions. [6]

$$\beta = 100$$

$$\alpha = 0.99$$

$$v_{BE(\text{Active})} = 0.7\text{ V}$$

$$v_{BE(\text{Saturation})} = 0.8\text{ V}$$

$$v_{CE(\text{Saturation})} = 0.2\text{ V}$$

Set: 2

Part b: A BJT common emitter amplifier with $V_S = 20$ V, $\beta = 60$, $R_L = 2$ k Ω and $R_I = 10$ k Ω has an input signal $v_{IN} = V_X + v_i(t)$ and an output signal $v_O = V_Y + kv_i(t)$ where $v_i(t) = 0.5 \sin(300\pi t)$.

- (i) **Determine** the operating point (V_X, V_Y) for maximum input voltage swing. [3]
- (ii) **Calculate** the value of the small signal gain k for the amplifier. [1]

Question 3 [CO1, CO4]

10

- (a) **Show** the IV characteristics graph of both MOSFET (i_D vs v_{DS}) and BJT (i_C vs v_{CE}). **Identify** the different operating regions in the graphs. [2+2]
- (b) Consider a MOSFET inverter (**SR model**) with the following circuit parameters: $V_S = 5$ V, $R_L = 10$ k Ω . Also, for the MOSFET, $V_T = 1$ V and $1/(k'_n V_{ov}) = 5$. **Determine** a W/L sizing for the MOSFET so that the inverter gate output of logical 0 is able to switch OFF the MOSFET of another inverter. [4]
- (c) Consider the static discipline $V_{OL} = 1.5$ V, $V_{IL} = 3.5$ V, $V_{IH} = 4.7$ V, $V_{OH} = 5.5$ V. **Calculate** the noise margins NM_0 and NM_1 . [2]

Question 4 [CO1, CO4]


10

- (a) **Design** a circuit using **Op-Amp comparator** to automatically turn ON (or OFF) the street lights. For this, you have a lux sensor installed on top of the street lights (facing above) that outputs a voltage proportional to amount of natural light, as listed below:

$v_{\text{night, 0 lux}} = 1$ V	$v_{\text{dusk, 20 lux}} = 2$ V	$v_{\text{dawn, 80 lux}} = 3$ V
---------------------------------	---------------------------------	---------------------------------

The lights require 20 V and should be ON if the amount of light goes **below** 20 lux (at dusk). [3]

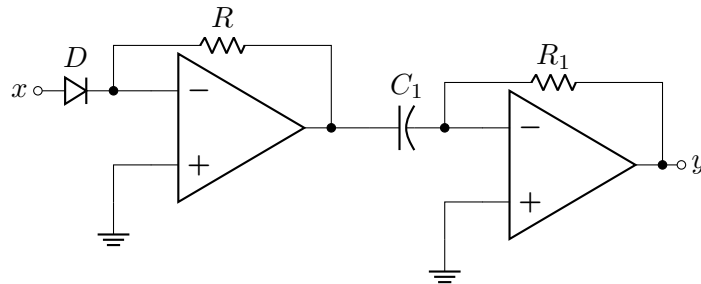- (b) **Design** a circuit using Op-Amp to implement the expression: $f = -\frac{1}{3} \int x dt + 2 \ln y + 4z$ [4]
- (c) **Analyze** the circuit below to find y as a function of x . For the diode, $I_S R = 1$ and $V_T = 1$. [3]



Equations for MOSFET

$$I_D = 0, \text{ if } V_{GS} < V_T$$

$$I_D = k \left[(V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right], \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} < (V_{GS} - V_T)$$

$$I_D = \frac{1}{2} k (V_{GS} - V_T)^2, \text{ if } V_{GS} \geq V_T \text{ and } V_{DS} \geq (V_{GS} - V_T)$$