

Assignment 3



BRAC University

Semester: Fall 2022

Course No: CSE251

Course Title: Electronic Devices and Circuits

Full Marks: 100

Deadline: **1 December 2022**


1. Design a circuit using an **Op-Amp comparator** to turn ON (or OFF) the street lights automatically. For this, you have a lux sensor installed on top of the street lights (facing above) that outputs a voltage proportional to the amount of natural light, as listed below:

$v_{\text{night, 0 lux}} = 1 \text{ V}$	$v_{\text{dusk, 20 lux}} = 2 \text{ V}$	$v_{\text{dawn, 80 lux}} = 3 \text{ V}$
---	---	---

The lights require 20 V and should be ON if the light goes below 20 lux (at dusk).

[Hints: you may start by building the circuit as a comparator.]

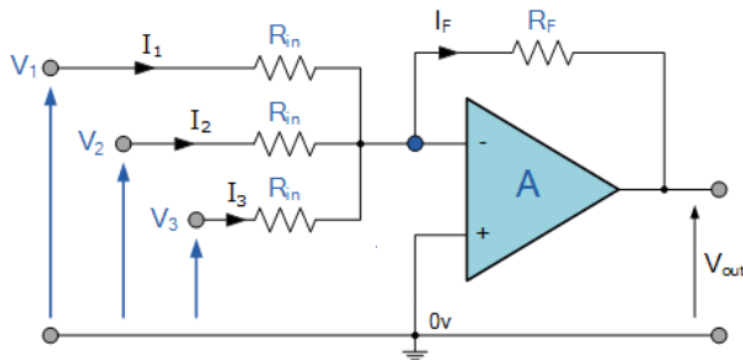(b) **Analyze** the following circuit and derive the expression for the output voltage (V_{out}) in terms of the inputs. If $V_1=1 \text{ V}$, $V_2 = 2\text{V}$, and $V_3 = 1.5 \text{ V}$, and all the resistors have equal values, calculate V_{out} .




(c) **Design** a circuit using Op-Amp to implement the following expressions:

$$z = \int x \, dt - 2 \frac{dy}{dt} - u$$

(i)

(ii) $y = 12x$

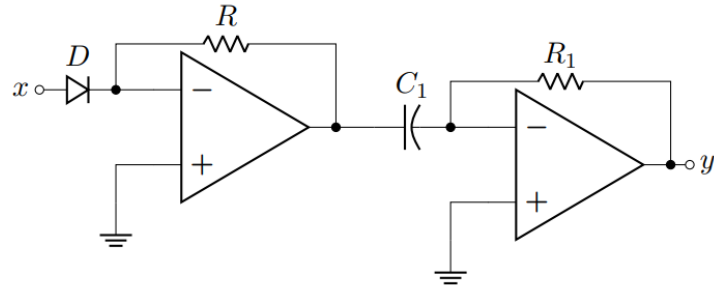(d) **Analyze** the circuit below to find y as a function of x . For the diode, $I_S R = 1$ & $V_T = 1$.



[30+10+10x2+10]

2. Implement using MOSFETs:

[10x3]

(a) $f = (A + B)C$

(b) $f = (\overline{A}B + CD)$

(c) $f = AB + A + CD$ (with and without simplifying the logic)